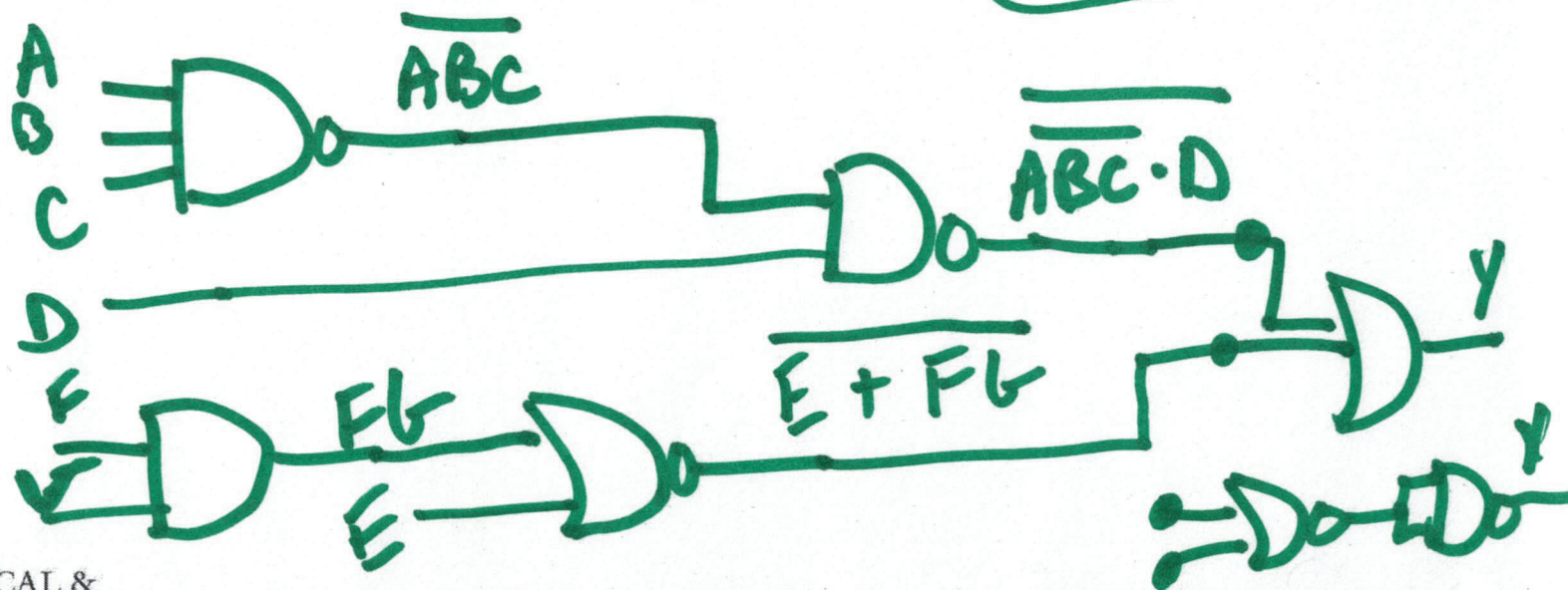




CPE 100 Digital Logic Design

March 8, 2021

Lecture 13
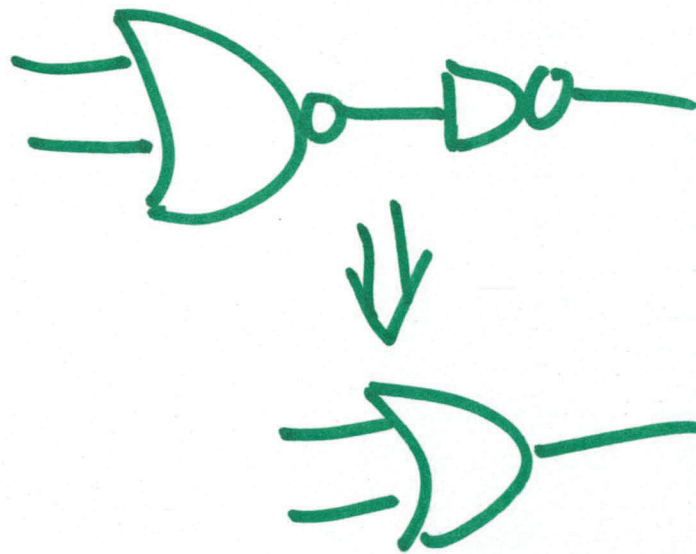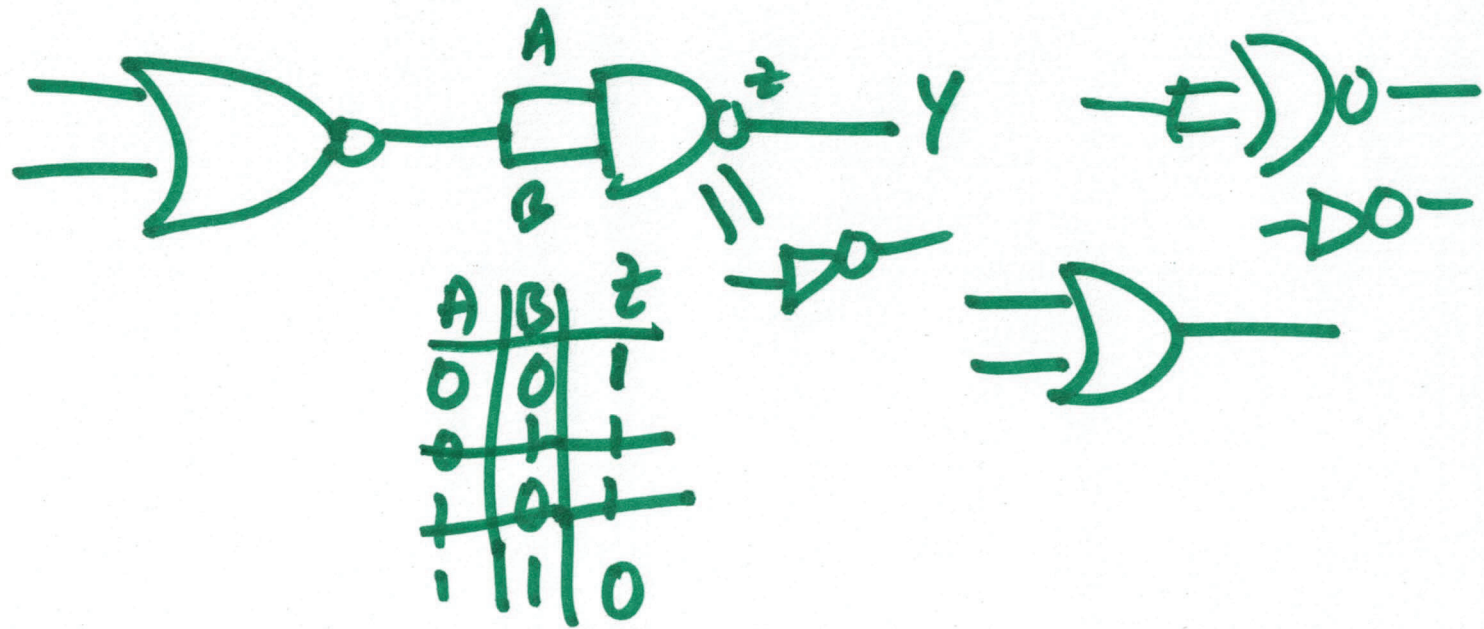
$$Y = \overline{\overline{ABC} \cdot D} + \overline{E + FG}$$







$$\begin{array}{r} 55 \\ \underline{32} \\ 23 \\ \underline{16} \\ 7 \end{array}$$

64 32 16 8 4 2 1

6-bits


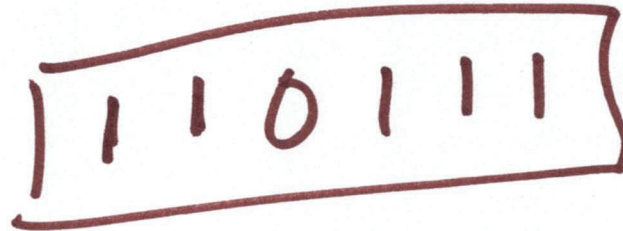

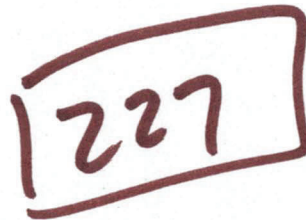
$$\begin{array}{r} 1110 \quad 0011 \\ 128 \quad 64 \quad 32 \quad 21 \end{array}$$



$$\begin{array}{r} 128 \\ \underline{64} \\ 192 \\ \underline{32} \\ 224 \\ 3 \end{array}$$

3)

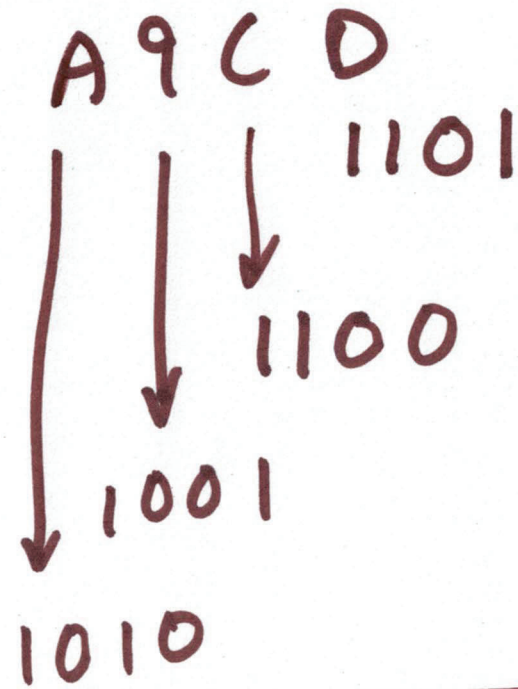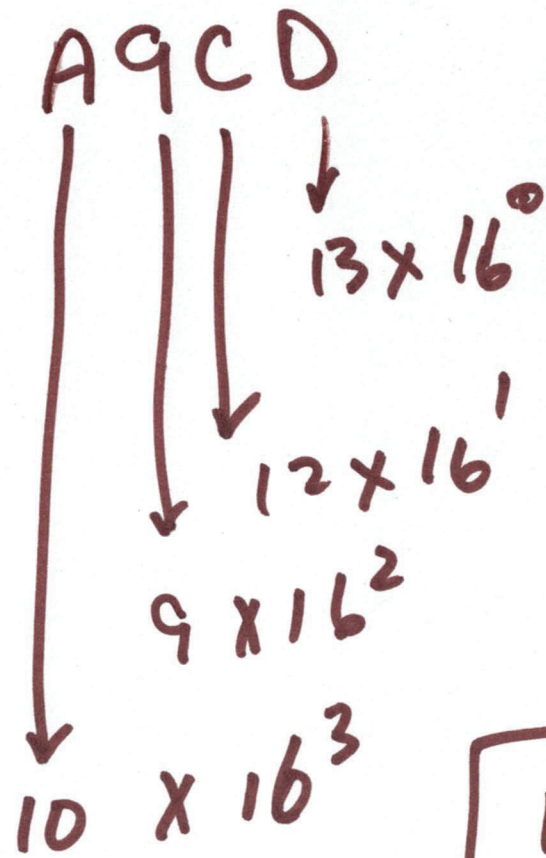

1010 1001 1100 1101

1247158

43,469

13
192
2304
40960

$$2^{3^2} - 1$$

$$0) 2^3 \\ 7 \rightarrow 2^3 - 1$$

-55

011 0111

100 1000
+ 1

100 1001

~~right~~

111

011 0111
100 1000
1

100 1001

7-bits

~~wrong~~
right

5)

$$\begin{array}{r}
 15 \\
 -9 \\
 \hline
 9 \\
 -15 \\
 \hline
 -6
 \end{array}$$

$$\begin{array}{r}
 01001 \\
 + 10001 \\
 \hline
 11010
 \end{array}$$



$$\begin{array}{r}
 01111 \\
 10000 \\
 \hline
 10001
 \end{array}$$

10001 → -15

$$\begin{array}{r}
 00110 \\
 11001 \\
 + 1 \\
 \hline
 11010 \text{ yay}
 \end{array}$$

6)

$$325 + 42 = 411$$

~~$$3 \times \bar{F}^3 + 2 \times \bar{F}^2 + 5 \times \bar{F}$$~~

$$3 \times \bar{F}^2 + 2 \times \bar{F}^1 + 5 \times \bar{F}^0$$

$$+ 4 \times \bar{F}^1 + 2 \times \bar{F}^0$$

$$= 4 \times \bar{F}^2 +$$

$$3 \times \bar{F}^2 + 6 \times \bar{F} + 7 =$$

$$4 \times \bar{F}^2 + \bar{F} + 1$$

$$1 \times \bar{F}^1 + 1 \times \bar{F}^0$$


$$3F^2 + 6F + 7 = 4F^2 + F + 1$$

$$0 = F^2 - 5F - 6$$


$$0 = (F - 6)(F + 1)$$

$$F = 6$$

$$A\bar{C} + B + A \rightarrow A + B$$

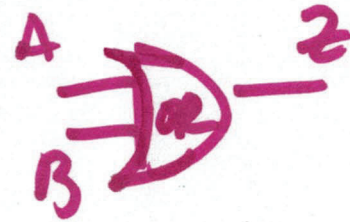

A	B	C	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

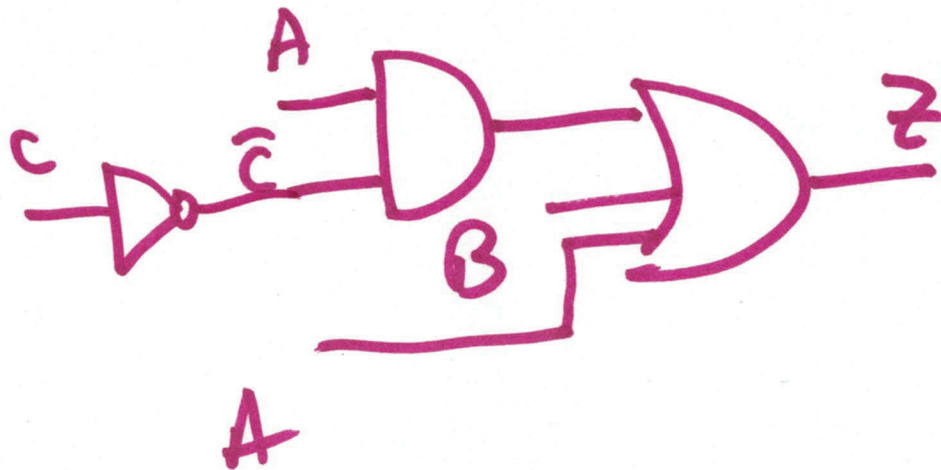


$$Y = AC + \bar{A}\bar{B}C$$

$$= C(A + \bar{A}\bar{B})$$

$= C(A + \bar{B}) \rightarrow CA + C\bar{B}$
 11?
 AC + C \bar{B}
 yes!

	AC	00	01	11	10
B	0	0	1	1	0
1	0	0	1	0	

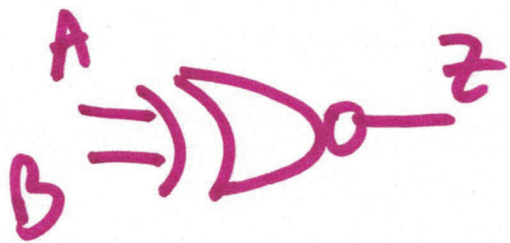


A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1



$$\bar{A}\bar{B} + AB$$

no bar

$$(\bar{A} + B) \cdot (A + \bar{B})$$

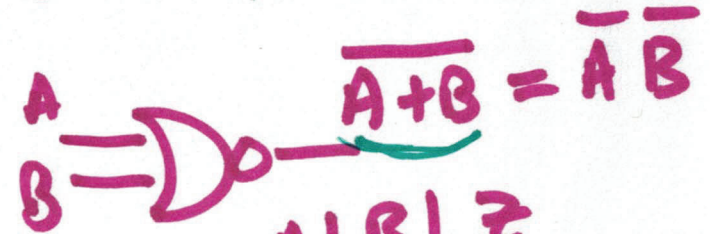

A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0

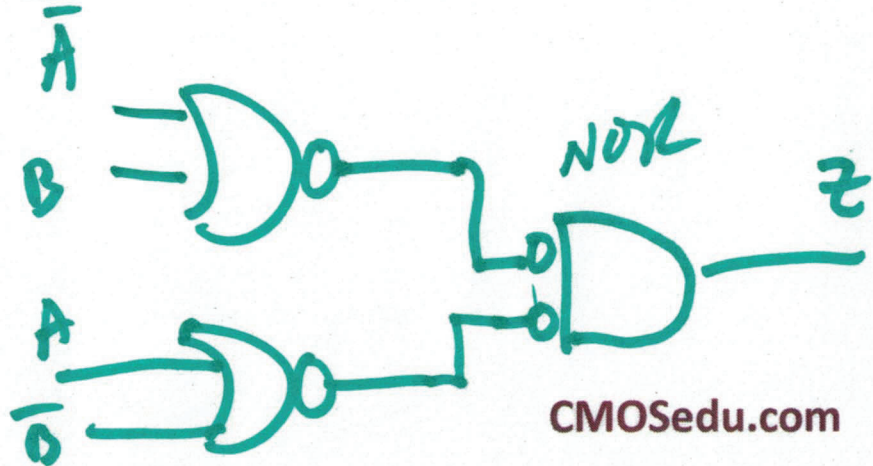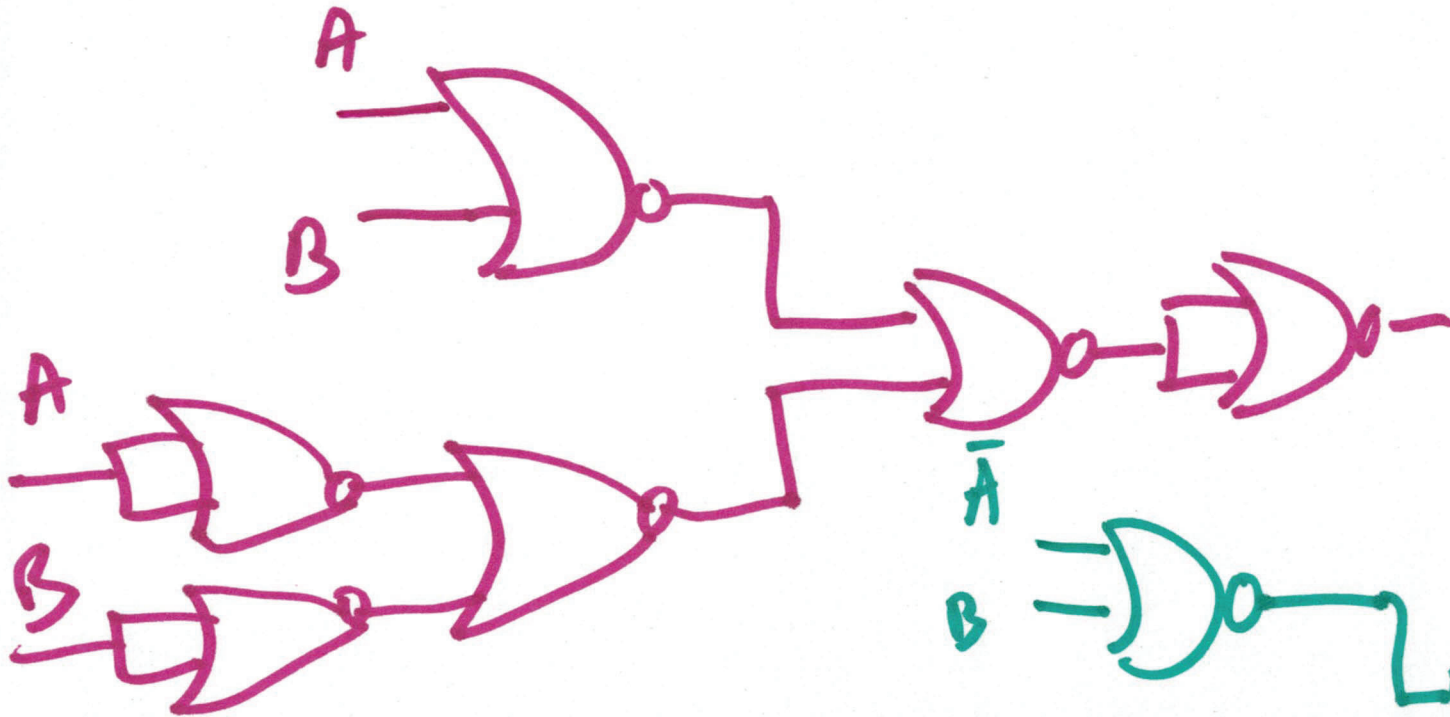


Tuesday \rightarrow $A_2 A_1 A_0$
0 1 1 (3)

Thursday \rightarrow 1 0 1 (5)




$A_2 A_1$	A_0	00	01	10	11
0	X				
1			1		1

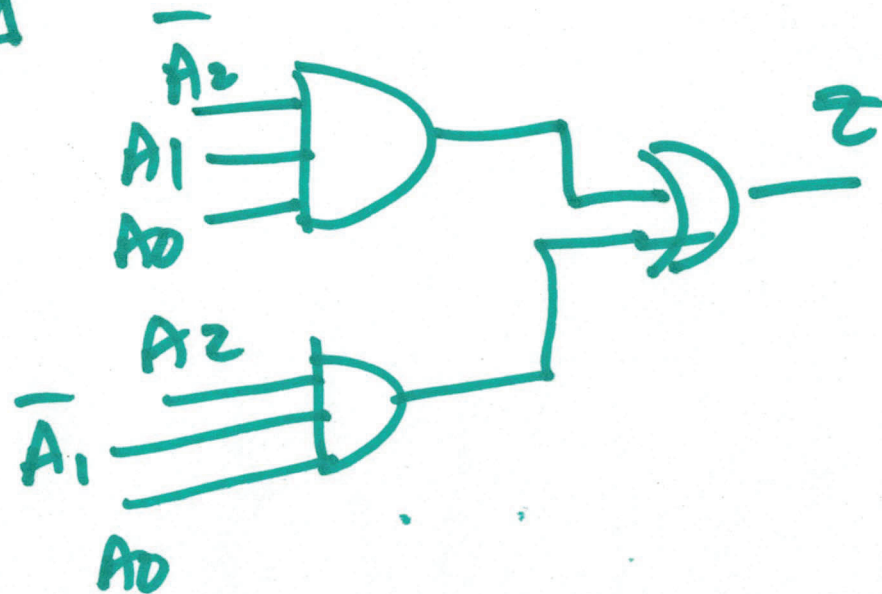
$$Z = \bar{A}_2 \cdot A_1 \cdot A_0 + A_2 \bar{A}_1 A_0$$



3-bit decoder

$A_2 = 0$
 $A_1 = 0$
 $A_0 = 0$

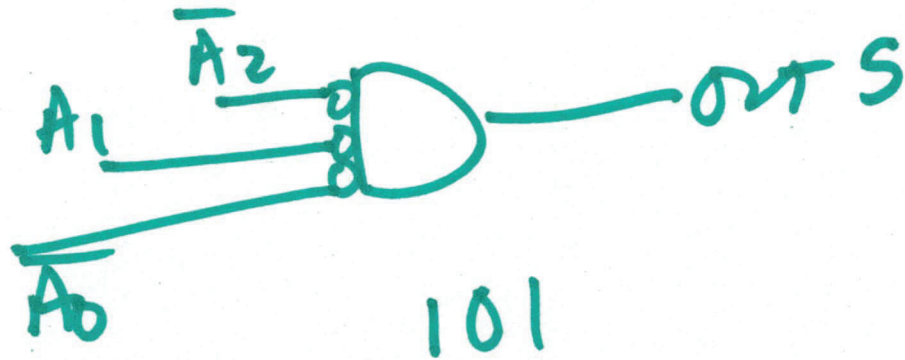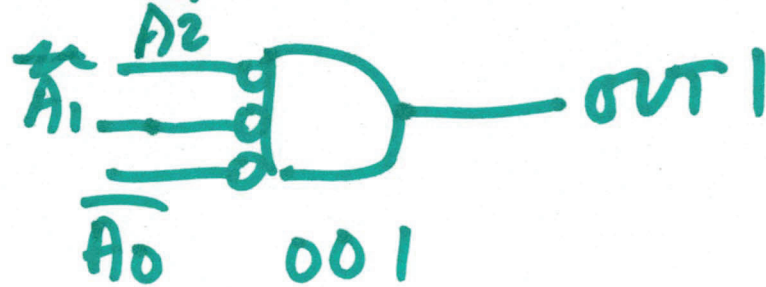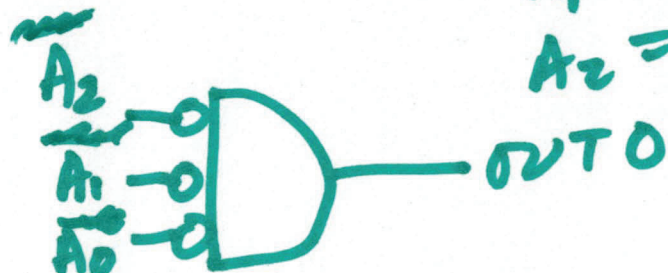

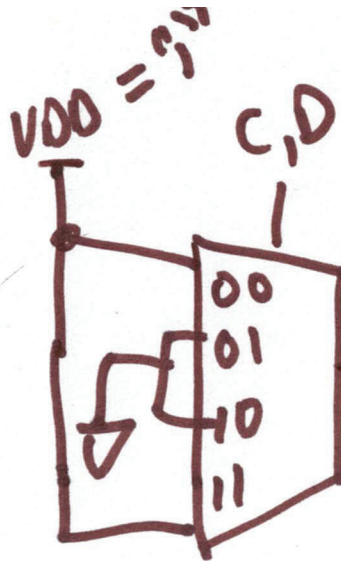

$$z = \cancel{X} \cancel{X}$$

$$X + Y\bar{X} = X + Y$$

$$Y = A + \bar{A}(\bar{C}\bar{D} + CD)$$

$$Y = A + \bar{C}\bar{D} + CD$$

AC		00	01	11	10
		D	1	0	1
D	0	1	0	1	1
	1	0	1	1	1

