

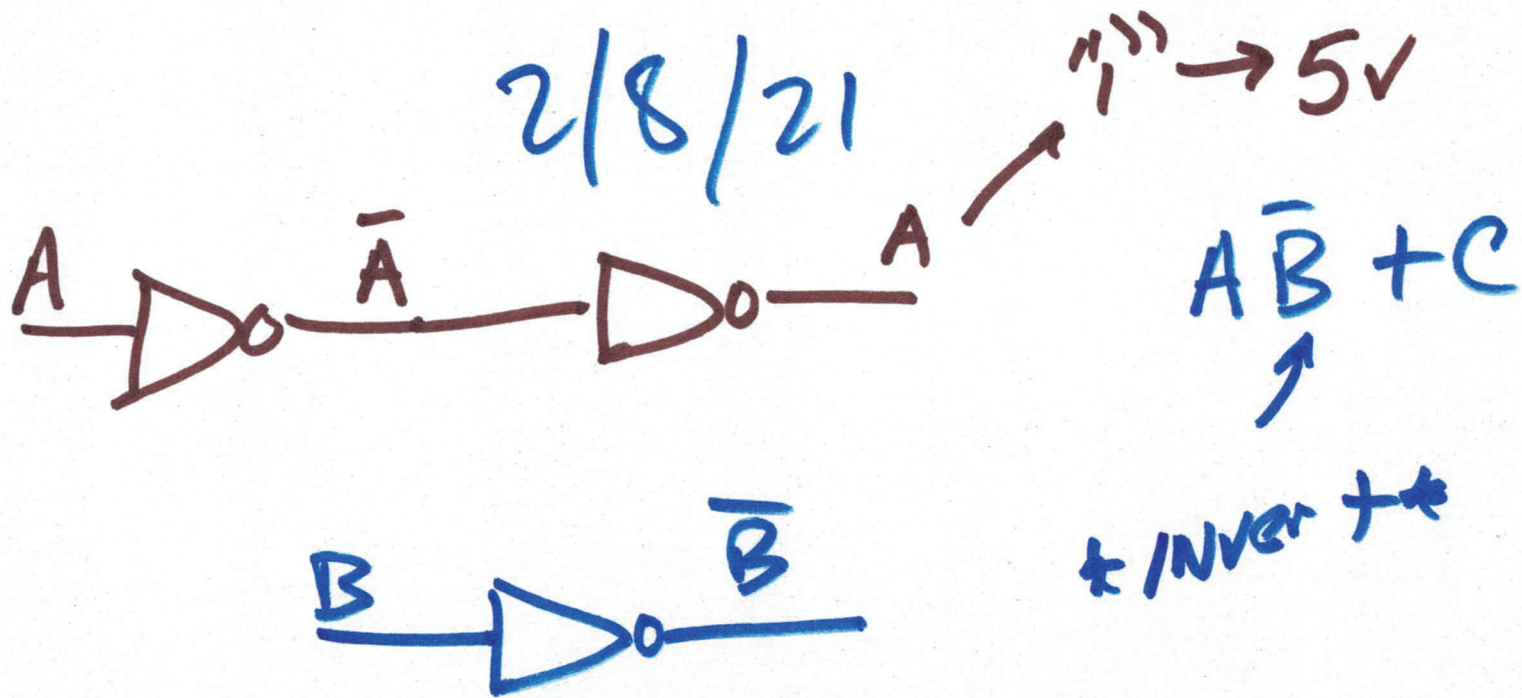
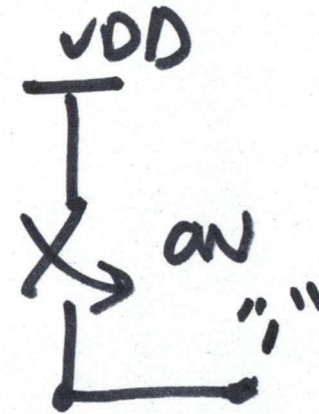
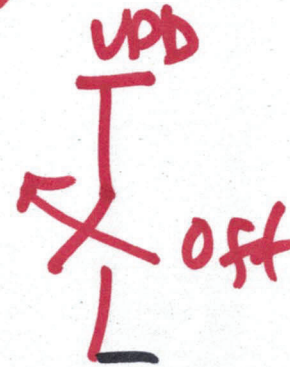
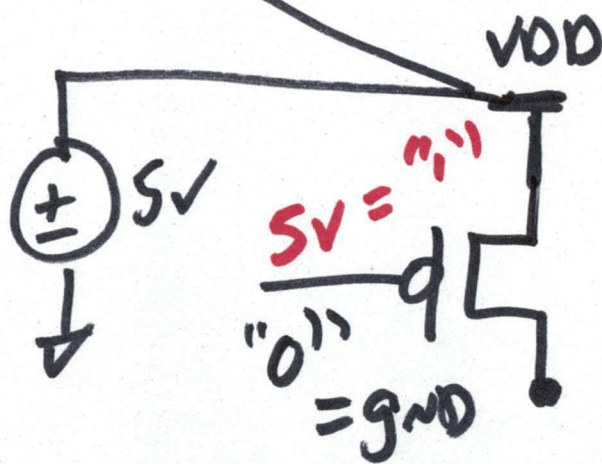
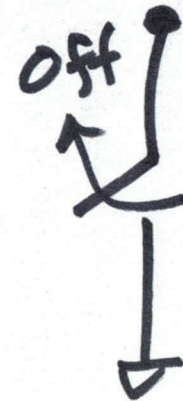
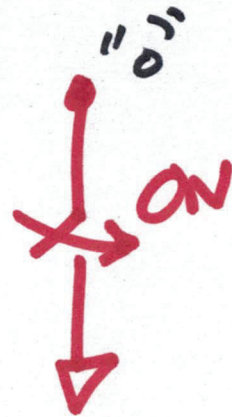



# CPE 100 Digital Logic Design

## Lecture 6

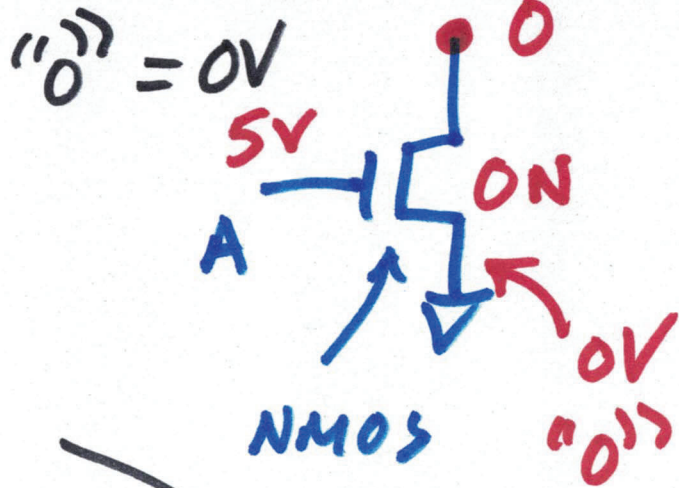

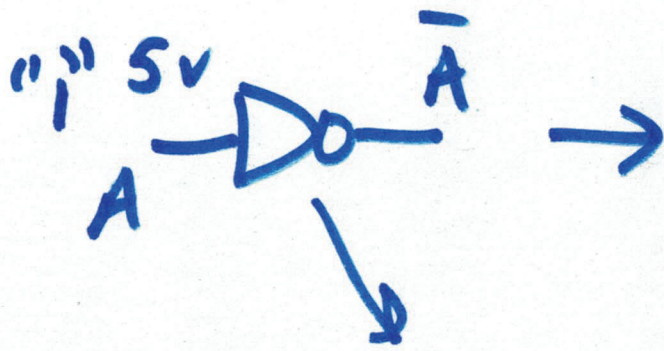

2)

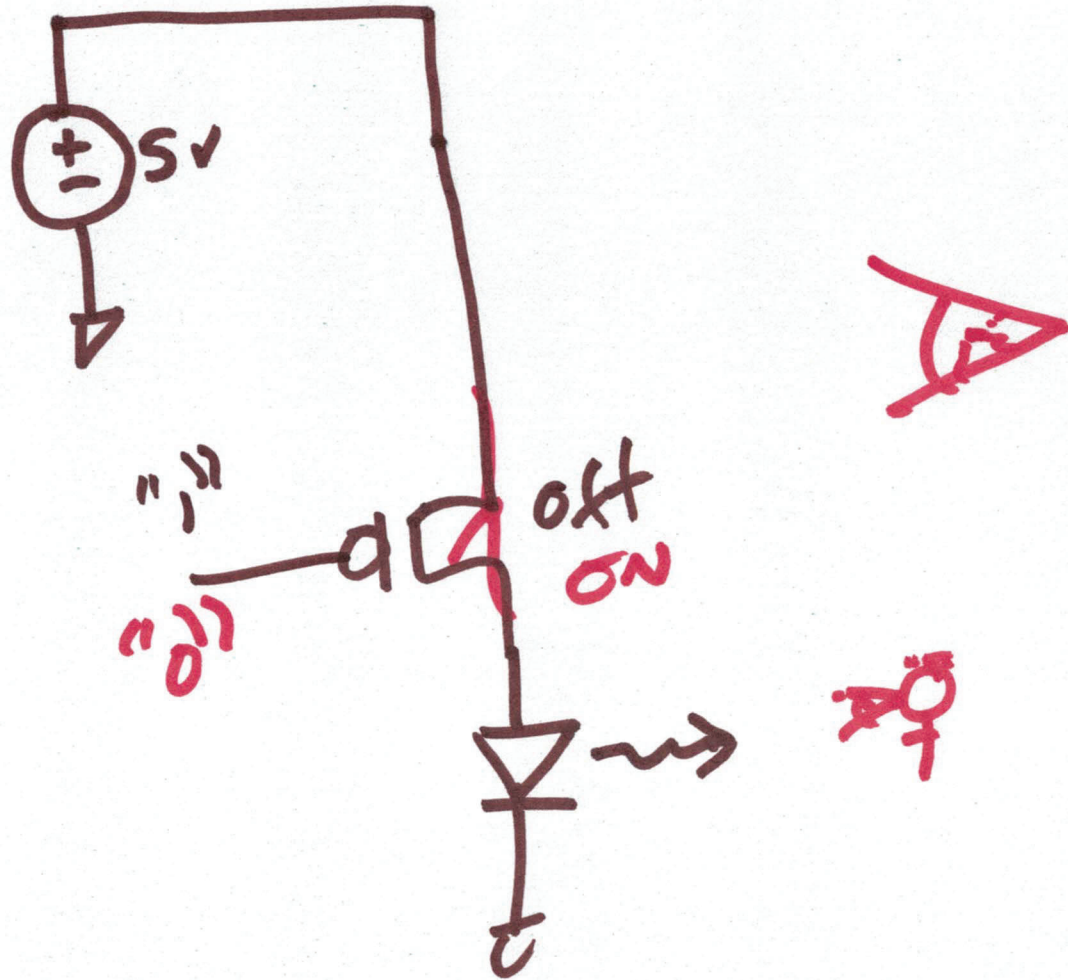


3)

$$z = A\bar{B} + C$$

1 0    ↑ OR

inverts  
AND  
OR

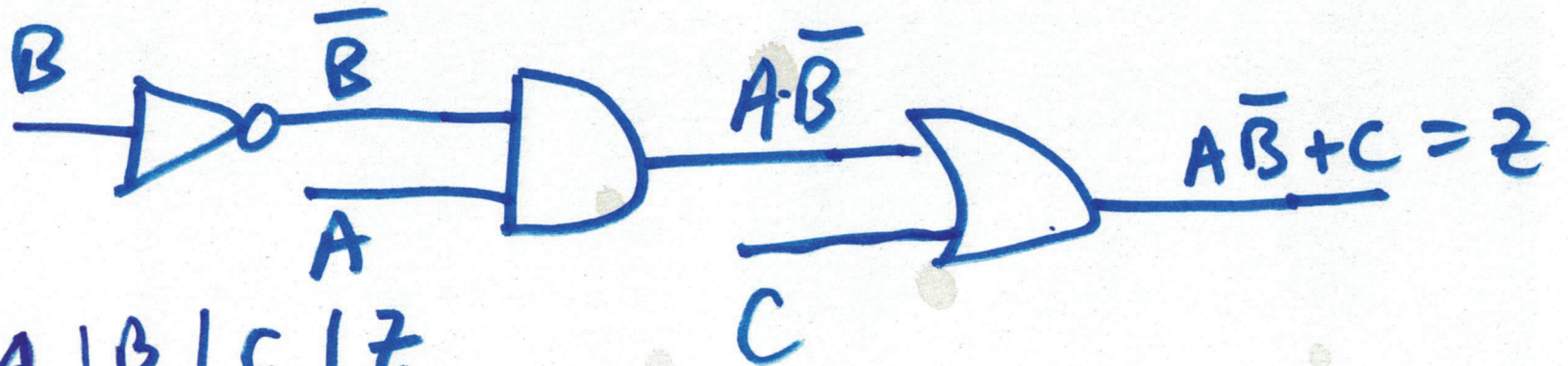


A	B	C	z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

4)

$$A + \bar{A} = 1 \rightarrow A + 1 = 1$$

$$A\bar{A} = 0 \quad A \cdot 0 = 0$$
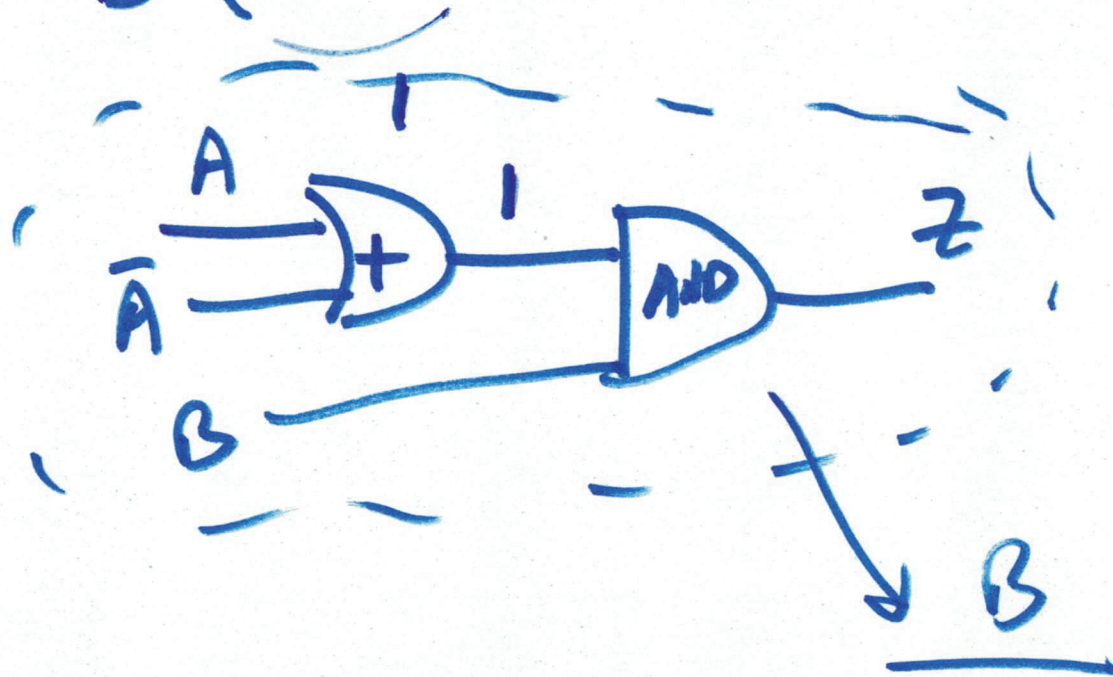
$$B \cdot (A + \bar{A}) = Z \quad 1 \cdot B = B$$



A	B	XOR
0	0	0
0	1	1
1	0	1
1	1	0

$$\overline{A} \cdot B + A \cdot \overline{B} = \text{XOR}$$

Sum of products

$$(A + B) \cdot (\overline{A} + \overline{B}) = \text{XOR}$$

Product of sums

