

Quiz #10 CpE 100 Spring 2021

Name: _____

Open book and closed notes.

Show your work for credit and place a box around your answers.

1. Simplify the logic function in Exercise 2.13(b) (not (a) or (c)) using Karnaugh maps. Then sketch the logic gate implementation. (4 points)