

Quiz #11 CpE 100 Spring 2021

Name: \_\_\_\_\_

Open book and closed notes.

**Show your work for credit and place a box around your answers.**

1. Write the Boolean equation describing the logic circuit seen in Fig. 2.84 of the book. (3 points)