

Open book and closed notes.

Show your work for credit and place a box around your answers.

1. The following two traces are applied to a DFF. The D (data) input is the top trace in blue while the clock input (CLK) is the bottom trace in black. Sketch the corresponding Q output of the DFF. (3 points)

