

Open book and closed notes.

Show your work for credit and place a box around your answers.

1. The following shows a clock signal (the black waveform below) clocking a D Flip-Flop. Assuming the Q output is initially a logic 0 sketch how the Q output changes on the rising edge of the clock signal. (3 points)

