

Quiz #16 CpE 100 Spring 2021

Name: _____

Open book and closed notes.

Show your work for credit and place a box around your answers.

1. Sketch the state diagram for a state machine that can detect the serial input sequence 01010. (4 points)