

Quiz #17 CpE 100 Spring 2021

Name: _____

Open book and closed notes.

Show your work for credit and place a box around your answers.

1. Sketch the state diagram, and hardware implementation for a state machine that can detect a 0 to 1 transition, that is, the sequence 01. (4 points)