

Quiz #18 CpE 100 Spring 2021

Name: _____

Open book and closed notes.

Show your work for credit and place a box around your answers.

1. Sketch the gate-level implementation of a full-adder. (4 points)