

Quiz #20 CpE 100 Spring 2021

Name: _____

Open book and closed notes.

Show your work for credit and place a box around your answers.

1. Design a 3-bit row decoder using only 3-input NAND gates. Hint: an inverter is formed with a 3-input NAND gate by tying all inputs of the NAND gate together. (4 points)