

Quiz #21 CpE 100 Spring 2021

Name: _____

Open book and closed notes.

Show your work for credit and place a box around your answers.

1. Design a 3-bit row decoder using only 3-input NOR gates. (4 points)