

Quiz #22 CpE 100 Spring 2021

Name: _____

Open book and closed notes.

Show your work for credit and place a box around your answers.

1. Design a 4-bit down counter using D Flip-Flops. (4 points)