

Quiz #6 CpE 100 Spring 2021

Name: _____

Open book and closed notes.

Show your work for credit and place a box around your answers.

1. Write the truth table for $A\bar{C} + B$ and sketch the logic gate implementation. (3 points)