

Quiz #8 CpE 100 Spring 2021

Name: _____

Open book and closed notes.

Show your work for credit and place a box around your answers.

1. Sketch the implementation of a 2-input XOR gate using 2-input NAND gates. (4 points)