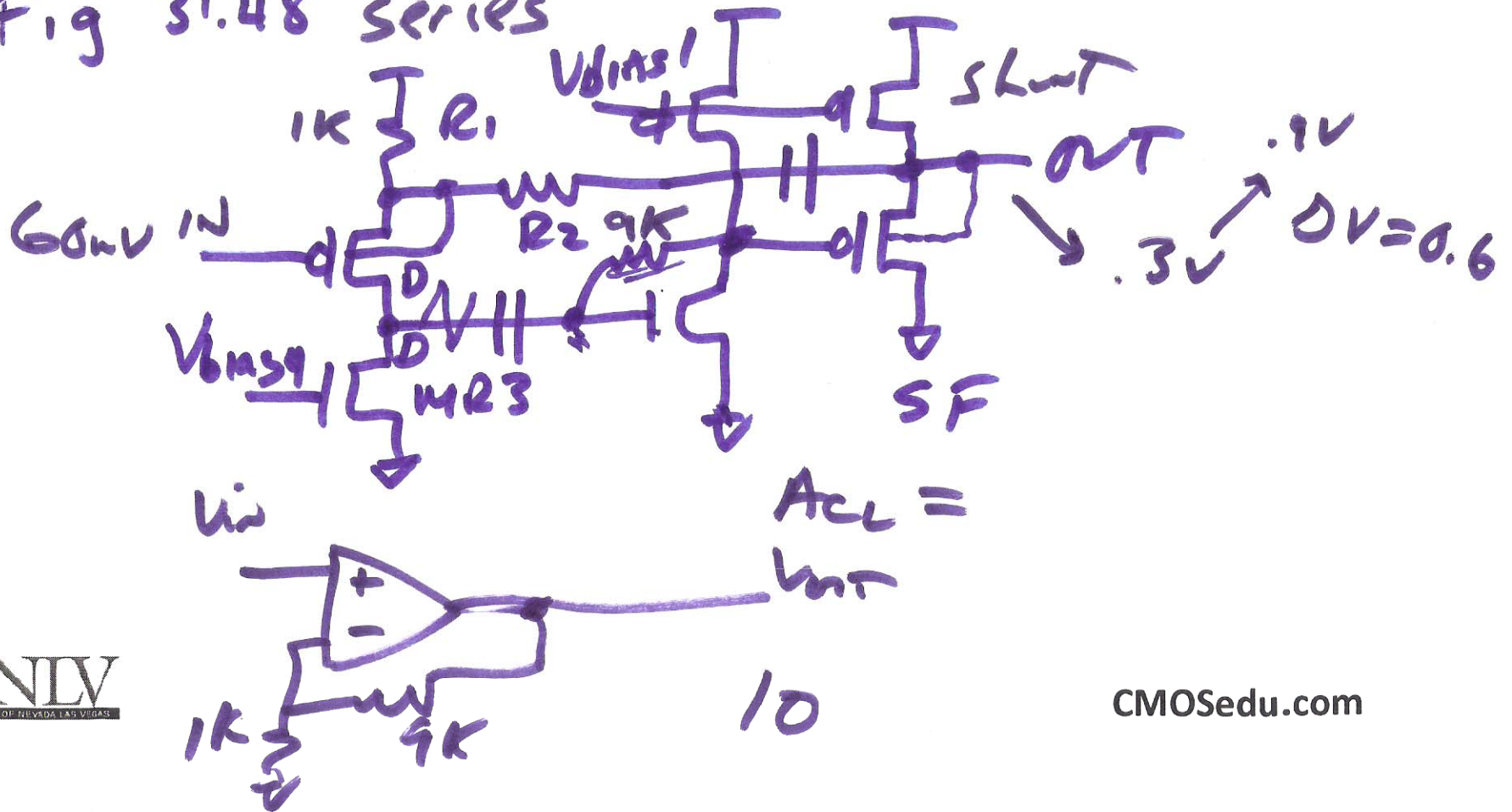




# ECE-720 Advanced Analog IC Design


OCT. 7, 2013

Lecture 12

Fig 31.48 series



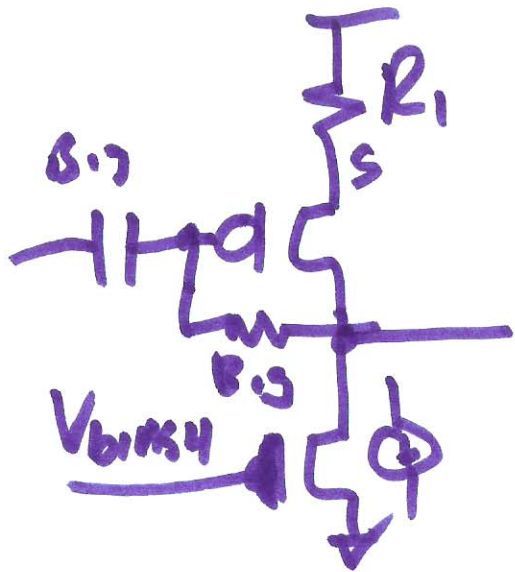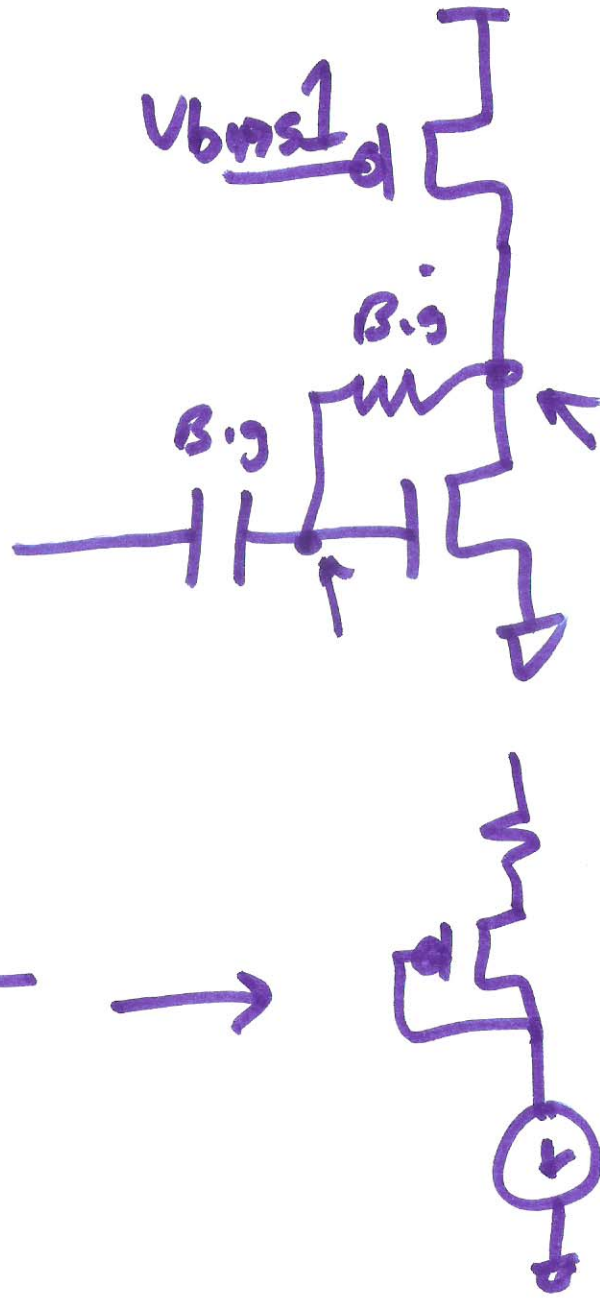

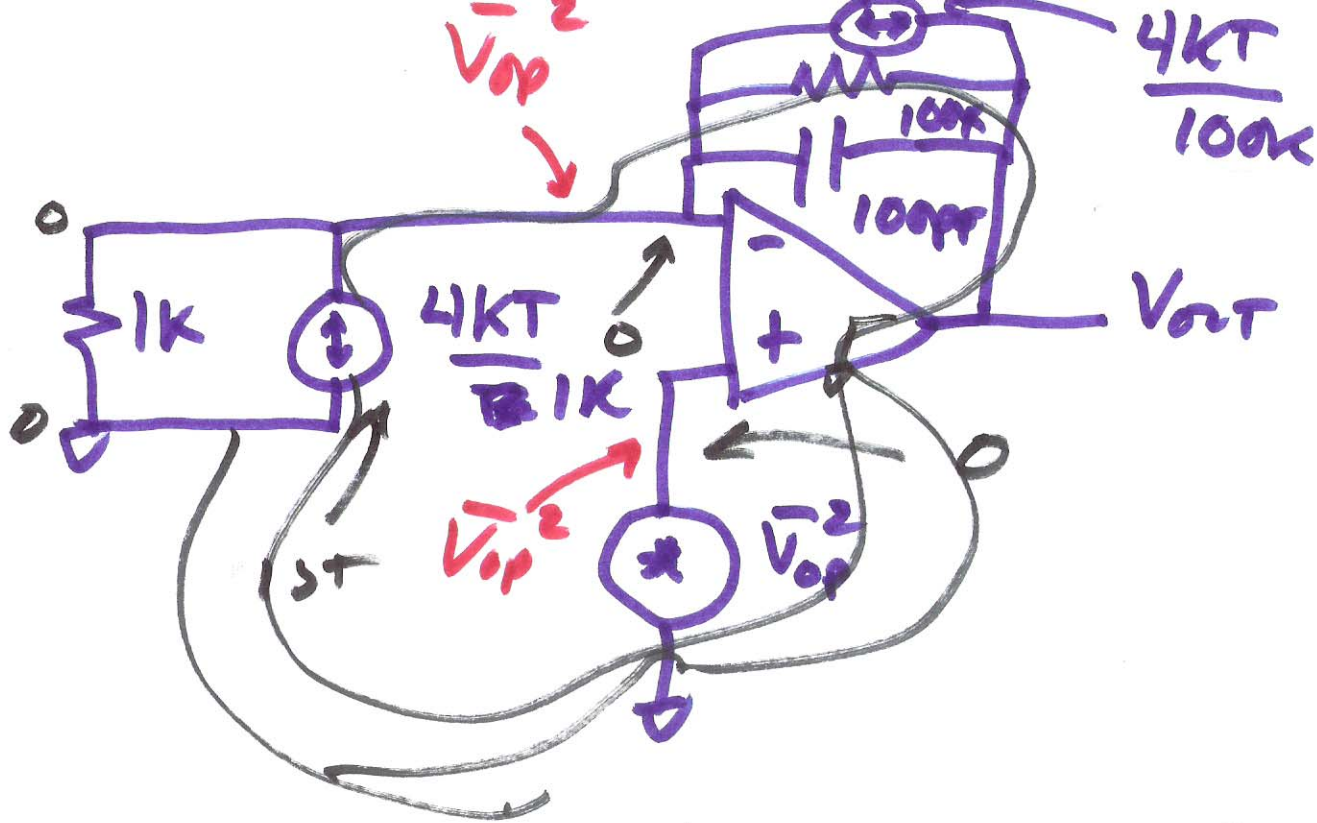


$$|A_{CL}(0)| = 100$$

$$100k = 10^5$$

$$100p = 10^{-10}$$

$$\overline{V_{noise}^2} = \left( \frac{4KT}{1k} + \frac{4KT}{100k} \right) \cdot \left| \frac{100k}{1 + j\omega \cdot 10^{-5}} \right|^2$$

$$+ \overline{V_{op}^2} \left( \frac{1 + \left| \frac{100k}{1 + j\omega \cdot 10^{-5}} \right|}{1k} \right)^2$$

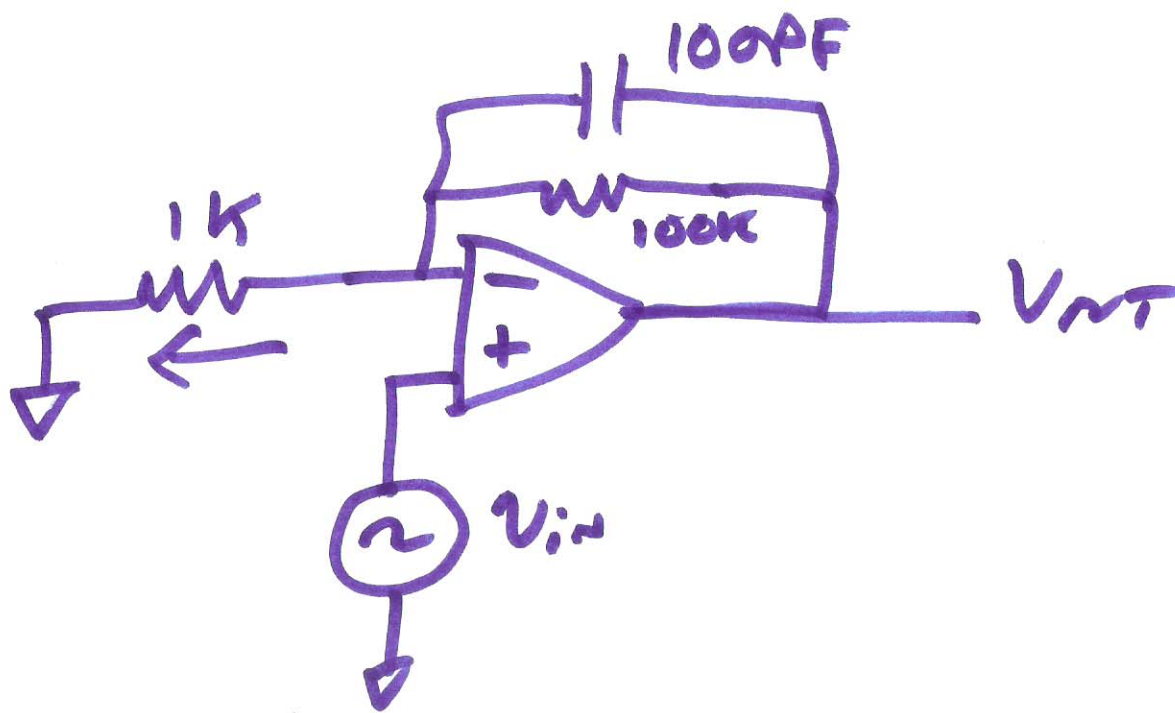

$$\frac{v_{in}}{1k} = \frac{v_{out} - v_{in}}{100k} \cdot \frac{1}{1 + j\omega \cdot 10^{-5}}$$

$$v_{in} \left( \frac{1}{1k} + \frac{1}{\frac{100k}{1 + j\omega \cdot 10^{-5}}} \right) = \frac{v_{out} \cdot \frac{100k}{1 + j\omega \cdot 10^{-5}}}{\frac{100k}{1 + j\omega \cdot 10^{-5}}}$$

4)

$$\frac{V_{out}}{V_{in}} = 1 + \frac{100k}{1k} \frac{1}{1 + j\omega 10^{-5}}$$



$$= 1 + \frac{100k}{1k} \frac{1}{1 + j\omega 10^{-5}}$$

AT  $f_{3dB}$

$$\frac{V_{out}}{V_{in}} = 0.707 \cdot (101)$$

$$f_{3dB} \approx \frac{1}{2\pi 10^{-5}} = 15.9 \text{ kHz}$$
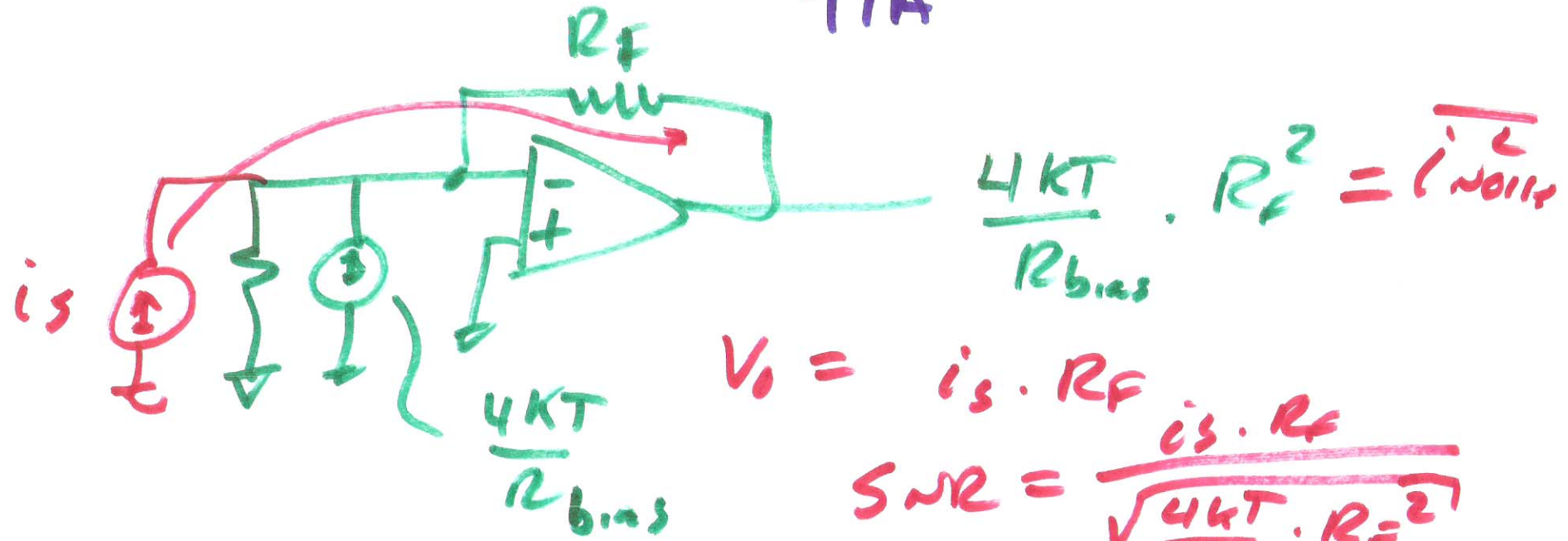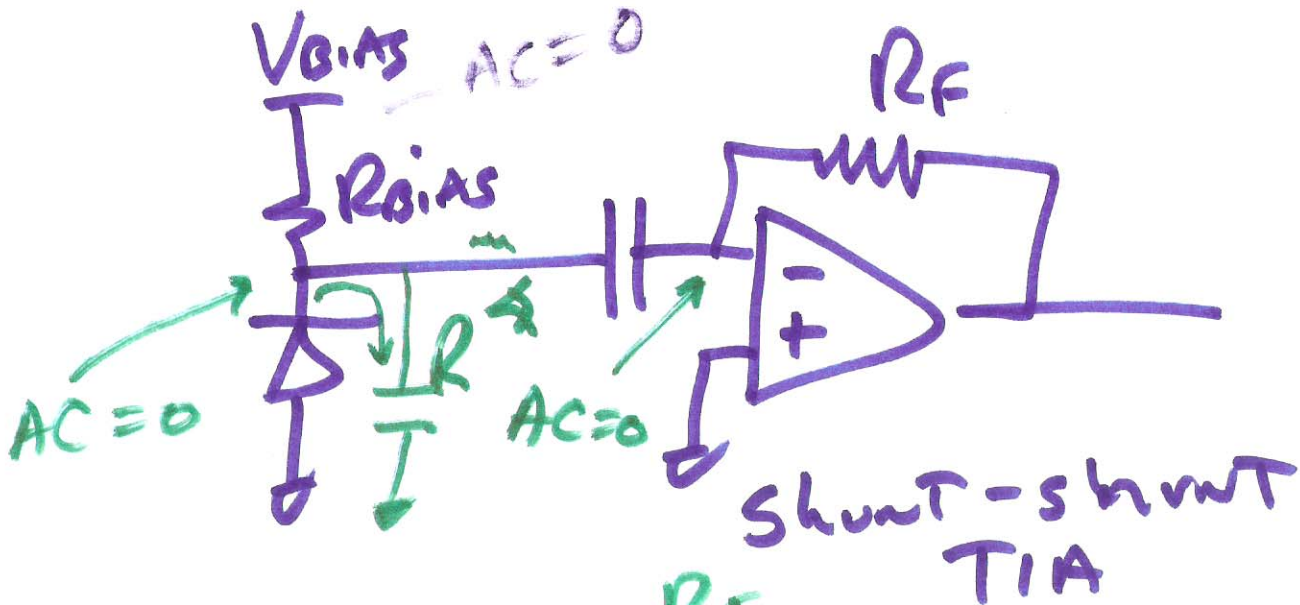
$$\Delta V = \Delta I \cdot R \rightarrow 0$$





$$\frac{4kT}{R_{bias}} \cdot R_F^2 = \overline{i_{noise}^2}$$

$$V_o = i_s \cdot R_F$$

$$SNR = \frac{i_s \cdot R_F}{\sqrt{\frac{4kT}{R_{bias}} \cdot R_F^2}}$$

6)

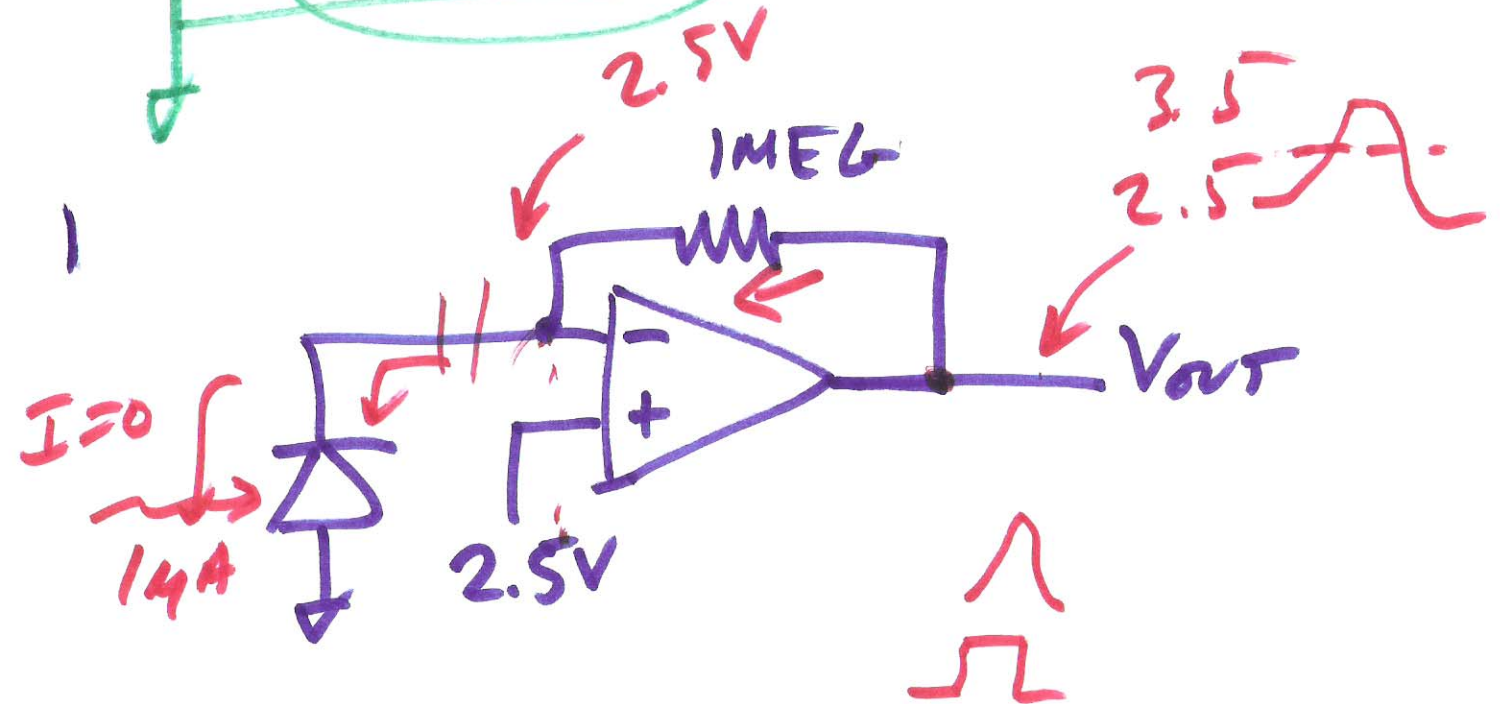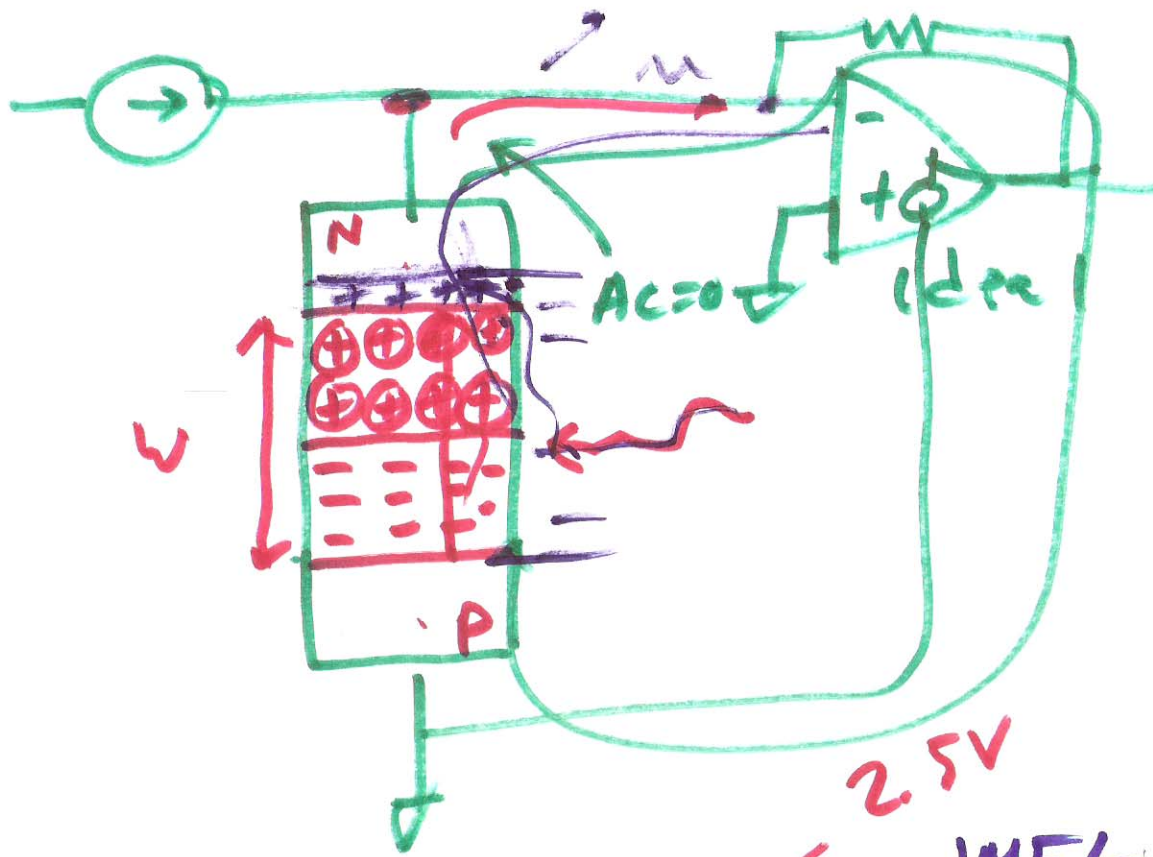

7)