


ELG 720

Advanced Analog

IC Design

Feb. 19, 2016




Lecture 10

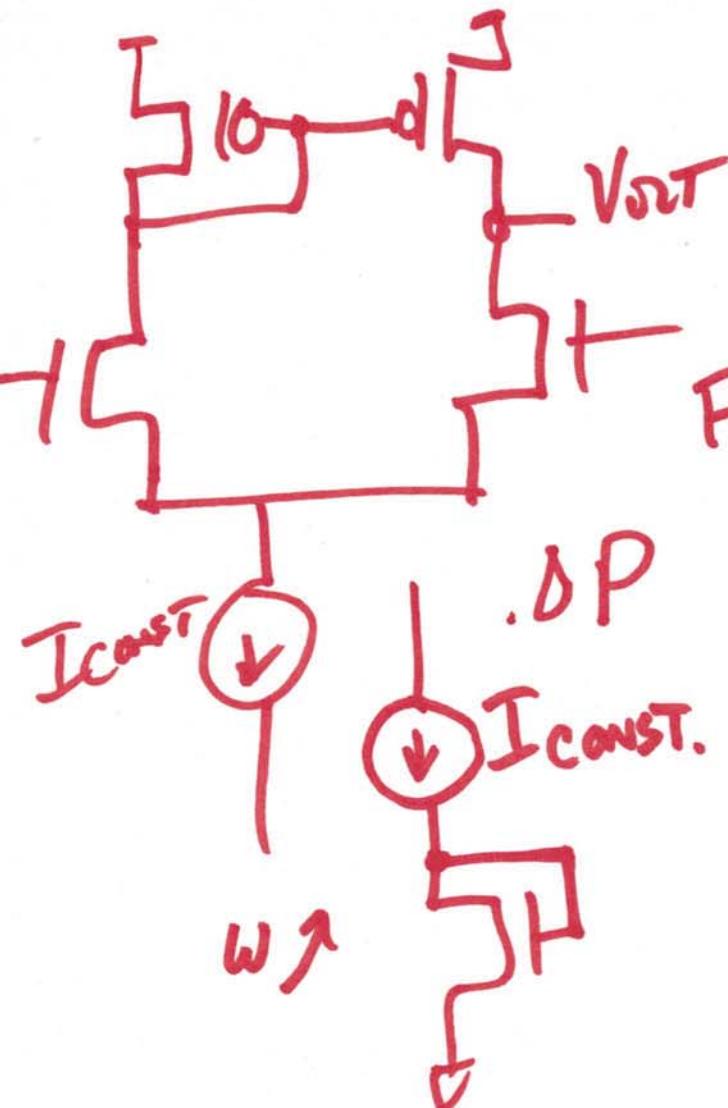

$V_{BS} \downarrow f_T \downarrow g_m r_o = \cancel{const.} \uparrow$

$$g_m \approx \sqrt{2kP_L \cdot I_D}$$

$$r_o \approx \frac{1}{\lambda I_D}$$

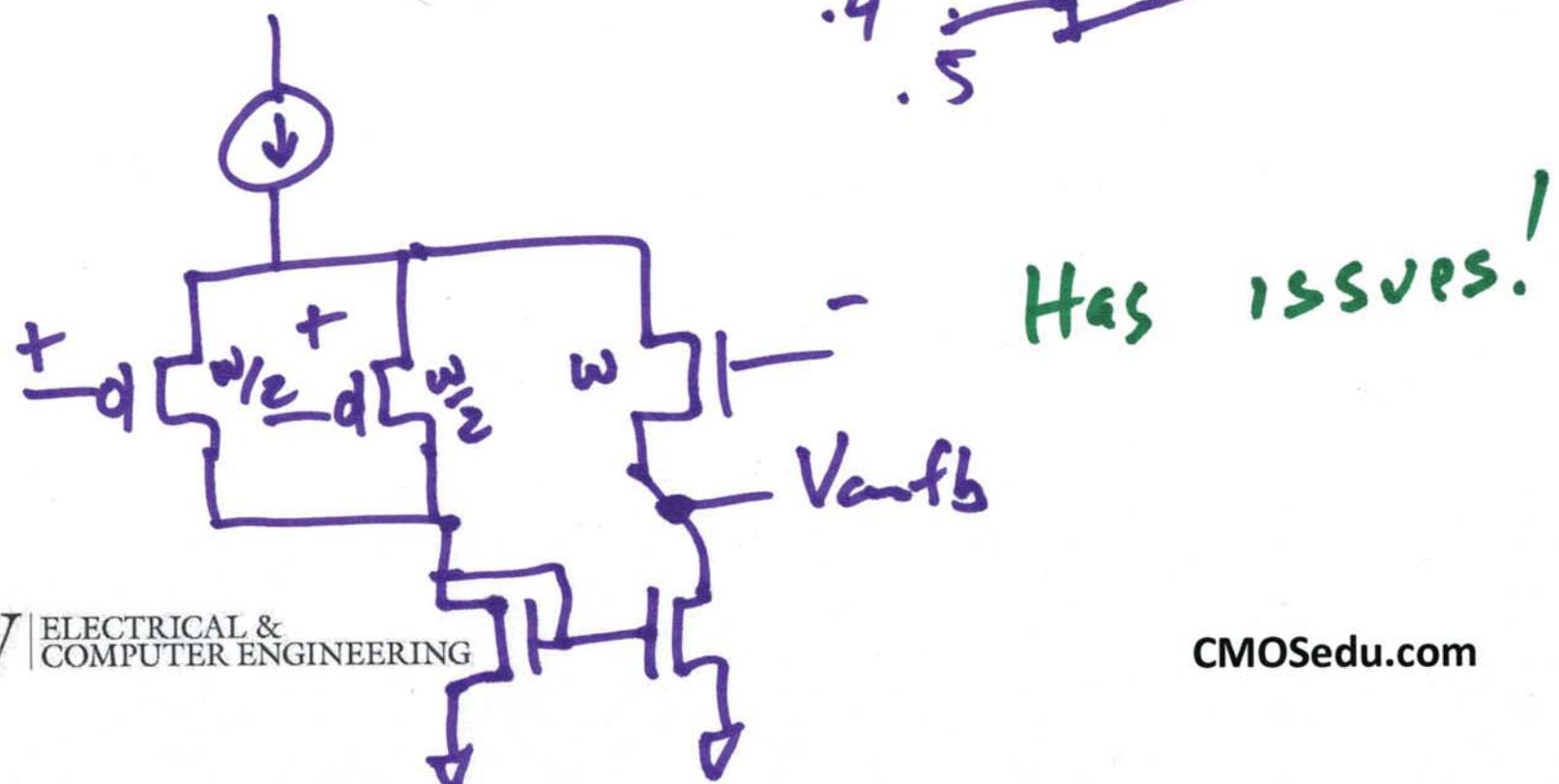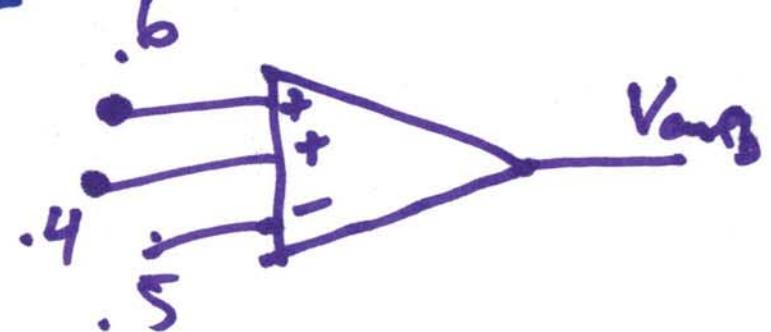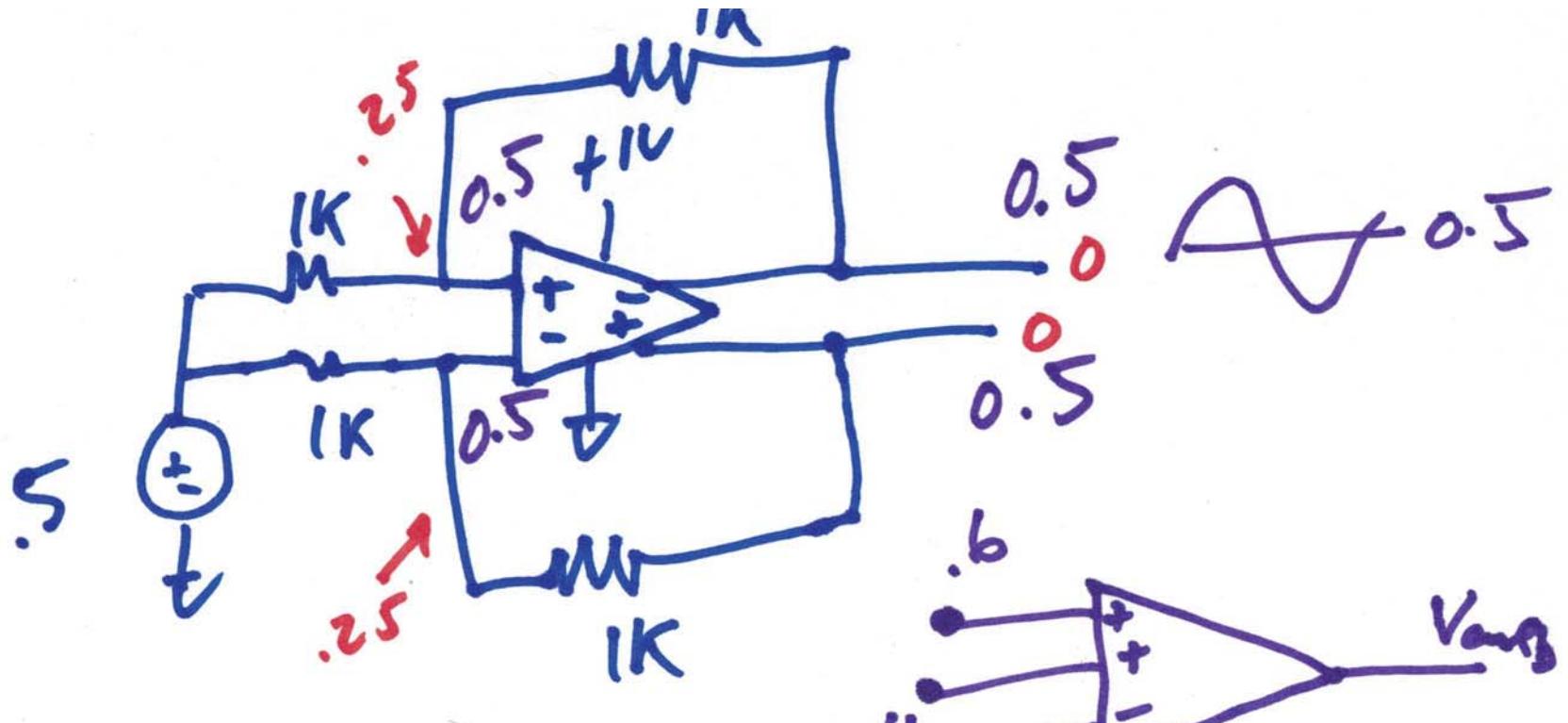

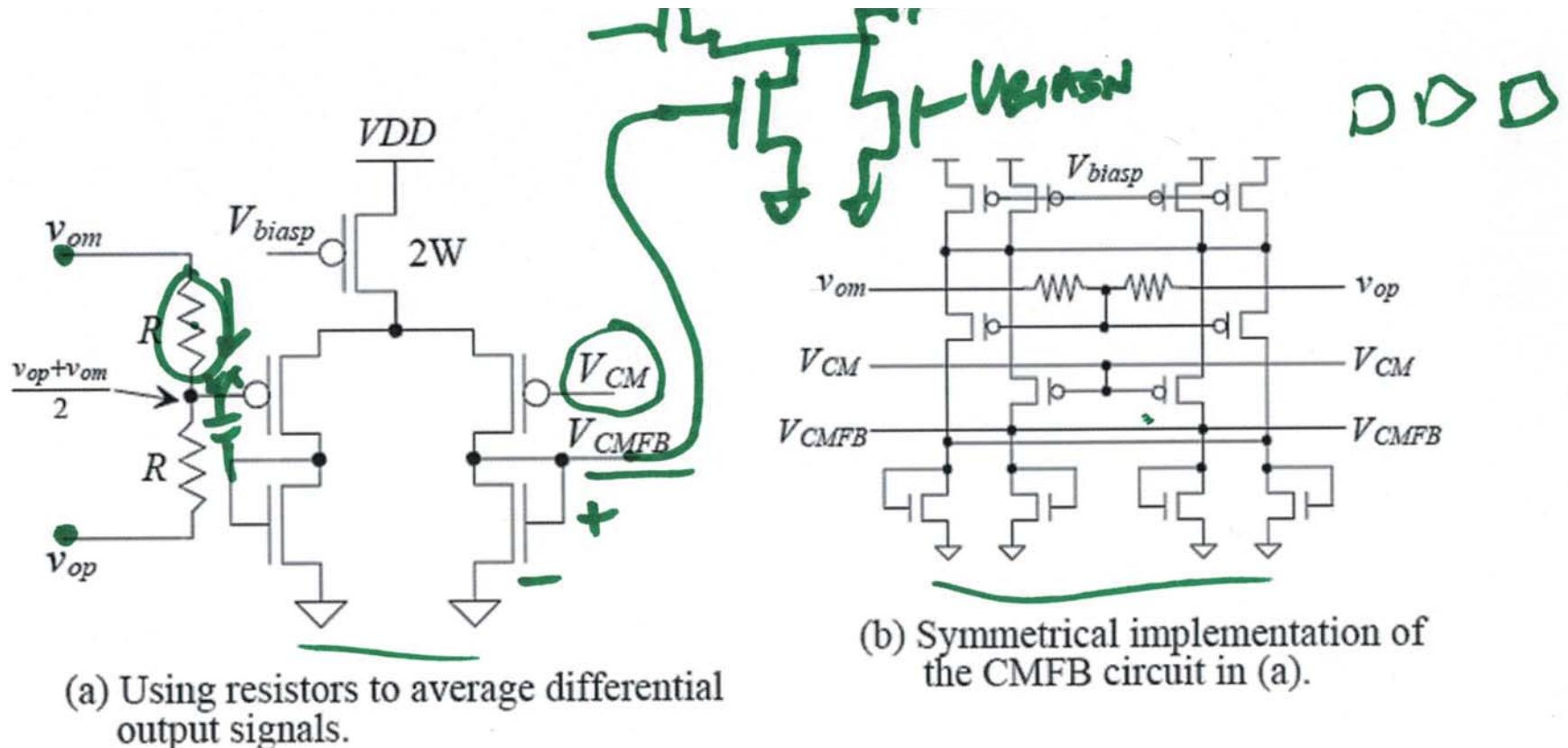


Figure 26.14 Increasing CMFB amplifier input range.

$$\frac{V_{om} - V_{op}}{2R}$$

$$\begin{aligned}
 V_x &= V_{om} - \frac{V_{om} - V_{op}}{2R} \cdot R \\
 &= \frac{2V_{om}}{2} + \frac{V_{op} - V_{om}}{2} \\
 &= \underline{\underline{\frac{V_{op} + V_{om}}{2}}}
 \end{aligned}$$

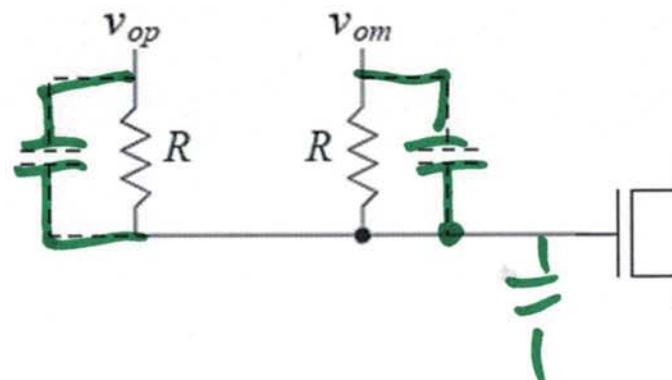


Figure 26.15 Adding parasitic capacitances across the resistors to compensate for the input capacitance of the MOSFET.

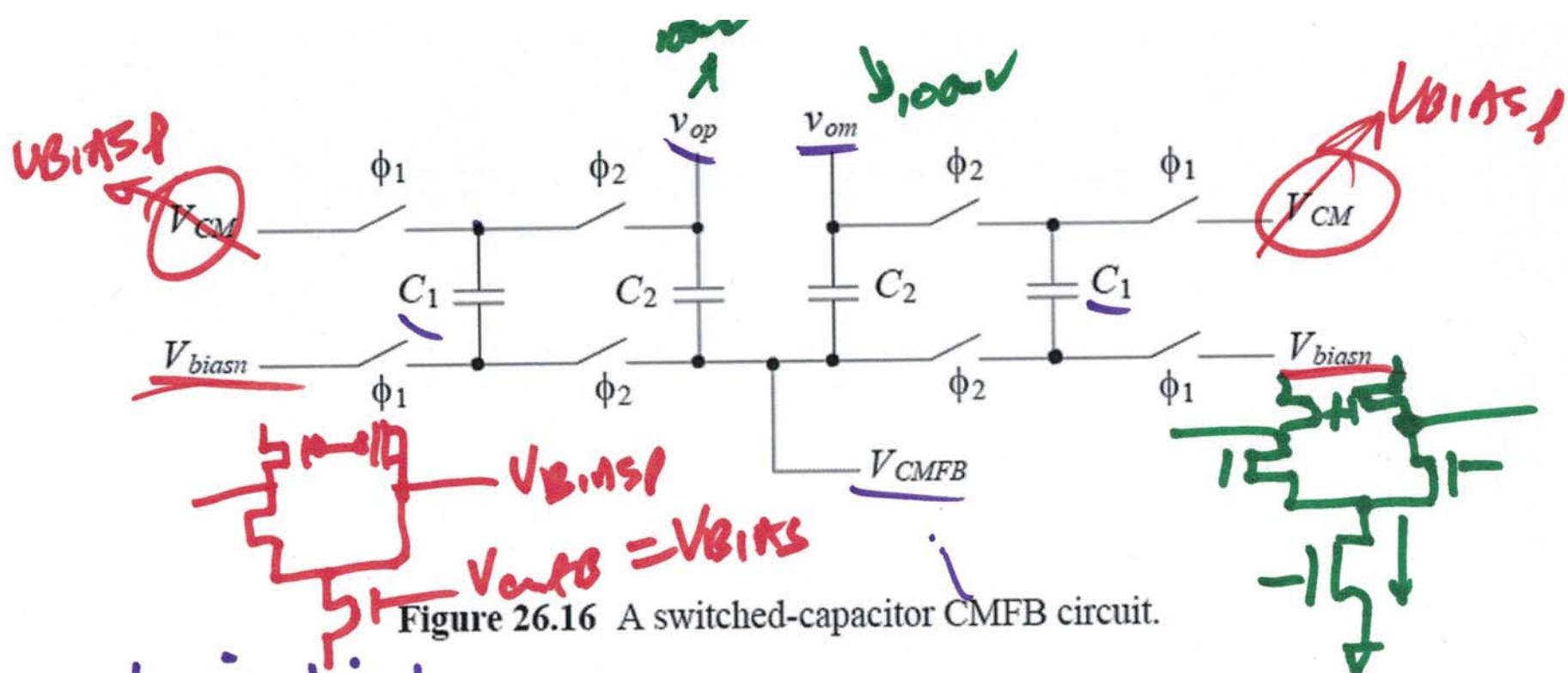


Figure 26.16 A switched-capacitor CMFB circuit.

ϕ_1 is high

$$q_1 = 2C_1(V_{biasn} - V_a) \quad .4 \quad .5$$

ϕ_2 is high

$$q_2 = C_1(V_{cmfb} - v_{op}) + C_1(V_{cmfb} - V_a) \quad .4 \quad .5$$

$$- .2 \quad + \textcircled{2}$$

$$\Delta V_{\text{diffB}} \cdot 2(C_1 + C_2) \propto (g_1 - g_2)$$

$$g_1 - g_2 = 2C_1 \left(V_{b, \text{esn}} - V_{\text{diffB}} + \frac{\frac{2g_1 + 2g_2}{2} - V_{\text{an}}}{Z} \right)$$

6)

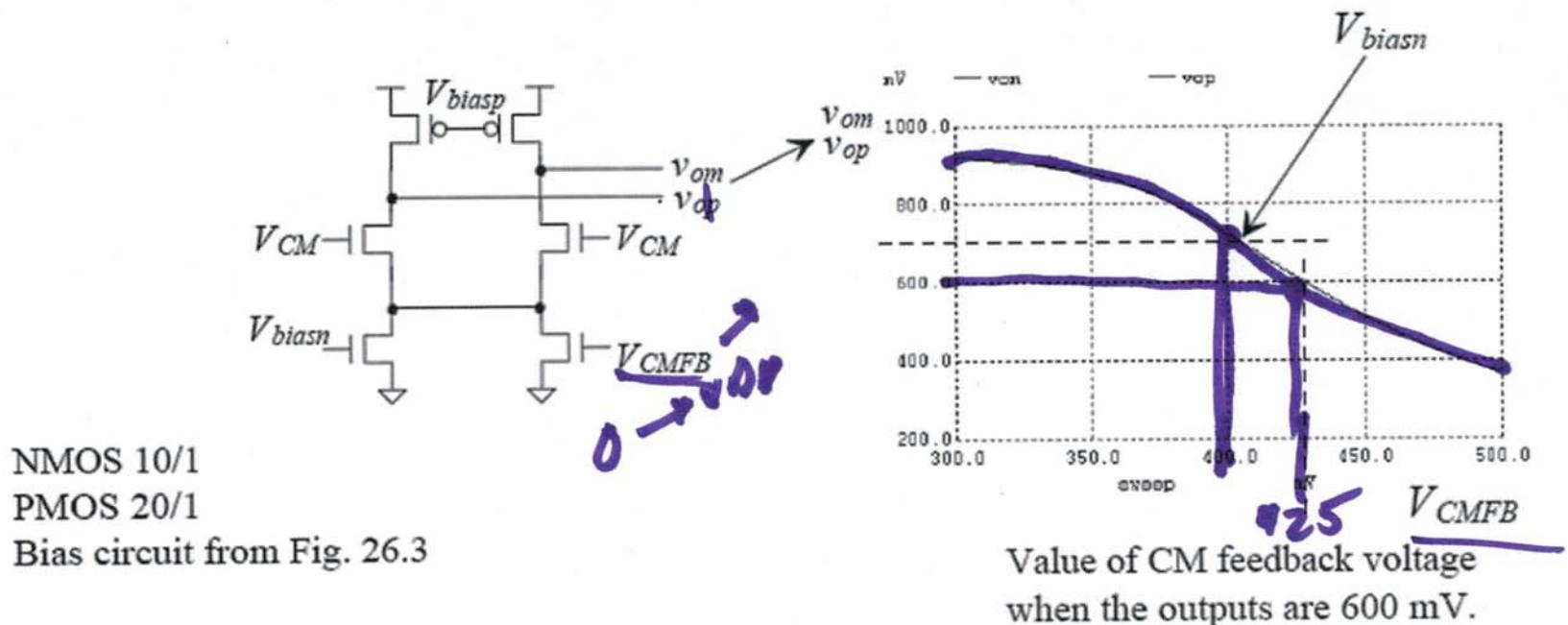


Figure 26.17 Plotting the output voltages as a function of the CM feedback voltage.

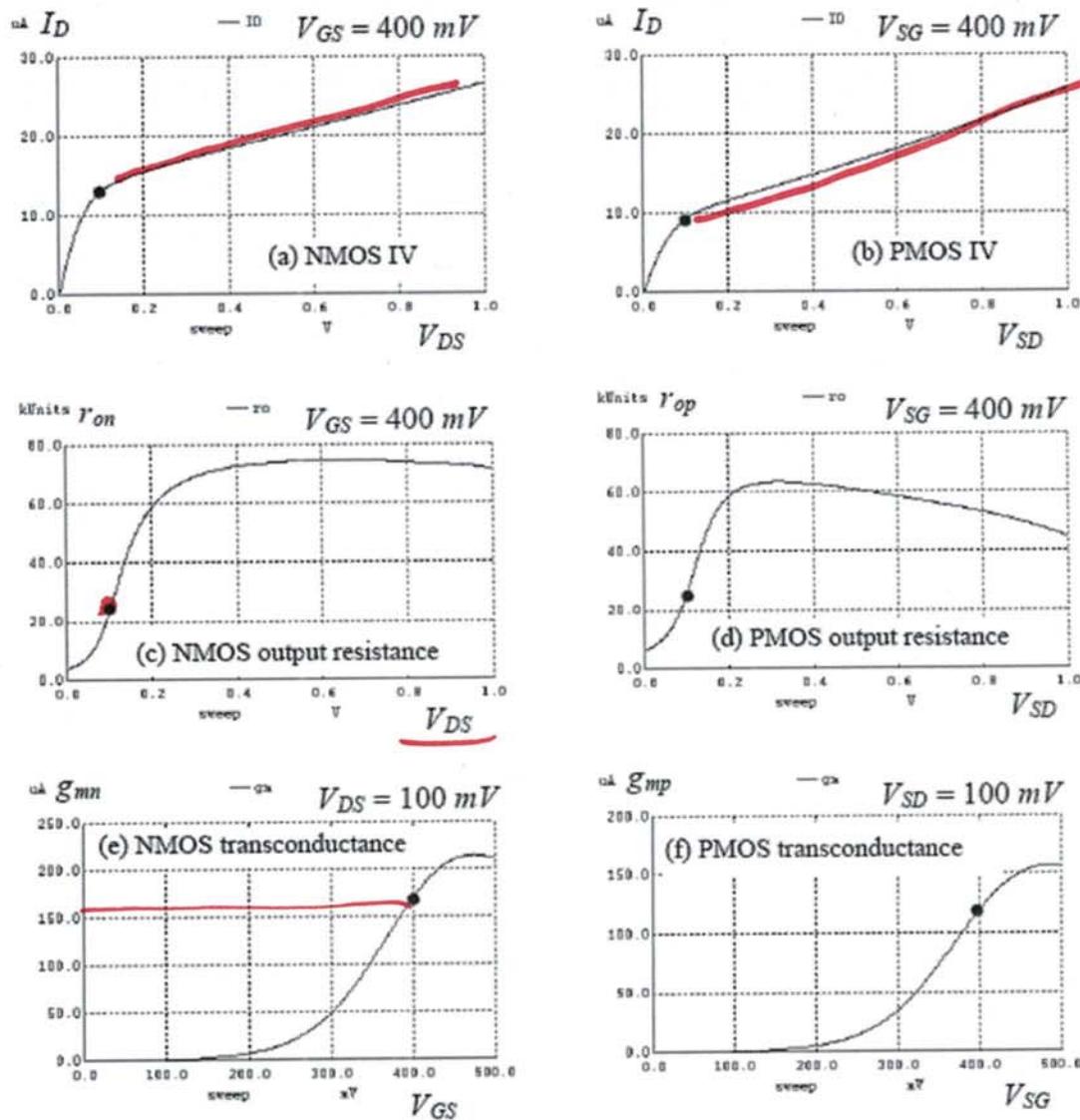


Figure 26.18 Characteristics of NMOS (10/1) and PMOS (20/1) devices.

$$\begin{aligned}
 & g_m r_0 \\
 & 30 \cancel{\times} kR = r_0 \\
 & \cancel{B} \\
 & g_m = 150 \times 10^4 \\
 & 0.03 \times 10^6 \times \\
 & 150 \times 10^{-6} \\
 & = \underline{4.5}
 \end{aligned}$$

NMOS are 10/1
PMOS are 20/1
Bias circuit in Fig. 26.3

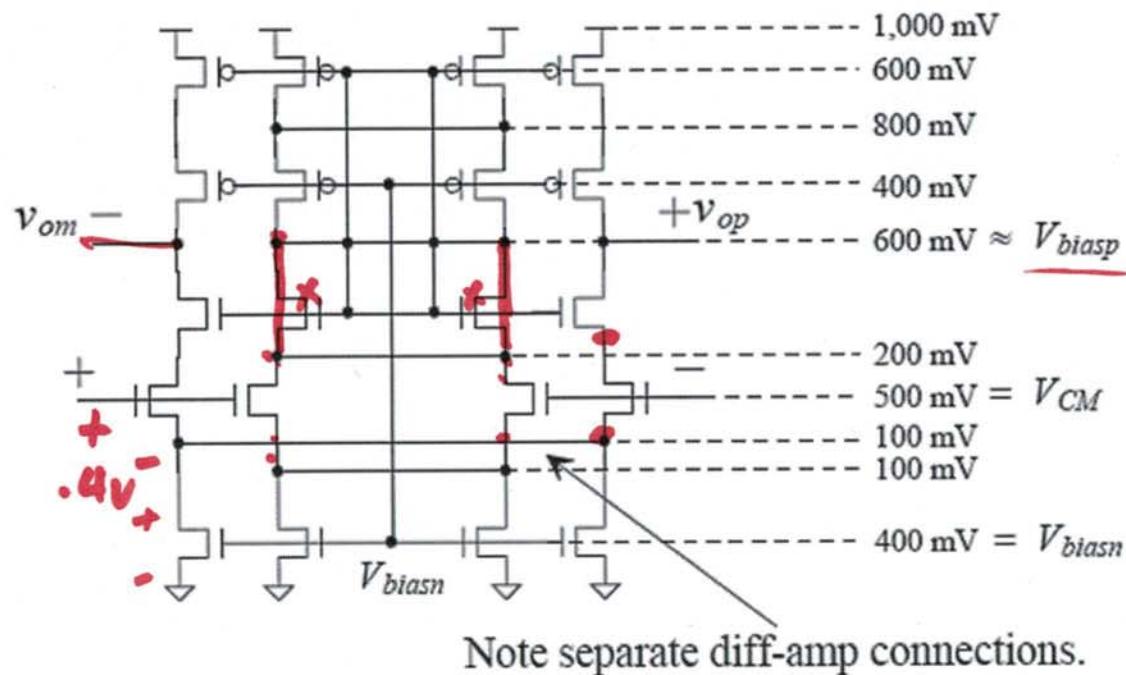


Figure 26.19 Fully-differential cascode diff-amp.



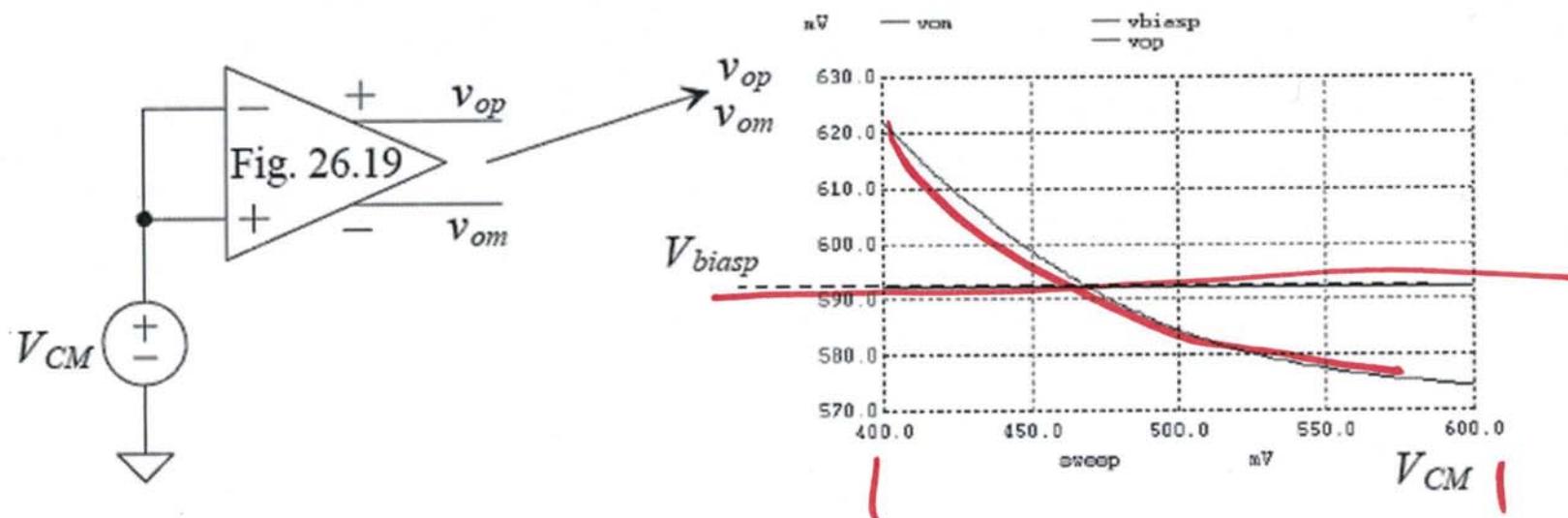
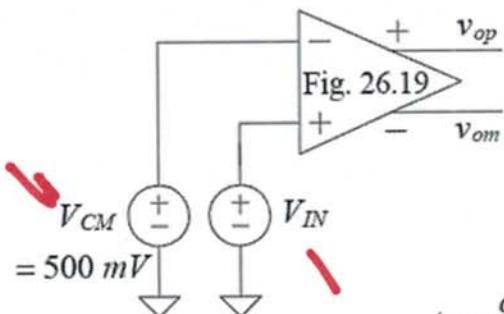


Figure 26.20 Varying the common-mode voltage and looking at the output.

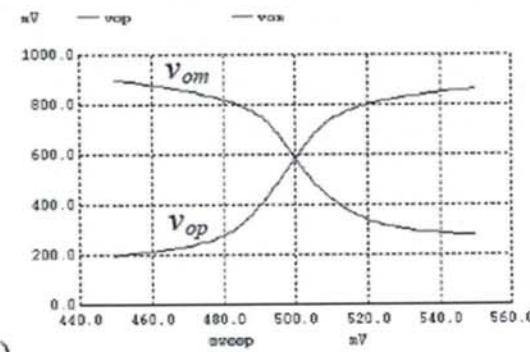
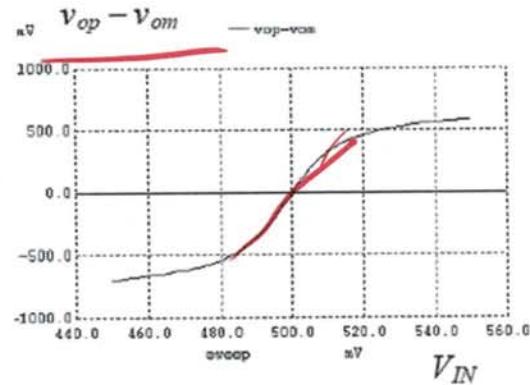
$$A_V = \frac{d(v_{op} - v_{om})}{dV_{IN}}$$



40

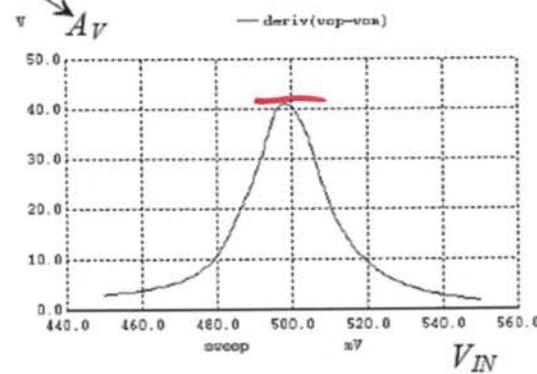


Figure 26.21 DC behavior and gain of the diff-amp in Fig. 26.19.

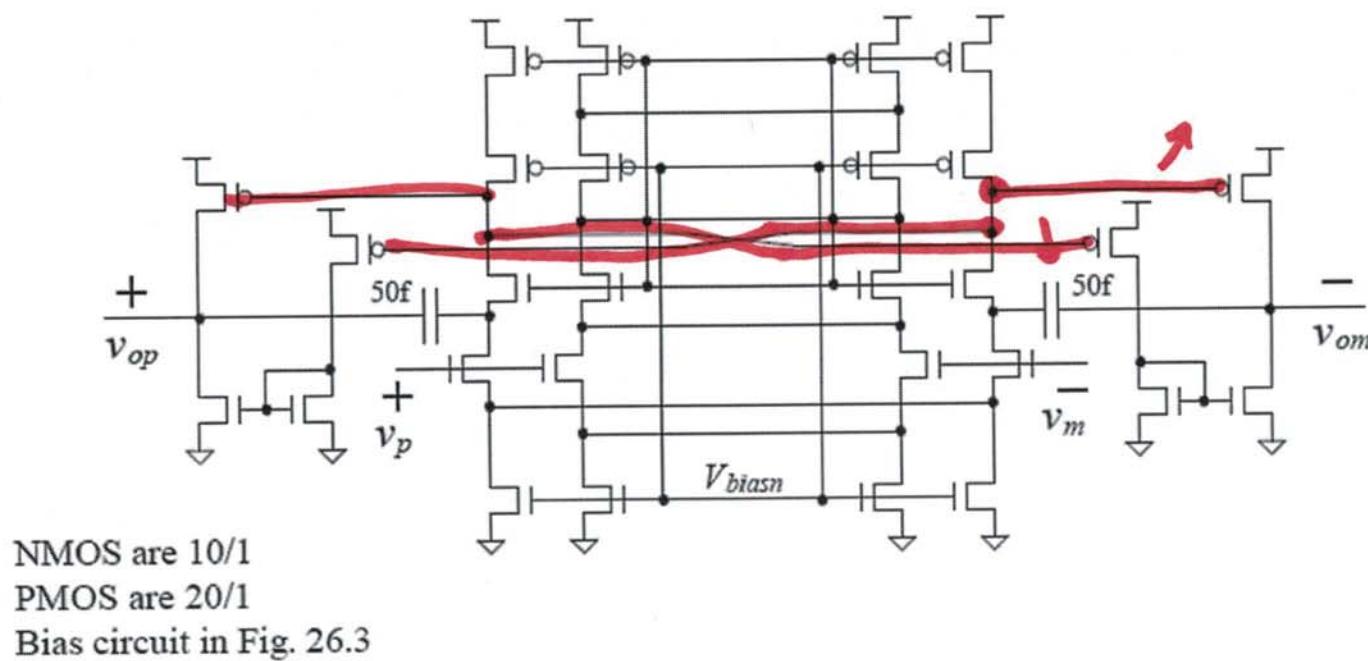


Figure 26.22 Basic two-stage op-amp without CMFB.


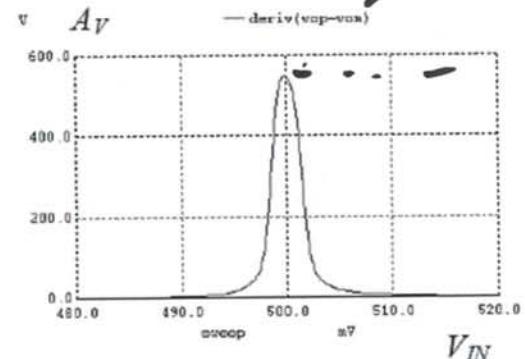
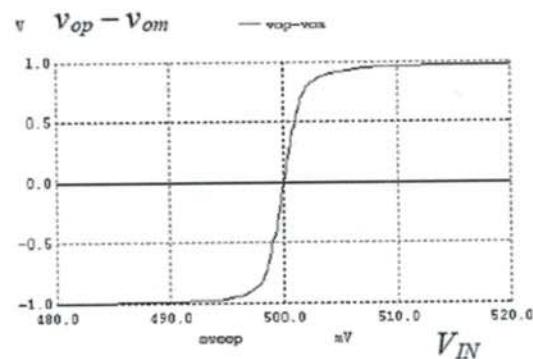
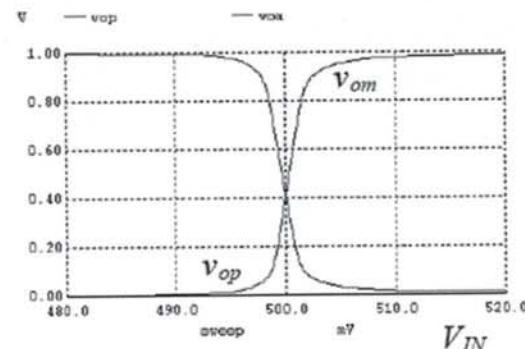
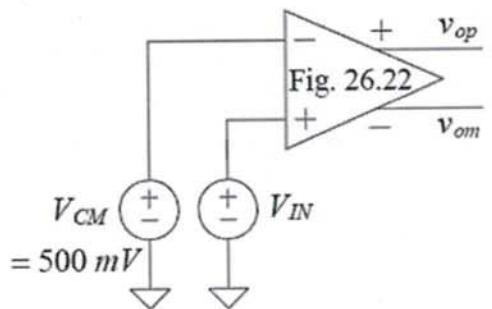


Figure 26.23 DC behavior and gain of the op-amp in Fig. 26.22.

$$.6 - .4 = 20 \text{mV}$$

~~-20mV~~
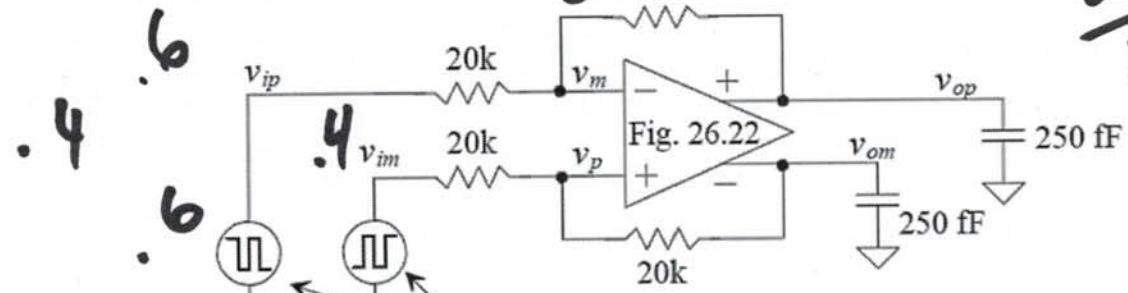
$$\frac{200 \text{mV}}{20k} = 10 \mu\text{A}$$



.6
.4
.6
Inputs swing from 300 mV to 700 mV around 500 mV.

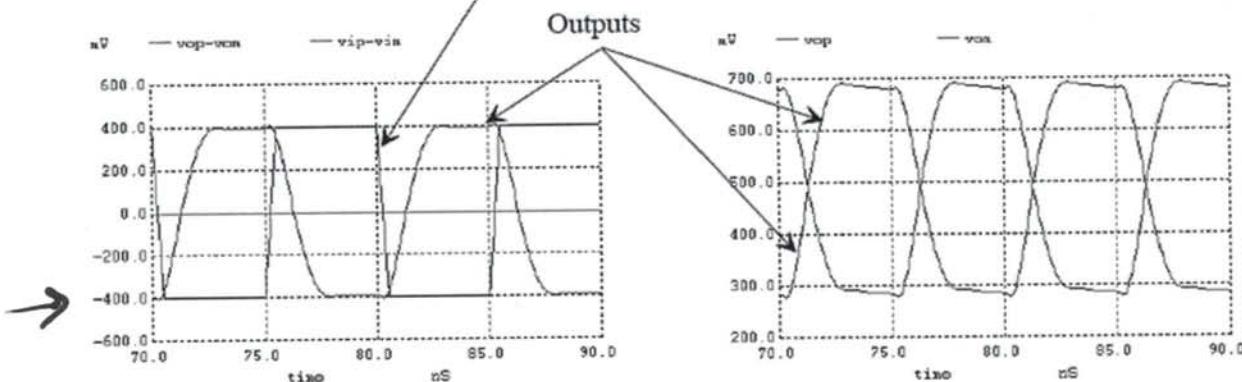


Figure 26.24 Step response of the op-amp in Fig. 26.22 driving 250 fF load capacitors and 20k feedback resistors.

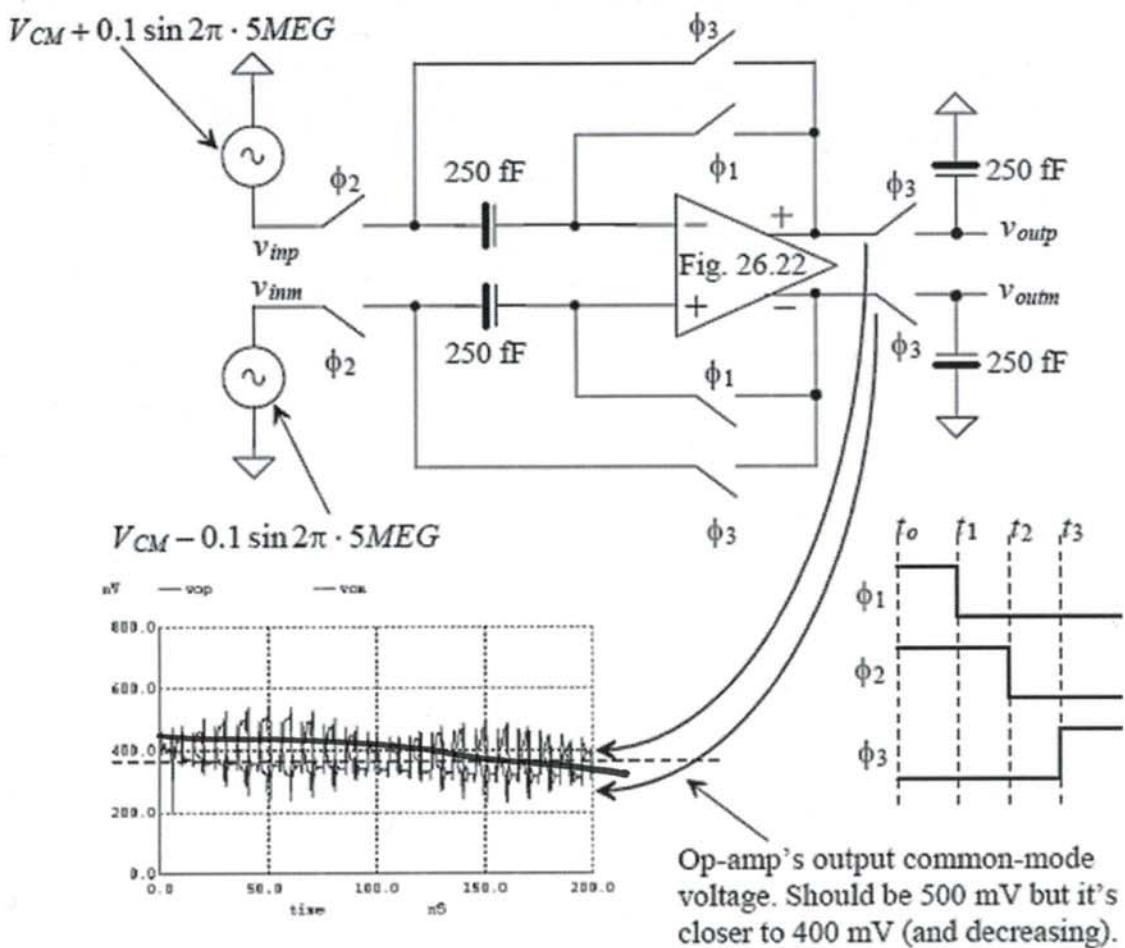


Figure 26.25 A sample-and-hold circuit. Notice how the output common-mode voltage is wandering.

15)

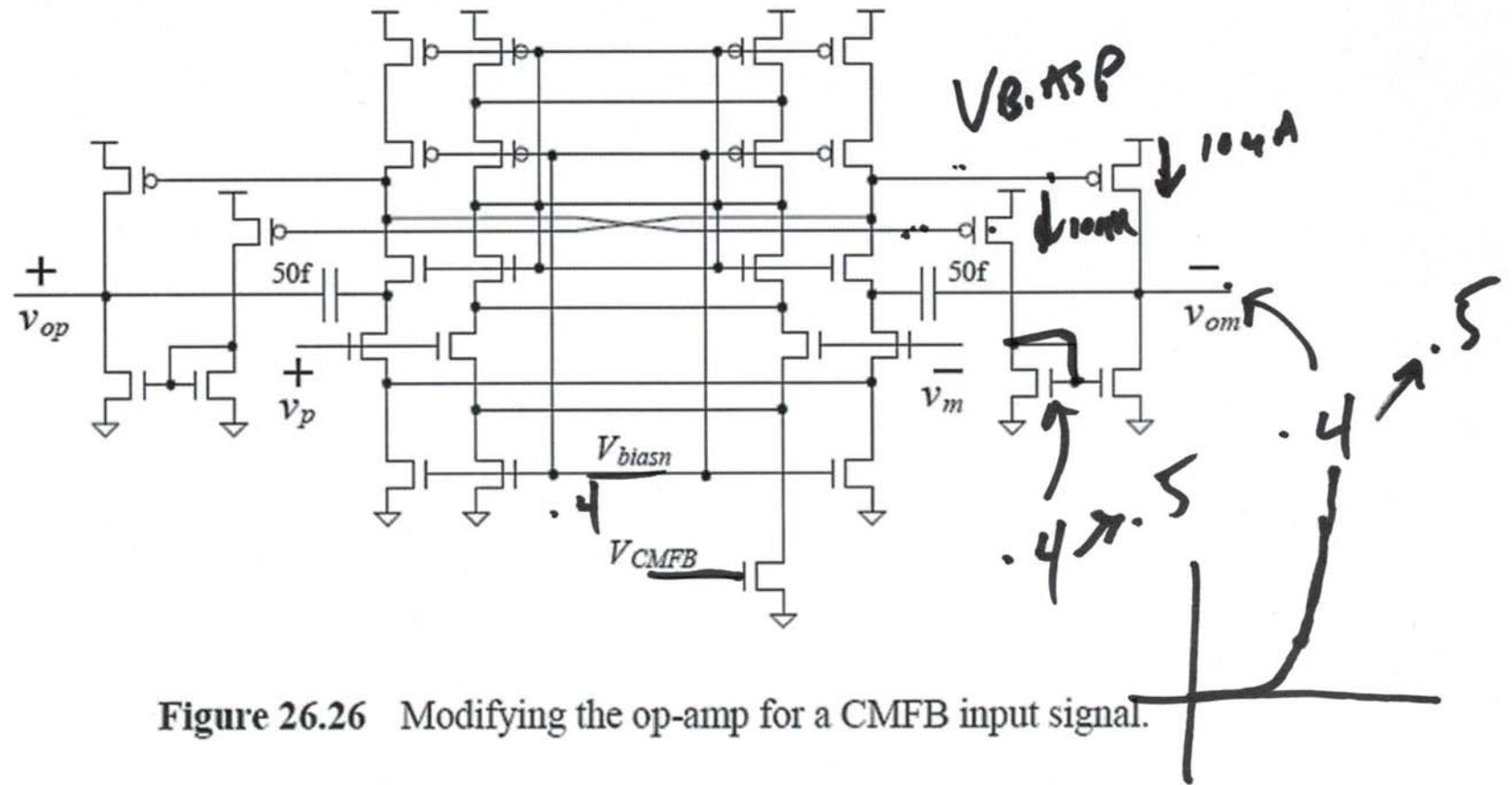


Figure 26.26 Modifying the op-amp for a CMFB input signal.

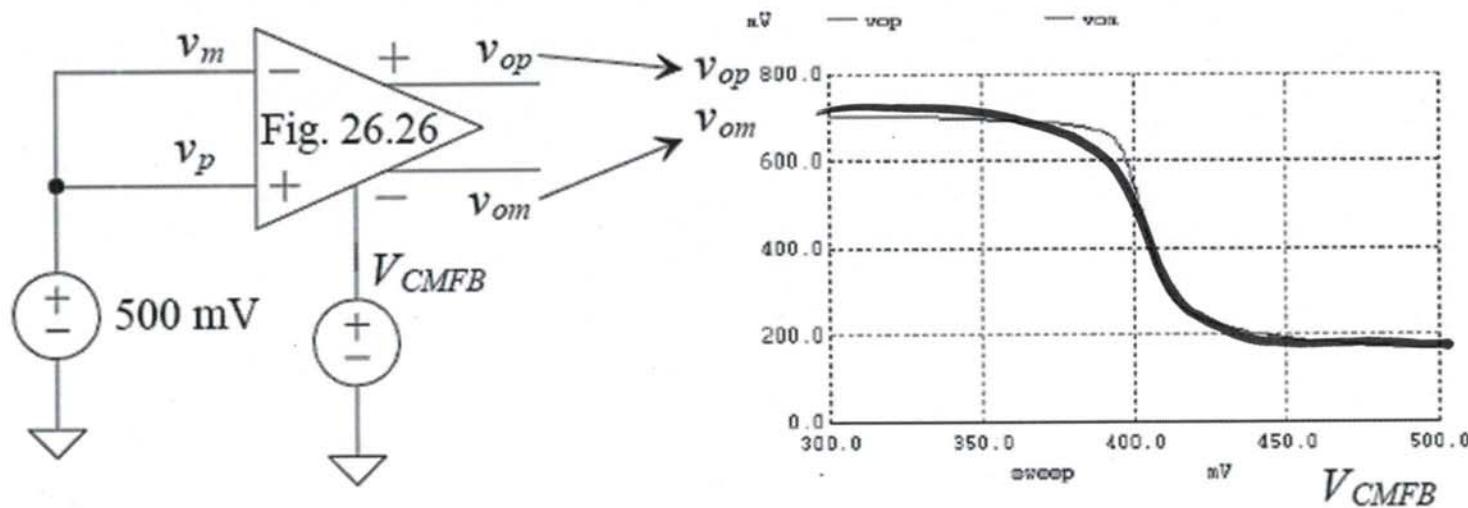


Figure 26.27 The CMFB input to output relationship. The gain is approximately 25 (considerably less than the forward differential gain).