
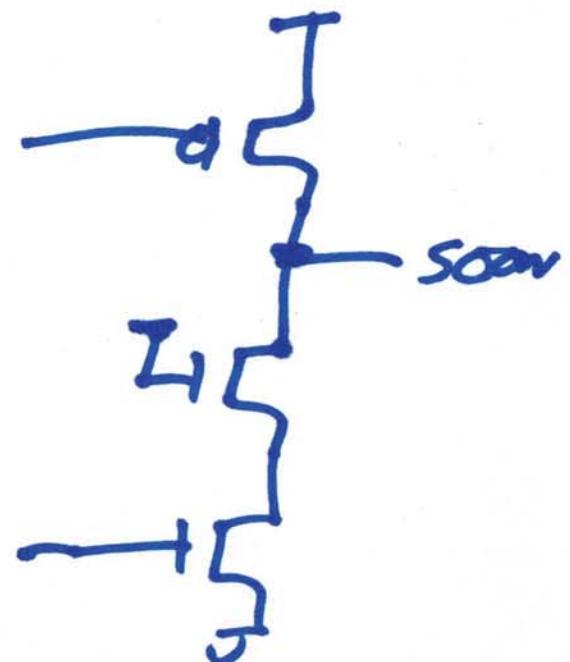


ECG 720

Advanced Analog IC  
Design

2/23/16

Lecture 11

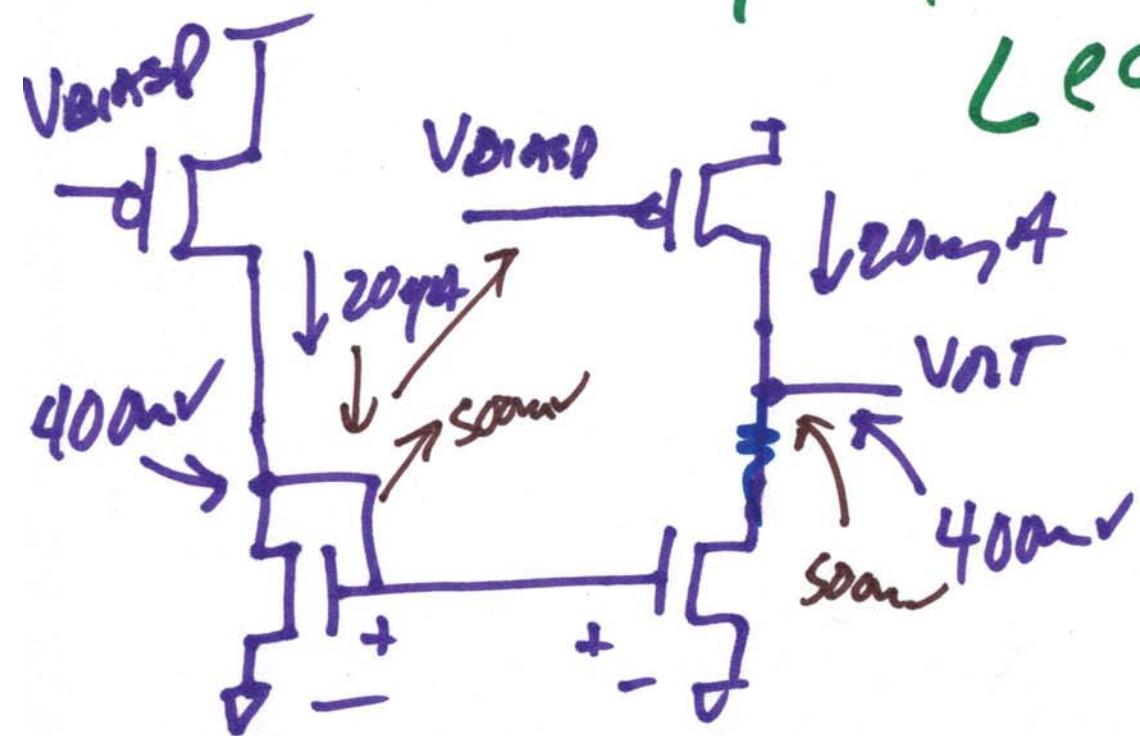




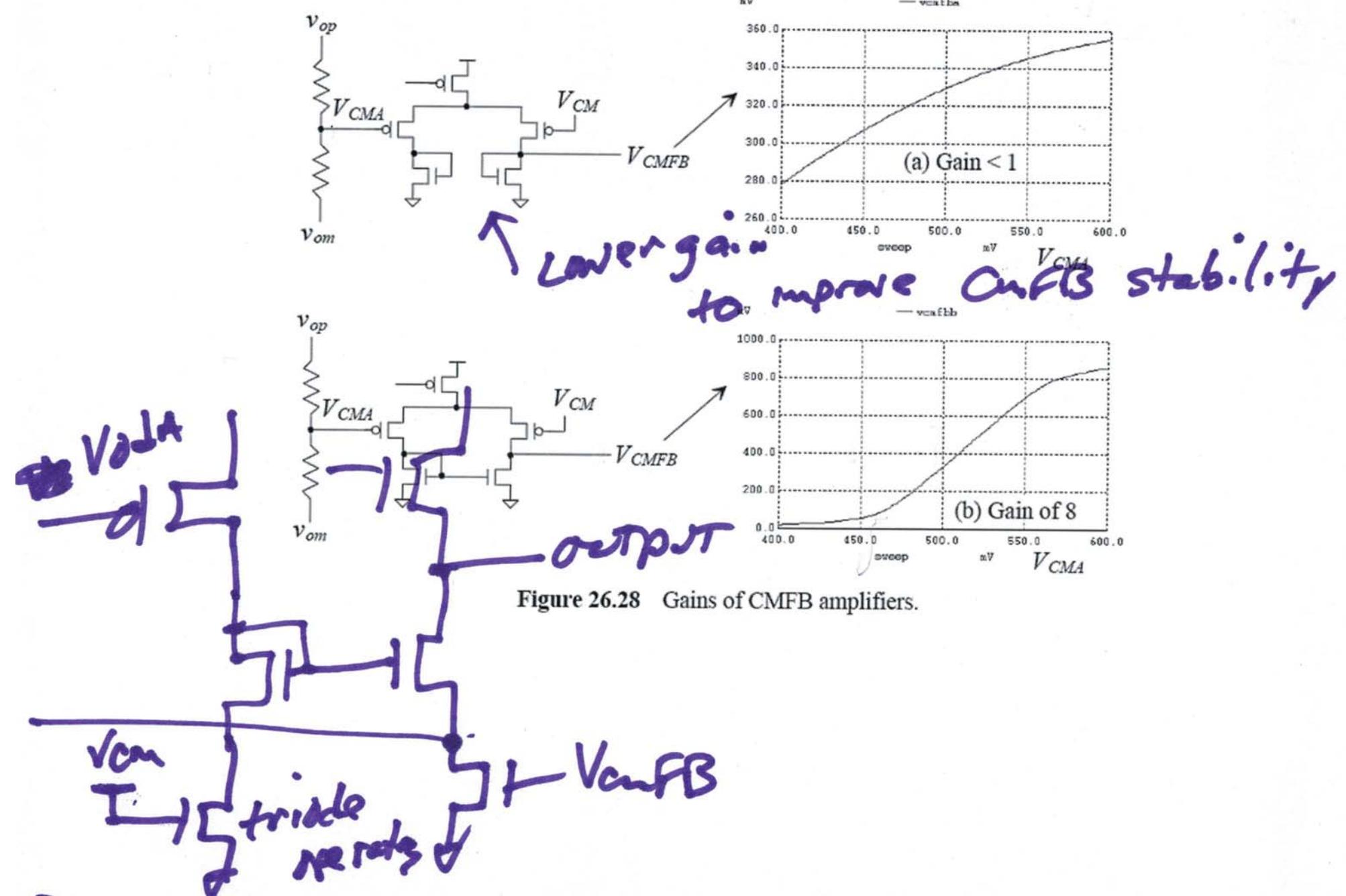


Figure 26.28 Gains of CMFB amplifiers.

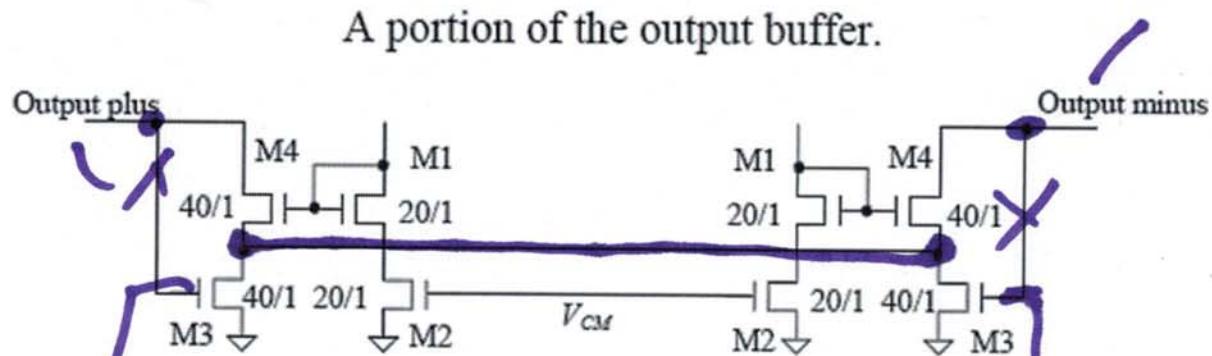


**Figure 26.37** Using triode-operating MOSFETs to balance the outputs (bad).

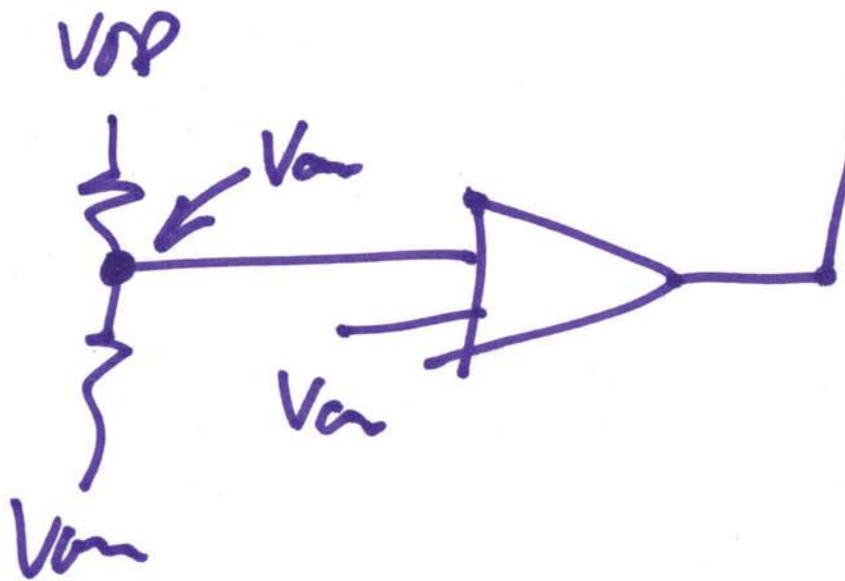

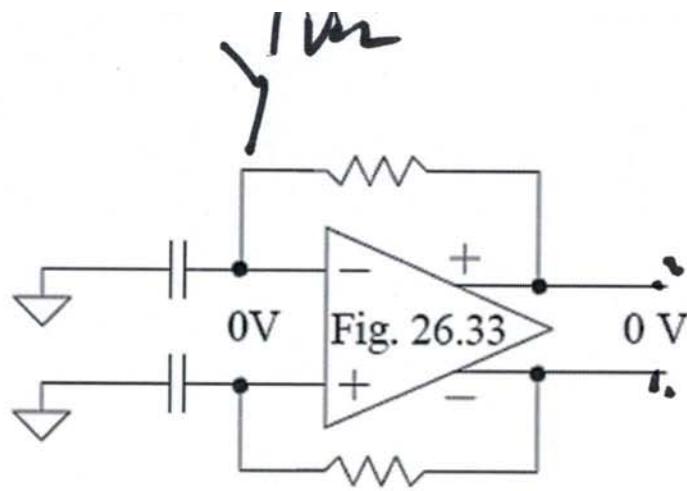


**Figure 26.38** The op-amp in Fig. 26.33 won't turn on in this topology.

*start-up problems*

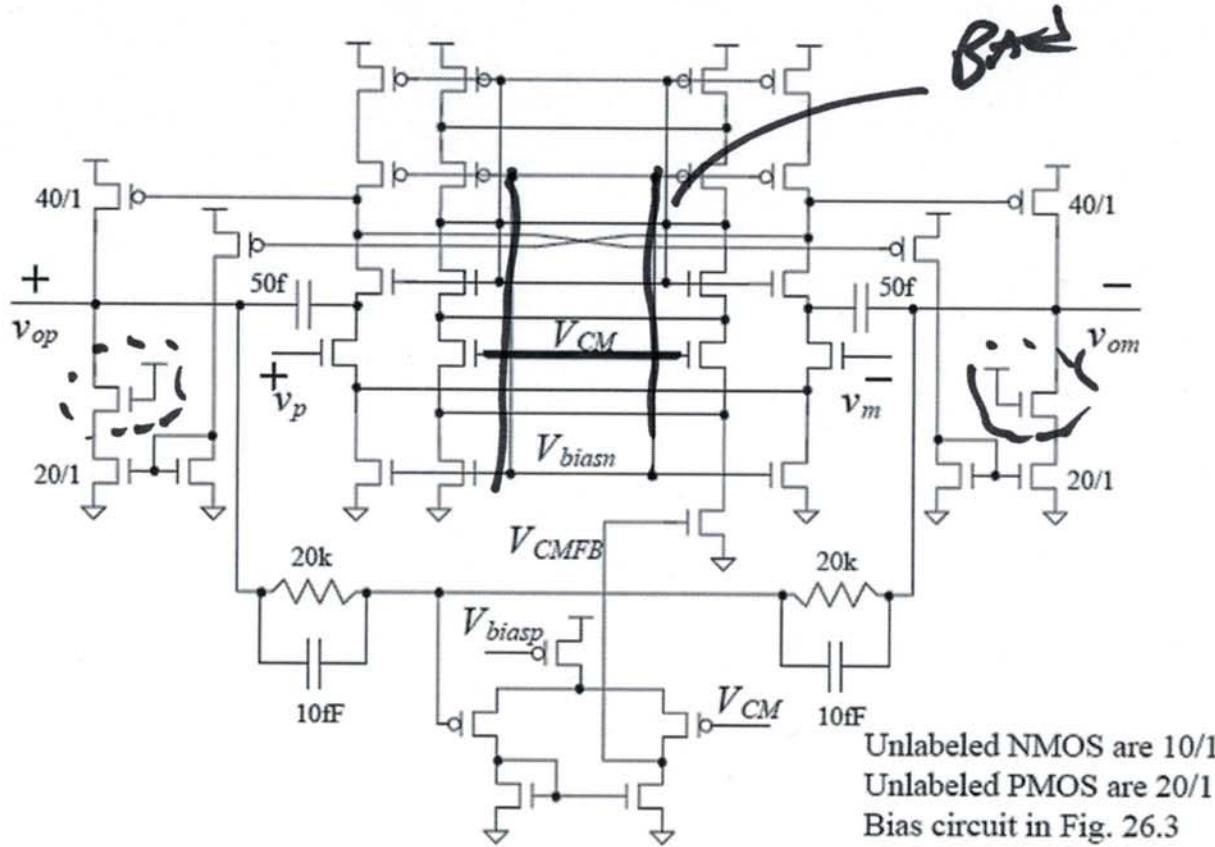


**Figure 26.39** Connecting the bias circuit diff-amp's inputs to the common-mode voltage.

5)

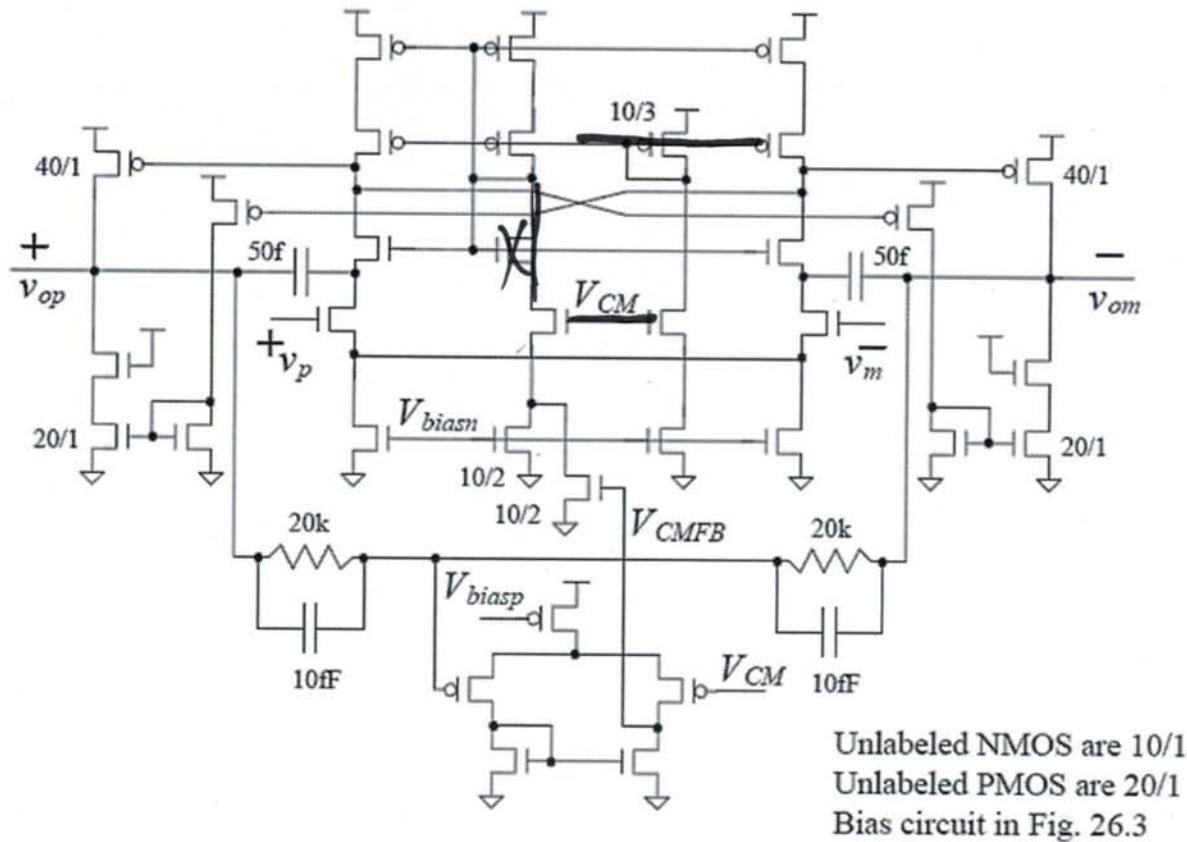


**Figure 26.40** Making the op-amp more practical.

b)

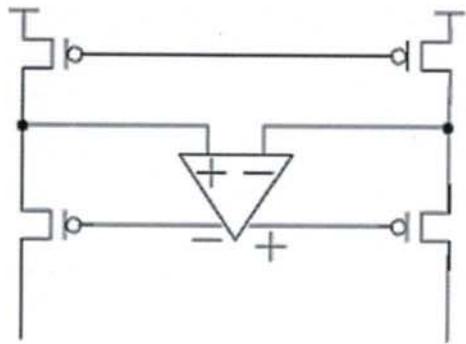


**Figure 26.41** How not to implement GE in an op-amp (unless the added amplifier employs CMFB).



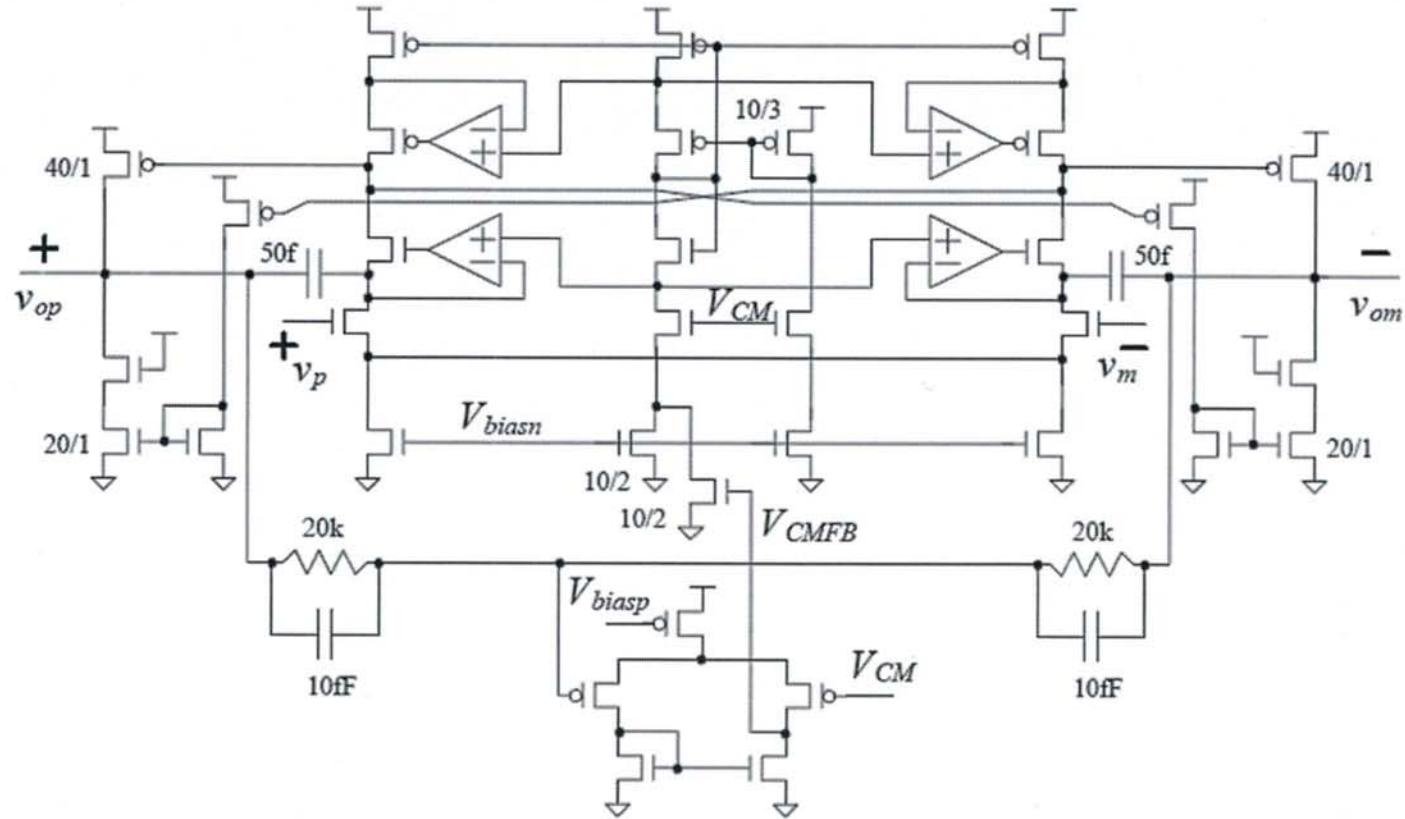


**Figure 26.42** Adding gain-enhancement to the op-amp.

8)

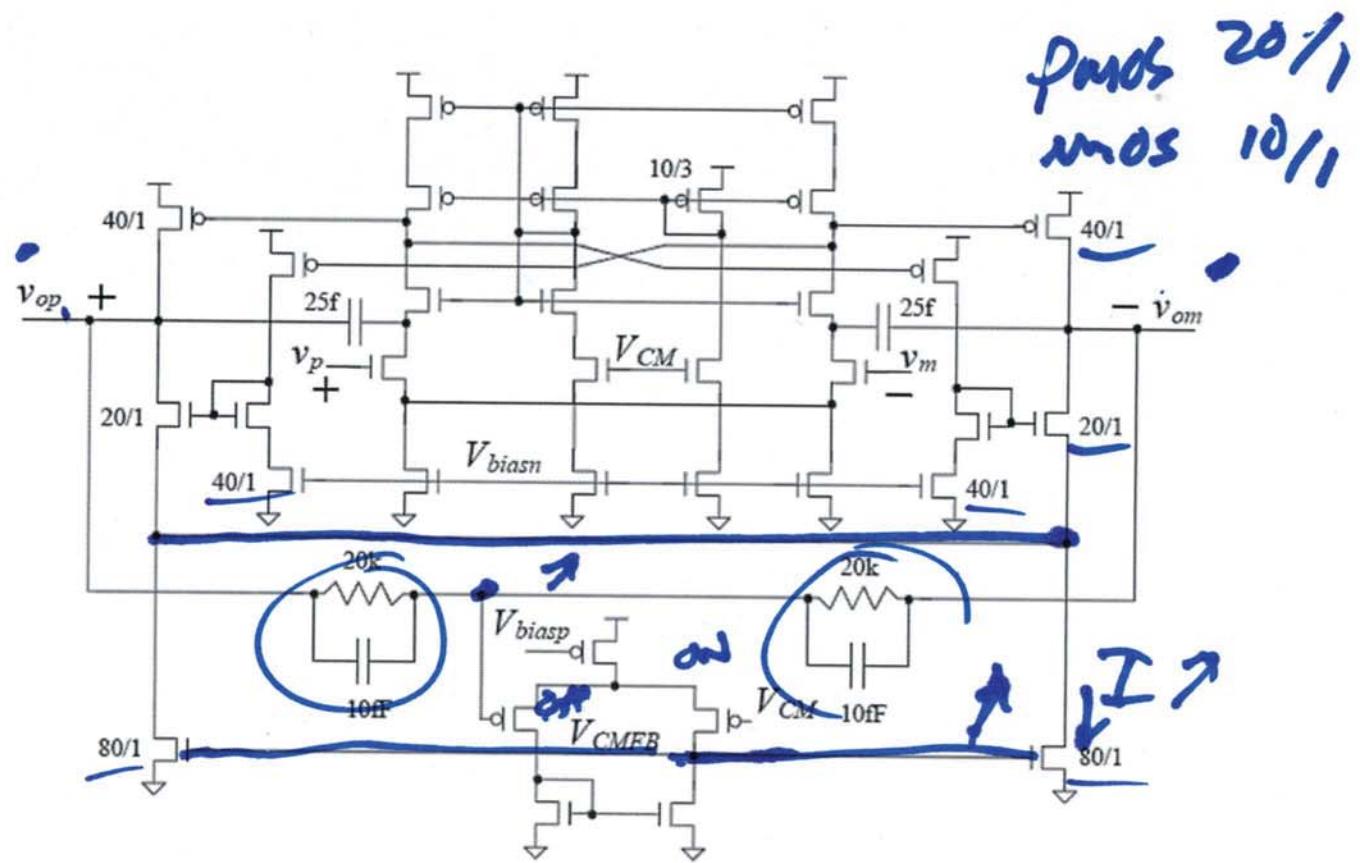


**Figure 26.43** Providing CMFB through just the output buffer. Using an amplifier with triode-operating MOSFETs for CMFB (good).

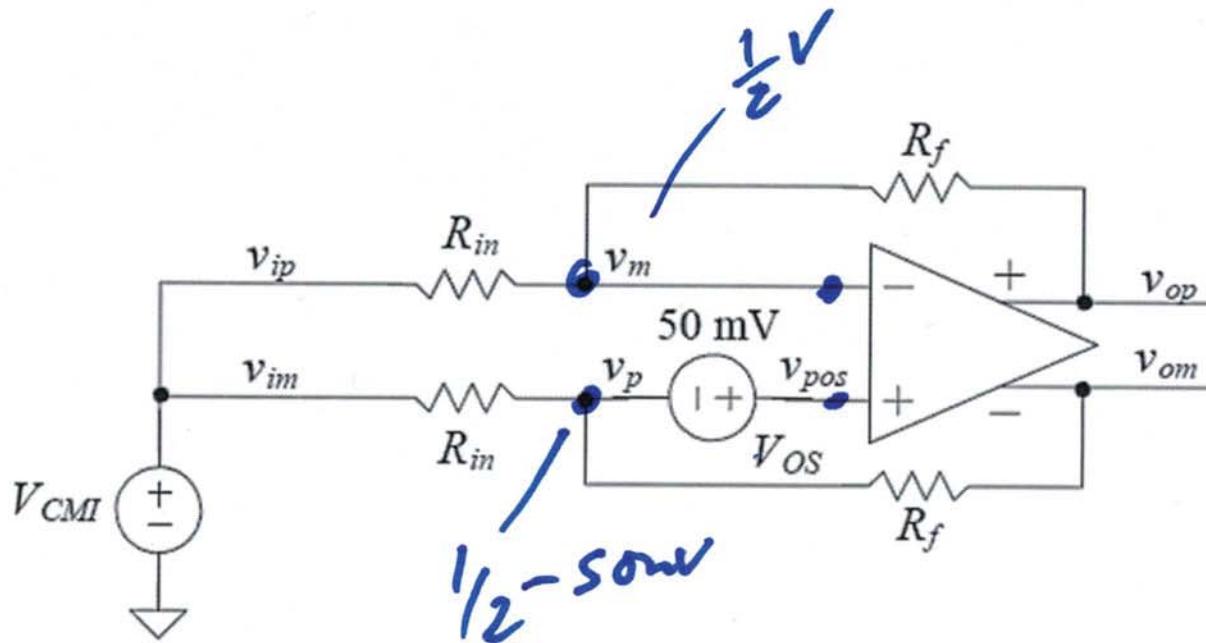

**Figure 26.46** How an offset voltage causes an imbalance in the outputs.


$$v_{op} = \frac{V_{OS}}{2} \left( 1 + \frac{R_f}{R_{in}} \right) + V_{cm}$$

*shift +  
in common-node*

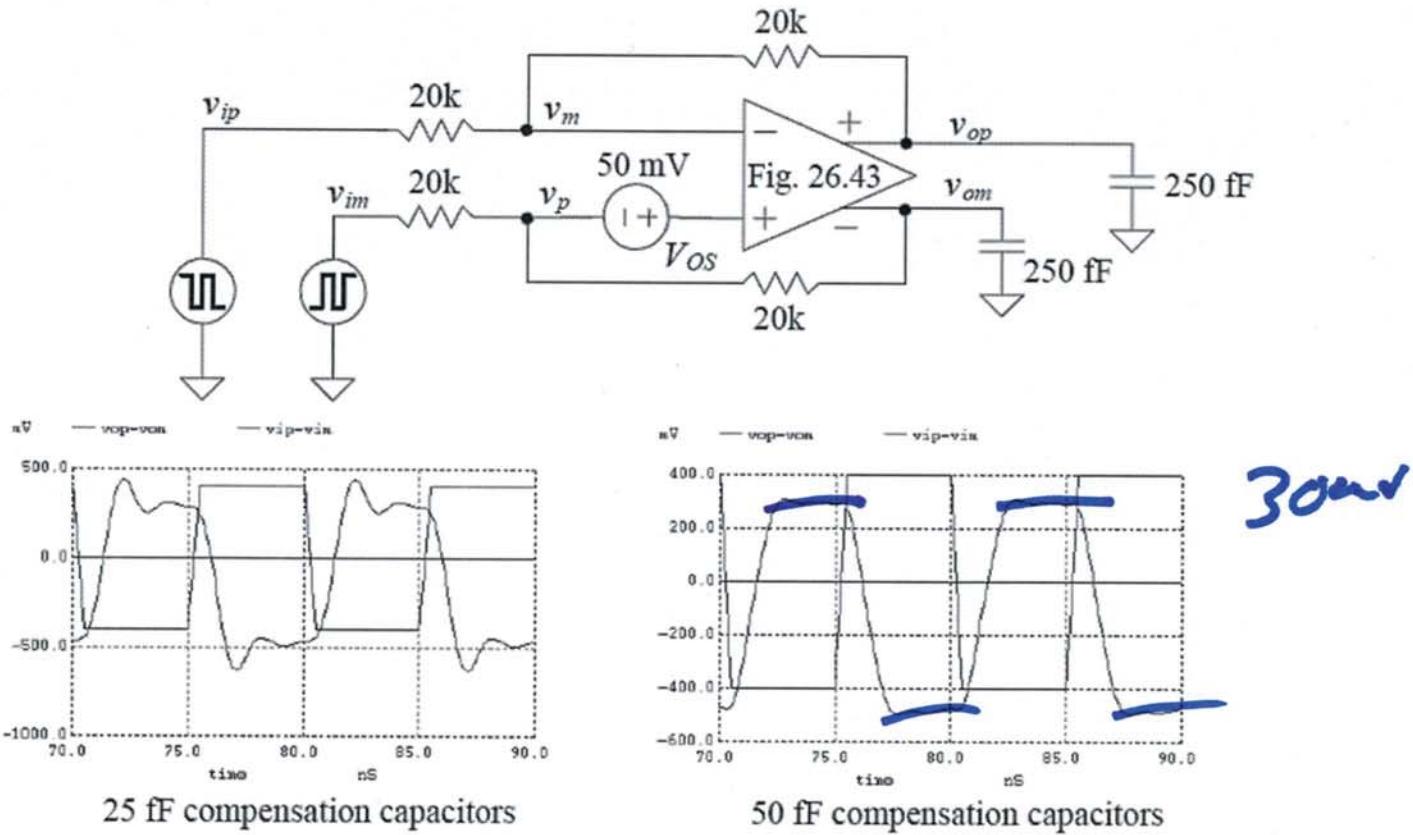

**Figure 26.45** How an offset can affect the step response (compensation).



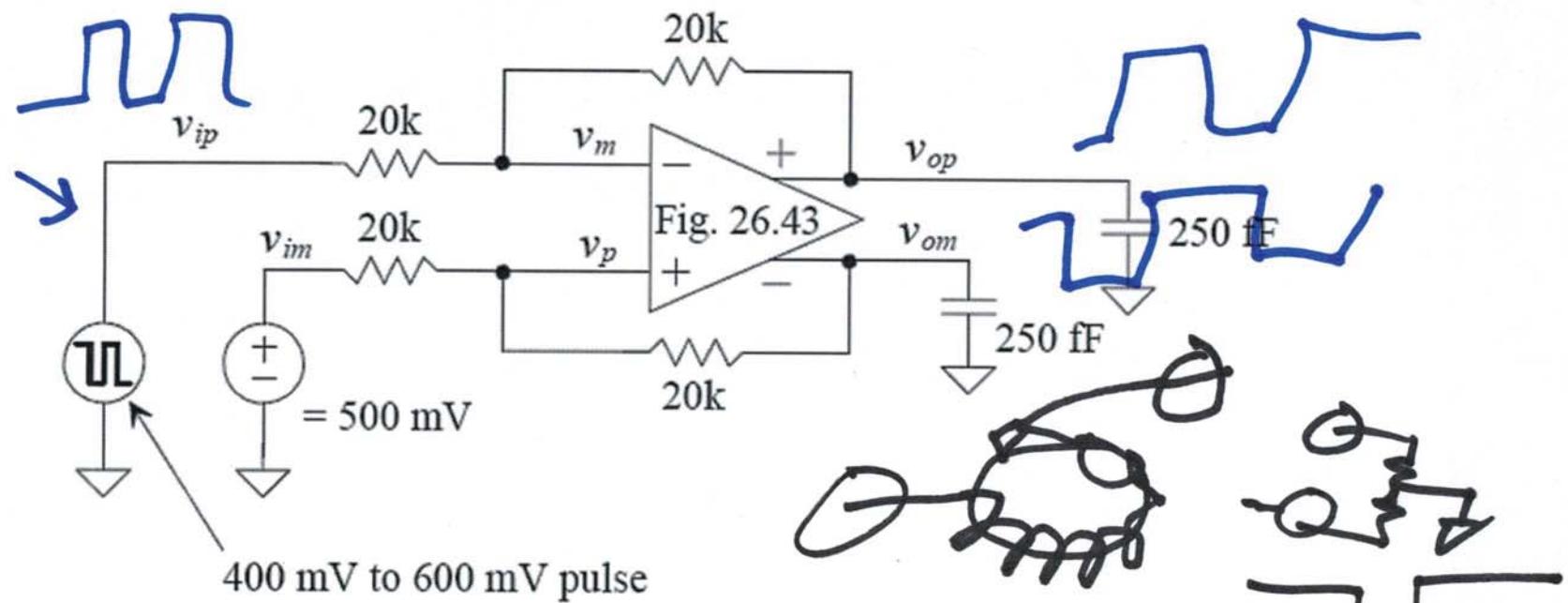

**Figure 26.47** Problems with single-ended input signals.

