
 


Lecture 12
Feb. 25, 2016

 


 


Figure 26.49 Generating nonoverlapping clocks for SC circuits.

 


 


Figure 26.50 A switched-capacitor CMFB circuit (see Fig. 26.16).
Switches implemented with transmission gates.

 


 


Figure 26.52 Biasing circuit for the op-amp developed in this section.

 

 


Figure 26.53 Diff-amp used with the bias circuit of Fig. 26.52.

 
 
 


Figure 26.54 First-stage diff-amp with SC CMFB.


 


Figure 26.56 Output buffer and CMFB.

 

 


Figure 26.58 Simulating the operation of the op-amp formed with the diff-amp in Fig. 26.54 and buffer in Fig. 26.56.

S/H