


EEG 720

Advanced Analog IC Design

Lecture 18

March 29, 2016

AOL for the example we did last time.

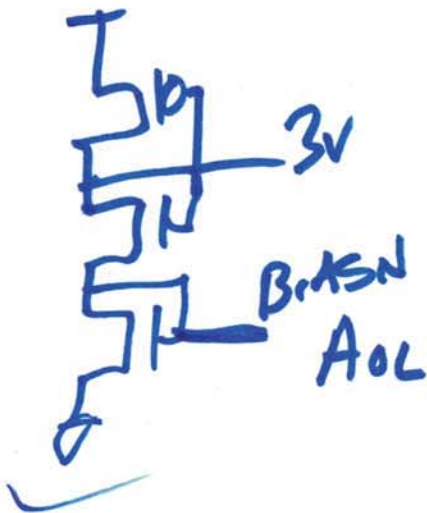




shunt-shunt

$$\beta = \frac{1}{30k}, \quad A_{cl} = \frac{1}{1 + \beta \cdot A_{OL}}$$


$$V_{out} = -i_{in} \cdot 30k \quad \frac{A_{OL} \cdot 30k}{1 + \beta \cdot A_{OL}}$$
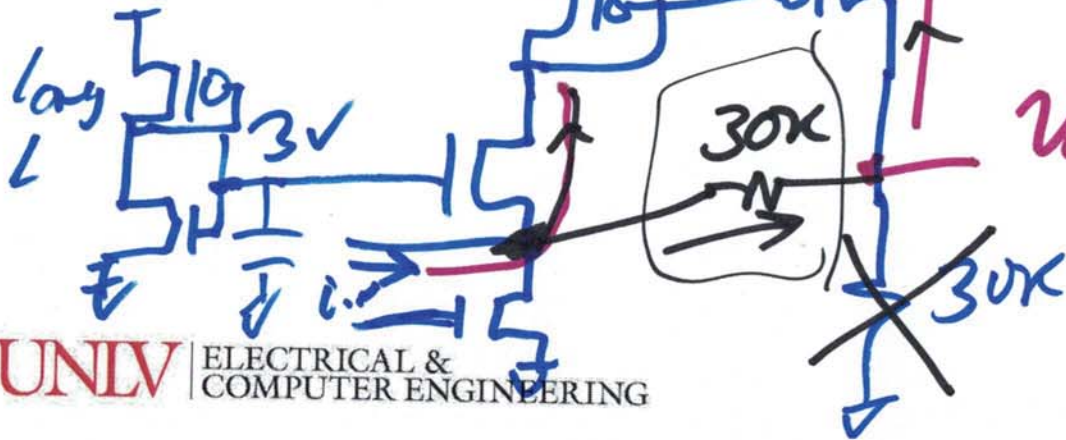
$$A_{cl} / A_{open} = \frac{1 + \beta \cdot A_{OL}}{1 + \beta \cdot \frac{30k}{15k}}$$



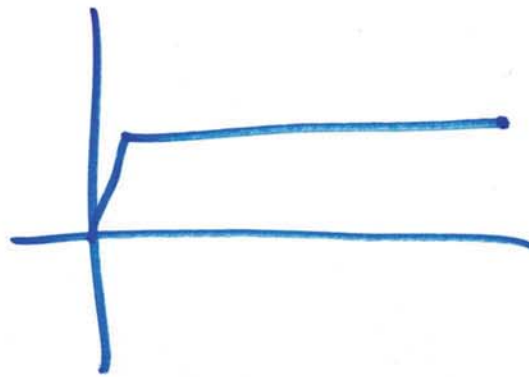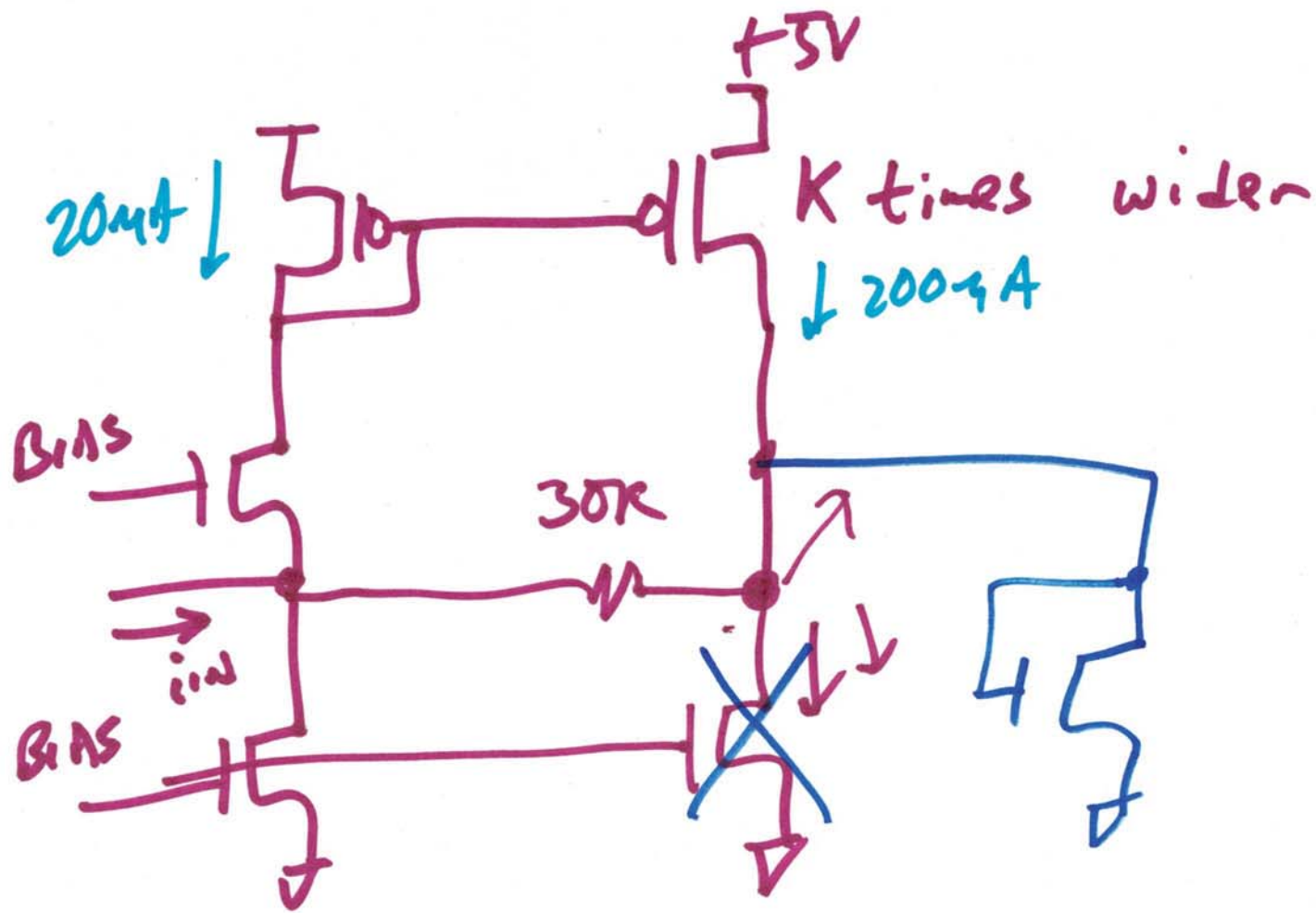

2)

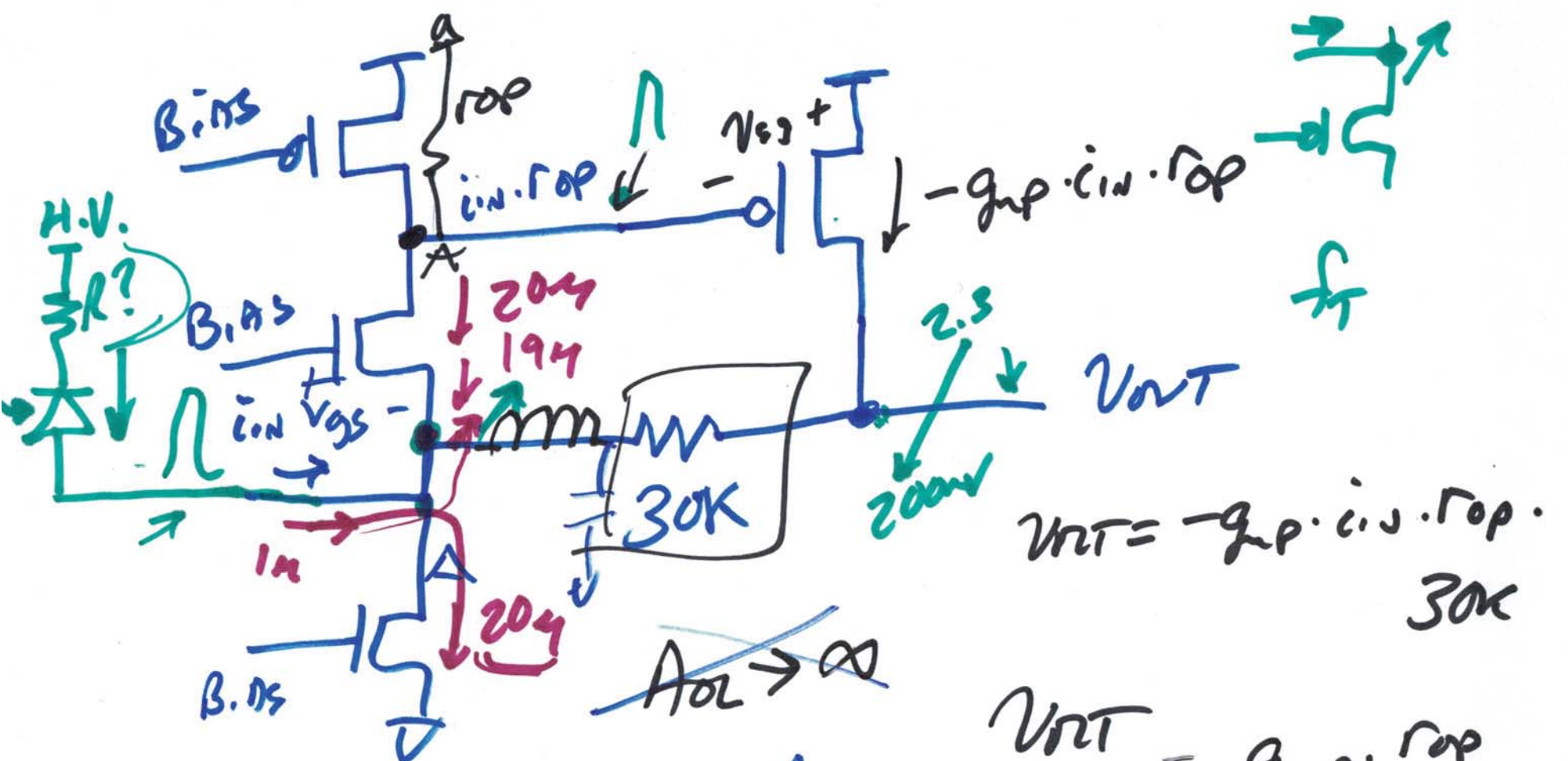

$$V_{OUT} = -g_{mP} \cdot i_{in} \cdot r_{op} \cdot 30k$$

~~$A_{OL} \rightarrow \infty$~~


$$A_{OL} = \frac{V_{OUT}}{i_{in}} = g_{mP} \cdot r_{op} \cdot 30k$$

$$A_{CL} = \frac{g_{mP} \cdot r_{op} \cdot 30k}{1 + \frac{1}{30k} \cdot g_{mP} \cdot r_{op} \cdot 30k} = \underline{\underline{30k}}$$

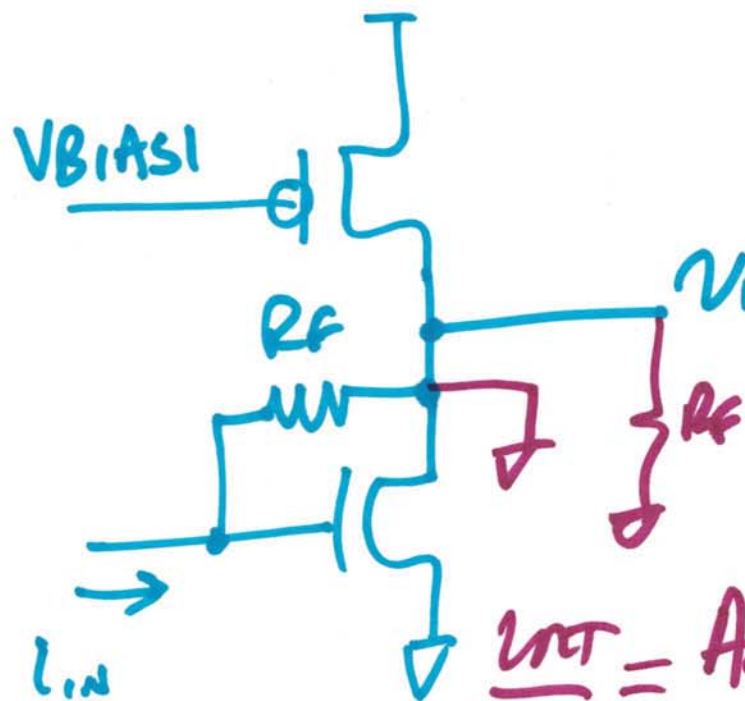3)

Another shunt-shunt f.b. Amp

$A_{OL} \Rightarrow$
 $v_{gs} = i_{in} \cdot R_F$



$v_{OUT} = R_F \parallel r_{op} \parallel r_{on} \approx R_F$
 $= g_m v_{gs} \cdot R_F$

$\frac{v_{OUT}}{i_{in}} = A_{OL} = -g_m R_F \cdot (R_F)$
 $= -g_m R_F^2$

$R_i = R_F$

$R_o = R_F \parallel r_{op} \parallel r_{on}$ $\beta = -\frac{1}{R_F}$

4)