

Lecture 9

EEG 720



$L \rightarrow$ Speed $L \uparrow$ speed \downarrow
 gain $L \uparrow$ gain \uparrow

$V_{ov} = V_{GS} - V_{THN}$

$V_{ov} \uparrow$ speed \uparrow
 gain \downarrow

width \downarrow needed current \uparrow

$V_{GS} = V_{ovn} + V_{THN}$

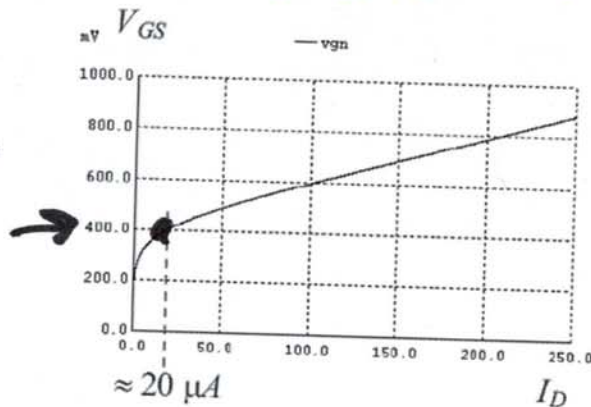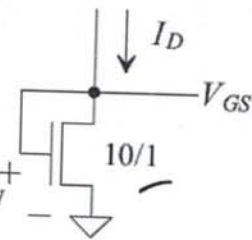

$V_{SG} = V_{ovp} + V_{THP}$


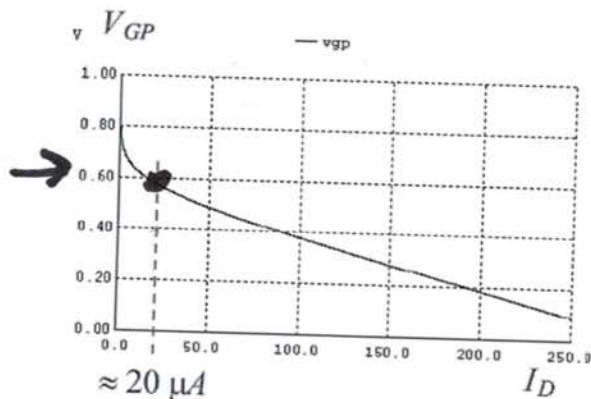


Figure 26.1 Gate-source voltages plotted against drain currents.

Advanced Analog

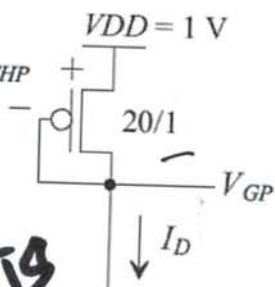

High-speed Minimum L

$$I = C \frac{dV}{dt} = C \cdot \frac{V_{DD}}{T_{clk}/2} = \frac{C \cdot V_{DD}}{T_{clk}}$$

$$\Rightarrow \sqrt{\frac{KT}{C}} \ll \ll 1 \text{ LSB}$$


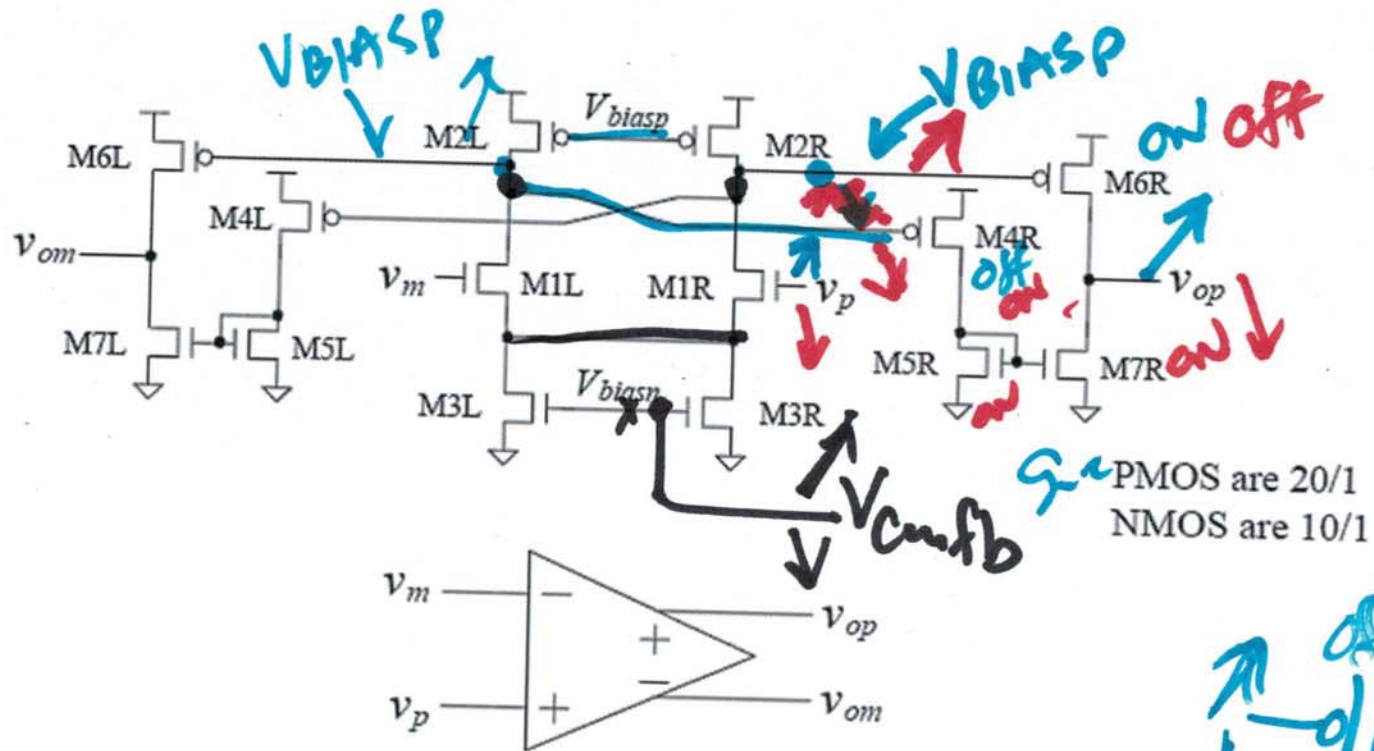


Figure 26.2 A two-stage fully-differential op-amp. Compensation and CMFB are not shown. Output stage operates class AB. See discussion in the next section concerning the output voltage of the diff-amp.

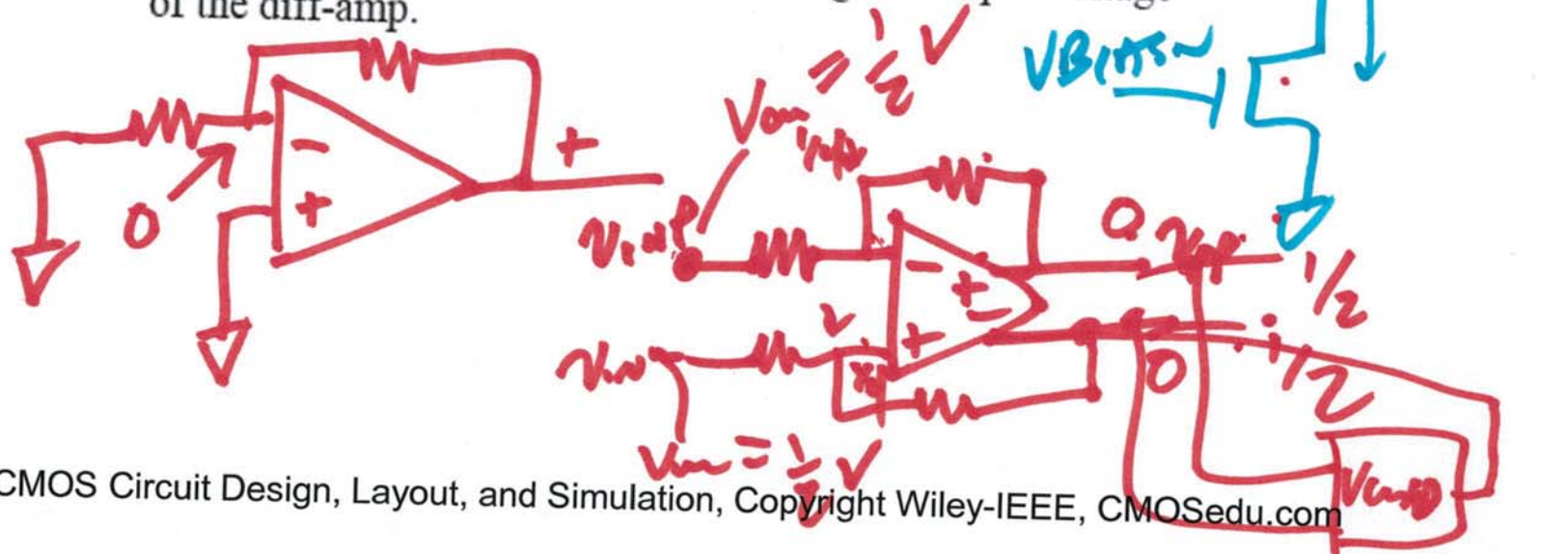



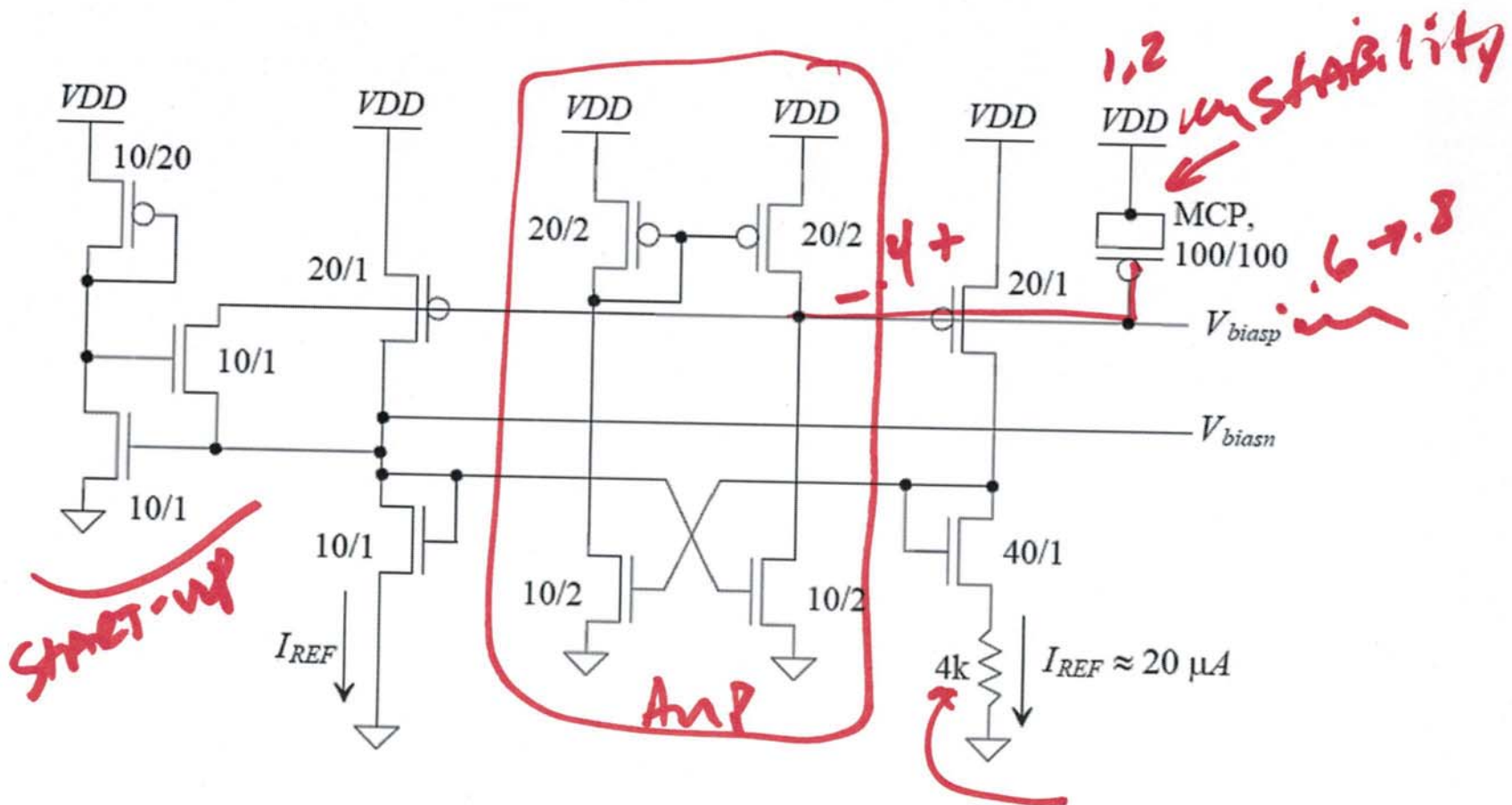


Figure 26.3 Biasing circuit used in this chapter. This bias circuit pulls approximately 50 microamps.

37

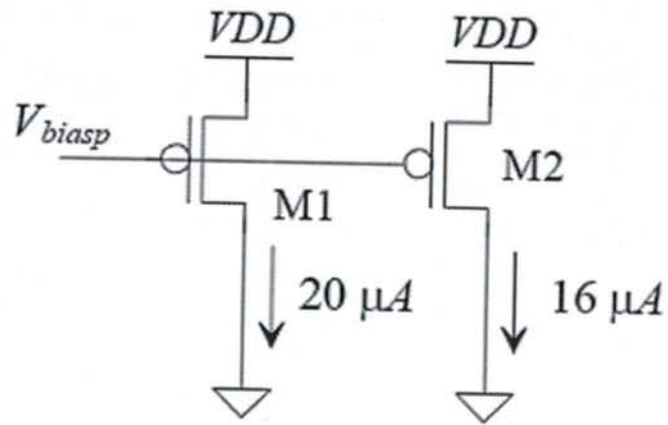


(a) M1 and M2 are mismatched.

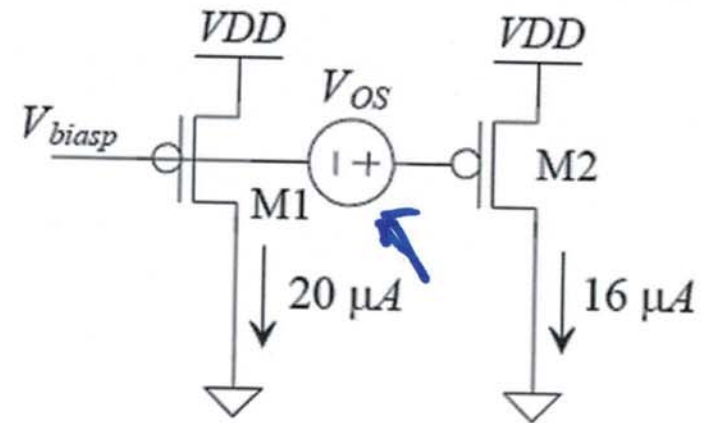


(b) M1 and M2 are perfectly matched (as in a SPICE simulation).

Figure 26.5 How we add an offset into the circuit to model mismatch.

4)

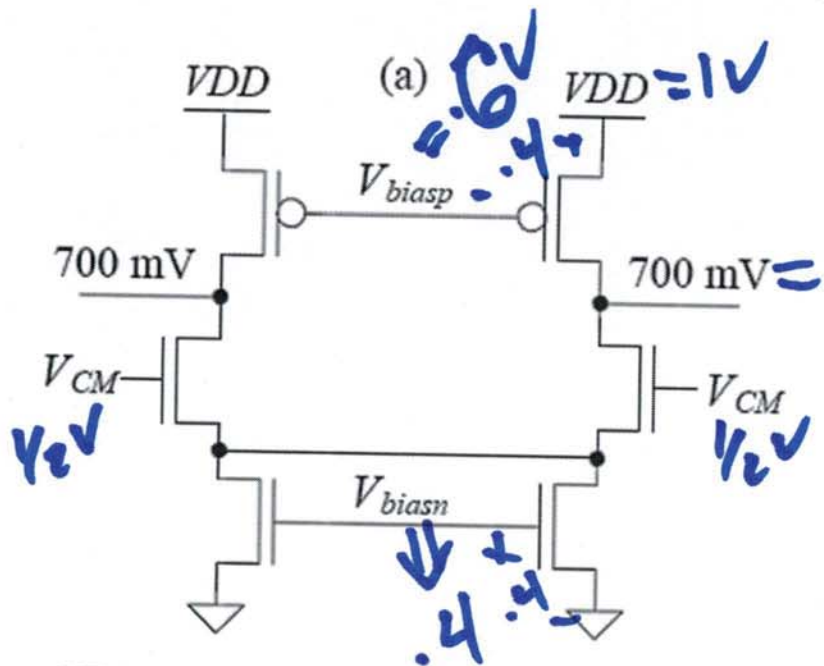

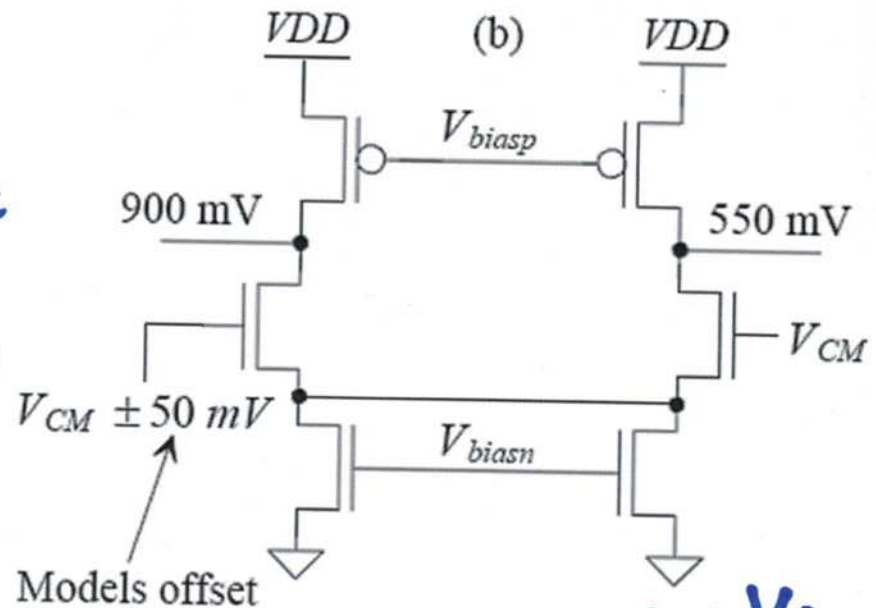NMOS are 10/1
 PMOS are 20/1
 Bias circuit seen in Fig. 26.3



$$V_{CM} = V_{DD}/2 = 500\text{ mV}$$

$$\frac{V_L + V_R}{2} = \frac{1.45}{2} = 0.725$$

Figure 26.6 Comparing the diff-amp's output voltages with and without an offset.



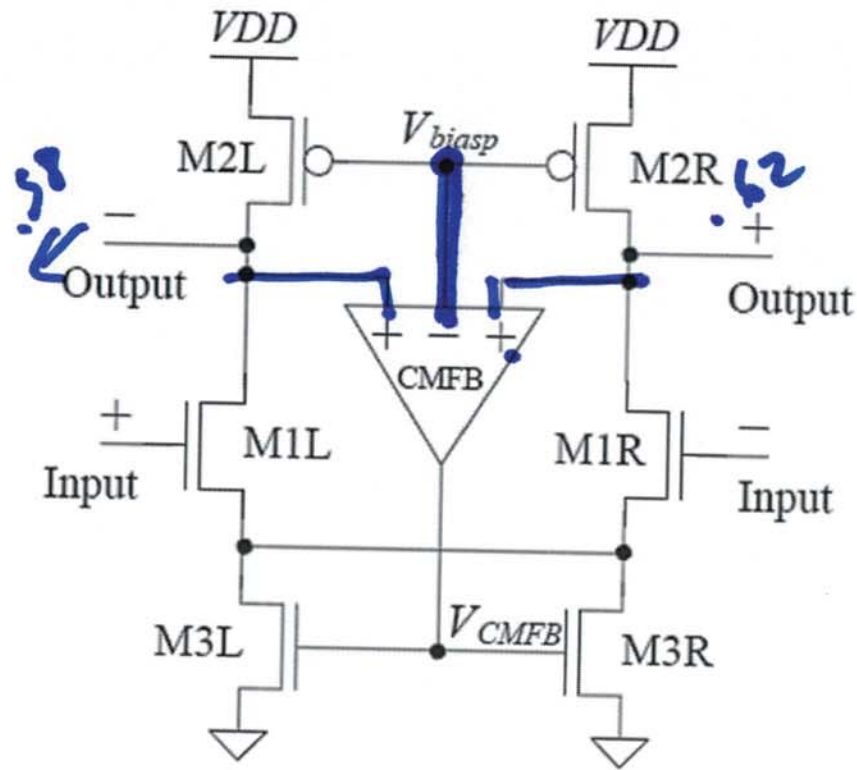
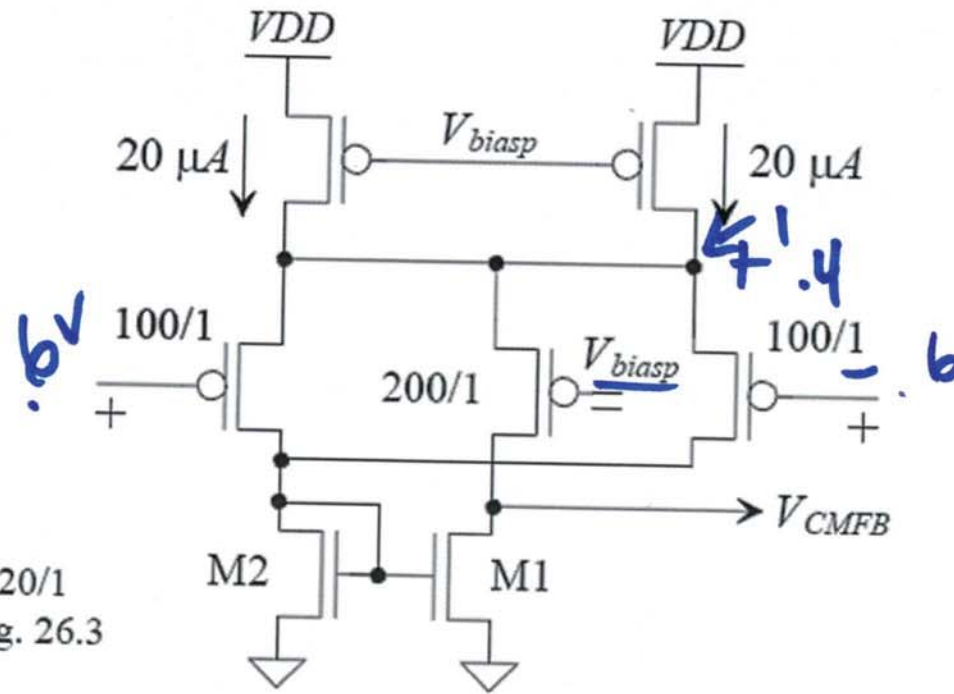
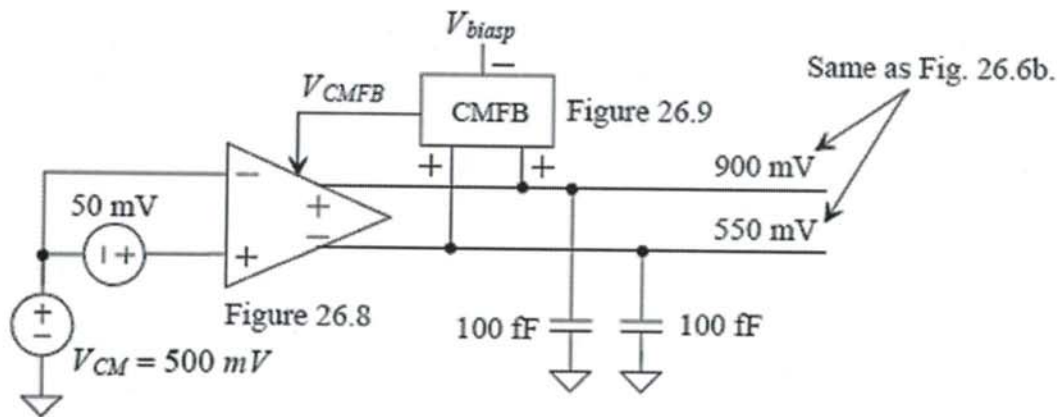
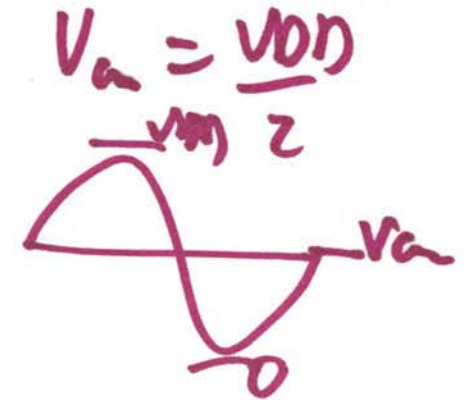


Figure 26.8 Using a common-mode feedback (CMFB) amplifier to set the output voltages.

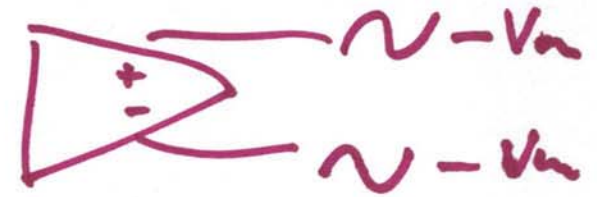

NMOS are 10/1
 Unlabeled PMOS are 20/1
 Bias circuit seen in Fig. 26.3


Figure 26.9 Implementation of the CMFB amplifier in Fig. 26.8.

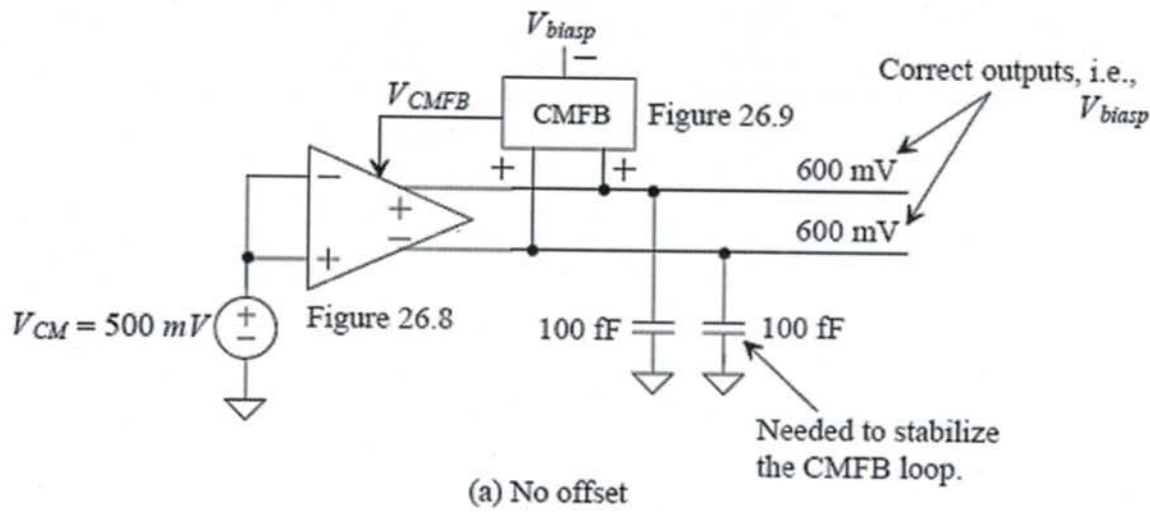

(b) With a 50 mV offset. Note how the CMFB isn't doing anything.

Figure 26.10 Simulating the operation of the CMFB circuit in Fig. 26.9.



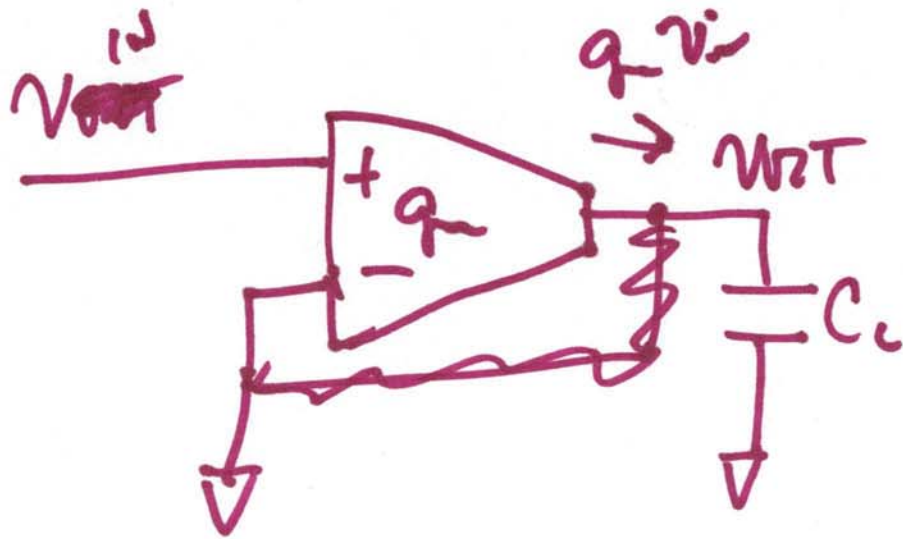

$$\beta = 1$$

$$A_{CL} = \frac{A_{OL}}{1 + A_{OL} \cdot \beta}$$

\swarrow
 -1 UNSTABLE


$$|A_{CL}| = 1$$

$$\angle A_{CL} = 180^\circ$$

$$v_{out} = \frac{1}{j\omega C_c} \cdot q \cdot v_{in}$$

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{q}{2\pi f C_c}$$
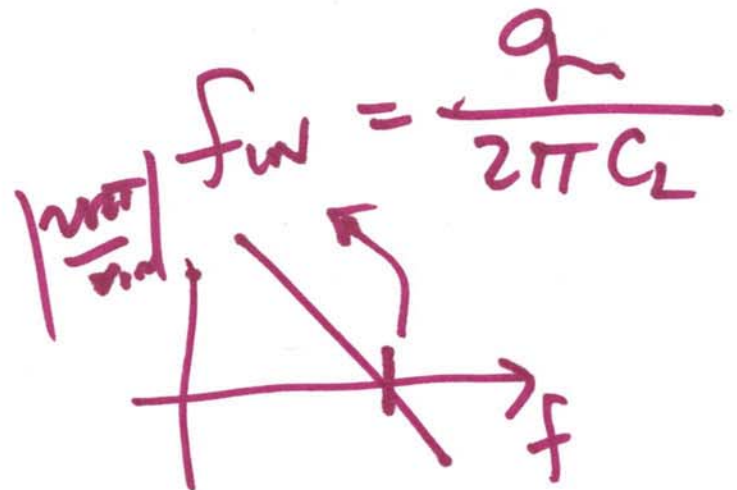
$$\angle \frac{v_{out}}{v_{in}} = -90^\circ$$



10)


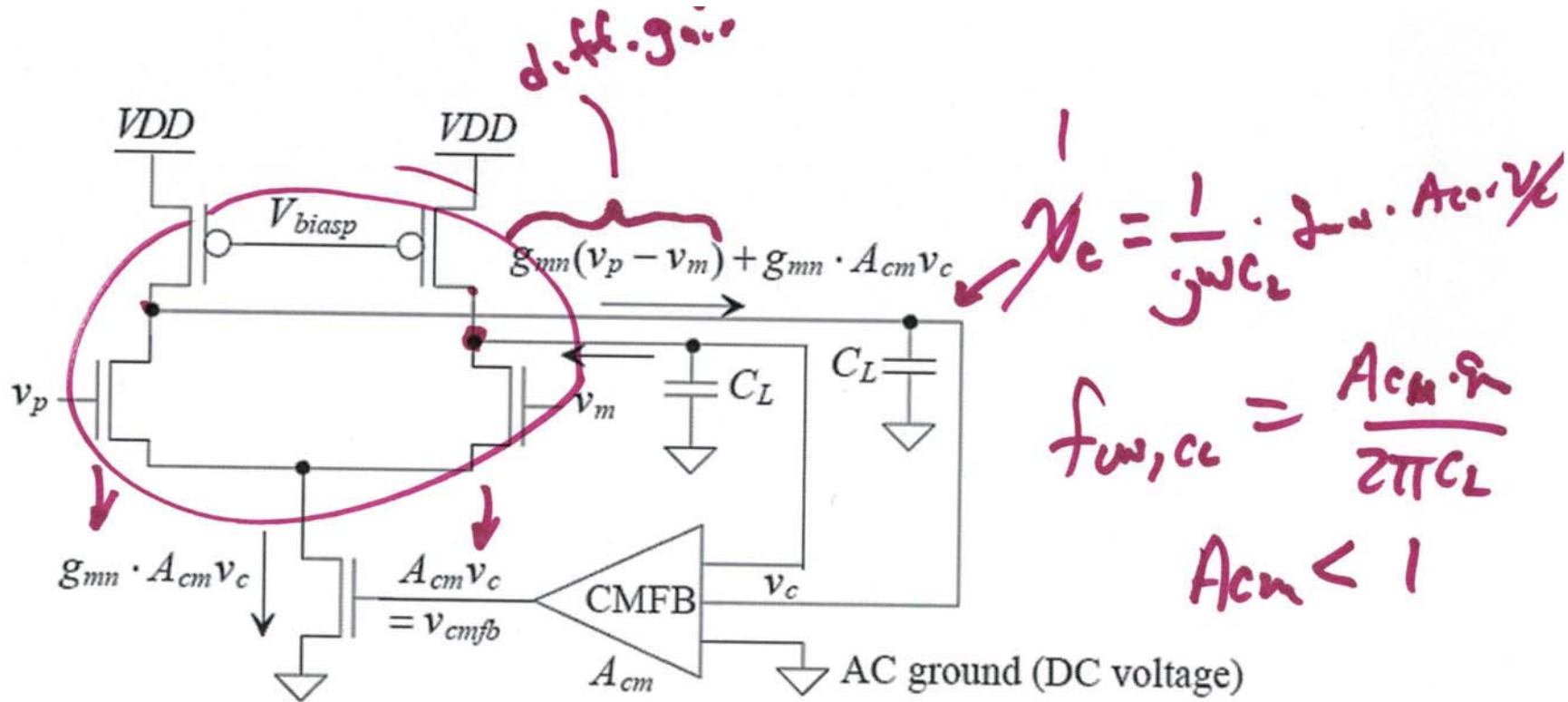


Figure 26.11 Schematic view of differential and CM feedback.

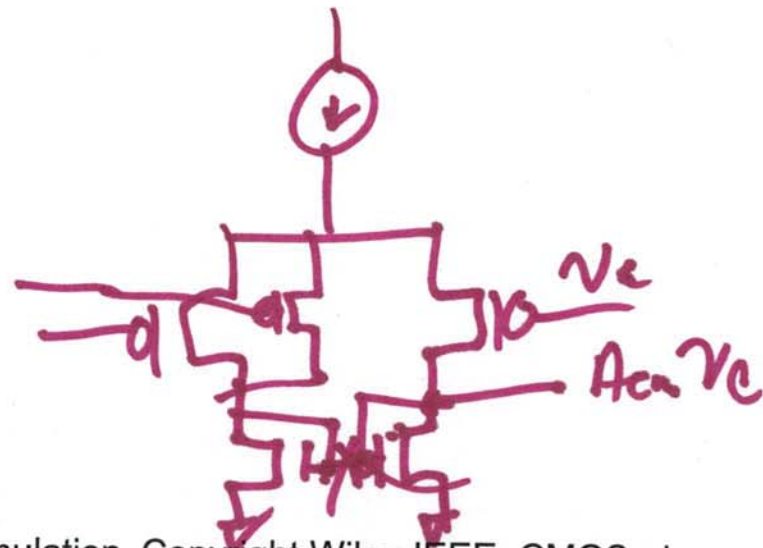


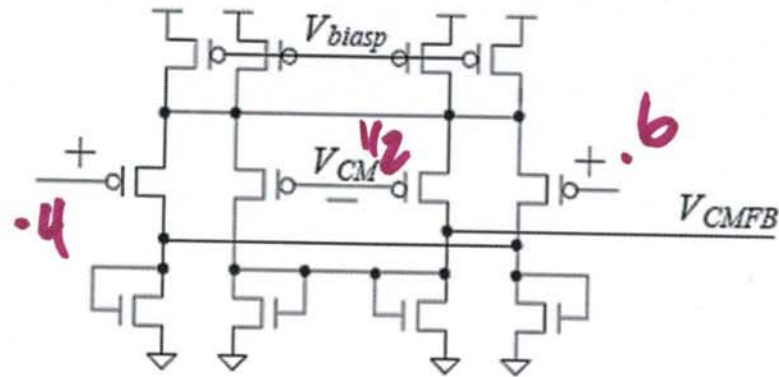


Figure 26.12 A CMFB amplifier with a gain of nominally unity.

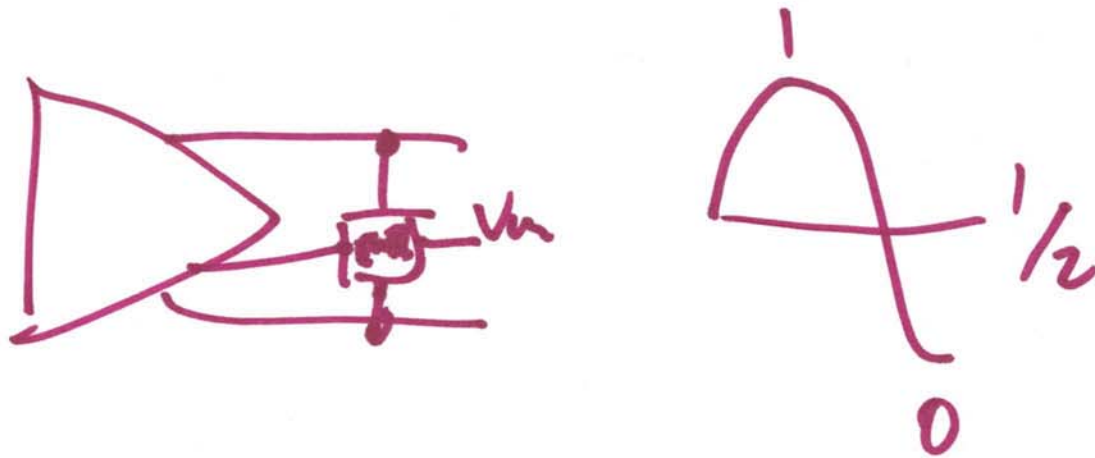

2)

