
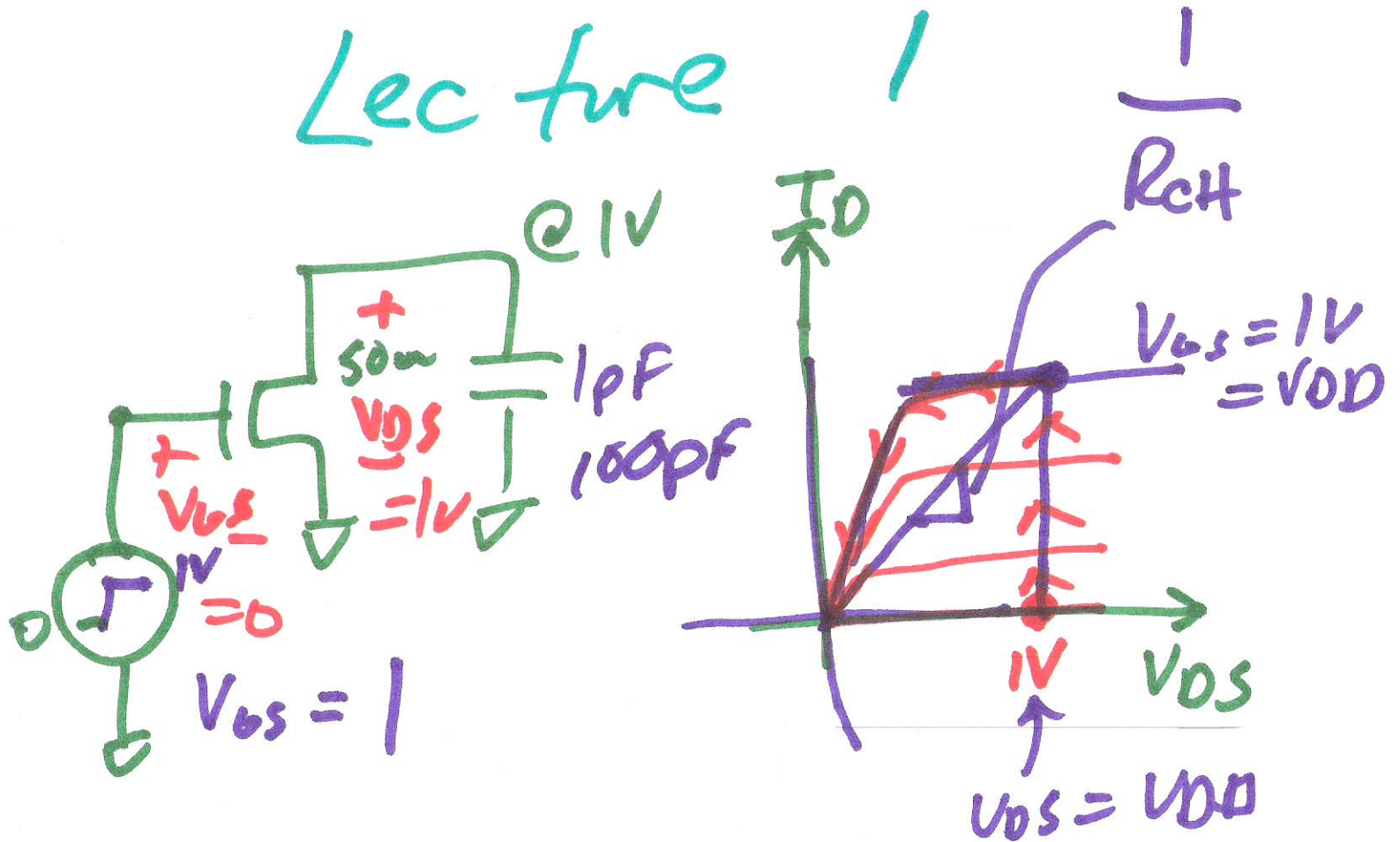


ECG 721

August 24, 2015

Lecture 1

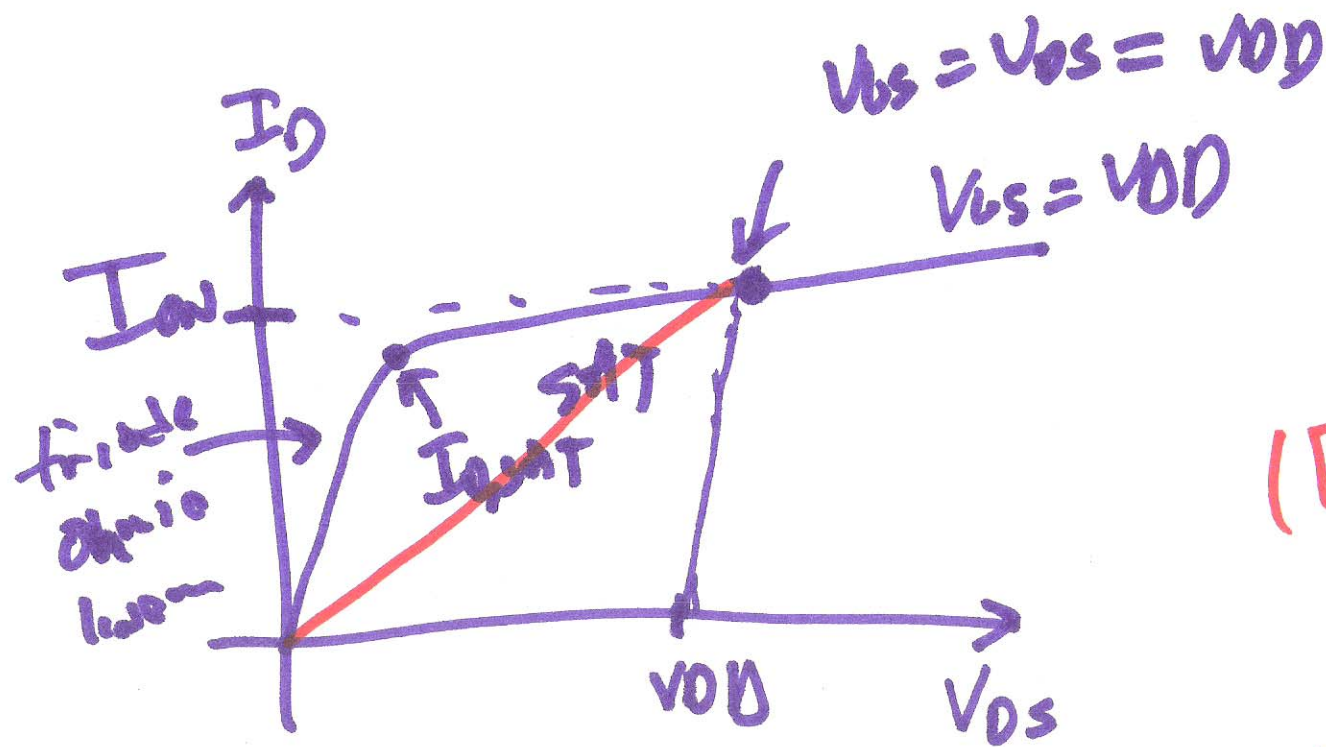



$$15 \frac{10}{1} = \frac{500n}{50n}$$


$$\frac{V_{DD}}{R_N} = \frac{V_{DD} = 1}{300\mu A} = \frac{1}{I_{D,sat} \cdot \frac{W}{L}}$$

30

$$R_N = R_N' \cdot \frac{L}{W} \quad R_N' = \frac{1}{30\mu A} = 33K$$

$$R_{d1}' = 33K$$


$$R_W = 3.3K$$

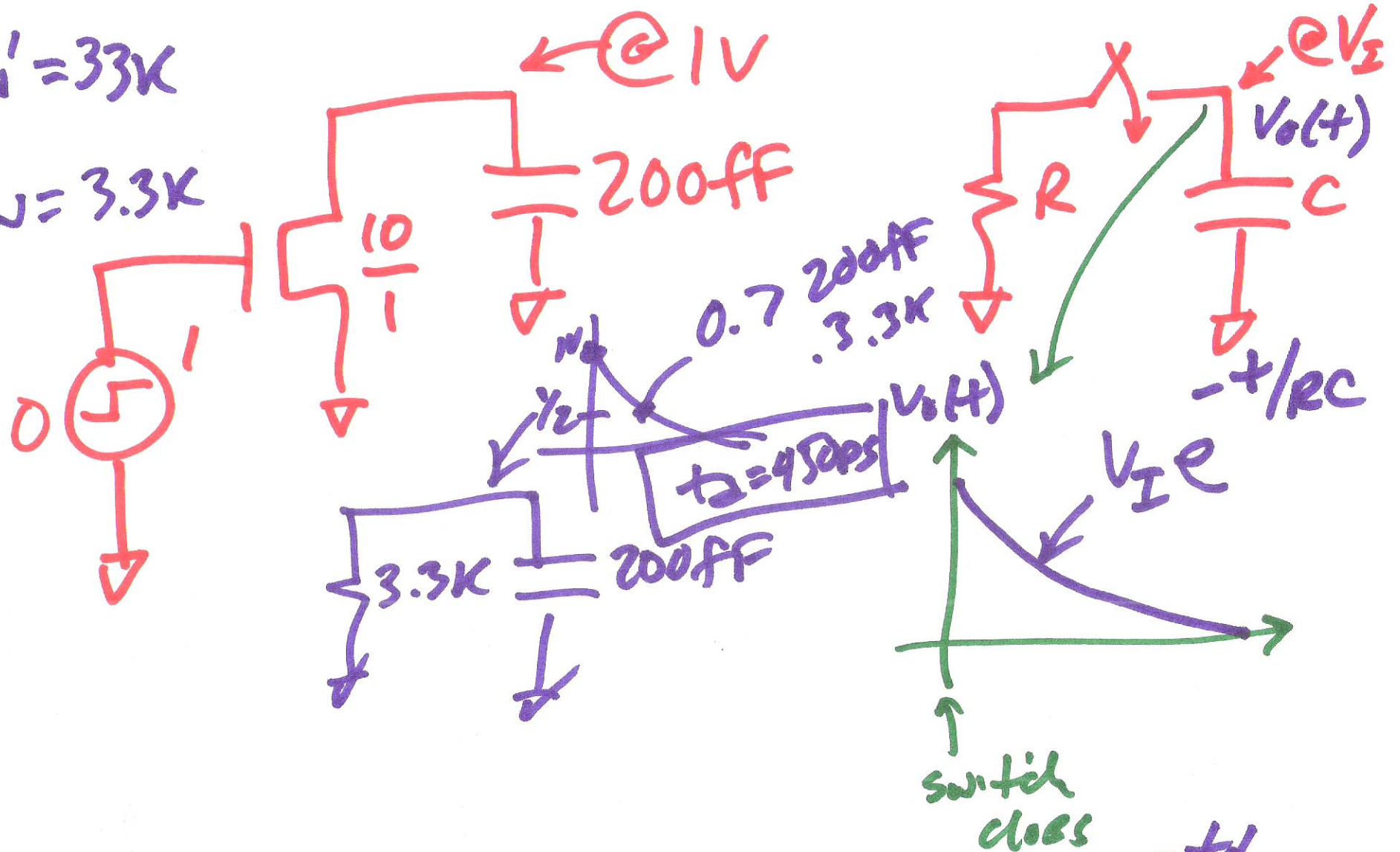

$$t_{50\%} = -RC \ln 0.5 = +0.69RC$$

$$\frac{V_I}{2} = V_I \cdot e^{-\frac{t}{RC}}$$

$$\boxed{0.7RC}$$

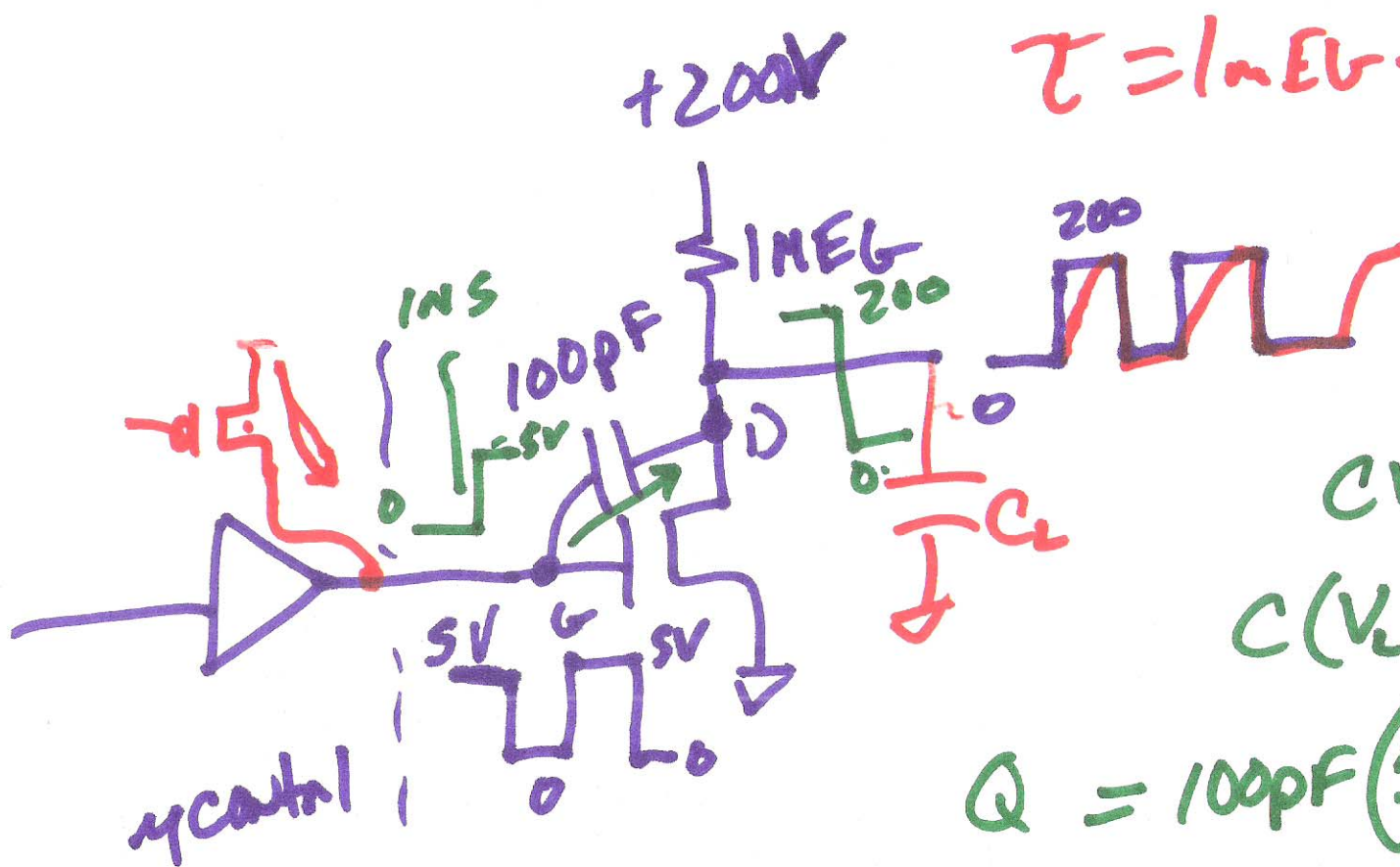

$$\tau = \ln EV \cdot C_L$$

$$CV = Q$$

$$C(V_L - V_R) = Q$$

$$Q = 100pF(5 - (-200))$$

$$1 + |A|$$



$$I = \frac{205nC}{1ns}$$

$$20500pE$$

$$20.5nE$$

$$I = 20.5A!$$

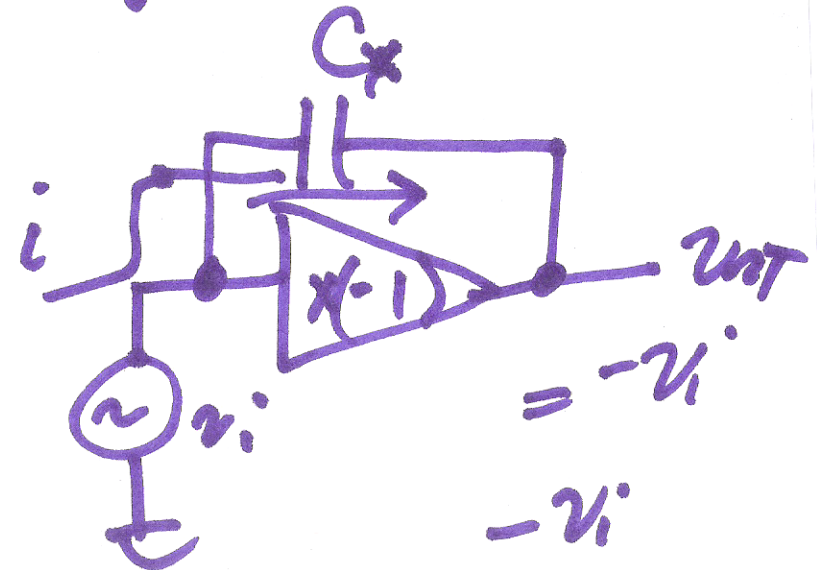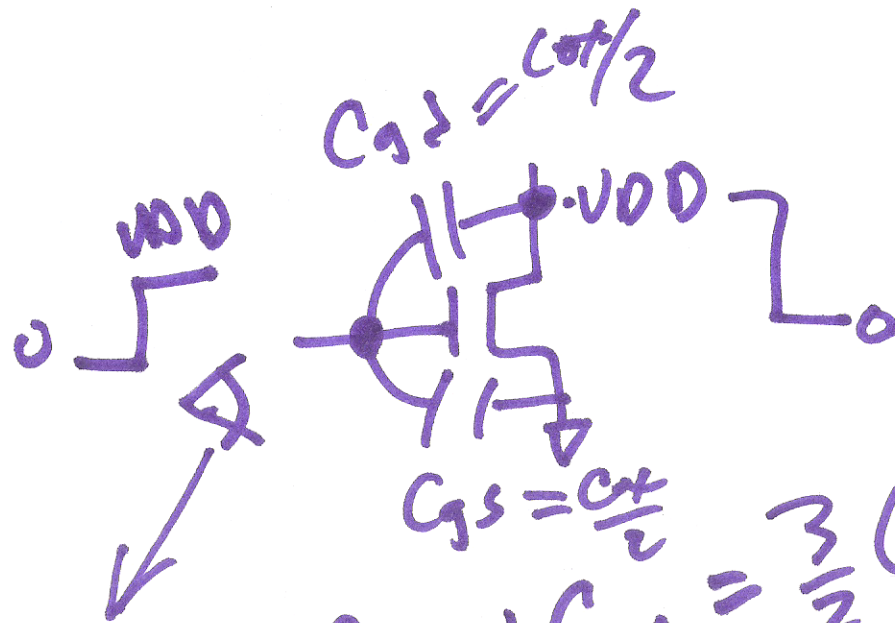Assume $C_{gd} \approx C_{gs} \approx C_{ox}/2$




$$C_{tot} = 2C_{gd} + C_{gs} = \frac{3}{2}C_{ox}$$

$$v_i - v_{out} = \frac{v_i - v_{out}}{1/j\omega C_x}$$

$$= \frac{2v_i}{1/j\omega C_x} = \frac{v_i}{1/j\omega 2C_x}$$

5)

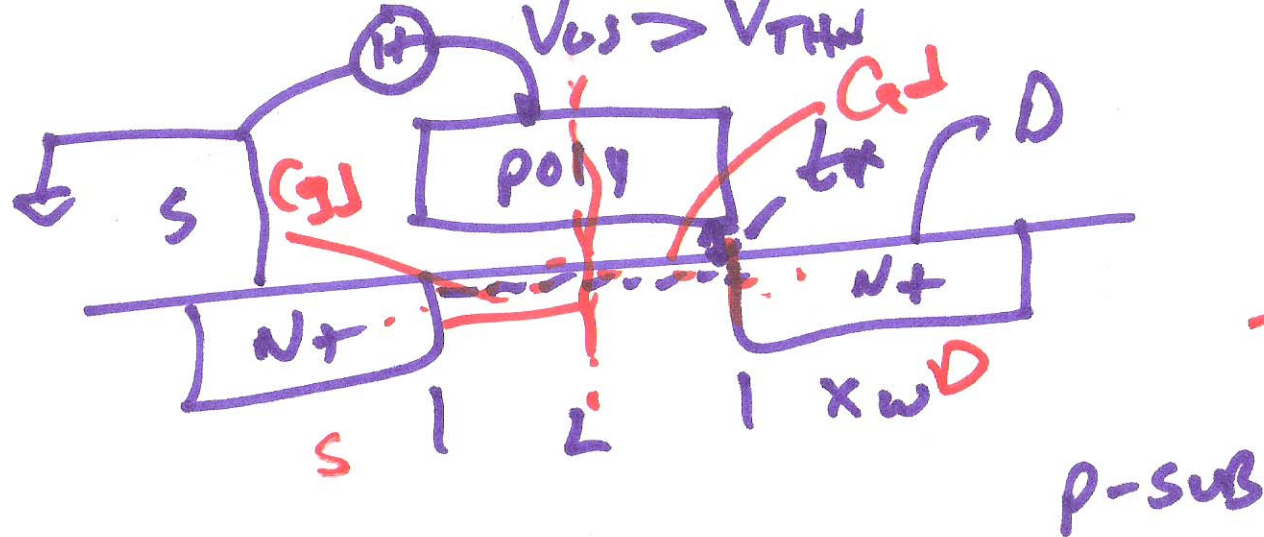


$$C_{ox}' = \frac{\epsilon_{ox}}{t_{ox}}$$

$$C_{ox} = C_{ox}' \cdot W \cdot L = \frac{\epsilon_{ox} \cdot W \cdot L}{t_{ox}}$$

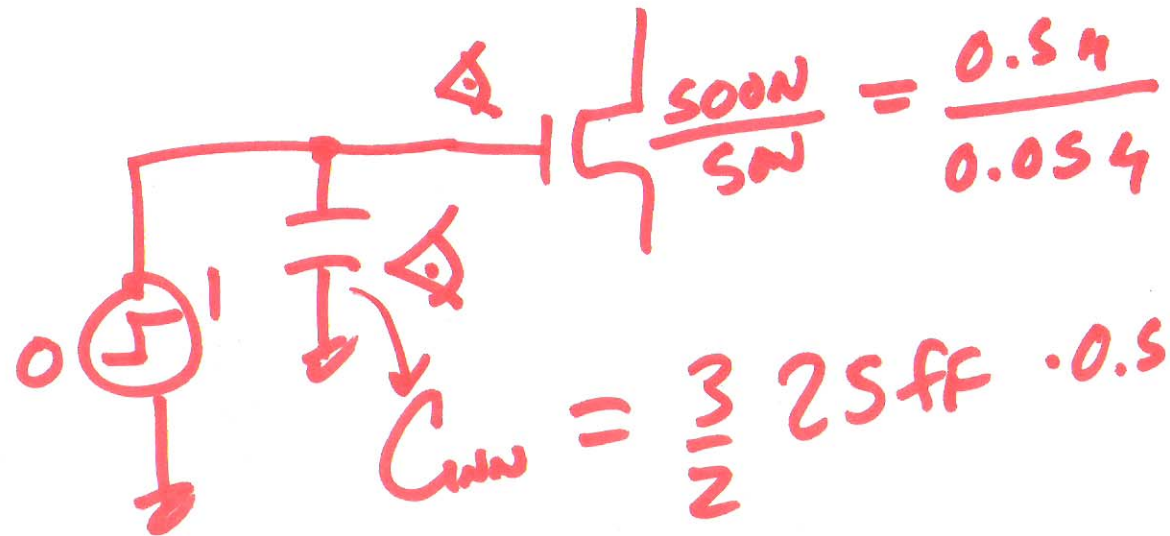6)

$$C_{ox}' = 25 \text{ fF}/\mu\text{m}^2$$



$$C_{inn} = \frac{3}{2} \cdot 25 \text{ fF} \cdot 0.5 \cdot 0.05$$

$$Q = C_{inn} \cdot 1 = 0.9375 \text{ fC}$$

$$\frac{Q}{T} = I$$

$$30 \mu\text{s} \cdot 30 \text{ pS} = 900 \text{ e-18} = .9 \text{ fC}$$