

Self-Biased PLL/DLL

ECG721

60-minute Final Project Presentation

Wenlan Wu

Electrical and Computer Engineering

University of Nevada Las Vegas



Outline

- Motivation
- Self-Biasing Technique
- Differential Buffer Delay
 - Symmetric Load
- Bias Generator
- Self-Biased DLL
 - Zero-offset charge pump
- Self-Biased PLL
 - Feed-forward Zero



Motivation

- High-speed I/O \longleftrightarrow High-freq. clock signal
- Jitter:
 - supply and substrate noise
 - process variation

Target: design a low jitter PLL/DLL




Jitter

- Definition: jitter is the deviation from, or displacement of true periodicity of a presumed signal in electronics and telecommunications, often is relation to a reference clock source.
- Jitter can be observed in frequency of successive pulses, the signal amplitude, or phase of periodic signals.




Jitter-Time Domain

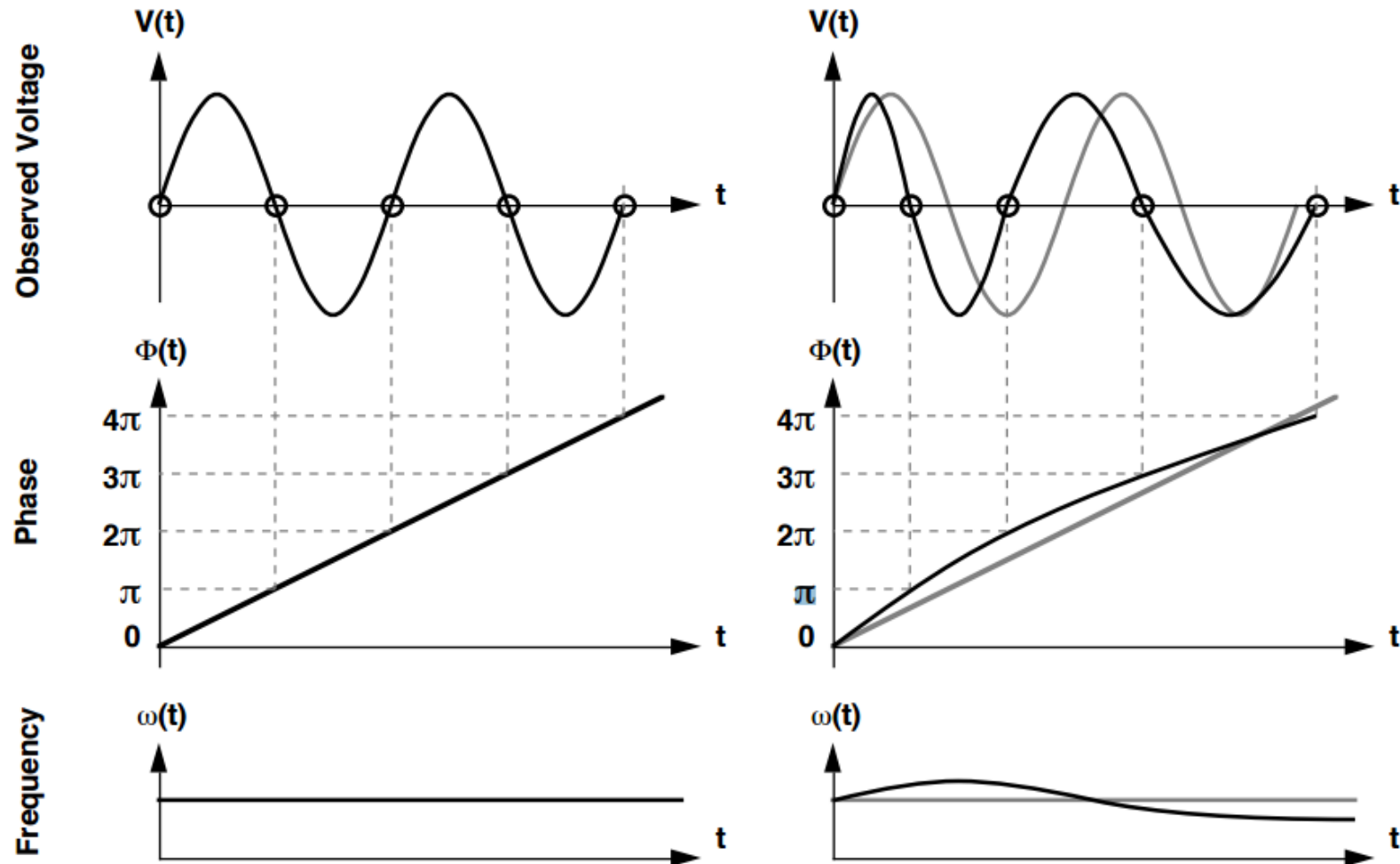



Jitter-Freq. Domain

 

Model



Outline

- Motivation
- **Self-Biasing Technique**
- Differential Buffer Delay
 - Symmetric Load
- Bias Generator
- Self-Biased DLL
 - Zero-offset charge pump
- Self-Biased PLL
 - Feed-forward Zero



Self-Biasing

- Avoid the need for external biasing circuit
- Allow circuits to choose the operating bias levels in which they function best
- Operating bias levels are essentially established by the operating frequency



Self-Biasing Merits

- Provide a bandwidth tracking the operating frequency
- Broad frequency range minimized supply and substrate noise
- Fixed damping factor
- Bandwidth to operating frequency ratio is determined by a ratio of capacitances giving effective process technology independence
- No need of external bias circuit





Outline

- Motivation
- Self-Biasing Technique
- **Differential Buffer Delay**
 - **Symmetric Load**
- Bias Generator
- Self-Biased DLL
 - Zero-offset charge pump
- Self-Biased PLL
 - Feed-forward Zero



Differential Buffer Delay

  - PLL/DLL needs buffer stage with low noise
- Symmetric load and replica-feedback biasing (half-replica bias circuit)





Symmetric Load

- Diode-connected PMOS in shunt with an equally sized biased PMOS
- Voltage-controlled resistor (Fig.19.57)

Output Swing
Vref to ground


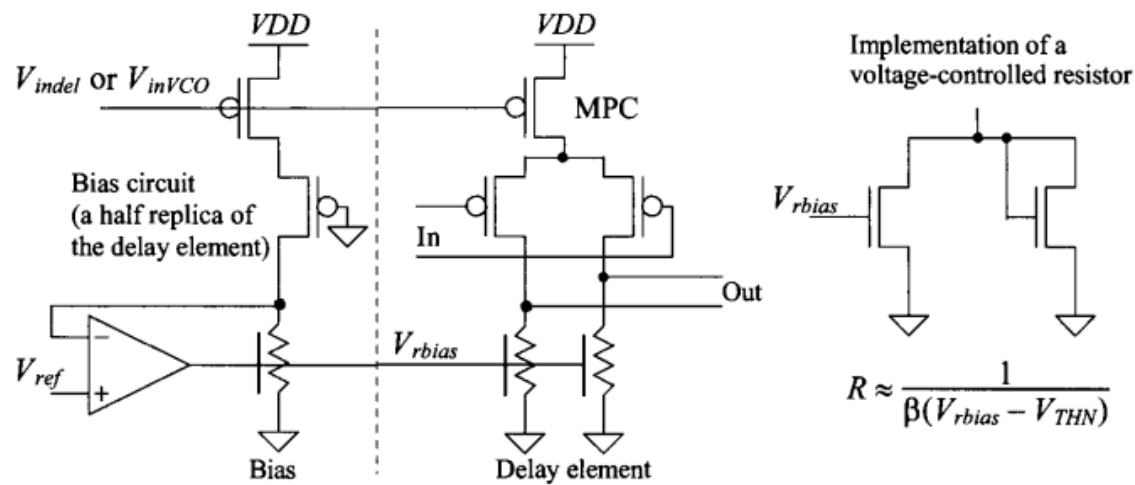


Figure 19.57 A differential delay element based on a voltage-controlled resistor. The bias circuit adjusts the value of the resistors used in the delay elements to sink the current sourced by the p-channel MOSFETs.

 

Symmetric Load

- V_{BN} dynamically changing the bias current which is two times of diode-connected PMOS with V_{ctrl} as gate voltage
- Different V_{ctrl} has different bias current
- Output swing is VDD to V_{ctrl}




Model



Symmetric Load

 - Load I-V curve is symmetric about the output center voltage
- Effective resistance changes with V_{ctrl}
→ buffer delay changes with the control voltage
- V_{BN} is changed by V_{ctrl} to maintain the symmetric IV characteristics





Differential Buffer Delay

- Good control delay
- High dynamic supply noise rejection
- V_{BN} can compensate drain and substrate voltage variations by dynamically biasing the NMOS current source
- The layout is very compact




Outline

- Motivation
- Self-Biasing Technique
- Differential Buffer Delay
 - Symmetric Load
- **Bias Generator**
- Self-Biased DLL
 - Zero-offset charge pump
- Self-Biased PLL
 - Feed-forward Zero



Bias Generator

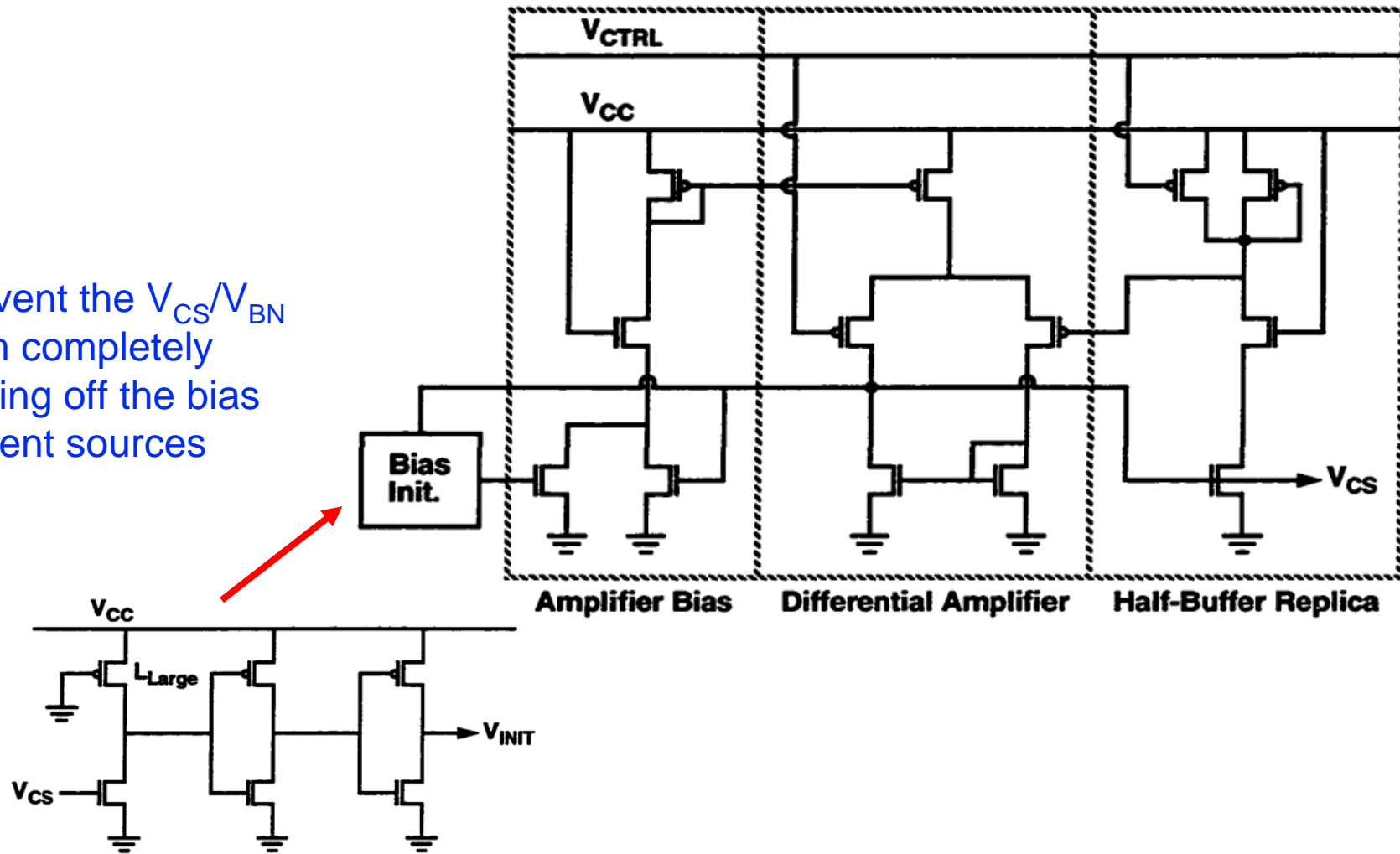
Prevent the V_{CS}/V_{BN} from completely turning off the bias current sources





Bias Generator

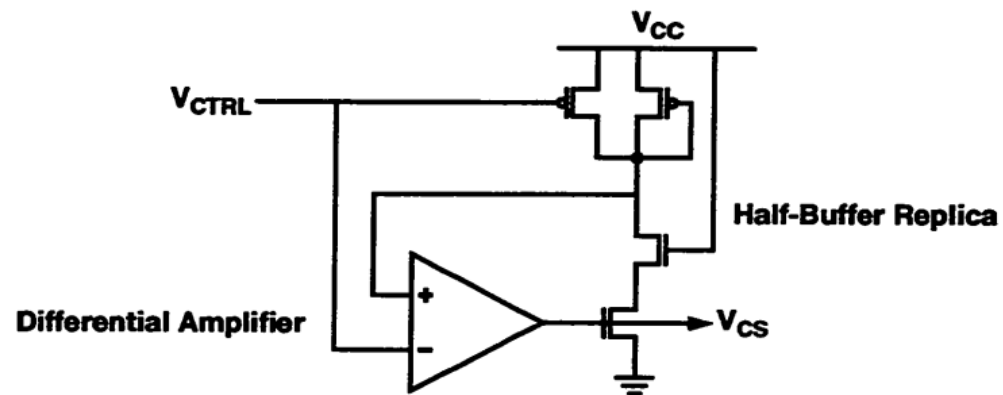- V_{BN} and V_{BP} produced by V_{ctrl}
- V_{BN} keeps **Bias current for buffer delay (constant and independent of supply voltage) by using a differential amplifier and a half-buffer replica**
- V_{BP} : Additional half-buffer replica to provide a buffer of V_{ctrl}






Outline

- Motivation
- Self-Biasing Technique
- Differential Buffer Delay
 - Symmetric Load
- Bias Generator
- **Self-Biased DLL**
 - **Zero-offset charge pump**
- Self-Biased PLL
 - Feed-forward Zero



Self-Biased DLL

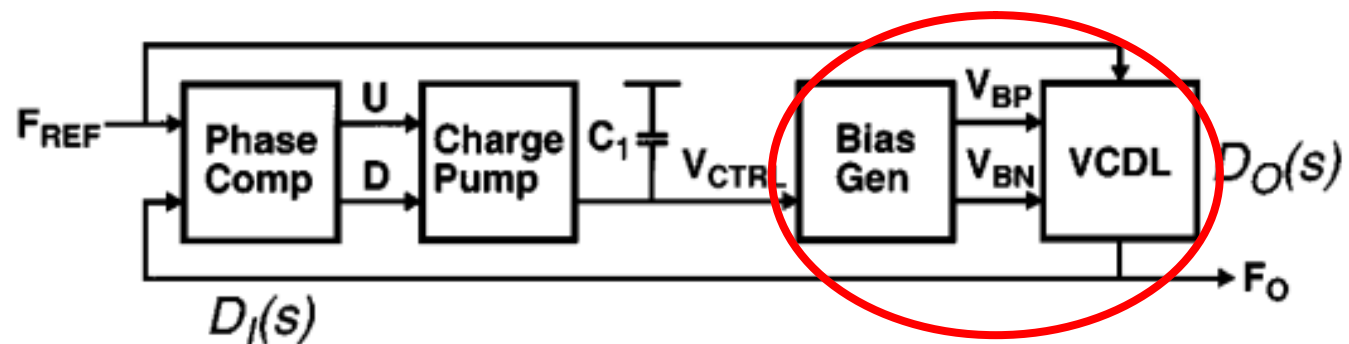- Phase detector/Phase comparator
- Charge pump
- Loop filter
- Bias generator
- VC DL






Self-Biased DLL

- DLL is designed to re-buffer the input clock without adding any effective delay
- PFD detects the phase error between the input and feedback output
- Forward path integrates the phase error and adjust the delay through VCDL
- Once in lock, the VCDL delay is the integer multiple of the input period




Zero-offset Charge Pump

 

- In-phase inputs requires the UP and DN with an equal and short period of time
- If the inputs of PFD produce no UP or DN pulses, it will take some finite phase difference before a large enough pulse is produced to turn on the charge pump, which leads to a dead-band region




Zero-offset Charge Pump

 

- Produce equal duration of UP and DN outputs when DLL is in lock
- Composed of Two NMOS source coupled pairs with separate same buffer bias current and connected by a current mirror made from symmetric loads




Zero-offset Charge Pump

 

- The left source-couple pair behaves like half-buffer replica and produce V_{ctrl} at the current mirror node
- The right PMOS has V_{ctrl} in its gate and drain




Zero-offset Charge Pump

 

- Zero static phase offset when both the UP and DN outputs of the phase comparator with equal duration on every cycle of in-phase inputs




Zero-offset Charge Pump

 


- $\Delta\omega = \omega_o - \omega_{ref} > 0$, UP pulse is longer than DN pulse. $I_{d1} = I_{d2}$, $I_{up} > I_{d2}$, so I_{cap} will discharge the cap of loop filter, reducing V_{ctrl} .
- $\Delta\omega = \omega_o - \omega_{ref} = 0$, UP and DN outputs for equal durations on every cycle. $I_{d1} = I_{d2} = I_{up}$



Zero-offset Charge Pump

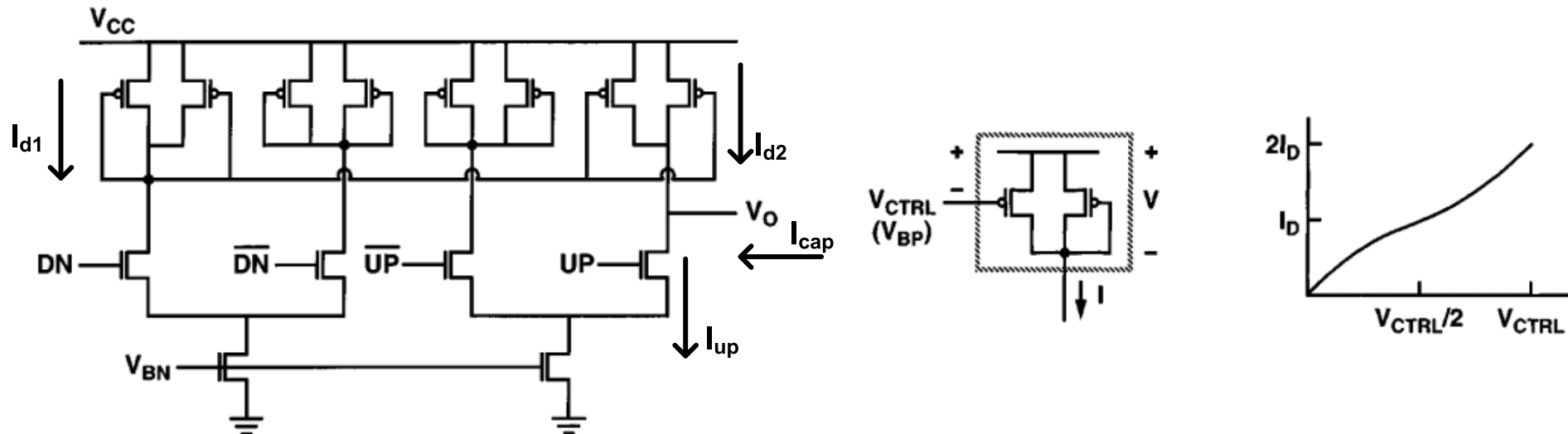


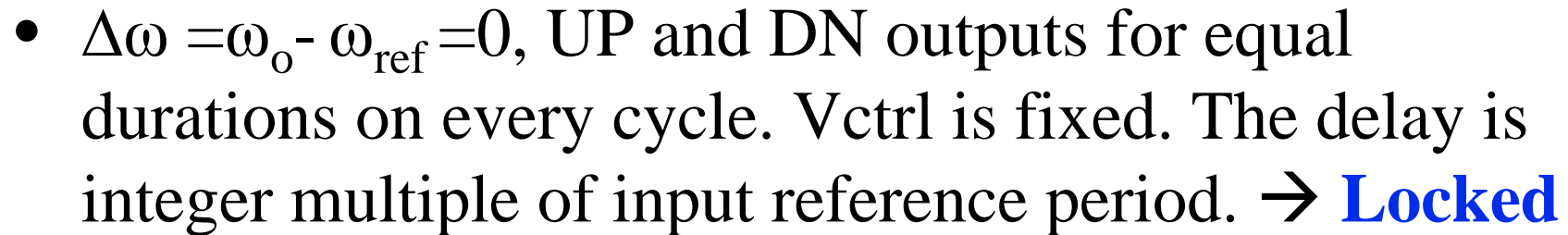- $\Delta\omega = \omega_o - \omega_{ref} > 0$, smaller V_{ctrl} makes the $V_{SG} = V_{DD} - V_{ctrl}$ larger, which means larger current and smaller effective resistance. Hence, large charge offset leads to reduce the delay or small phase offset → **Unlocked**





Self-Biased DLL

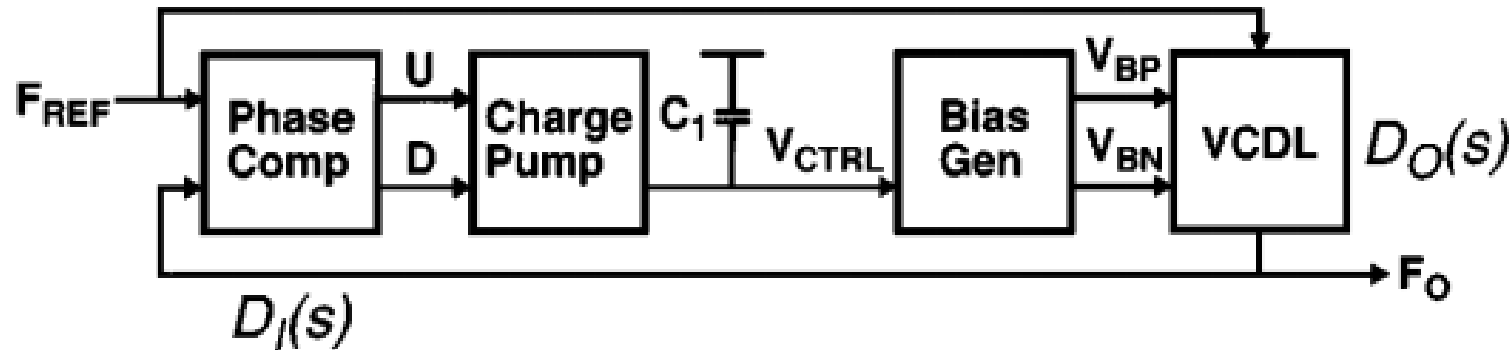

$\omega_o > \omega_{\text{ref}}$: UP longer pulse, discharging C_1 ,
reducing V_{ctrl} , larger current, smaller effective
resistance, smaller delay

$\omega_o < \omega_{\text{ref}}$: DN longer pulse, charging C_1 ,
increasing V_{ctrl} , smaller current, larger
effective resistance, larger delay



Self-Biased DLL

- Input tracking jitter will be further reduced by setting the loop bandwidth as close as possible to the operating frequency

- The loop bandwidth ω_N is given by

$$\omega_N = I_{CH} * K_{DL} * F_{REF} * \frac{1}{C1}$$

- If charge pump current I_{CH} and VCDL gain K_{DL} are constant, the loop bandwidth will track the operating frequency



Self-Biased DLL

- The VCDL gain for a n-stage is given by

$$K_{DL} = \left| \frac{dD}{dV_{ctrl}} \right| = \frac{C_B}{4 * I_D}$$

C_B is the total buffer output capacitance for all stages, D is the delay for an n-stage VCDL

- I_{CH} is set equal to the buffer bias current $2 * I_D$ cancelling the K_{DL} depending on $1/I_D$ and leading to loop bandwidth that track the operating frequency without constraining the operating frequency range



Self-Biased DLL

- I_{CH} can be set to some multiple x of the buffer bias current such that

$$I_{CH} = x * 2I_D$$

- The loop bandwidth to operating freq. ratio is given by

$$\begin{aligned} \frac{\omega_N}{\omega_{ref}} &= I_{CH} * K_{DL} * \frac{1}{C1} \frac{F_{REF}}{\omega_{ref}} \\ &= x * 2I_D * \frac{C_B}{4 * I_D} * \frac{1}{C1} * \frac{1}{2\pi} = \frac{x}{4\pi} \frac{C_B}{C1} \end{aligned}$$



Self-Biased DLL

The loop bandwidth to operating frequency ratio is given by

$$\frac{\omega_N}{\omega_{ref}} = \frac{x}{4\pi} \frac{C_B}{C1}$$

The capacitance ratio determined the loop bandwidth to operating frequency ratio and reduced the process technology sensitivity




Outline

- Motivation
- Self-Biasing Technique
- Differential Buffer Delay
 - Symmetric Load
- Bias Generator
- Self-Biased DLL
 - Zero-offset charge pump
- **Self-Biased PLL**
 - **Feed-forward Zero**



Self-Biased PLL

 

- Phase detector, charge pump, loop filter, bias generator, and VCO, feedback divider
- Loop filter needs one resistor for stability
- Once in lock, the VCO generates output frequency N times larger than input reference
- The PLL can be used to multiply and rebuffer an input clock without adding delay



Self-Biased PLL

- Use the second-order system knowledge to analyze the closed loop response to get the damping factor and natural frequency

$\xi = \frac{1}{2} \sqrt{\frac{1}{N} I_{CH} K_{VCO} R^2 C_1}$	$\xi = \frac{\omega_n}{2} RC_1$
$\omega_n = \frac{2\xi}{RC_1}$	$\omega_n = \sqrt{\frac{K_D K_{VCO}}{NC_1}}$



Self-Biased PLL

- Make both damping factor and $\omega_n/\omega_{\text{ref}}$ are constant to get no limit on the operating frequency range and so that the jitter performance can be improved

$$\xi = \frac{1}{2} \sqrt{\frac{1}{N} I_{CH} K_{VCO} R^2 C_1}$$

- Constant damping factor = I_{CH} equal to the buffer bias current + R vary inversely proportionally to $\sqrt{\text{buffer bias current}}$



Self-Biased PLL

$$\xi = \frac{\omega_n}{2} RC_1$$

- Constant ξ makes ω_n is proportional to the $\sqrt{\text{buffer bias current}}$
- In order to keep $\omega_n/\omega_{\text{ref}}$ constant, the VCO operating frequency should also be proportional to the $\sqrt{\text{buffer bias current}}$




Self-Biased PLL

- VCO frequency is proportional to $V_{ctrl} - V_{th}$ which is the square root of I_D , the slope is constant means K_{VCO} is constant. So the reference frequency is proportional to the square root of the buffer bias current




Feed-Forward Zero

 

- Transformation of the loop filter for the integration of the loop filter resistance
- Make the resistor is proportional to $1/\sqrt{I_{buffer}}$
- diode-connected PMOS with resistance $1/g_m$, which is inversely proportionally to the $\sqrt{\text{buffer bias current}}$



Self-Biased PLL

 

- Voltage drop across capacitor and resistor are generated separately and summed to form the control voltage V_{CTRL} , as long as the same charge pump current applied to each of them
- Bias generator can conveniently implement this voltage source and resistor since it buffers V_{CTRL} to form V_{BP} with finite output resistance
- The self-biased PLL can be completed by adding an additional charge pump current to generate V_{BP}



Self-Biased PLL

- The operating frequency for an n-stage VCO is

$$F = \frac{\sqrt{2 * k * I_D}}{C_B}$$

- VCO gain K_{VCO} is given by

$$K_{VCO} = \frac{k}{C_B}$$

- The charge pump current and loop filter resistor are

$$I_{CH} = x * (2 * I_D) \quad R = \frac{y}{\sqrt{8 * k * I_D}}$$



Self-Biased PLL

- The damping factor is then given by

$$\xi = \frac{1}{2} \sqrt{\frac{1}{N} I_{CH} K_{VCO} R^2 C_1} = \frac{y}{4} \sqrt{\frac{x}{N}} \sqrt{\frac{C_1}{C_B}}$$

- The loop bandwidth to operating frequency ratio is given by

$$\frac{\omega_n}{\omega_{ref}} = \frac{2\xi}{RC_1} \frac{1}{2\pi F_{ref}} = \frac{\sqrt{xN}}{2\pi} \sqrt{\frac{C_B}{C_1}}$$



Self-Biased PLL

- The damping factor is a constant times the square root of the ratio of two capacitances
- The loop bandwidth to operating frequency ratio is also a constant times the square root of the ratio of the same two capacitances
- The loop bandwidth will track operating frequency and sets no constraint on the operating frequency range
- Constant $\omega_n / \omega_{\text{ref}}$, ξ can be set to minimize jitter accumulation over all operating frequencies



References

1. John G. Maneatis, "Low-Jitter Process-Independent DLL and PLL Based On Self-Biased Techniques," in IEEE Journal of Solid-State Circuits, Vol.33, No.11, Nov 1996.
2. John G. Maneatis, "Precise Delay Generation Using Coupled Oscillators," in ProQuest Dissertations and Theses, 1994.
3. ece.wpi.edu/analog/resources/plljitter.pdf



Q & A

