

# Design of Analog Phase-Locked Loops (A tutorial)

---

BY DAVID SANTIAGO

ECG 721 – MEMORY CIRCUIT DESIGN, FALL 2021


# Guideline of APLL Design

---

- General Phase-Locked Loop Design
- Types of Phase-Locked Loops
- The Phase Detector
- Filters
- Voltage-Controlled Oscillators
- Simulation of The Analog Phase-Locked Loop

# General Phase-Locked Loop Design

---

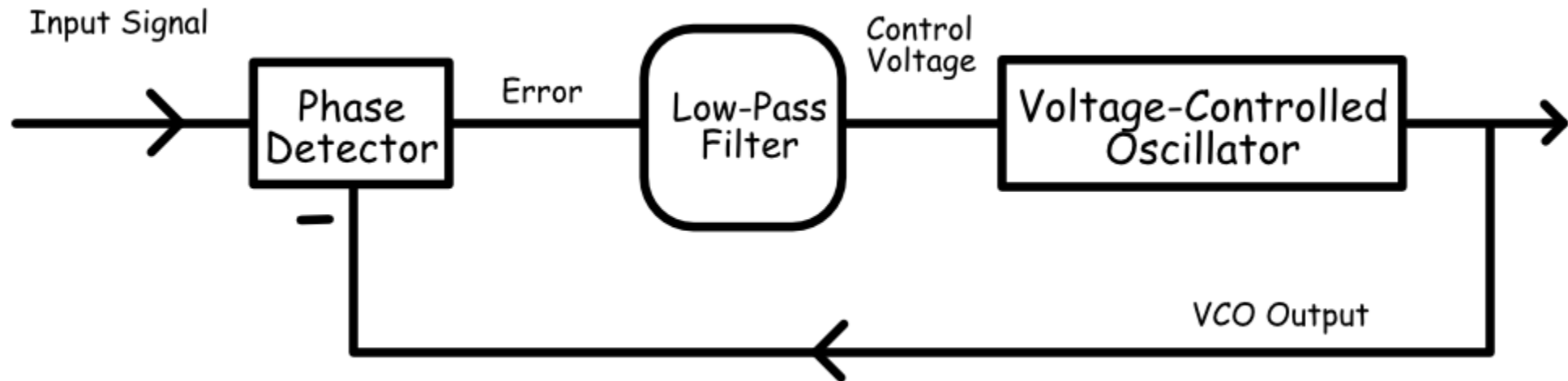

- The Phase-Locked Loop (PLL) is a feedback system that creates a frequency from a Voltage Controlled Oscillator (VCO) that is synchronous to the input signal.
- The output of the VCO is subtracted to the input signal to produce an error signal that would control the VCO frequency that minimizes the error signal.

# Types of Phase-Locked Loop Systems

---

## ❑ Analog PLL (APLL)

- ❑ Contains analog circuitry
- ❑ Multiplier circuit used as a phase detector
- ❑ Low-Pass Filter used to filter out undesired signal. Can be active LPF.
- ❑ VCO made using inverters


## ❑ Digital PLL (DPLL)

- ❑ XOR or Phase Frequency Detector (PFD) used as a phase detector
- ❑ Low-Pass used to filter out undesired signal. Can also be active LPF
- ❑ A clock divider used to generate signal for the XOR clock input.

## ❑ All-Digital PLL (ADPLL)



- ❑ Same structure as DPLL
- ❑ All components replaced with its digital counterpart (Digital Filter replacing LPF, Digital VCO replacing VCO).

# The Analog Phase-Locked Loop (APLL)

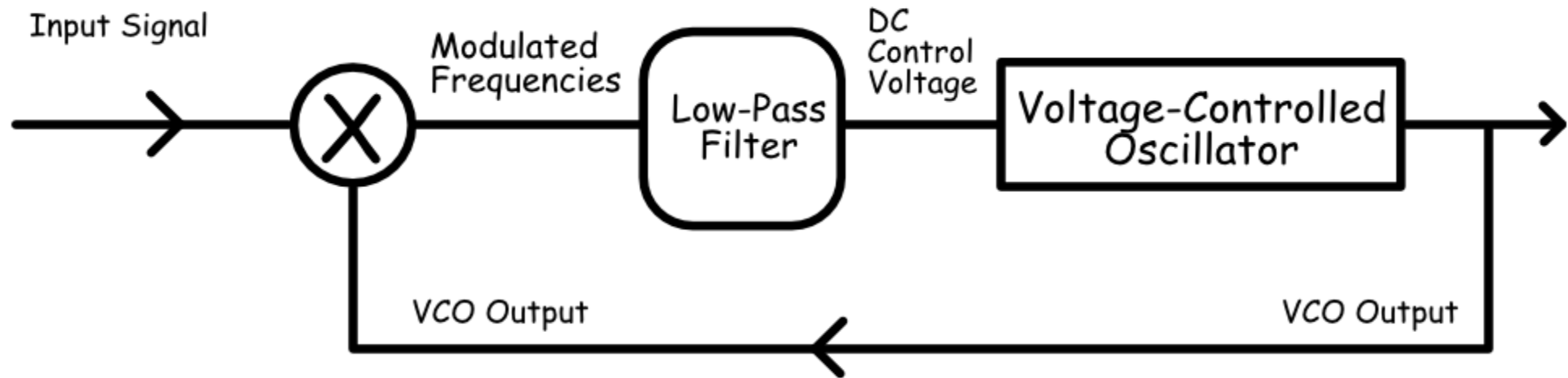

- The first component of the APLL is the multiplier. The multiplier in this application will serve as the phase detector.
- The Low-Pass Filter will see two frequencies (discussed later) and filter out the high frequency. This can be achieved with an RC filter.
- The VCO will output a certain frequency depending on the output of the LPF.

# The Multiplier Circuit

 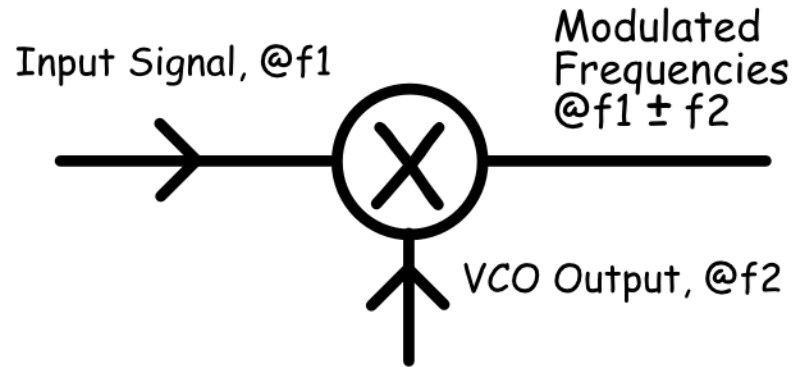

- The multiplier circuit will take in two input signals with different frequencies and produces two new modulated frequencies.
- In this application, the difference between the two frequencies will serve as a phase deviation.
- If the frequencies are in phase, then the result is a constant DC error.
- Else, a frequency slightly above DC will be produced.

# Multiplier Mathematics

---

$$V_{in}(t) = V_{in} \cdot \cos(2\pi f_1 \cdot t + \theta_1)$$

$$V_{clk}(t) = V_{clk} \cdot \cos(2\pi f_2 \cdot t + \theta_2)$$

Recalling the trigonometric identity:

$$\cos(A) \cdot \cos(B) = \frac{\cos(A+B) + \cos(A-B)}{2}$$

$$V_{mult}(t) = \frac{V_{in} \cdot V_{clk}}{2} \cdot [\cos(2\pi f_1 \cdot t + \theta_1 + (2\pi f_2 \cdot t + \theta_2)) - \cos(2\pi f_1 \cdot t + \theta_1 - (2\pi f_2 \cdot t + \theta_2))]$$

If  $f_1 = f_2 = f$  :


$$V_{mult}(t) = \frac{V_{in} \cdot V_{clk}}{2} \cdot [\underbrace{\cos(4\pi \cdot t + \theta_1 + \theta_2)}_{\text{High Frequency to Filter in LPF}} - \underbrace{\cos(\theta_1 - \theta_2)}_{\text{DC Phase Error}}]$$

High Frequency to  
Filter in LPF

DC Phase Error

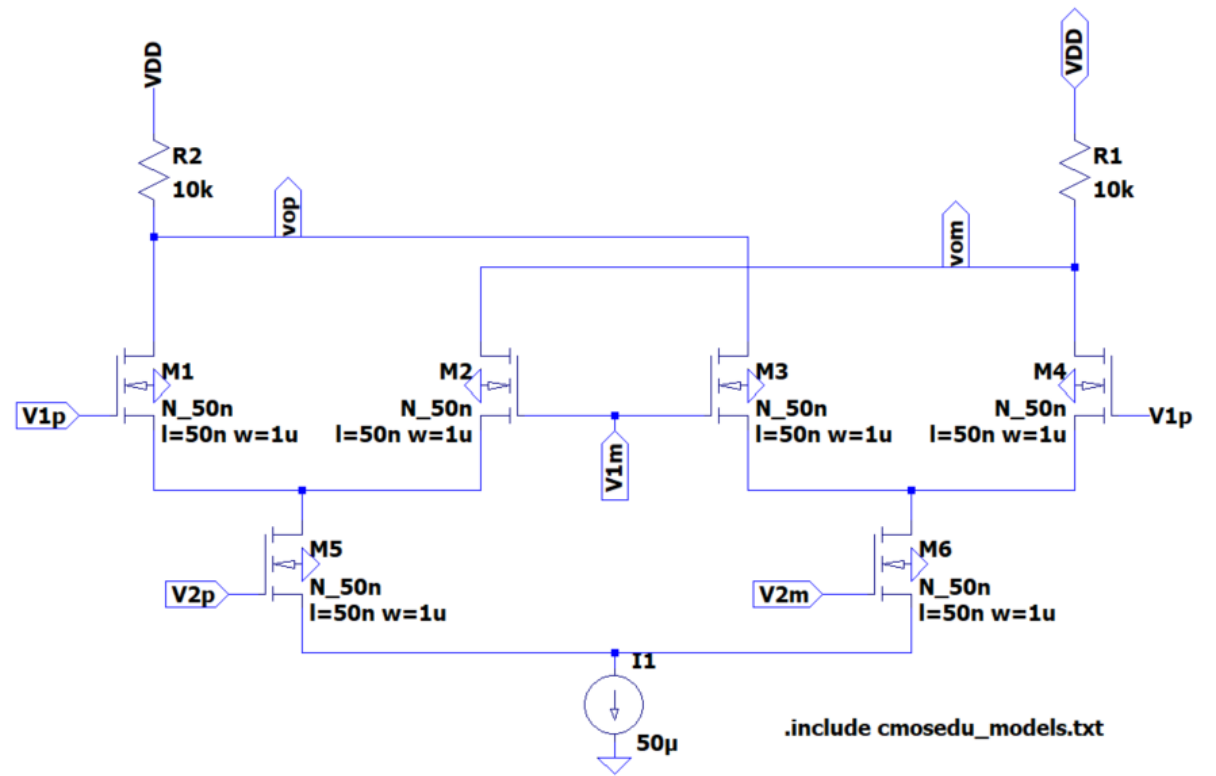
# Multiplier Circuit: LTSpice

- The multiplier circuit used is a 4-Quadrant multiplier, where the input and output signals are fully differential and require a positive and negative component.
- The sizes are chosen so that we use the smallest length for speed, and a width that would sink a nominal bias current of  $10\mu\text{A}$ . In this circuit, devices M1-4 each will nominally sink around  $12.5\mu\text{A}$ , which is sufficient current.







# Phase Detector (PD) Sim: $\phi = 0\pi$

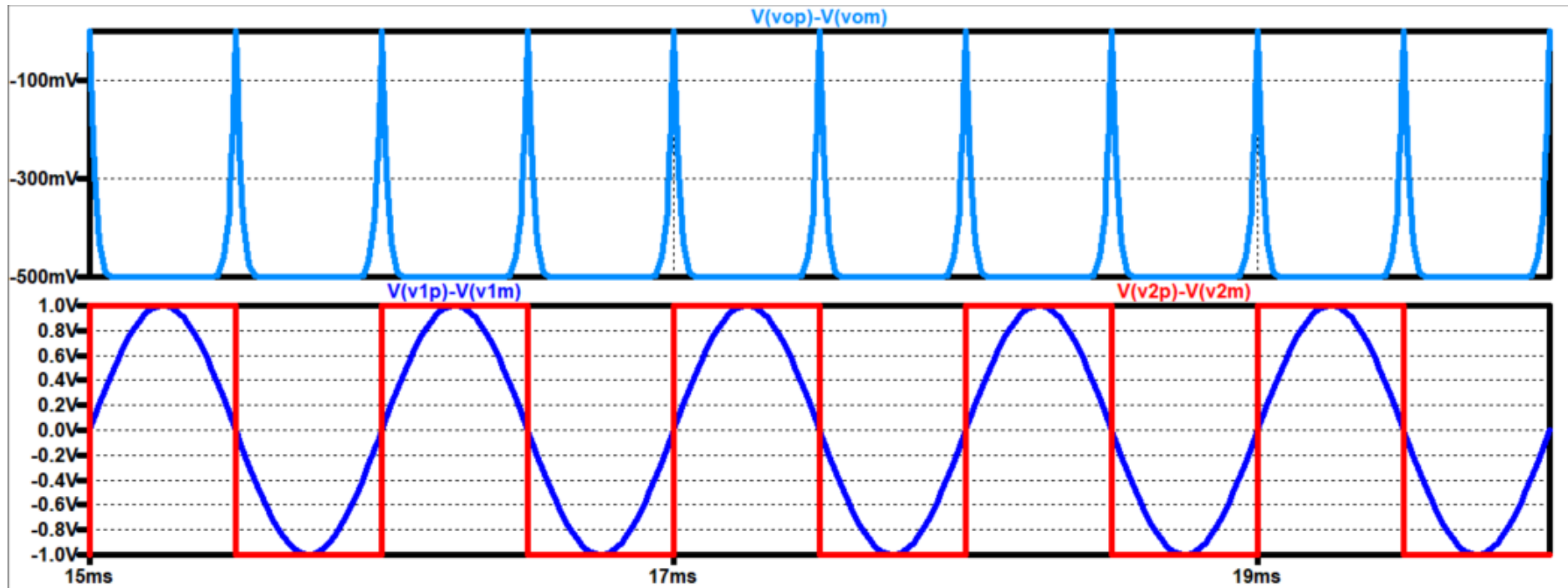


From above, the sine wave (input data) and square wave (from VCO) have no difference in phase, which results in a DC average voltage of -0.5V
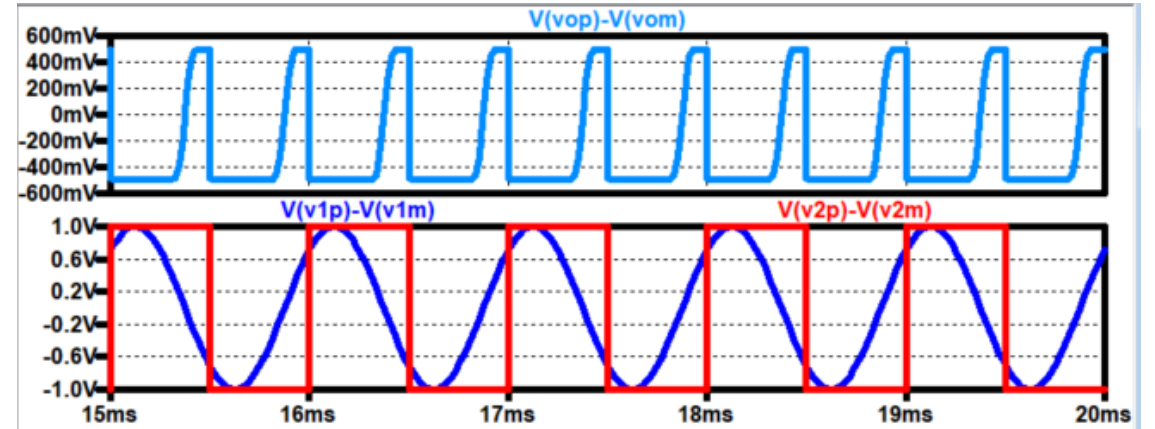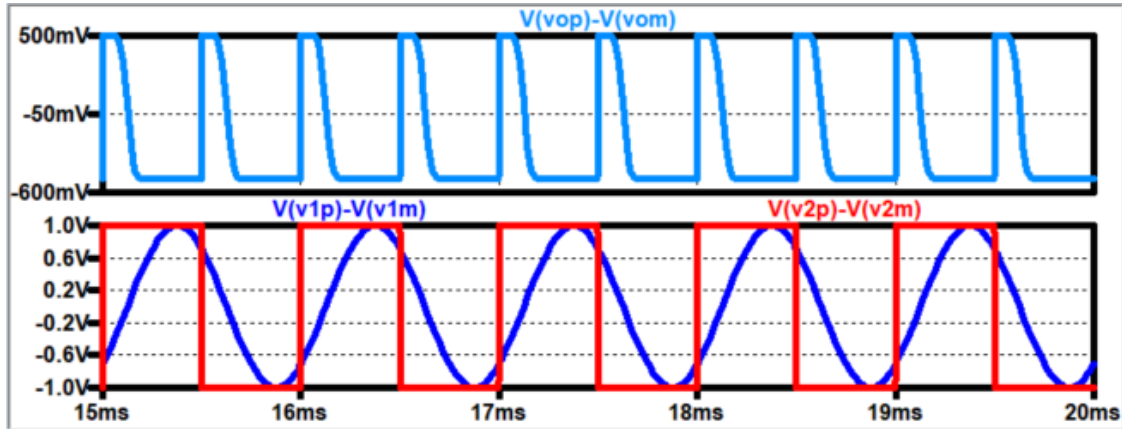
# Phase Detector (PD) Sim: $\phi = \frac{\pi}{4}$ (or $-\frac{\pi}{4}$ )




- Moving the phase of the input by either  $\frac{\pi}{4}$  or  $-\frac{\pi}{4}$ , we see that the average DC value will be slightly above -0.5V for both plots, which signifies that as we get to  $\pi$  or  $-\pi$ , we should get a max voltage of +0.5
 
# Phase Detector (PD) Sim: $\phi = \frac{\pi}{2}$




- From above, as the sine wave is shifted by  $\frac{\pi}{2}$ , we will have an average voltage of 0V

# Phase Detector (PD) Sim: $\phi = \pi$

 

- With the rising edges having a phase difference of  $\pi$ , the average voltage is 0.5V.

# Phase Detector Gain

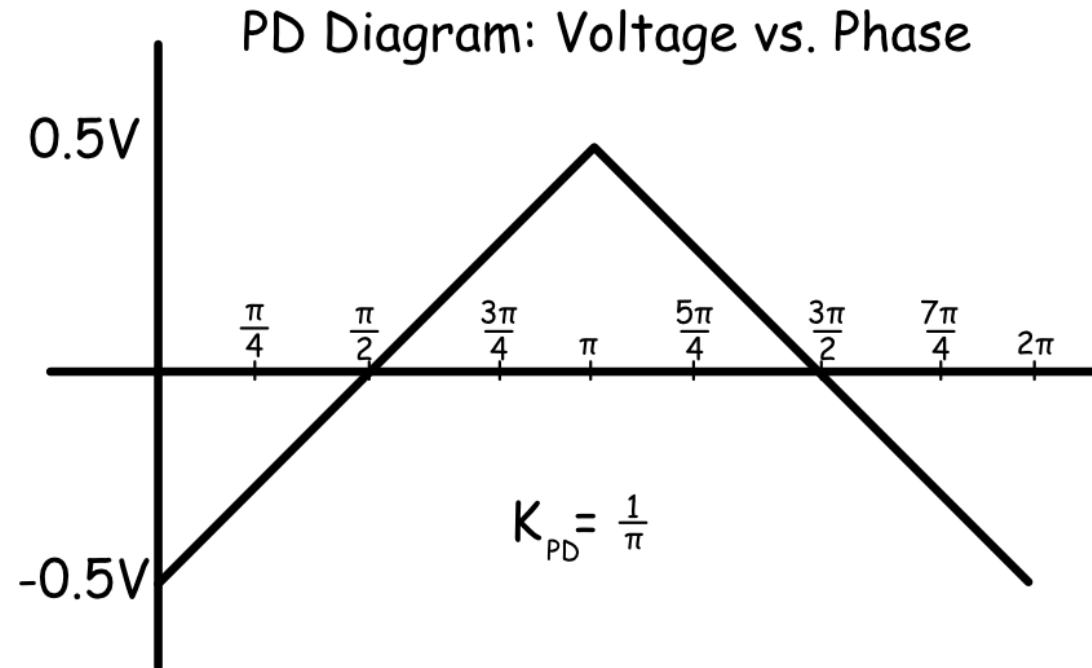

- From the above slides, the average voltage can be shown as a function of phase, which is estimated above.
- The gain of the phase detector is calculated as the average voltage over phase in radians

# Low-Pass Filter

- This stage will filter out any unwanted frequencies and harmonics that are a consequence of using a multiplier and square wave.

## □ Main Filters

- Passive: Uses resistors and capacitors
- Active: Amplifier is used


## • Single-Pole Filter:

- Simplest to tune
- Less components
- Prone to having poor damping factor

## • Lag-Loop Filter:


- Contains a single-zero in numerator
- Zero in numerator assists with phase
- Damping factor increased for shorter lock times

## Single-Pole RC Filter

 

$$K_F = \frac{1}{1 + j\omega R_1 C}$$

## Single-Pole, Single-Zero RC Filter

 


$$K_F = \frac{1 + j\omega R_2 C}{1 + j\omega (R_1 + R_2) C}$$
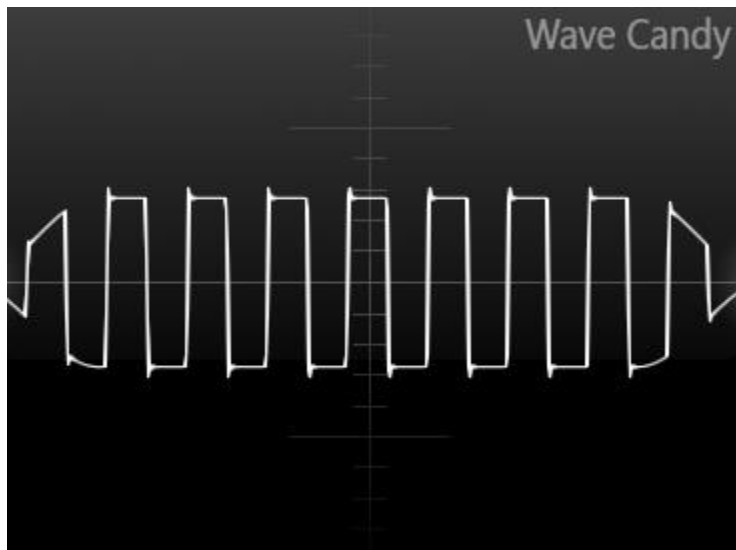
# Why use LPF?

- The Low-Pass Filter will feed into the VCO, which will require an average DC voltage, else, there is a chance that the PLL will have a bad VCO settling time
- A square wave is used as one of the inputs. Looking at the spectrum, we can see the following harmonics:

Fundamental Frequency: 264Hz  
(Middle C on Piano)



Harmonics of Square wave  
(Each bar-line represents a single sine wave)




# Why use LPF?

- By filtering out the high frequencies, the square wave will start to look more like a single frequency or even DC
- Since a sine wave has multiple harmonics (many sine waves), the multiplier circuit will also multiply with those frequencies and create unnecessary amounts of modulated frequencies
- Below is the spectrum of a filtered square wave, and the harmonics are mostly filtered out.
- If the loop filter is omitted, then multiple harmonics will be introduced and create too many nonlinearities



Bandwidth

 



# Small Signals Demonstration (Using FL Studio Music Software)

- The two signals of interest are a sine wave and square wave at the same fundamental frequency of 264Hz (middle C)
- When both signals are at the same frequency, there is a resulting frequency at DC and at twice the fundamental frequency (528Hz)
- By changing the sine wave's frequency, as both signals are multiplied together, the DC and the high frequency will come towards the fundamental frequency



f = 264Hz

f = 528Hz



Frequency @ DC  
moves to right!

f = 264Hz

Freq @ 528Hz moves  
to left!




# APLL Closed-Loop System

- The APLL will have the following block diagram
  - $K_D$  is the PD gain,  $F(s)$  is the LPF gain ( $F(s) = \frac{1}{1 + \frac{s}{\omega_1}}$ ,  $\omega_1 = \frac{1}{RC}$ ),  $A$  is an optional amplifier gain,  $K_O$  is the oscillator gain, and  $\frac{1}{s}$  signifies an integration.

- The closed-loop response of the APLL is:

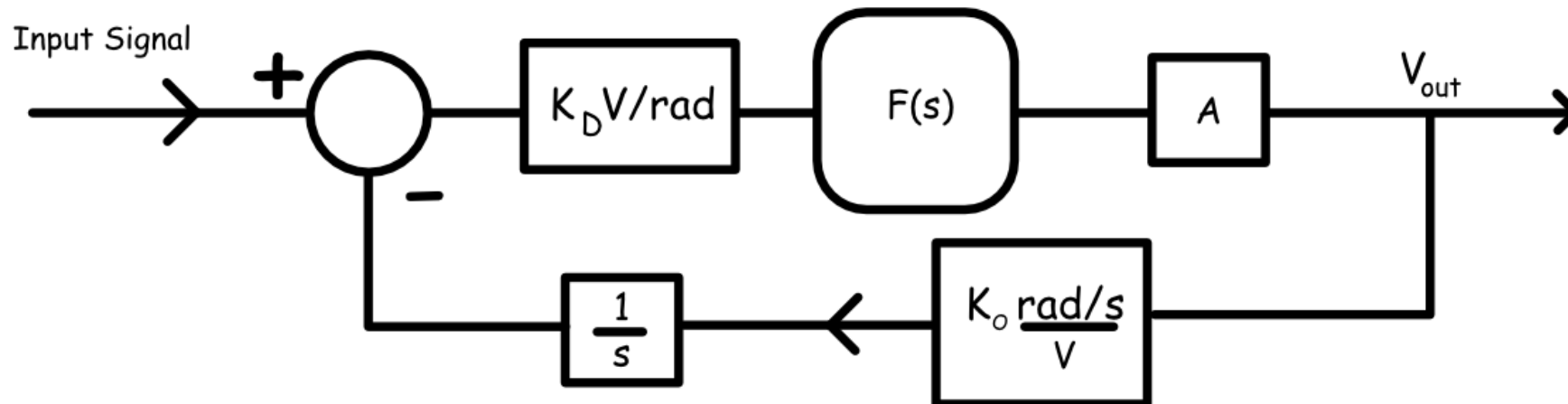- $$\frac{K_D \cdot F(s) \cdot A}{s + K_D \cdot F(s) \cdot A \cdot K_O} = \frac{1}{K_O} \cdot \frac{1}{1 + s \cdot \frac{1}{K_D \cdot F(s) \cdot A \cdot K_O}}$$
, the APLL closed-loop response



# APLL Closed-Loop System

---

- The complete transfer function will be a 2<sup>nd</sup> order system, which will be harder to design but will give great results if done properly
- The following is a general equation for the 2<sup>nd</sup> order APLL, with design parameters:

- $H(s) = \frac{1}{K_O} \cdot \frac{1}{1 + \frac{s}{G} + \frac{s^2}{\omega_1 G}}$ , where the loop gain,  $G = K_D K_O A$ , natural frequency,  $\omega_n = \sqrt{G \cdot \omega_1}$ , and the

damping factor,  $\zeta = \frac{1}{2} \cdot \sqrt{\frac{\omega_1}{K_V}}$


- Using the linearized VCO from Fig. 19.18 in the CMOS textbook, the center frequency is 100MHz, and the gain of the VCO is

$$K_O = 1.57 \cdot 10^9 \frac{rad}{V} \cdot s, \text{ and the gain of the PD is } K_D = \frac{1}{\pi} \cdot \frac{V}{rad}$$

- The Bandwidth is chosen to be  $\omega_1 = \frac{1}{20ns} = 50MHz$ , therefore R=10k and C=2pF

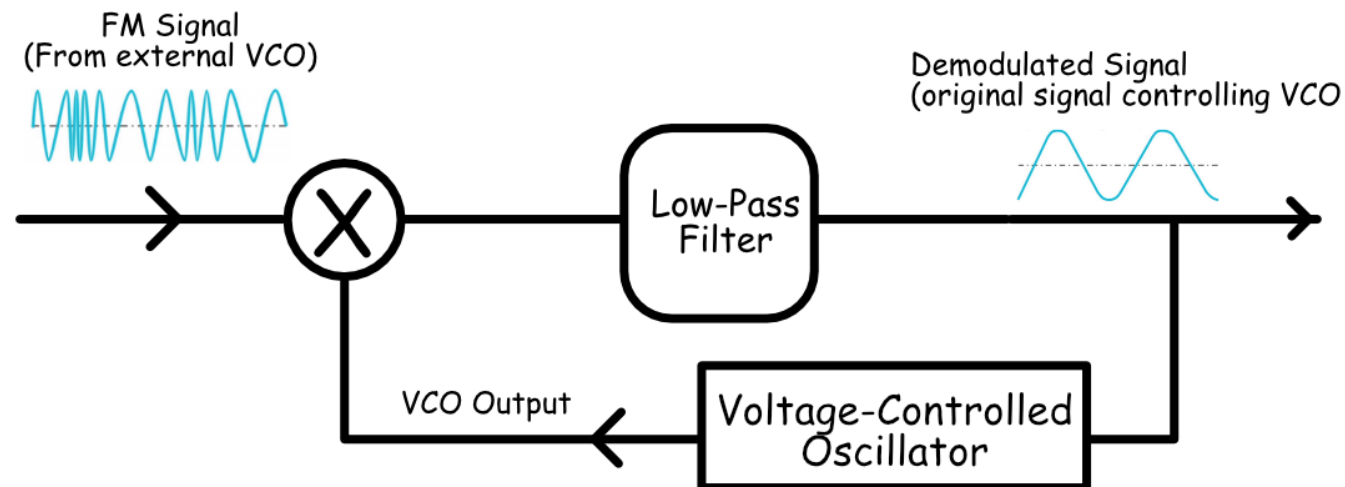
# FM Demodulation

- One of the main applications of an APLL is in the use of Frequency Modulation.
- A testbench can be setup where the input signal is the FM signal (from an external VCO), and the output demodulated signal is the result of filtering the error signal.
- The demodulated signal is also controlling the local VCO, and the difference between the external and internal VCO's results in a low frequency oscillating demodulated signal



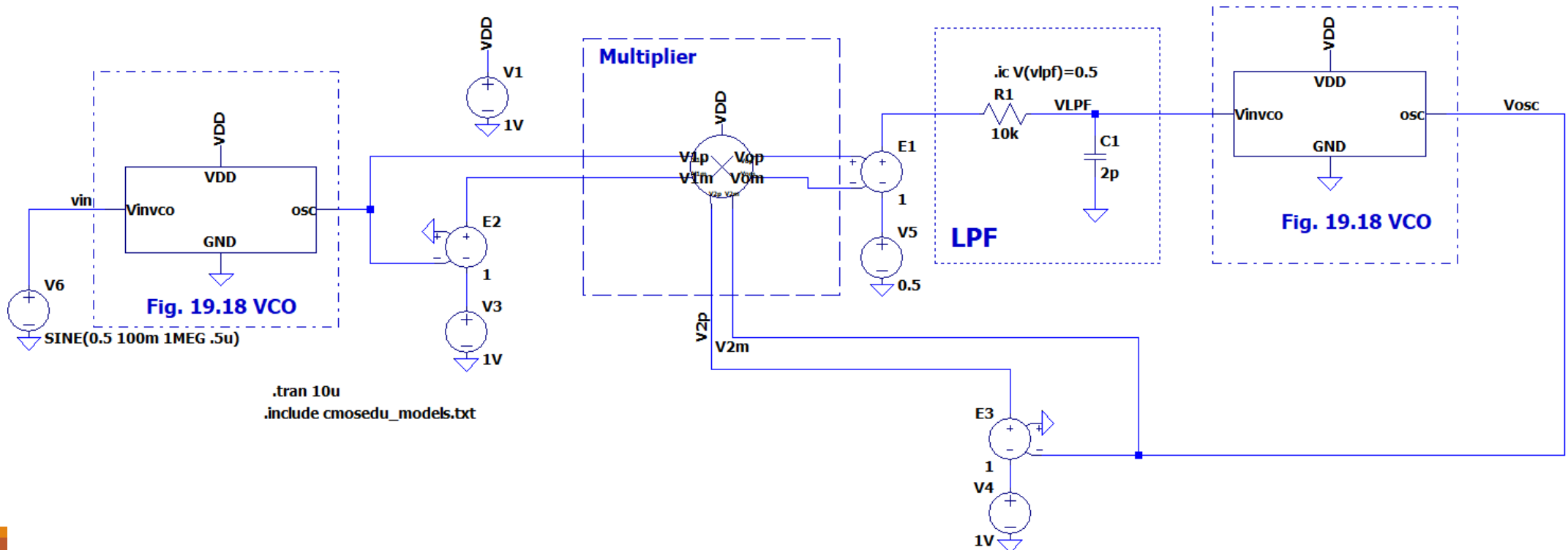
# FM Demodulation

- The following experiment has been created, where the input signal is a low-frequency sine wave (1MHz) that feeds into a VCO and generates the FM signal. The APLL will take in the signal and the error will filter out harmonics which will result in a demodulated signal at  $V_{OSC}$ .


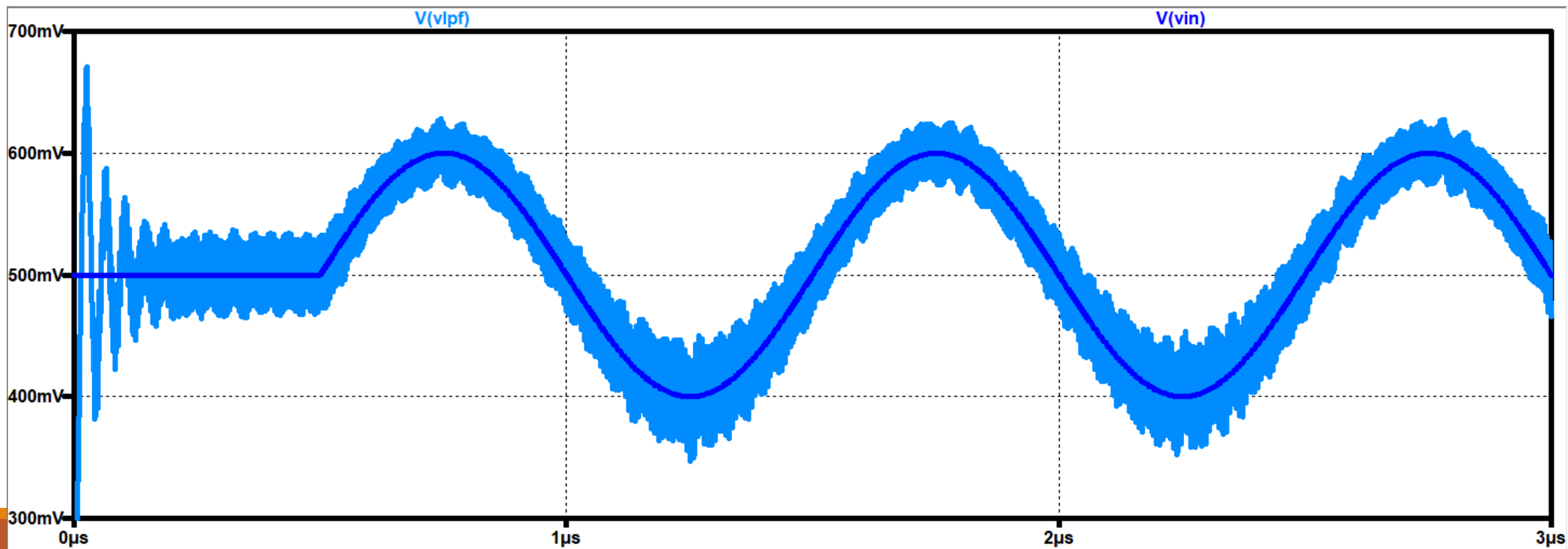
# FM Demodulation

- $V(vin)$  is the original signal, and  $V(vlpf)$  is the demodulated signal.
- There is some ringing and the signal still contains harmonics.
- This can be fixed by utilizing the lag-loop filter and adding an additional zero.




# Lag-Loop Filter:

- The lag-loop filter has the following transfer function:

$$F(s) = \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}}, \omega_z = \frac{1}{R_2 C}, \omega_p = \frac{1}{(R_1 + R_2) \cdot C}$$


- From above, if  $R_2=0$ , we get the original RC circuit. If  $R_1$  is small, we see that we have a pole/zero cancellation (bad!!). When this occurs, it's like the filter did not exist at all and all the harmonics pass through the VCO, defeating the purpose of the lag-loop filter.
- For general lag-loop design,  $R_1 \gg R_2$ , and  $C$  can be tuned to decrease the bandwidth (filter more frequencies)
- For the Lag-loop,  $\omega_z = \frac{1}{5ns} = 200MHz$  and  $\omega_p \approx \frac{1}{100ns} = 10MHz$
- A value of  $R_1=20k$ ,  $C_1=5pF$ , and  $R_2=1k$  are chosen for the next simulation

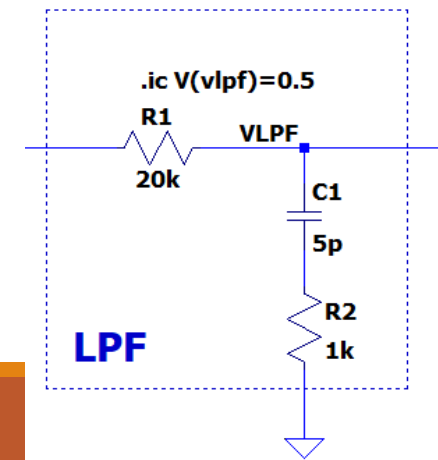


 
# FM Demodulation: W/Lag-Loop Filter

- By adding a lag-loop filter, the APLL has a better settling time and damping factor.
- The resulting signal is a cleaner demodulated signal, which can be filtered again to remove the high frequency harmonics.
- The values of the filter are chosen so that the capacitor is larger than what is used in a single-pole RC circuit, and the feed-forward resistance is high, else there is a pole/zero cancellation that effectively defeats the purpose of the lag-loop filter.



# References

---

- Baker, R. Jacob, *CMOS - Circuit Design, Layout, and Simulation, 4th ed.* IEEE Press, 2019
- “Digital PLL, All Digital PLL, Analog PLL.” *Movellus*, 11 Apr. 2021, <https://www.movellus.com/all-digital-pll-phase-locked-loop/>.
- “How to Demodulate an FM Waveform: Radio Frequency Demodulation: Electronics Textbook.” *All About Circuits*, <https://www.allaboutcircuits.com/textbook/radio-frequency-analysis-design/radio-frequency-demodulation/how-to-demodulate-an-fm-waveform/>.
- “MT-086: Fundamentals of Phase Locked Loops (PLLs).” *Analog Devices*, <https://www.analog.com/media/en/training-seminars/tutorials/MT-086.pdf>.
- Roy, Ansuman, “A Tutorial Approach to Analog Phase-Locked Loops”, [angsumanroy.com/presentations.html](http://angsumanroy.com/presentations.html)