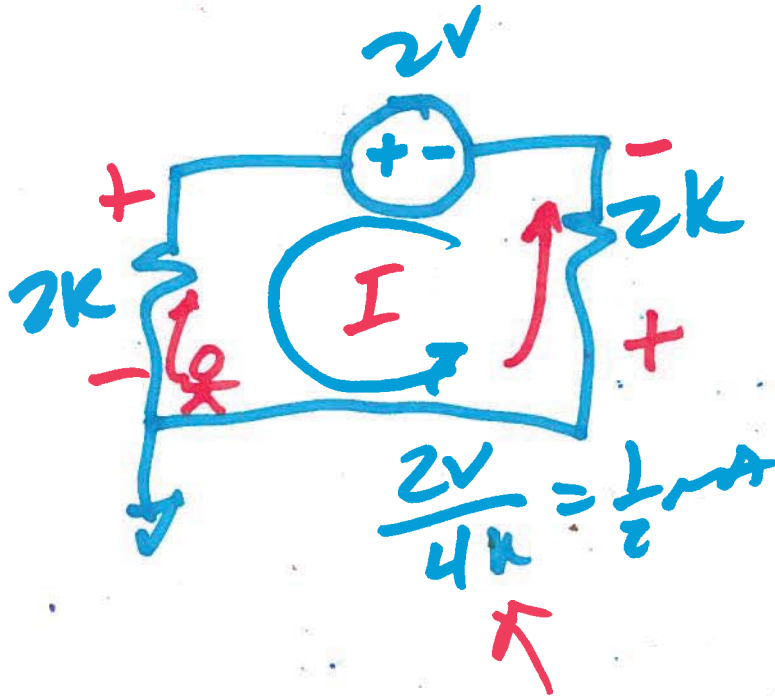



EE 220 circuits I

Lecture 13



$$2k \cdot I - 2 + 2kI = 0$$

$$I = \frac{2}{4k}$$

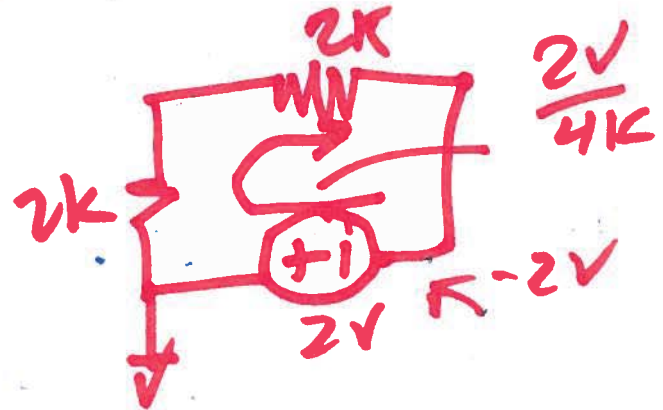


Q 2 +1

Quiz #1 EE 220 Fall 2016 Name: _____

Closed book and notes.

Show your work for credit!

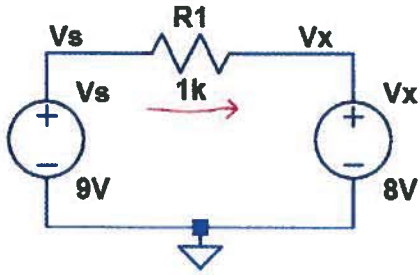1. Find the voltages V_s and V_x as well as the current flowing in the direction shown. (5 points)




Quiz #2 EE 220 Fall 2016 Name: _____

Closed book and notes.

Show your work for credit!

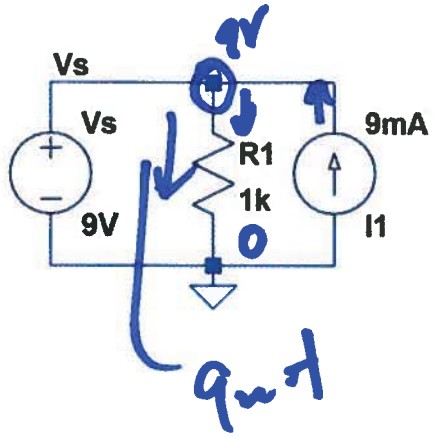1. Determine the current through V_s . Again, show your work for credit. (5 points)




3)

Quiz #3 EE 220 Fall 2016 Name: _____


Closed book and notes.

Show your work for credit!

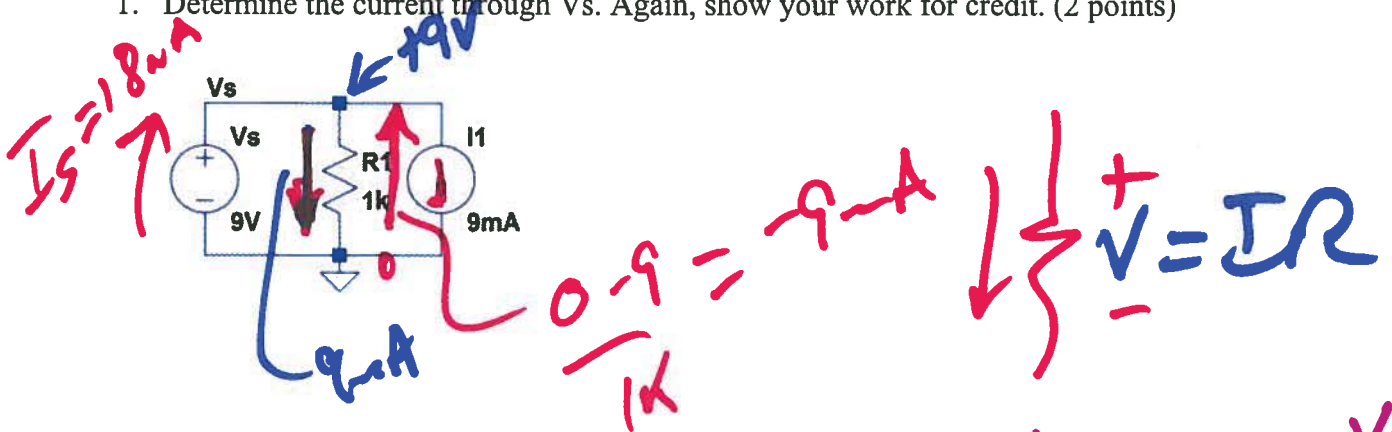1. Determine the current through V_s . Again, show your work for credit. (2 points)



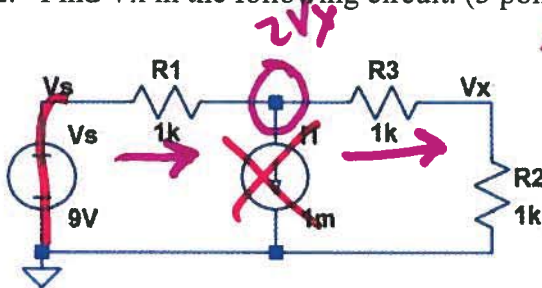2. Find V_x in the following circuit. (5 points)




9V source

$$V_x = 9 \cdot \frac{1k}{1k + 2k} = 3V$$

1mA source

$$V_x = -0.333V$$

$$V = -I \cdot R$$

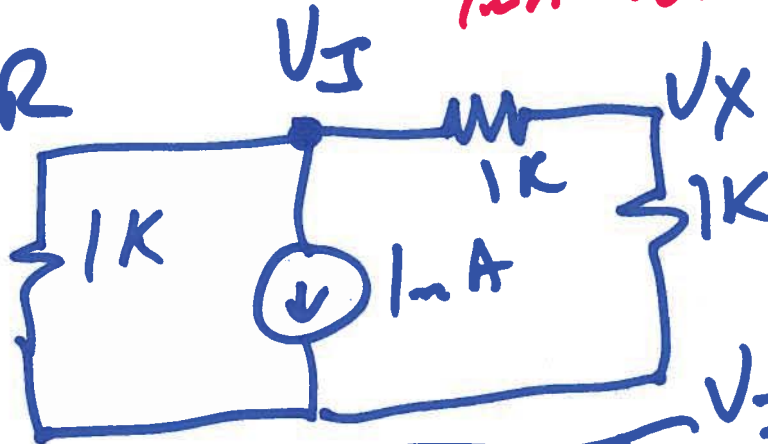

4)

$$V_x = 3 - 0.333V = 2.666V$$


$$V_I = -\frac{2}{3}V = -0.666V = -0.666V$$

Quiz #4 EE 220 Fall 2016 Name: _____

Closed book and notes.


Show your work for credit!

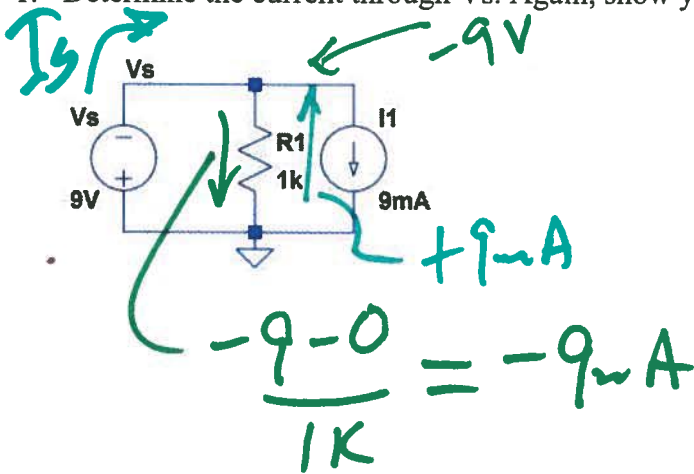1. Determine the current through V_s . Again, show your work for credit. (2 points)



$$I_s = -9mA + 9mA = \underline{\underline{0}}$$

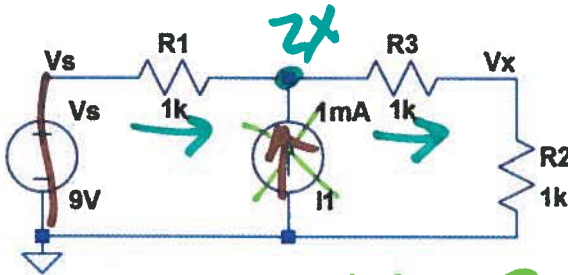2. Find V_x in the following circuit. (5 points)





$$\frac{9 - 2V_x}{1K} + 1mA = \frac{V_x}{1K}$$

$$9 - 2V_x + 1 = V_x$$

$$10 = 3V_x$$

$$V_x = \underline{\underline{3.33V}}$$

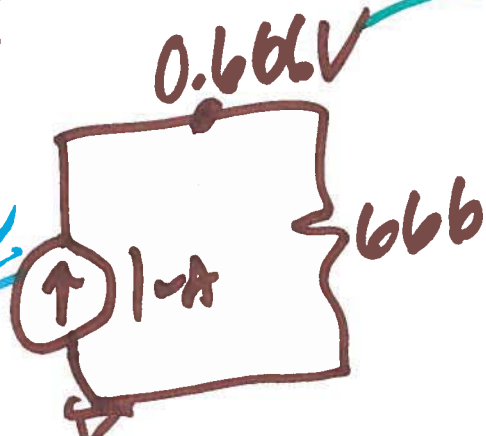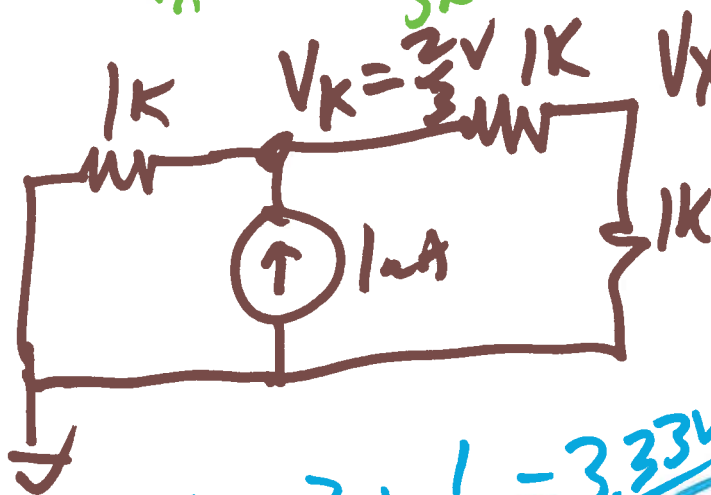

$$V_x = 3 + \frac{1}{3} = \underline{\underline{3.33V}}$$


5)

Quiz #5 EE 220 Fall 2016 Name: _____

Closed book and notes.


Show your work for credit!

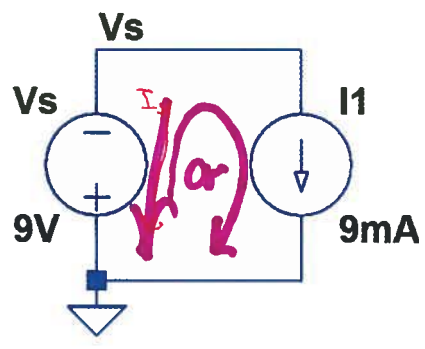1. What is I_s as defined in the direction seen below? Just write the answer. (1 point)



$$I_s = -9 \mu A$$

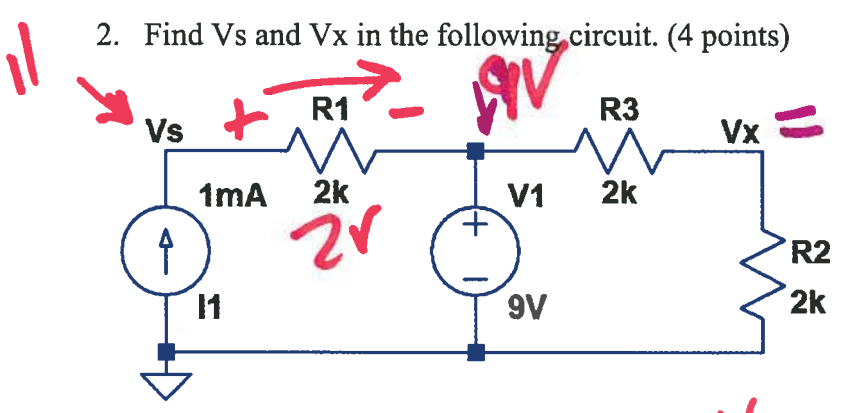2. Find V_s and V_x in the following circuit. (4 points)



$$V_x = 9 \cdot \frac{2k}{2k + 2k} = \underline{\underline{4.5V}}$$

$$V_s = 9V + 1 \mu A \cdot 2k$$

$$\underline{\underline{V_s = 11V}}$$


4)

Quiz #6 EE 220 Fall 2016 Name: _____

Closed book and notes.

Show your work for credit!

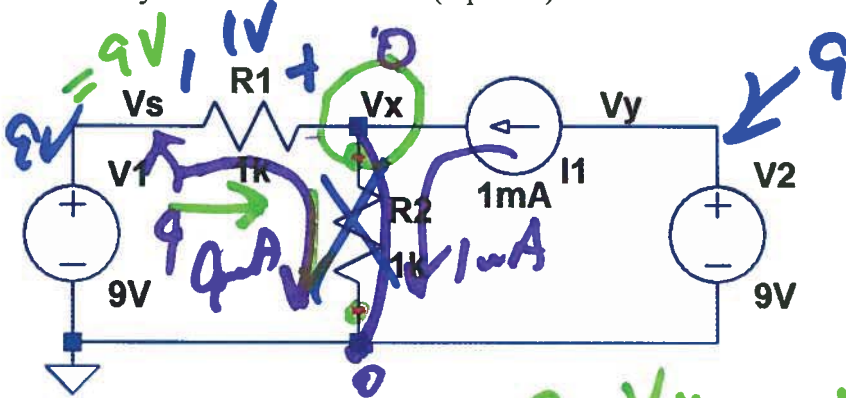- Find the Thevenin and Norton equivalent circuits, with R2 removed, at the terminals marked by red dots seen below. (5 points)




$$V_x = \frac{9 - V_x}{1k} + 1mA$$

~~1k R2~~

$$V_x = 9 - V_x + 1$$

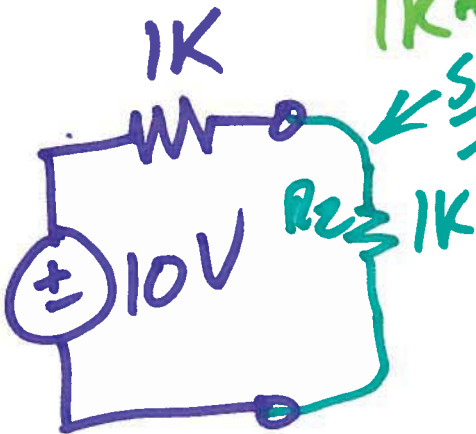
$$2V_x = 10, \quad \underline{\underline{V_x = 5V}}$$



$$V_{TH} = 10V$$

$$I_{sc} = I_n = 10mA$$

$$R_{TH} = 1k$$

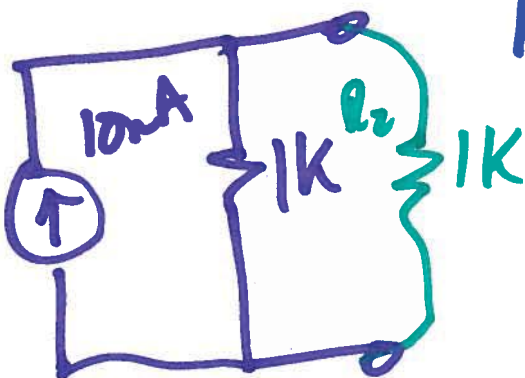

$$V = 500 \cdot 10mA = \underline{\underline{5V}}$$

↓
1k || 1k


7)

Quiz #7 EE 220 Fall 2016 Name: _____

Closed book and notes.

Show your work for credit!

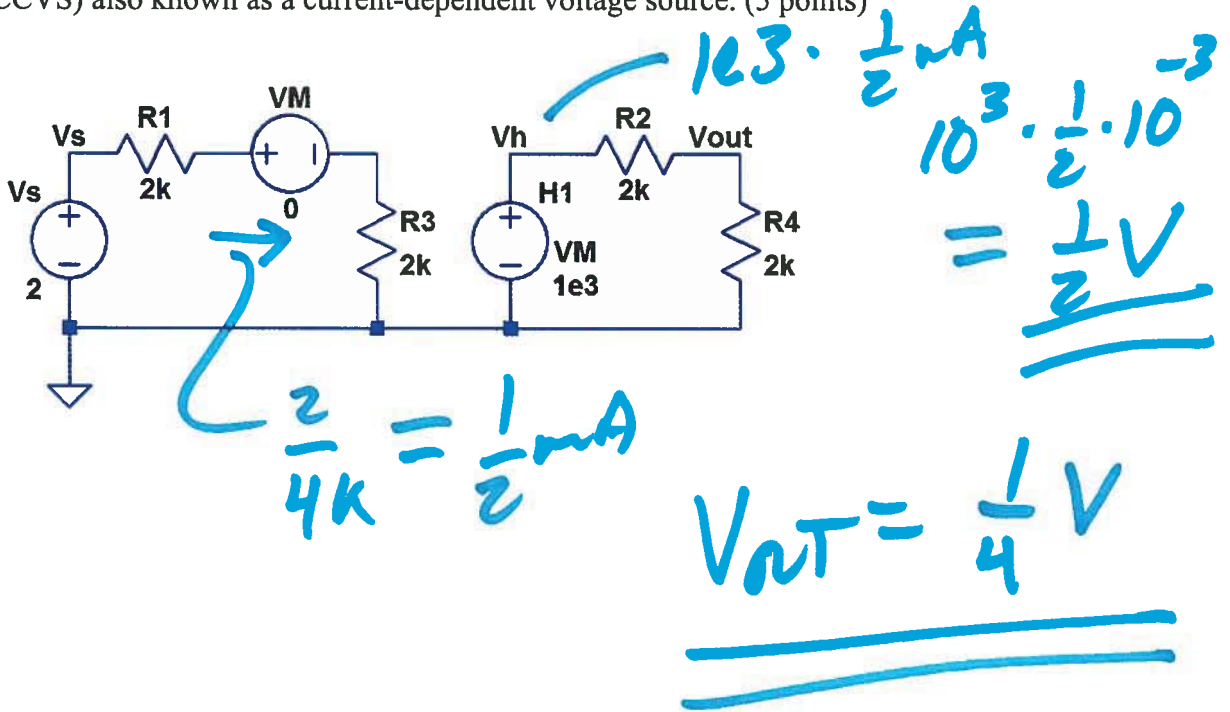1. Find V_{out} in the following circuit. Note that H1 is a current-controlled voltage source (CCVS) also known as a current-dependent voltage source. (5 points)




8)

Quiz #8 EE 220 Fall 2016 Name: _____

Closed book and notes.

Show your work for credit!

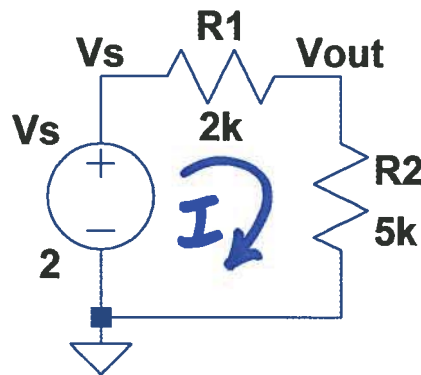1. Find the voltage across R1. As always, show your work for credit. (3 points)



$$I = \frac{2}{7k}$$

$V_{\text{drop across } R_1}$

$$= R_1 \cdot I$$


$$= 2k \cdot \frac{2}{7k}$$

$$= \underline{\underline{\frac{4}{7} \text{ V}}}$$


a)

Show your work for credit!

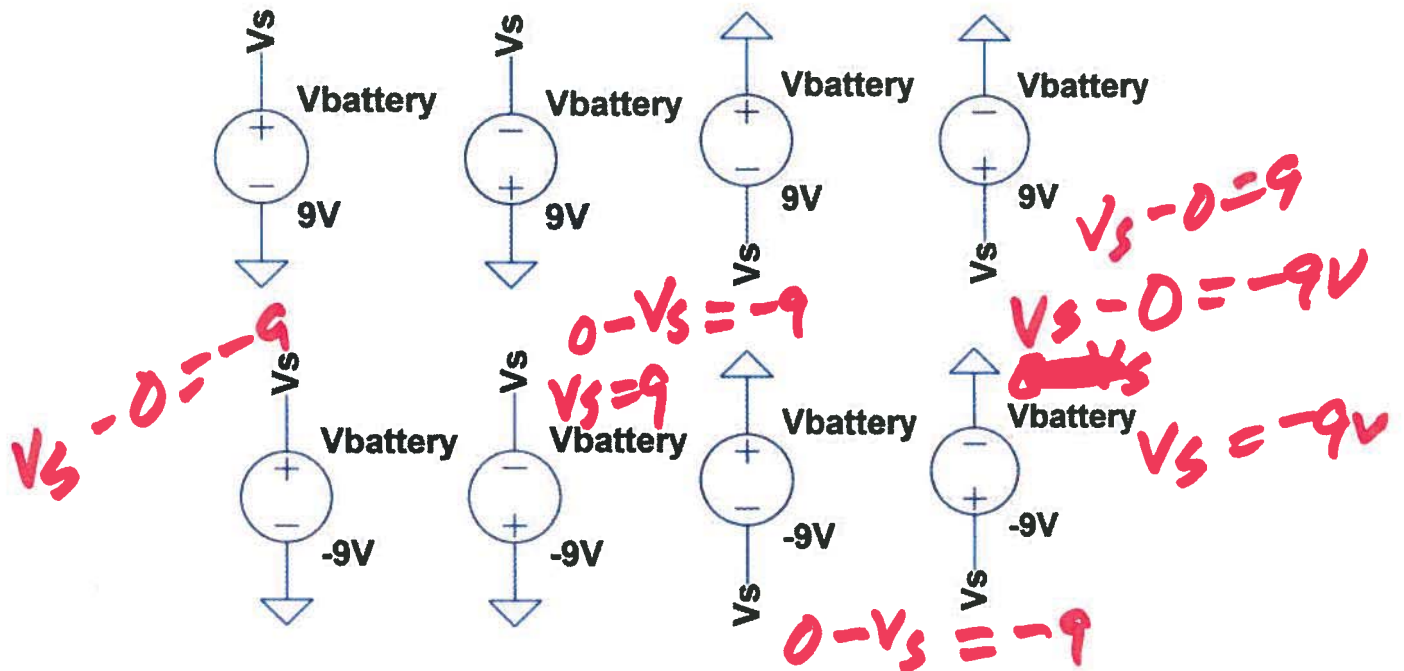
- What is the voltage, V_s , in each of the following circuits? It's okay to simply write your answer next to each V_s in the schematics. (0.5 points each)



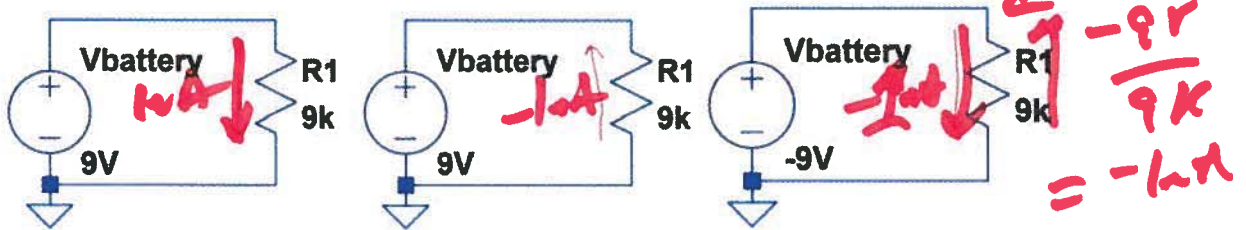- What is the current flowing in the following circuits? Give answers for the current flowing in the directions indicated on each schematic. (3 points)



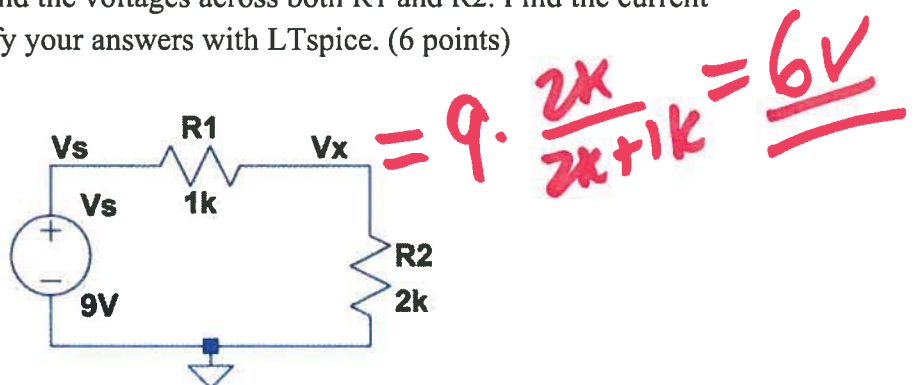
- Find the voltages V_s , V_x , and the voltages across both R_1 and R_2 . Find the current flowing in the circuit. Verify your answers with LTspice. (6 points)



H.W. #2 EE 220 Fall 2016










Show your work for credit!

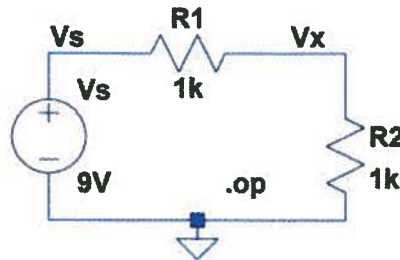- Write a text file containing the LTspice netlist for the following circuit. Verify that the simulation results match your hand calculations. (3 points)



Comment
 vs vs 0 DC 9
 R1 vs vx 1k
 R2 vx 0 1k

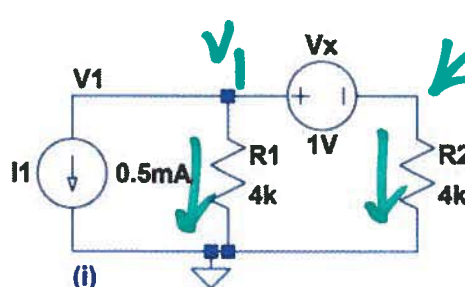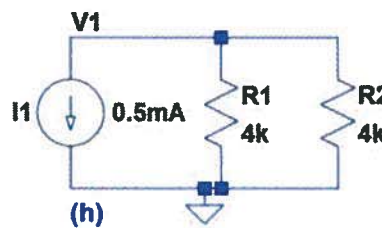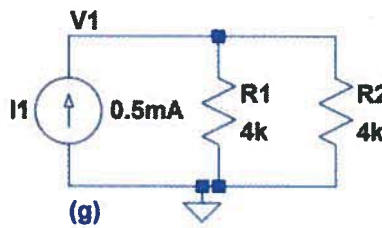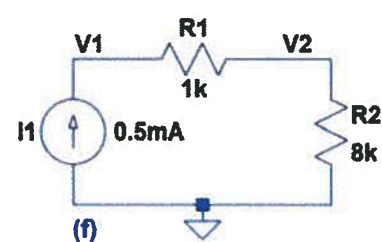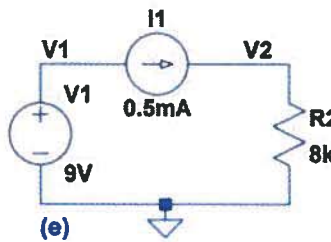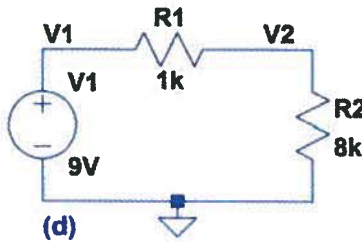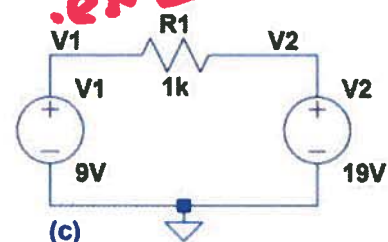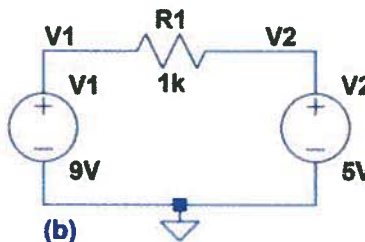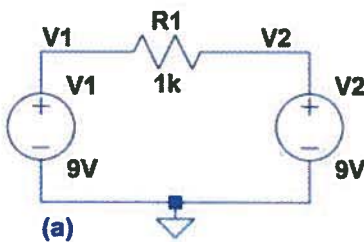- Find the voltages and currents in each of the following circuits. Verify your answers with LTspice. (9 points)





Handwritten notes for circuit (i):
 $V_1 - 1$
 $0.5\mu A + \frac{V_1}{4K}$
 $+ \frac{V_1 - 1}{4K} = 0$

11)


H.W. #3 EE 220 Fall 2016

Show your work for credit!

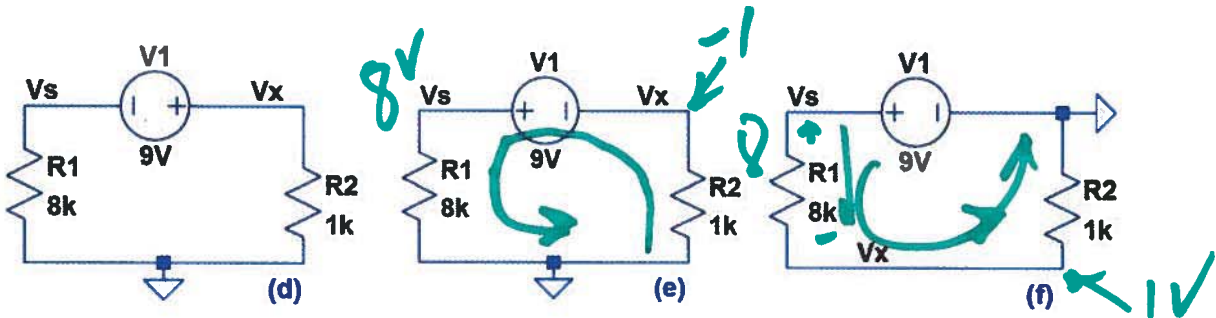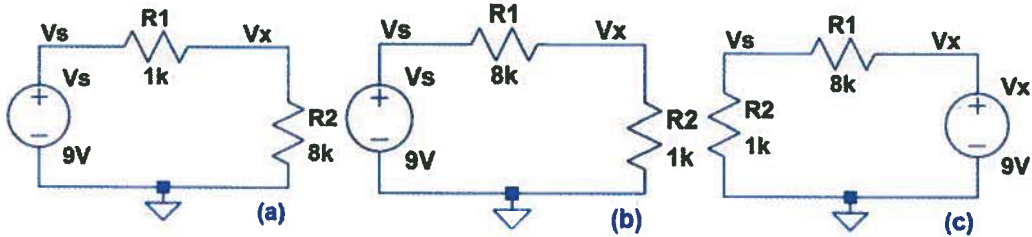
- Find the voltages V_x and V_s in each of the following circuits. Verify your hand calculations using LTSpice. (6 points)



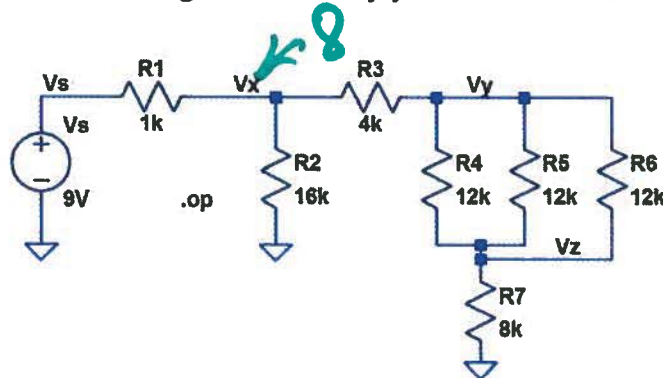- Find the voltages in the following circuit. Verify your hand calculations using LTSpice. (6 points)



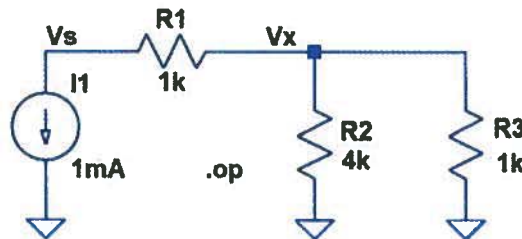- Show how to derive the voltage divider equation and the current divider equation for a two resistor circuit. Ensure your derivation includes the two schematics you are using. Provide an example for each derivation. (4 points)
- Calculate V_s , V_x , and the current that flows in R_2 and R_3 . Verify your hand calculations using LTSpice. (4 points)





$$1 \text{mA} + \frac{V_x}{1\text{k}} = 9 - \frac{V_x}{1\text{k}}$$



H.W. #4 EE 220 Fall 2016

Show your work for credit!

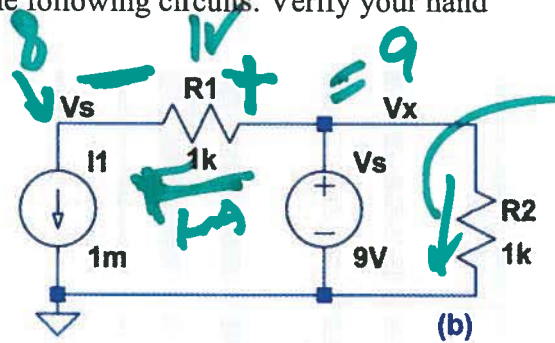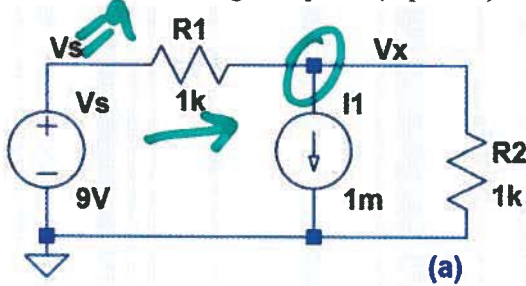
1. Find the voltages V_x and V_s in each of the following circuits. Verify your hand calculations using LTSpice. (4 points)



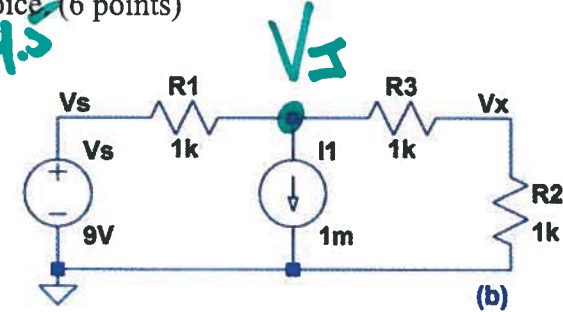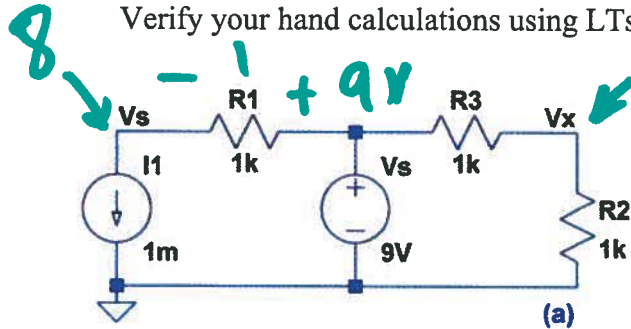2. Find the voltages V_x and V_s and the current through V_s in each of the following circuits. Verify your hand calculations using LTSpice. (6 points)



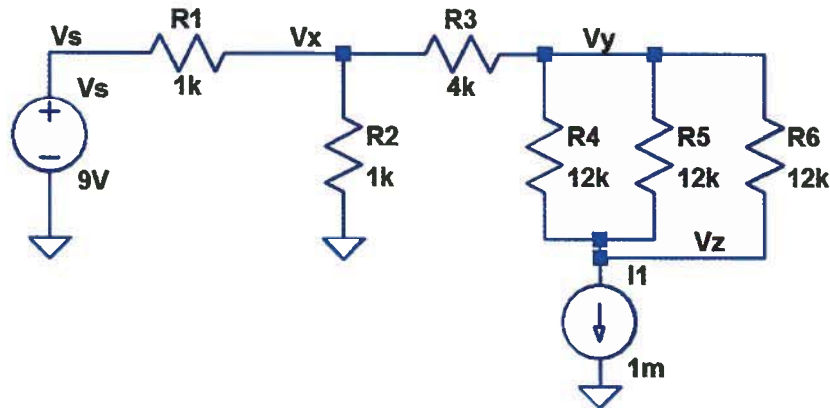3. Find the voltages in the following circuit. Verify your hand calculations using LTSpice. (6 points)





13)



H.W. #5 EE 220 Fall 2016

Show your work for credit!


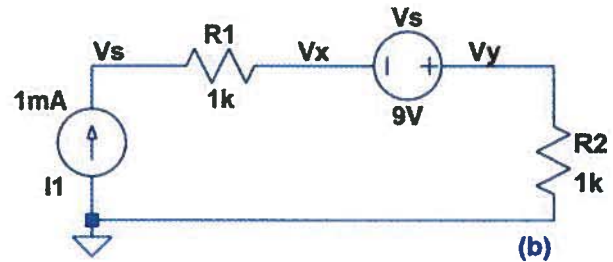
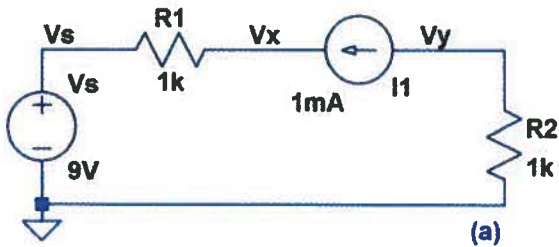
- Find the voltages V_x and V_y in each of the following circuits. Verify your hand calculations using LTspice. (4 points)



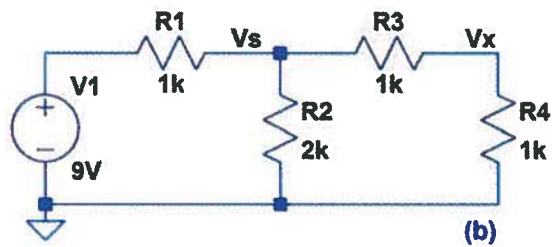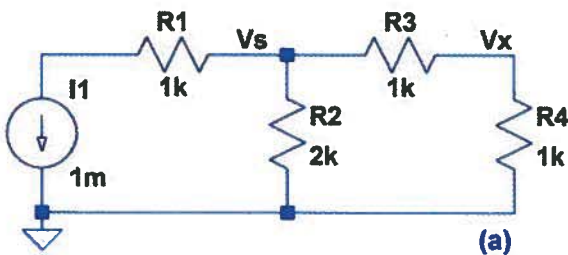- Find the voltages V_s and V_x and the current through R_2 in each of the following circuits. Verify your hand calculations using LTspice. (6 points)



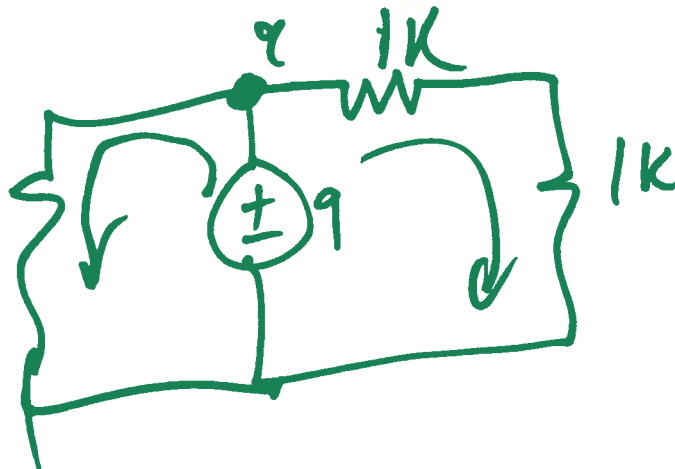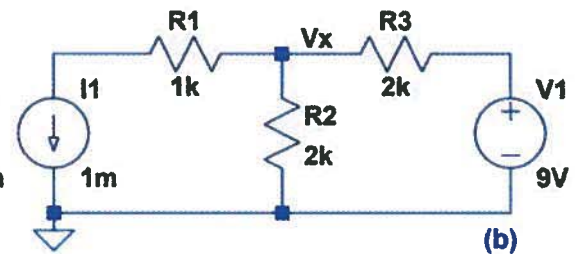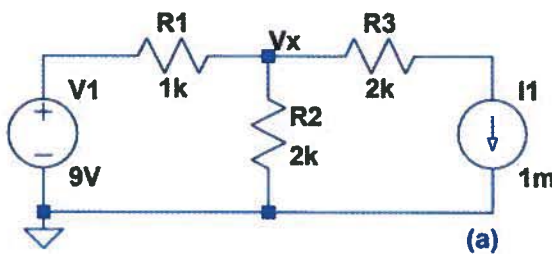- Using superposition show how to find V_x in the following circuits. Verify your hand calculations using LTspice. (6 points)







14)


H.W. #6 EE 220 Fall 2016

Show your work for credit!

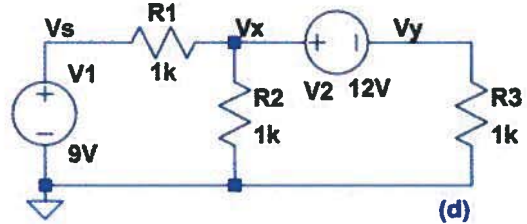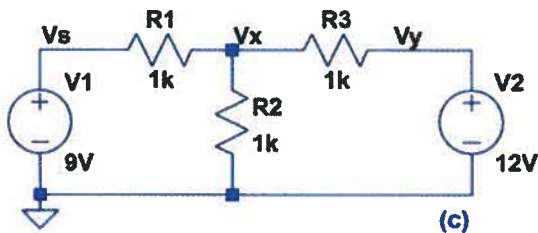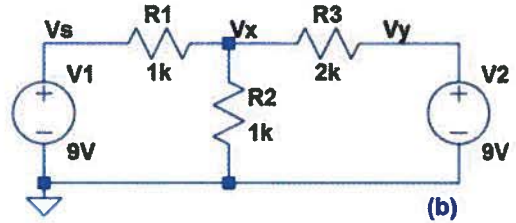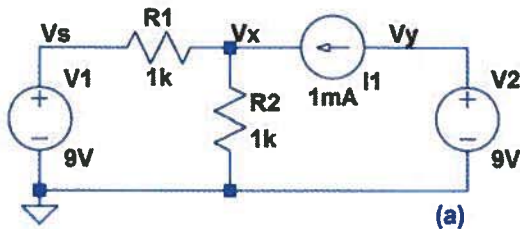- Find the voltages and currents in each of the following circuits **using mesh analysis**. Verify your hand calculations using LTspice. (8 points)




- Repeat problem 1, but no need to repeat the LTspice simulations, **using superposition**. (8 points)
- Find the Thevenin and Norton equivalent circuits for the circuitry to the left of the two terminals marked with red dots below. Show that V_{out} is the same for: 1) the circuit seen below, 2) the Thevenin equivalent circuit connected to R_3 and 3) the Norton equivalent circuit connected to R_3 . Verify your answers with three LTspice simulations. (3 points)

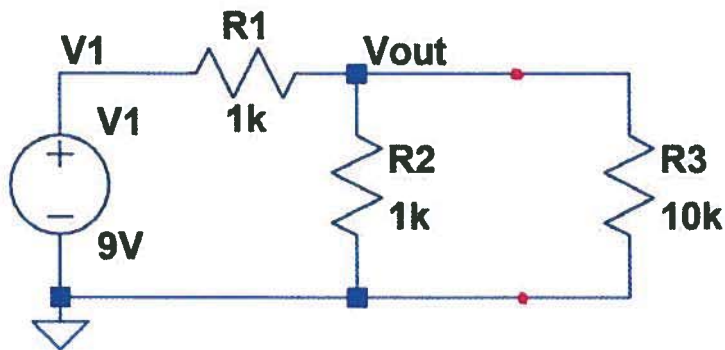


H.W. #7 EE 220 Fall 2016

Show your work for credit!

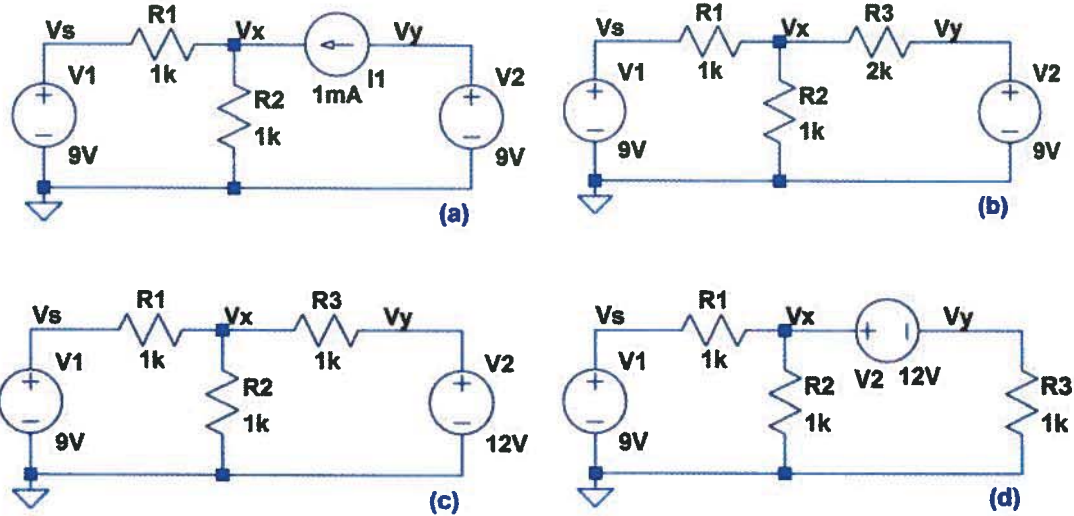
- In problem 1 from HW#6, circuits seen below, find the Thevenin and Norton equivalent circuits between V_x and ground with R_2 removed. Show that when you connect R_2 to the Thevenin and Norton equivalents that you get the same value for V_x . Verify your hand calculations using LTSpice. (8 points)



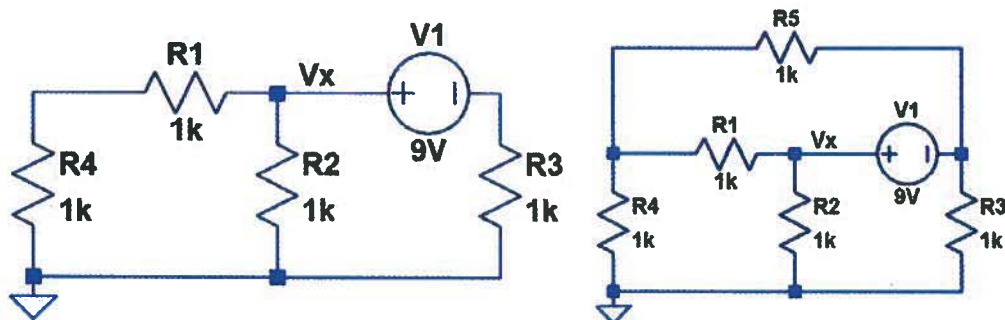- Determine the currents and voltages in the following circuit using mesh analysis. Verify your hand calculations using LTSpice. (4 points)



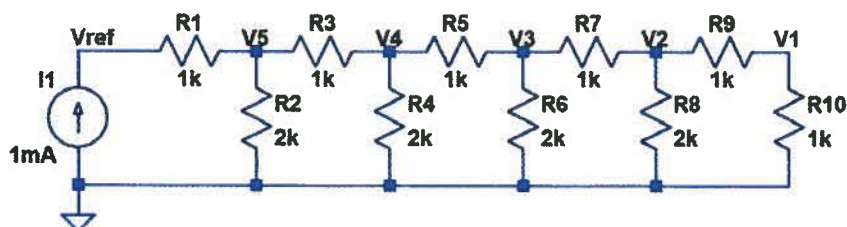
- Find all voltages in the following circuit. Verify your hand calculations using LTSpice. As always, show your work for credit. (2 points)




H.W. #8 EE 220 Fall 2016

Show your work for credit!

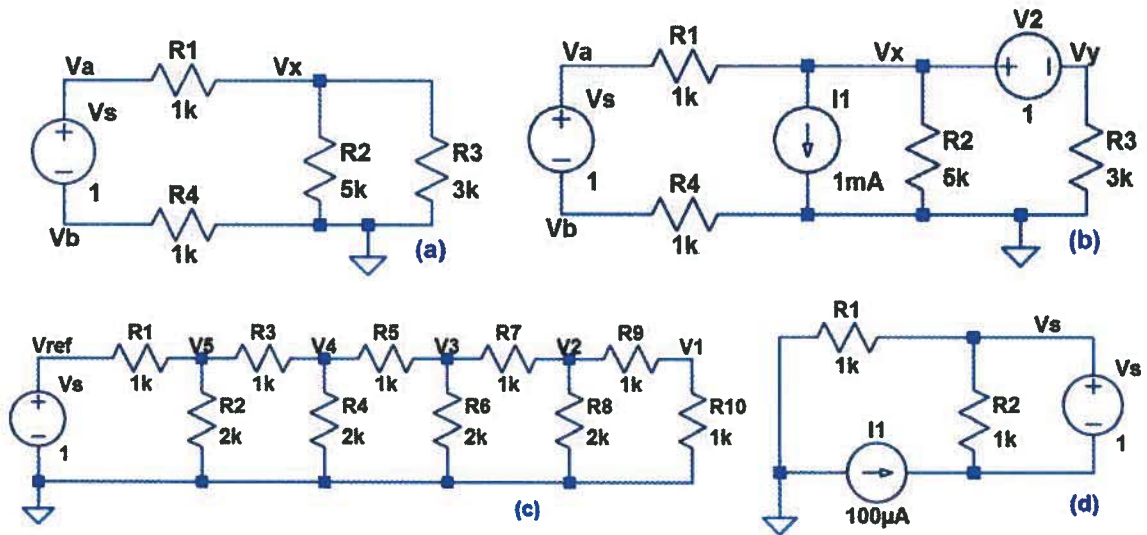- Find the voltages in the following circuits using any method you would like. Verify your hand calculations using LTspice. (4 points)



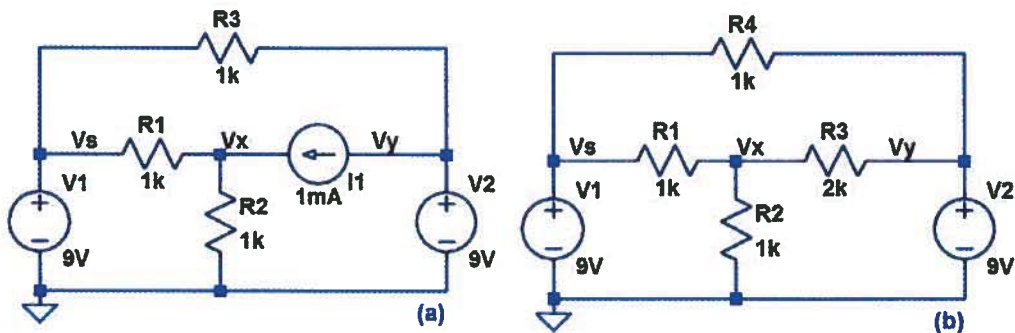
- Determine the currents and voltages in the following circuits using superposition and mesh analysis. Verify your hand calculations using LTspice. (6 points)







- For the circuits in problem 2 find the Thevenin and Norton equivalent circuits from V_x to ground without R_2 in the circuit. Show, with R_2 back in the circuit, that you get the same value for V_x that you calculated in problem 2. Verify your Thevenin and Norton circuits are correct using LTspice. (4 points)

Show your work for credit!

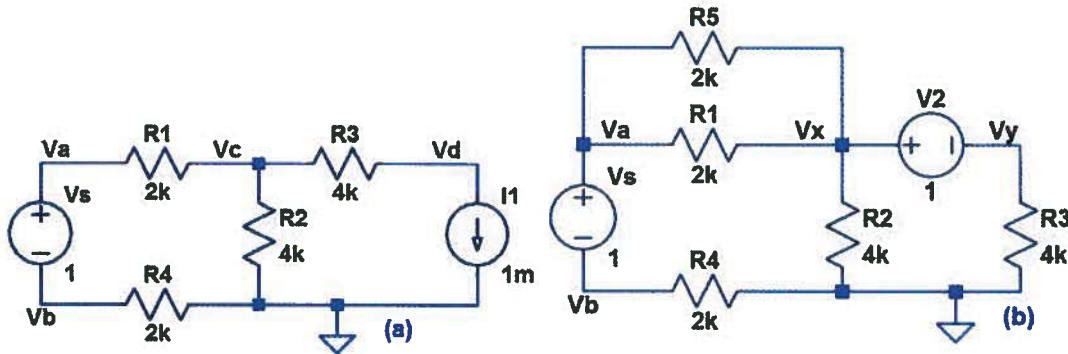- Find the voltages and currents in the following two circuits. Verify your hand-calculated answers using LTSpice. (4 points)




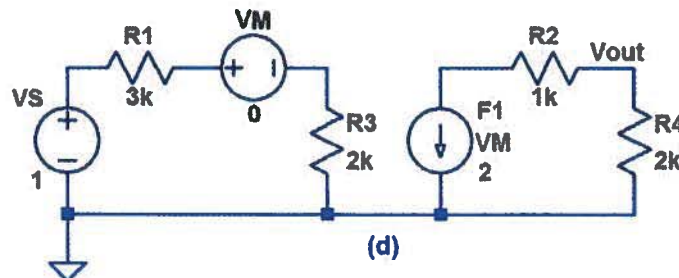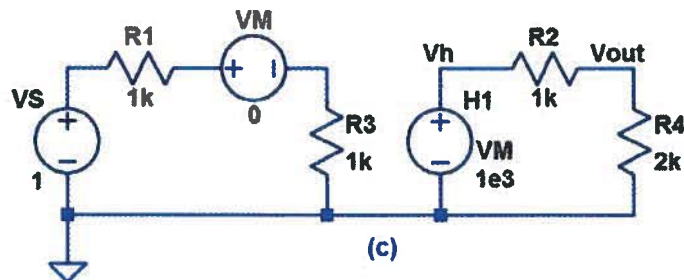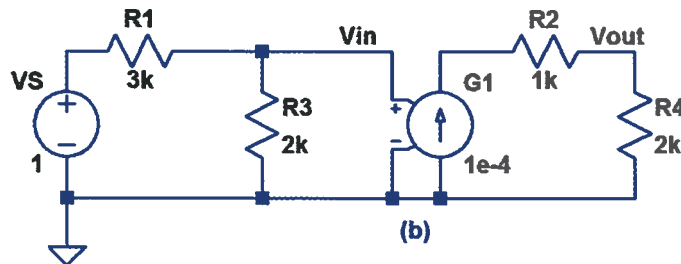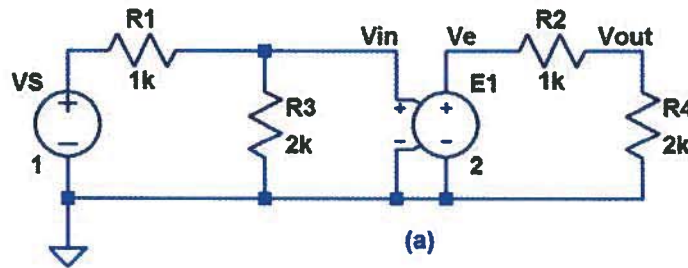- Find V_{out} in each of the following circuits. Verify your hand-calculated answers using LTSpice. (8 points)




Show your work for credit!

- The first two circuits from HW#9 are reproduced below. For each circuit calculate the power dissipated by each resistor and the power supplied by each source. No need to repeat finding the currents and voltages from problem 1 in HW#9. Simply list, and use, the results from HW#9 problem 1 in this one. Does the power dissipated by the resistors equal the power supplied by the sources? Do not turn in LTspice results (if you do I will ask the grader to take points off for not following the directions) but feel free to use LTspice to ensure that you did the problem right. (2 points)

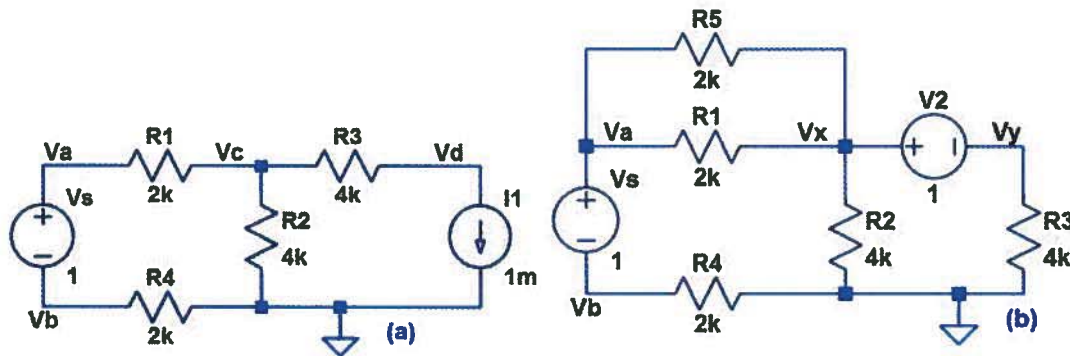


- Find the Thevenin and Norton equivalent circuits (models) at the terminals where R_2 is connected (without R_2 in the circuit) in the above two circuits. Use LTspice, with R_2 back in the circuit and connected to your Thevenin and Norton equivalent circuits, to verify your models are correct. (4 points)
- Can Thevenin and Norton equivalent circuits be determined for circuits with dependent sources? Why or why not? Using the (a) and (c) circuits from problem 2 in HW#9, pasted below, verify your answer. Assume that you are finding Thevenin and Norton equivalent circuits between V_{out} and ground, without R_4 in the circuit. Verify your answer with LTspice simulations by connecting R_4 to your Thevenin/Norton circuits and showing the same output voltage, V_{out} . (6 points)

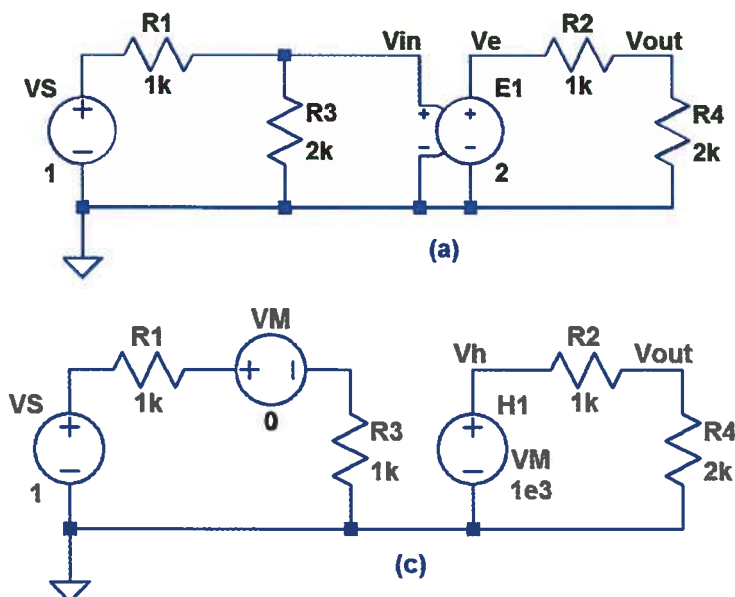


Show your work for credit!

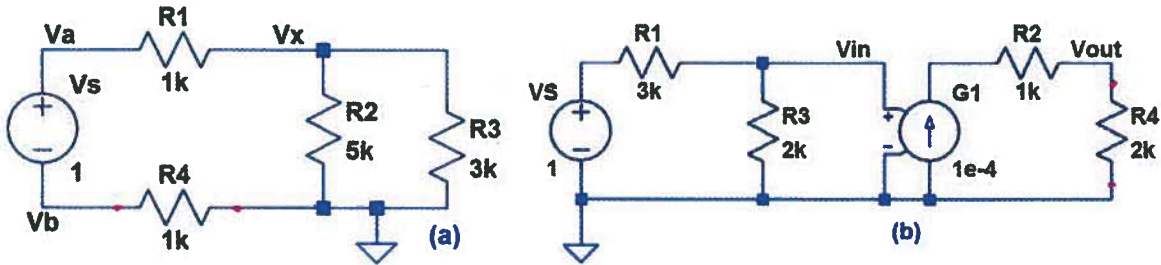
- Calculate the voltage across R_4 in the below circuits. Next find the Thevenin and Norton equivalent circuits at the port indicated by the red dots in the below schematics (this means without R_4 in the circuit). Show that your equivalent circuits are correct and then verify with LTspice. (6 points)



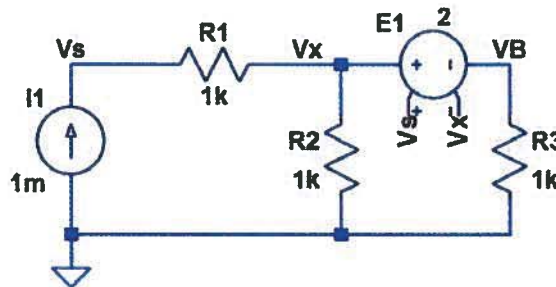
- Find the voltage V_B in the following circuit. Verify your answer with LTspice. (3 points)



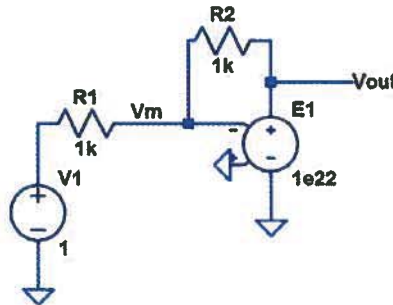- Find V_{out} in the following circuit. For all intents and purposes you can assume the gain of the VCVS is infinite. (3 points)




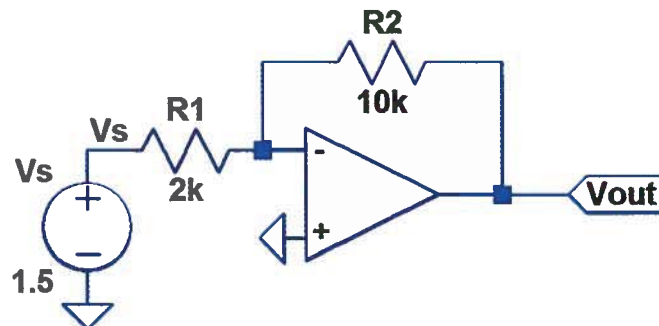- Find V_{out} in the following circuit. Verify your answer with LTspice. As always, show your work for credit. (2 points)




Show your work for credit!

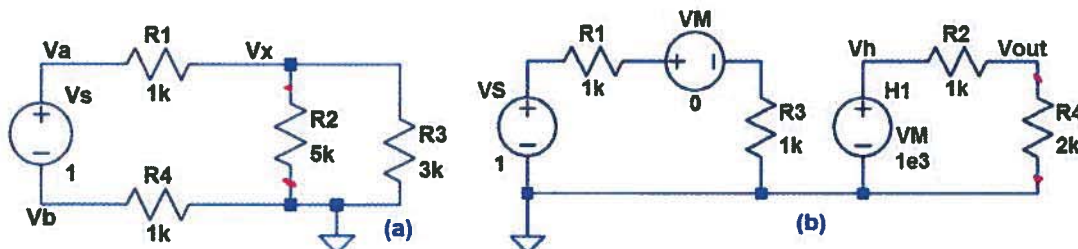- Calculate the voltage across V_x and V_{out} in the following circuits. Next find the Thevenin and Norton equivalent circuits at the port indicated by the red dots in the below schematics (this means without R_2 or R_4 in the circuit). Show that your equivalent circuits are correct and then verify with LTspice. (6 points)



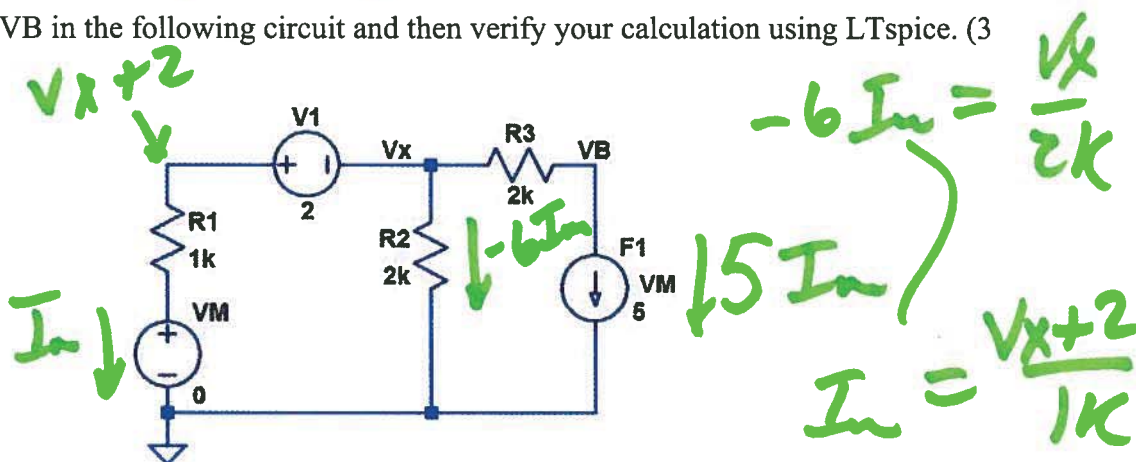- Calculate V_B in the following circuit and then verify your calculation using LTSpice. (3 points)



- Write an equation for V_{out} as a function of V_{in} in the following circuits. Plot V_{out} if V_{in} varies from -1 to 1 V in each circuit. Verify your answers, including your plots, using a DC sweep in LTspice. (6 points)

