

EE 220 circuits I

Lecture 14

$$I = V \cdot \frac{1}{R}$$


Conductance Ω
Mhos Υ

$$\frac{I}{V} = \frac{1}{R}$$



transconductance
Amp.

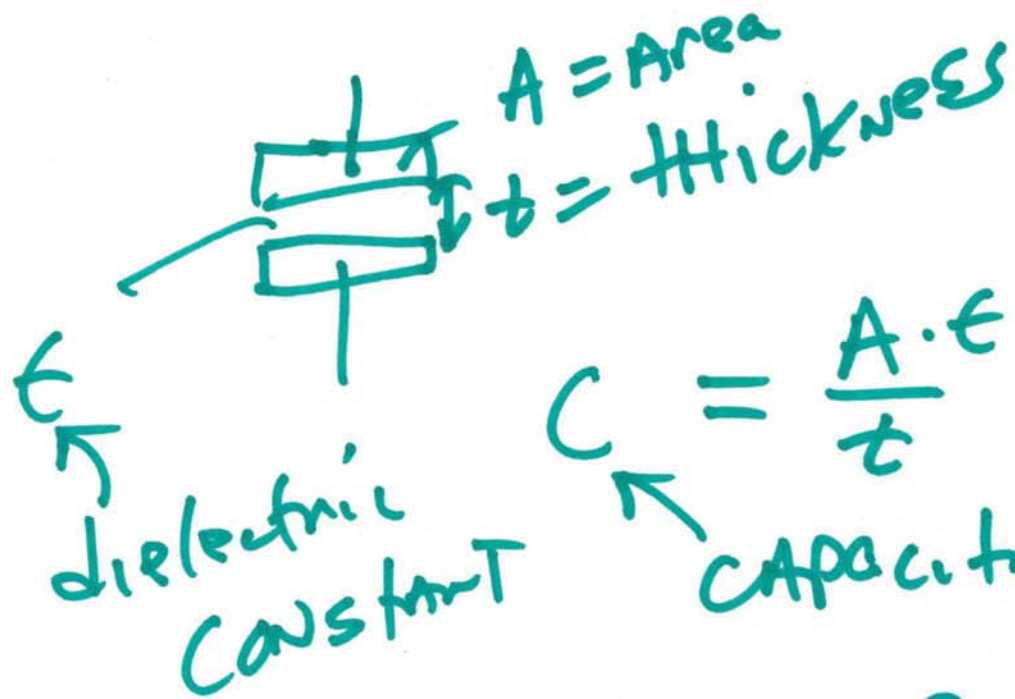CAPACITORS
(formerly known
AS A CONDENSER)




inductor

$$C = \frac{A \cdot \epsilon}{t}$$

CAPACITANCE

$$8.85 \times 10^{-18} / 4m$$



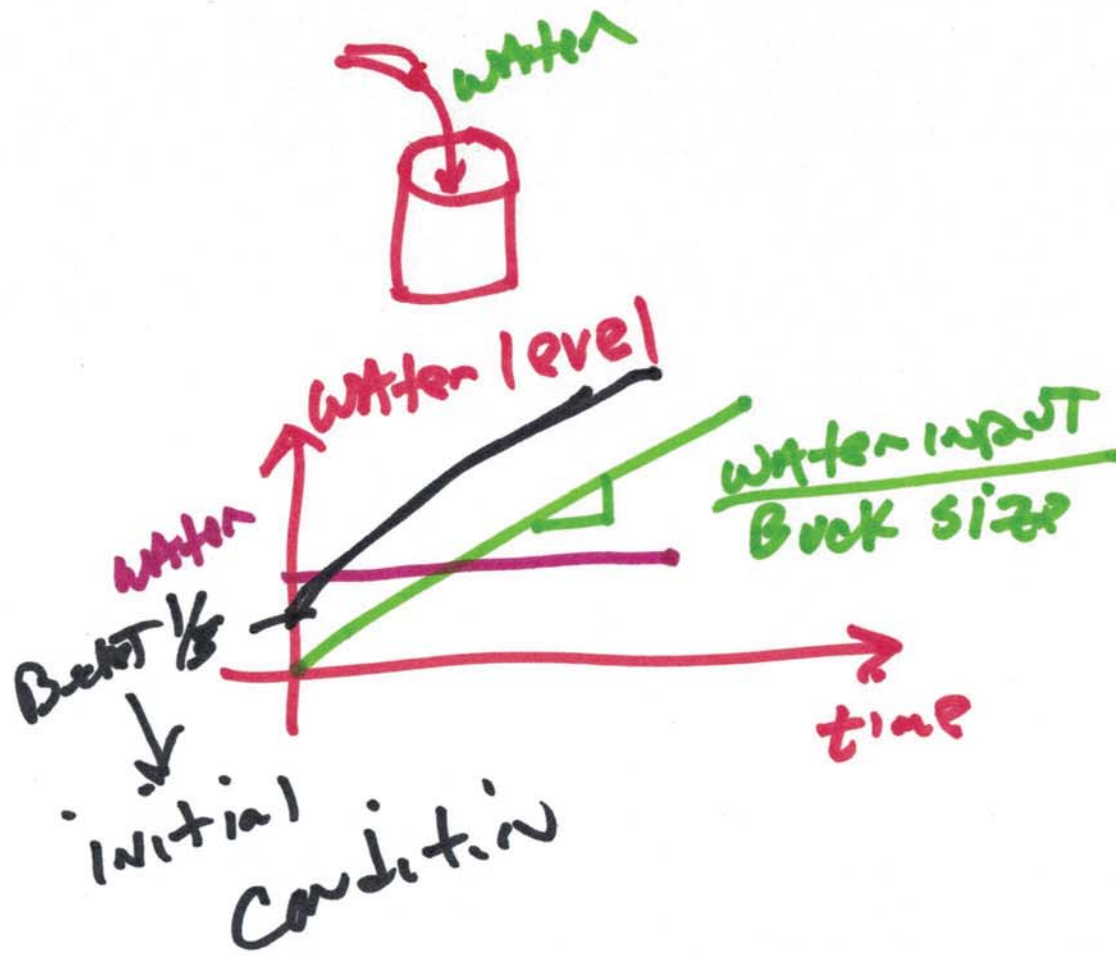






$$Cv = Q$$

$$I = C \frac{dV_c(t)}{dt}$$



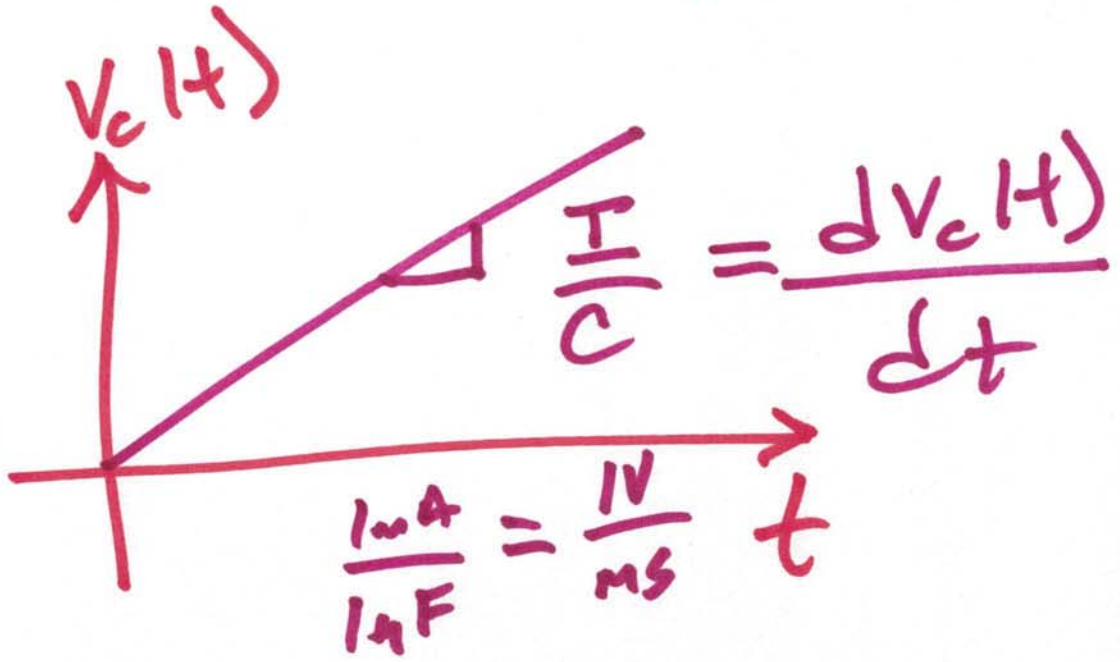$V_c(t)$ initial discharged $v=0$
 $C \cdot v = Q$
 $Q = 0$
 FARAD



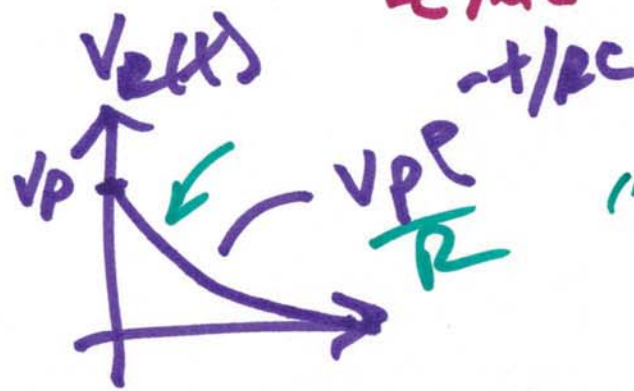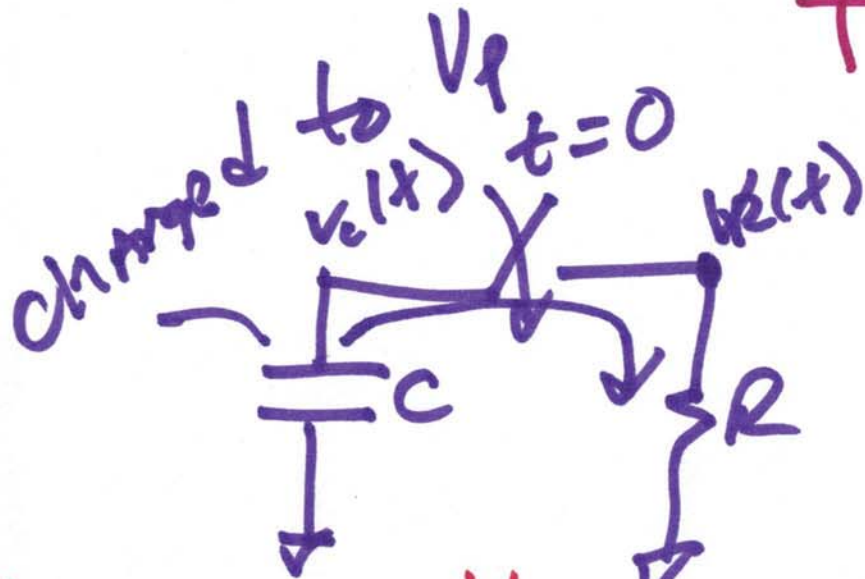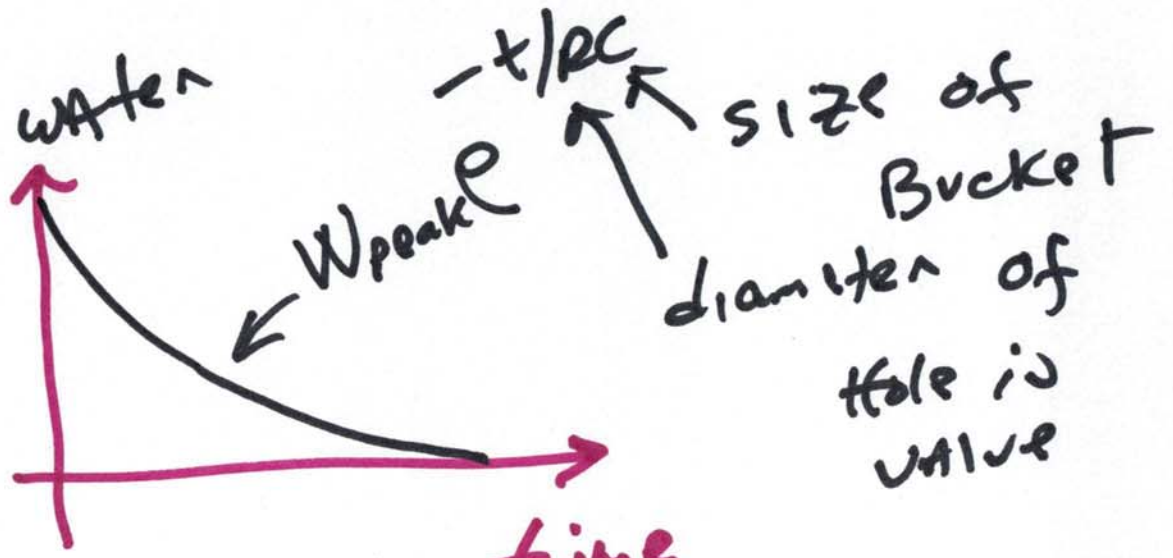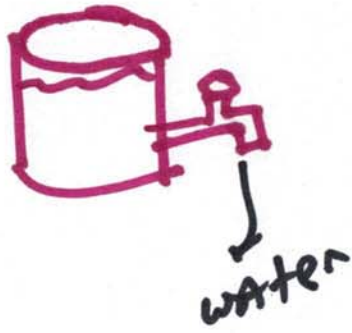

"electron Boom"

super naker Taz

$$I = -C \frac{dv}{dt}$$


$$I = \frac{v}{R}$$

$$CV = Q$$

$$I = C \frac{dv}{dt}$$

$$v_c(t) = \frac{1}{C} \int I \cdot dt$$

5)

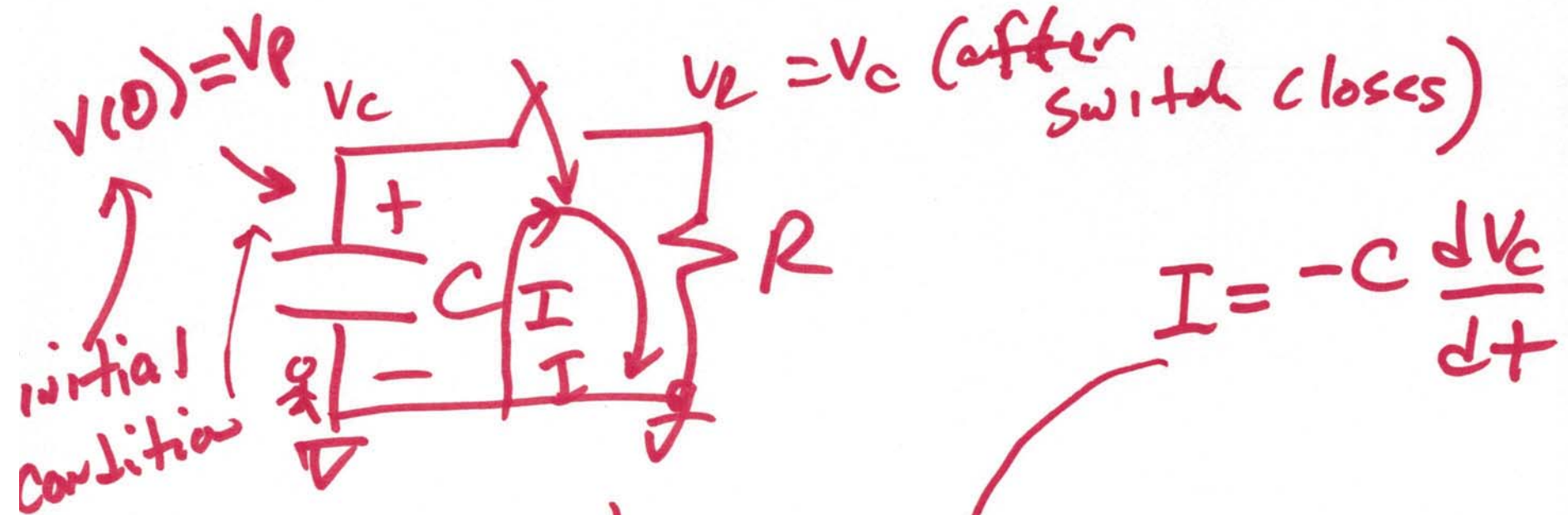

first-order differential Eqn.
separation of variables

$$v_c - IR = 0$$

$$v_c + RC \cdot \frac{dv_c}{dt} = 0$$


$$-\frac{t}{RC} = \int_0^t \frac{dt}{-RC} = \int_{V_{init}}^{V_f} \frac{dv_c}{v_c} = \ln V_f - \ln V_{init}$$

CMOSedu.com

cannot instantaneously
change q
cap



$$\frac{t}{RC} = \ln \frac{V_f}{V_{init}}$$

$$e^{-t/RC} = \frac{V_c(t)}{V_{init}}$$

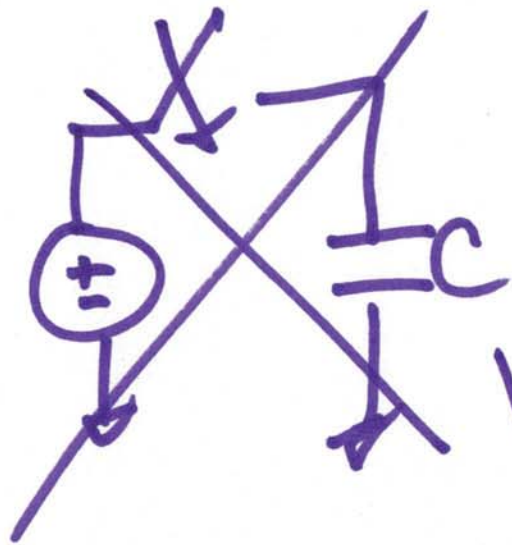

$$V_c(t) = V_{init} \cdot e^{-t/RC}$$

$$V_c(t) = V_p e^{-t/RC}$$

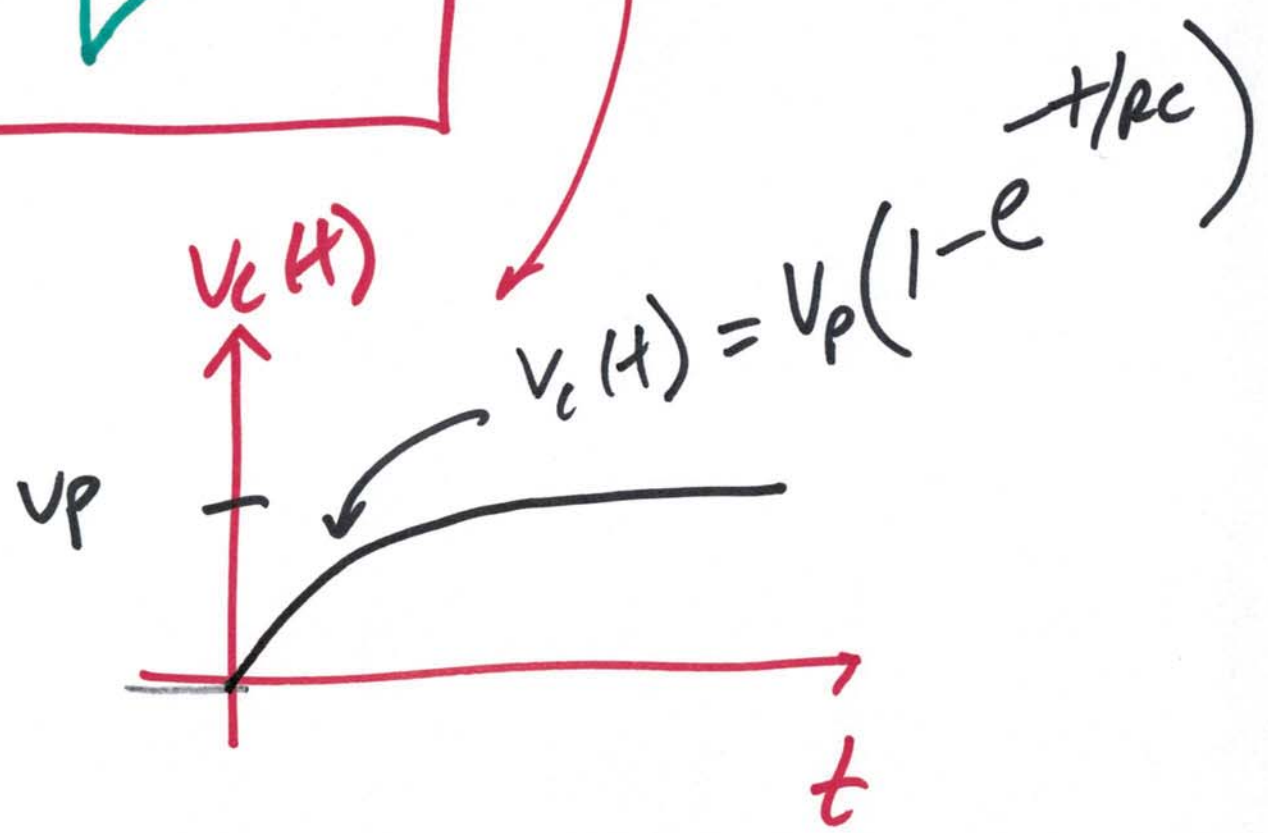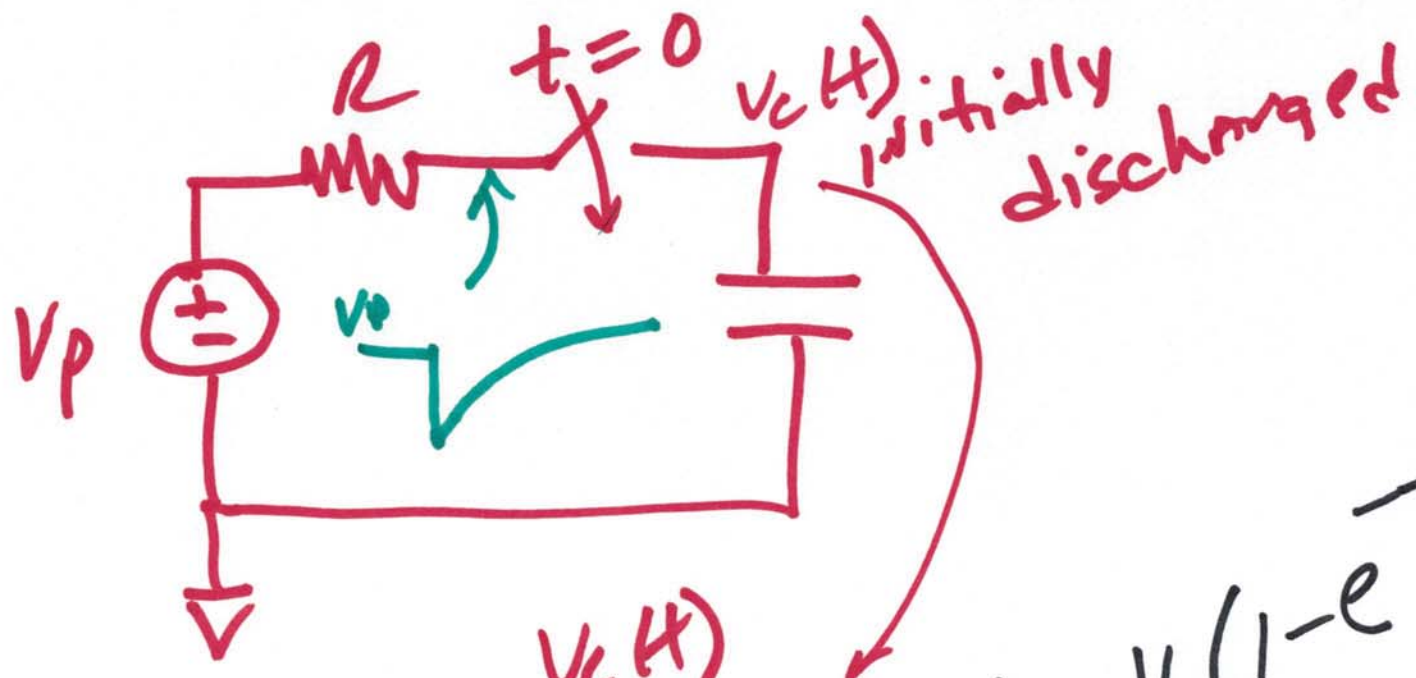

AC

b)