

EE 220

Circuits I

Lecture 15

$C = \text{FARADS}$

$Q = \text{Columbs}$


$V = \text{Volts}$

$$CV = Q$$

$$I = C \frac{dV}{dT}$$



$$V = \frac{1}{C} \int_{t_{\text{init}}}^{t_{\text{final}}} I \cdot dt$$

$$\frac{1}{T} \downarrow$$

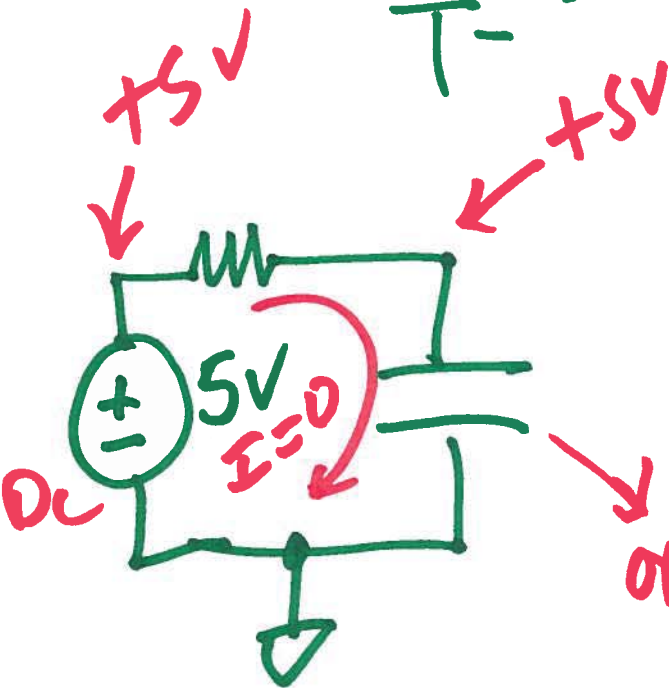


open for DC

$+3V$
 $-2V$
 $t=0$
 $t=t_0$
 V_{out}

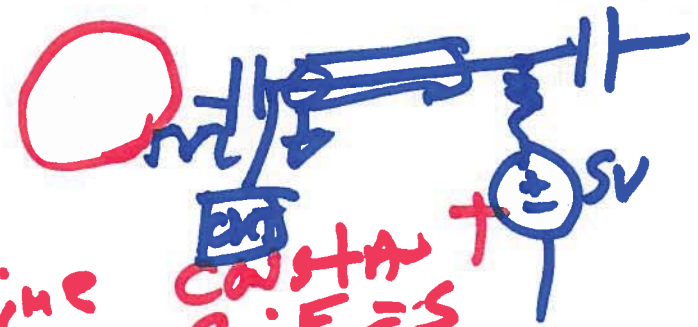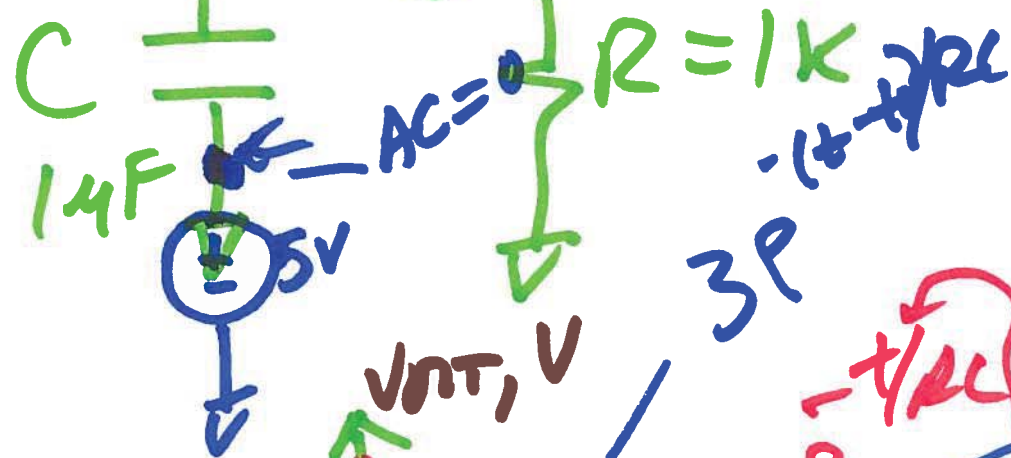


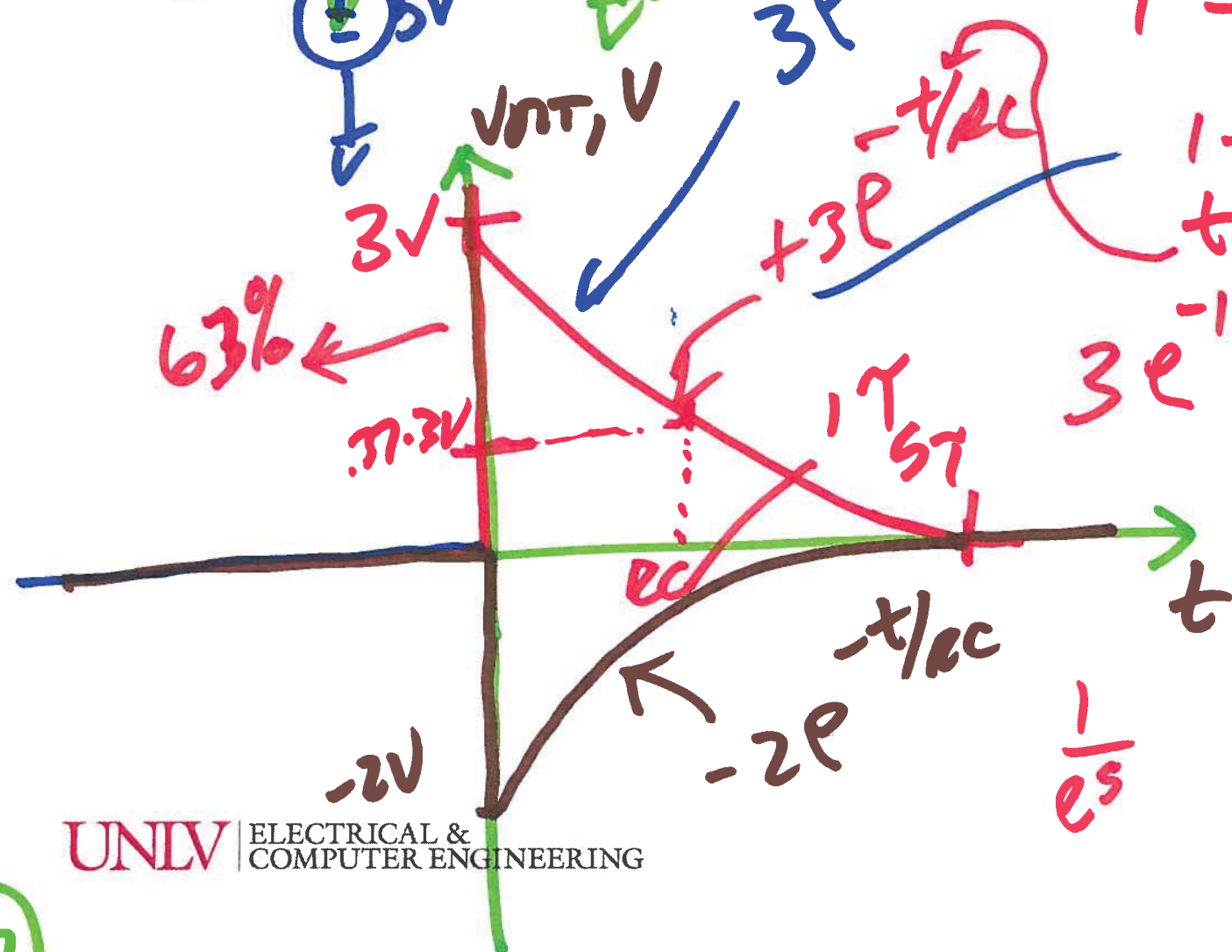time constant
 $\tau = R \cdot C$
 $\tau = 1 \text{K} \cdot 14 \text{F} = 14 \text{s}$



1 - time constant
 $t = RC$
 $3e^{-1} = \frac{3}{e} = 3 \cdot .37$
or
37% of 3V

31

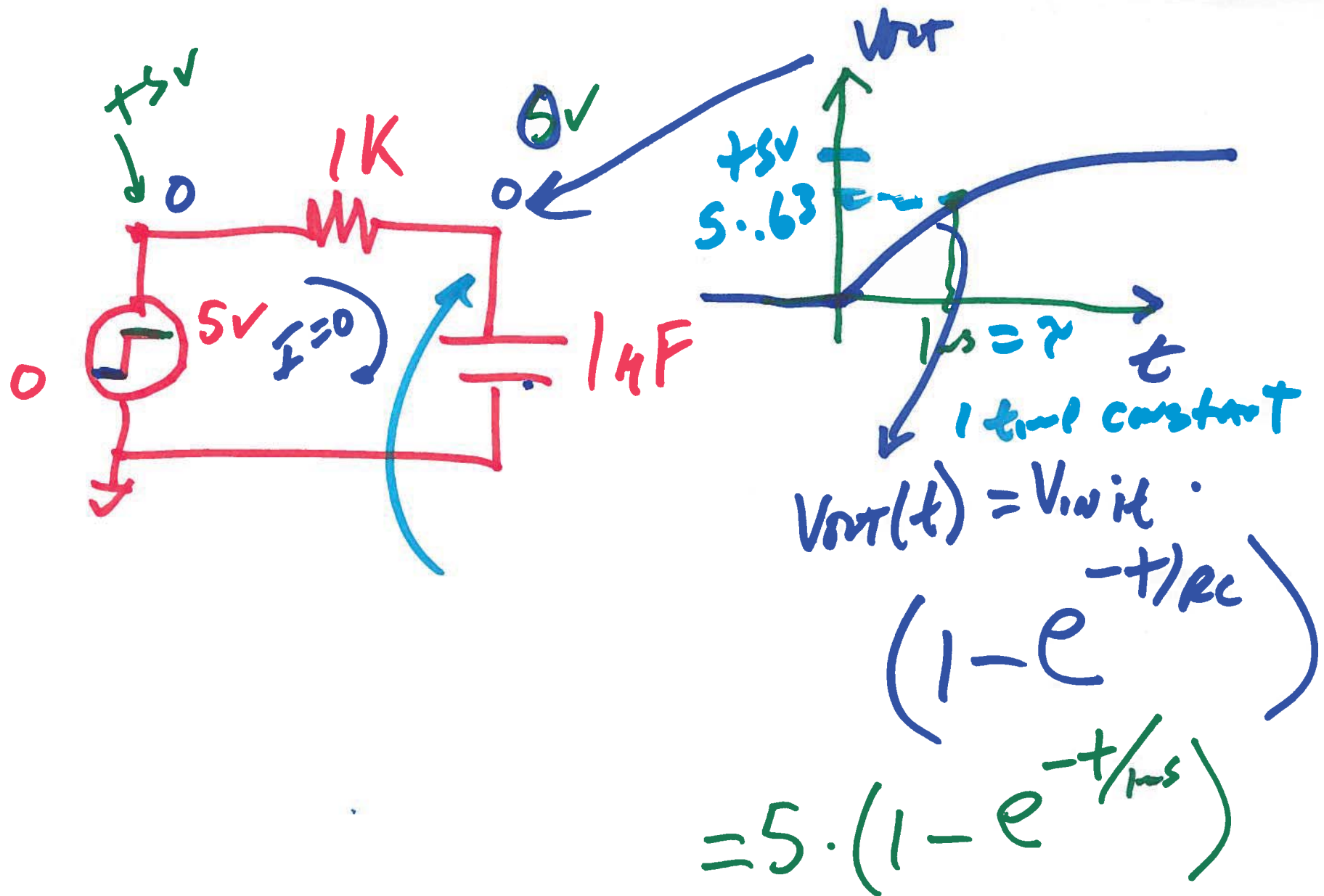

4)




$V_{NT} = ?$

EQ & sketch
 $V \cdot (1 - e^{-\frac{t-1-s}{0.8ms}})$



$$1 \cdot (1 - e^{-\frac{t-1-s}{0.8ms}})$$

$$V_{NT} = \frac{1K}{1K + 4K} \cdot 5$$


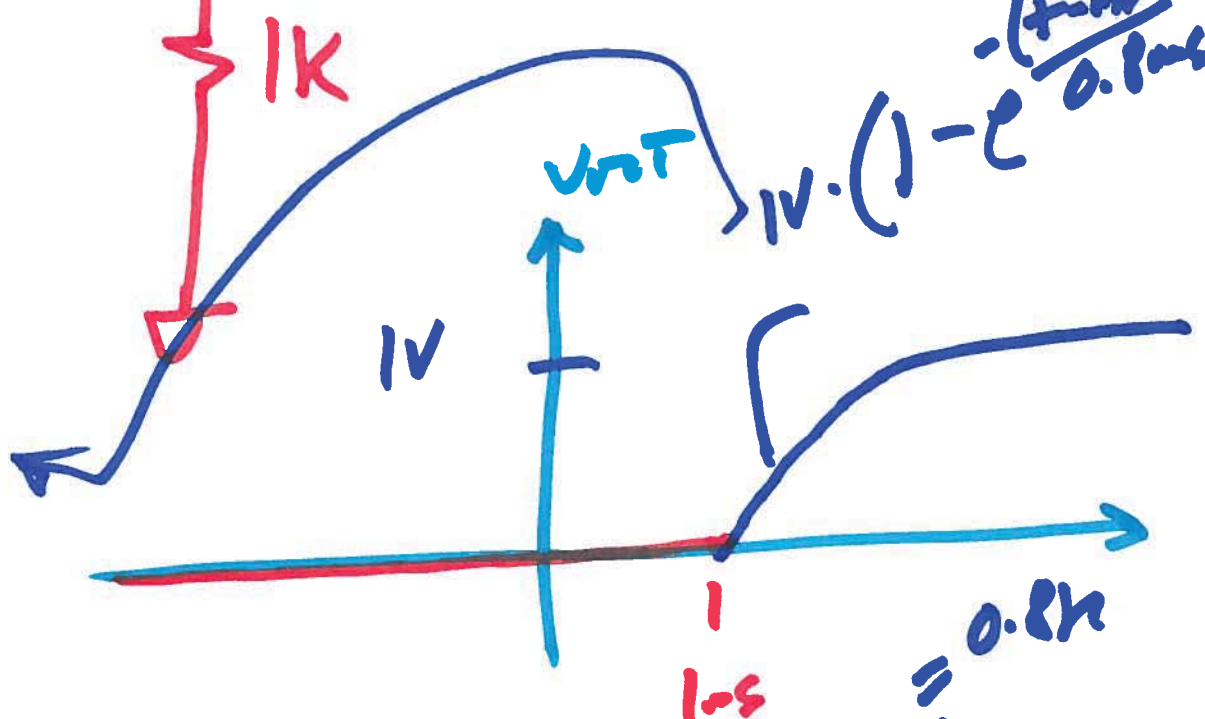


$$\frac{1K \cdot 4K}{4K + 1K} = R_K = 800$$

$$= 1V$$

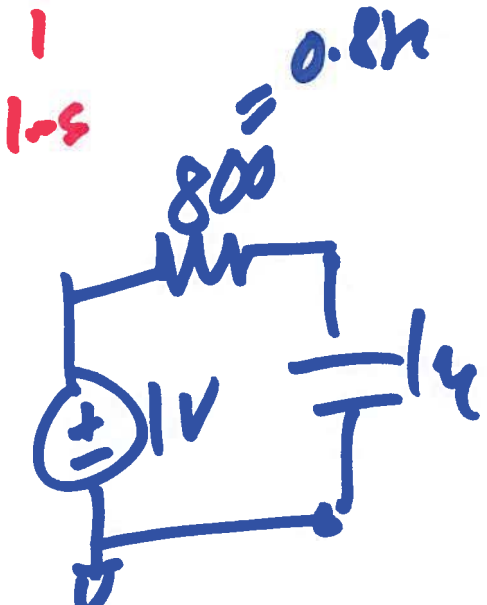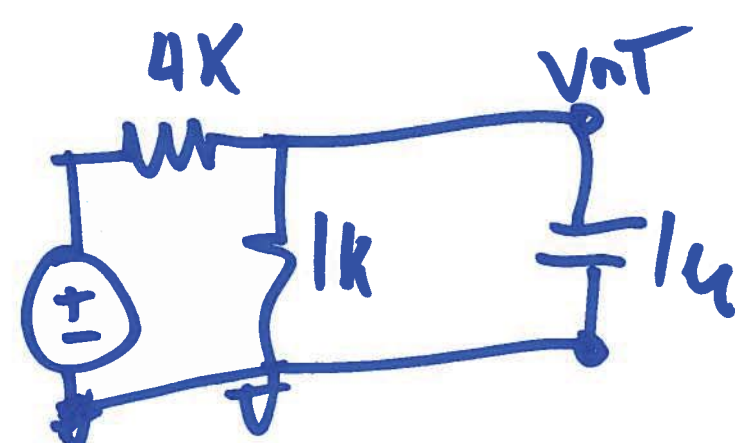

5)

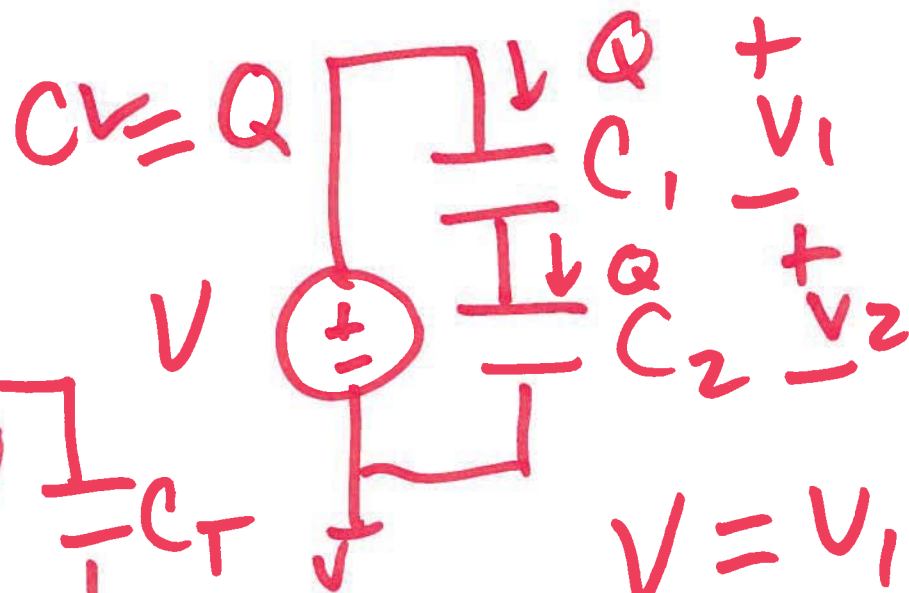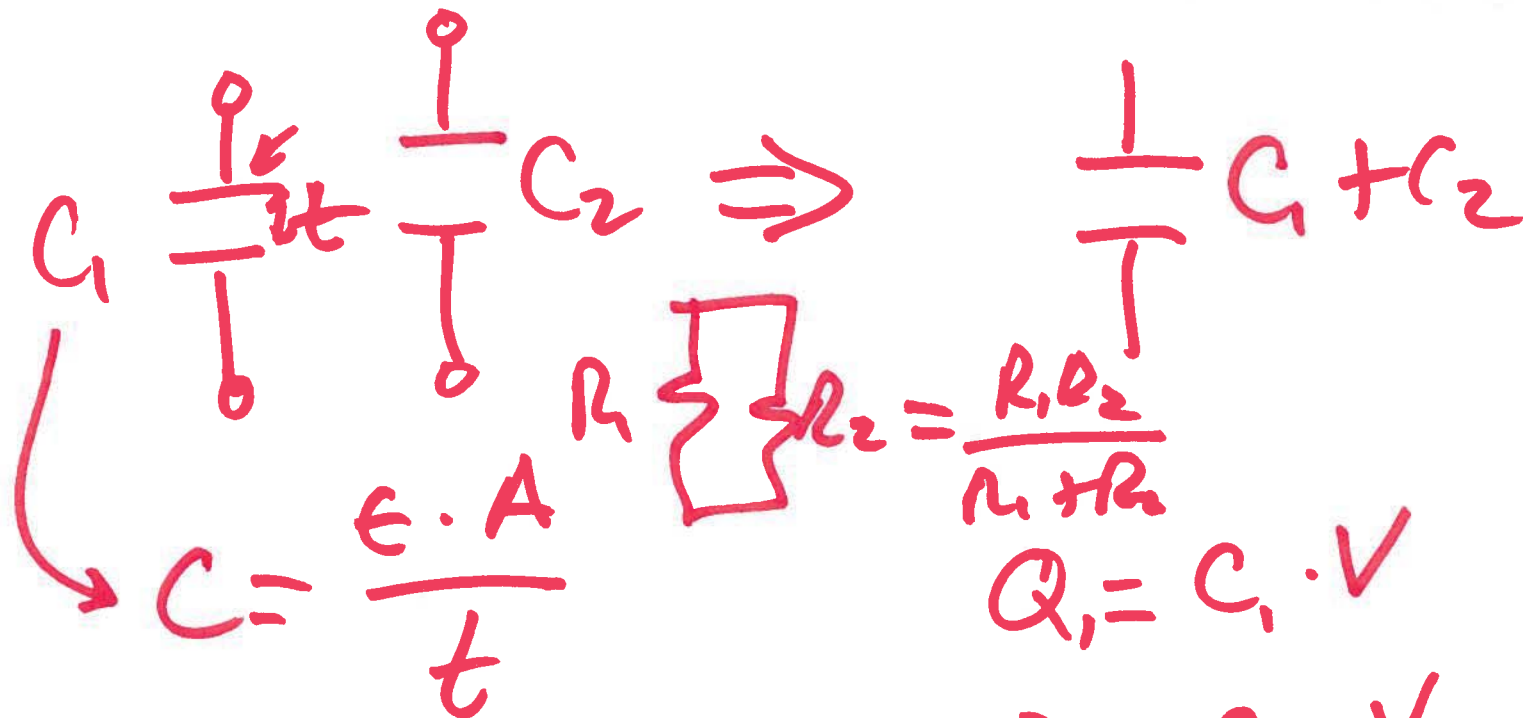

$$V = V_1 + V_2$$

$$C_1 V_1 = Q = C_2 V_2 \quad \left. \begin{array}{l} C_1 + C_2 \\ C_T V = Q \end{array} \right\}$$

$$C_T \cdot V = Q = C_T \cdot (V_1 + V_2)$$

$$V_1 = \frac{Q}{C_1}$$

$$V_2 = \frac{Q}{C_2}$$

$$C_T \cdot \overset{V_1 + V_2}{\cancel{V}} = C$$

$$C_T \left(\frac{Q}{C_1} + \frac{Q}{C_2} \right) = Q$$

$$C_T = \frac{C_1 \cdot C_2}{C_1 + C_2}$$

$$\frac{1}{C_T} = \frac{1}{C_2} + \frac{1}{C_1}$$

