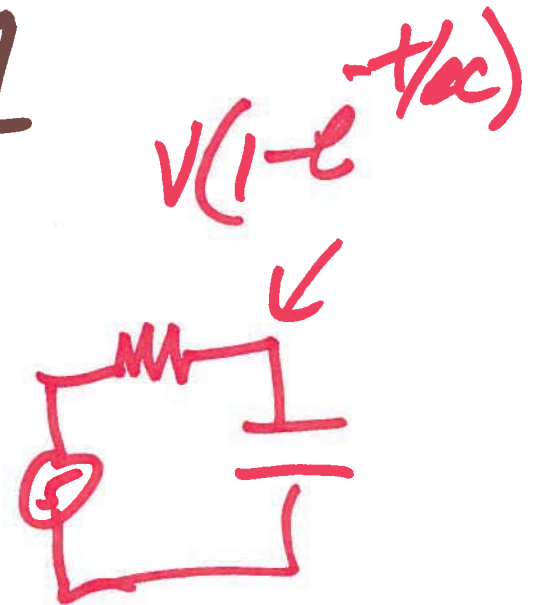


EE 220 circuits 1

Lecture 17



$$0 \leq t \leq 60\text{ns}$$


$$60\text{ns} \leq t$$


$$V_C(t) = 5(1 - e^{-t/RC})$$

$$V_C(t) = 5 - 5(1 - e^{-\frac{(t-60\text{ns})}{10\text{ns}}})$$


first-order

LR circuits

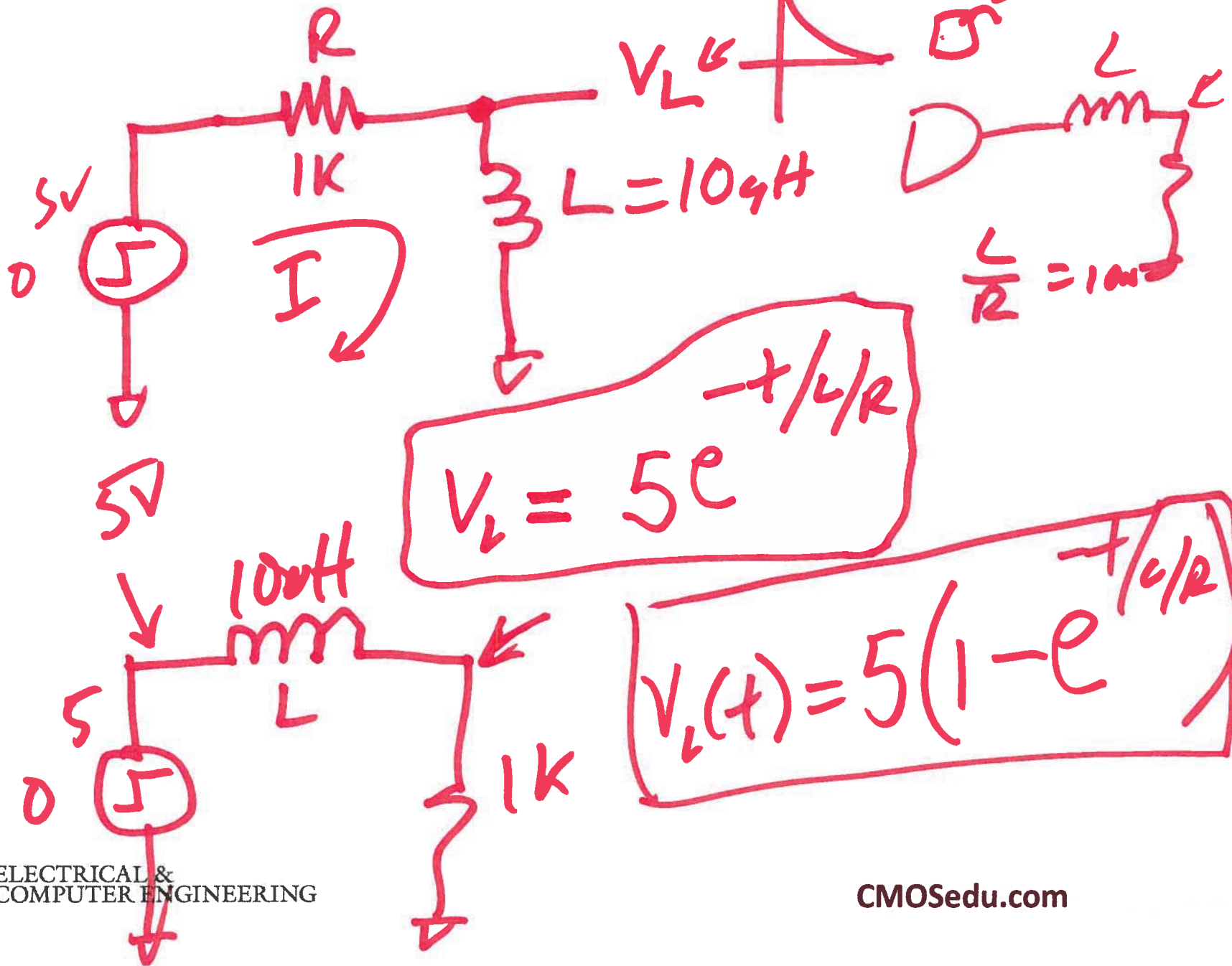

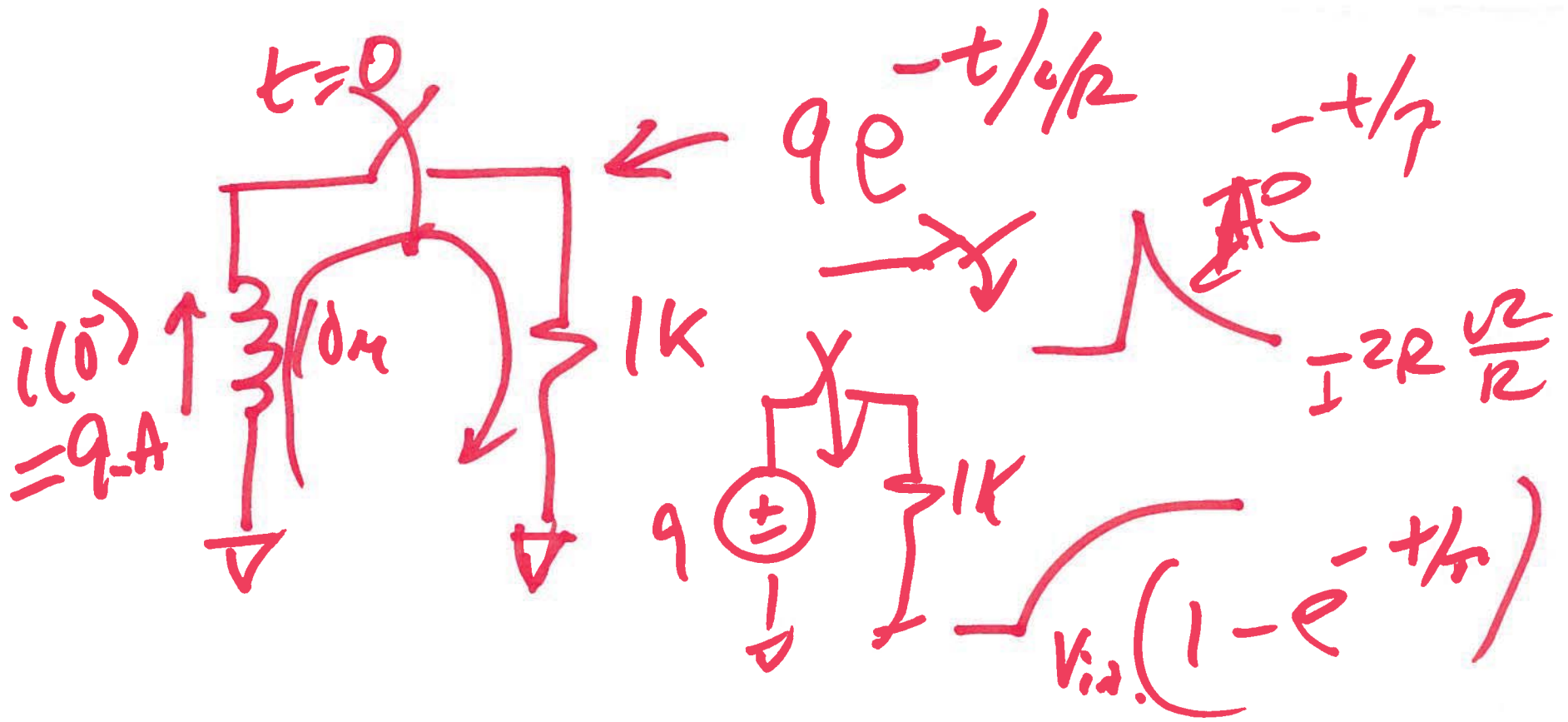

2)

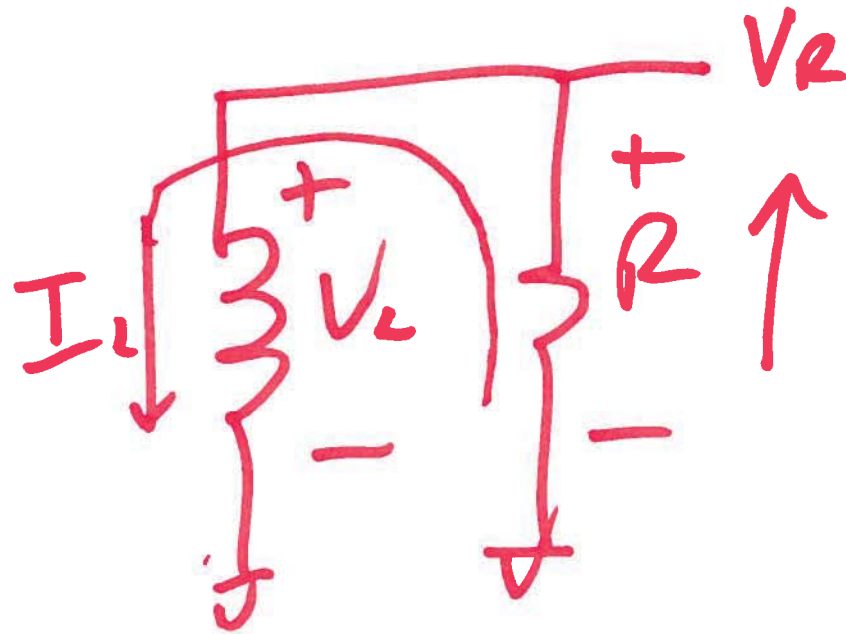

$$V_L = L \frac{dI_L}{dt}$$

$$I_L = \frac{1}{L} \int V_L \cdot dt$$

$$V_L = V_R = -I_L \cdot R \quad \Rightarrow \int \frac{+}{-} V = IR$$

$$L \cdot \frac{dI_L}{dt} = -I_L \cdot R \quad \uparrow \int \frac{+}{-} V = -IR$$


$$\int \frac{dI_L}{I_L} = \int_0^t -\frac{R}{L} \cdot dt$$


$$\int_{I_{init}}^{i_L(t)} \frac{dI_L}{I_L} = \int_0^t -\frac{R}{L} \cdot dt$$
$$= \ln \frac{i_L(t)}{I_{init}} = -\frac{(t-0)}{L/R}$$

$$\ln i_L(t) - \ln I_{init} = -t/L/R$$

$$i_L(t) = I_{init} \cdot e^{-t/L/R}$$
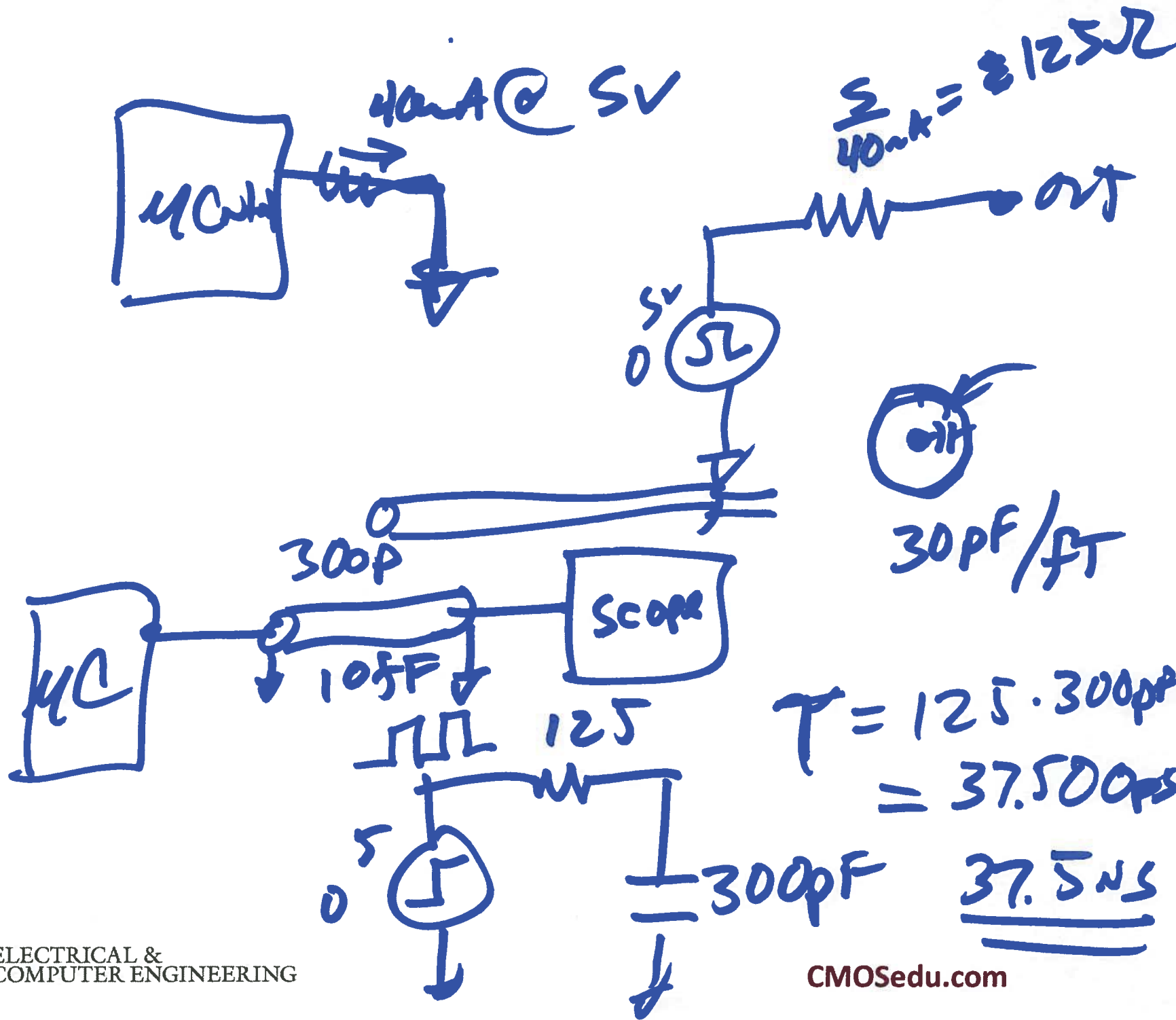
$$V_R(t) = R \cdot I_{init} \cdot e^{-t/L/R}$$



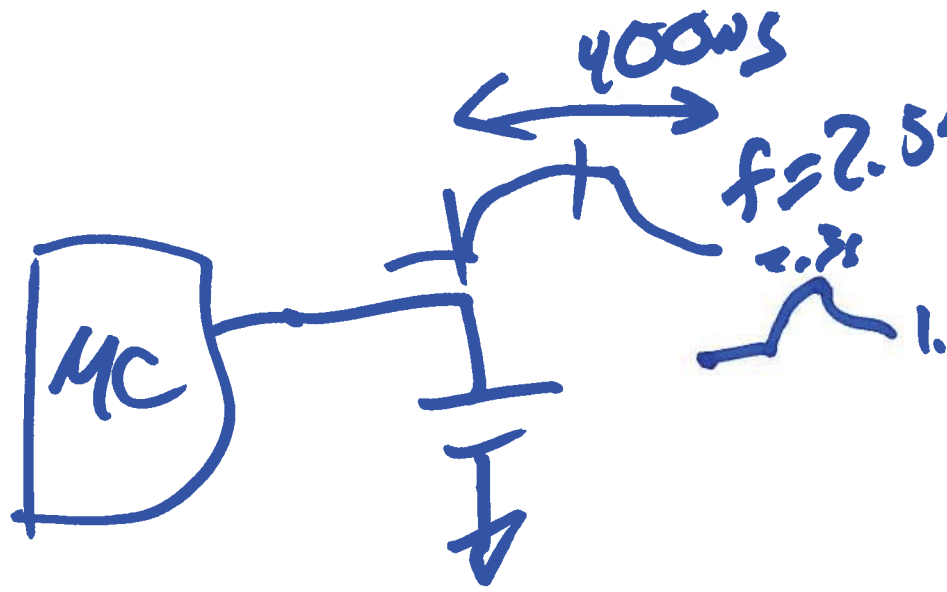


$$T = 37.5 \text{ ns}$$


$$5T = 187.5 \text{ ns}$$

$$f = 10 \text{ MHz}$$

$$T = 100 \text{ ns}$$

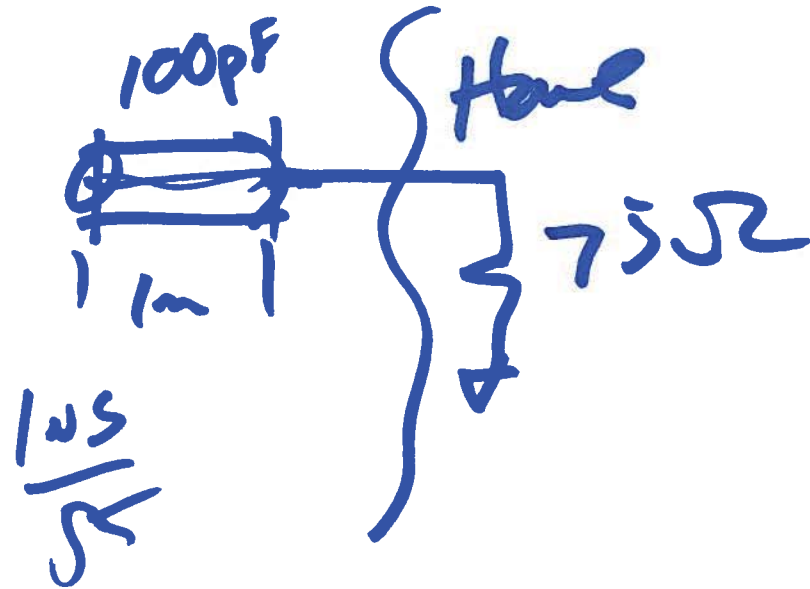

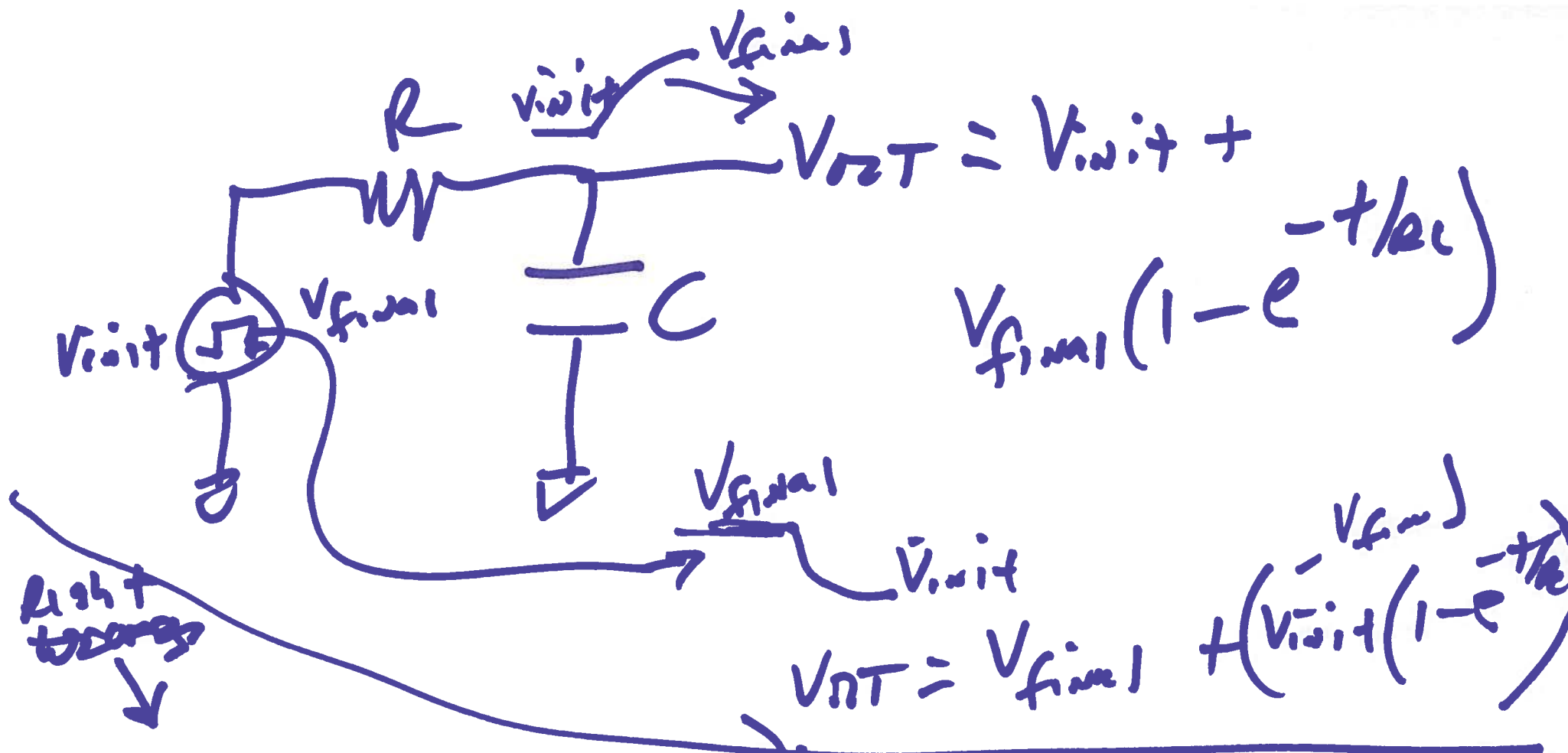
$$T = \frac{30 \text{ pF} \cdot 1 \text{ cm}}{fT}$$





$$V_{out}(t) = (V_{final} - V_{init})e^{-t/RC} + V_{init}$$

9)

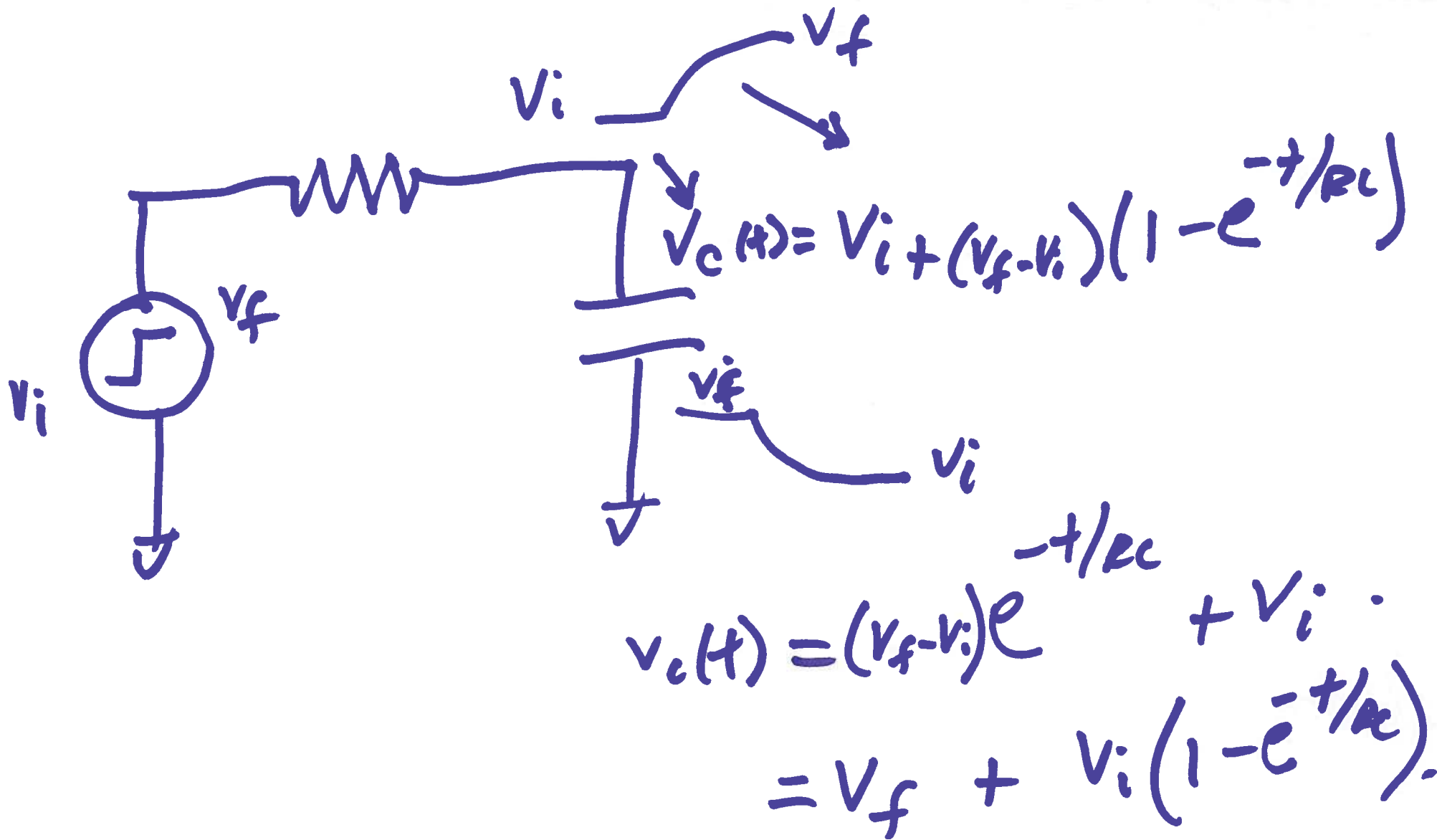

9)

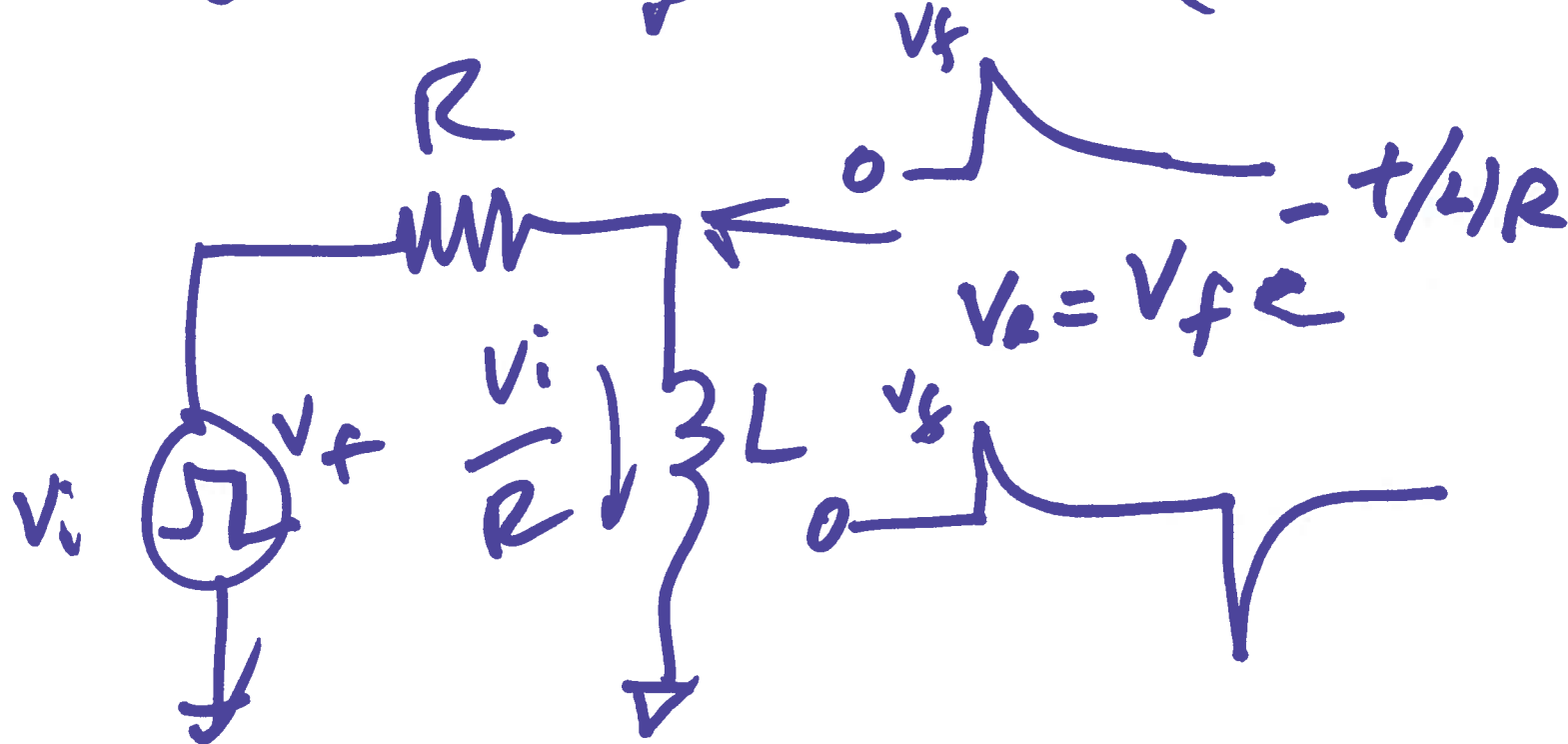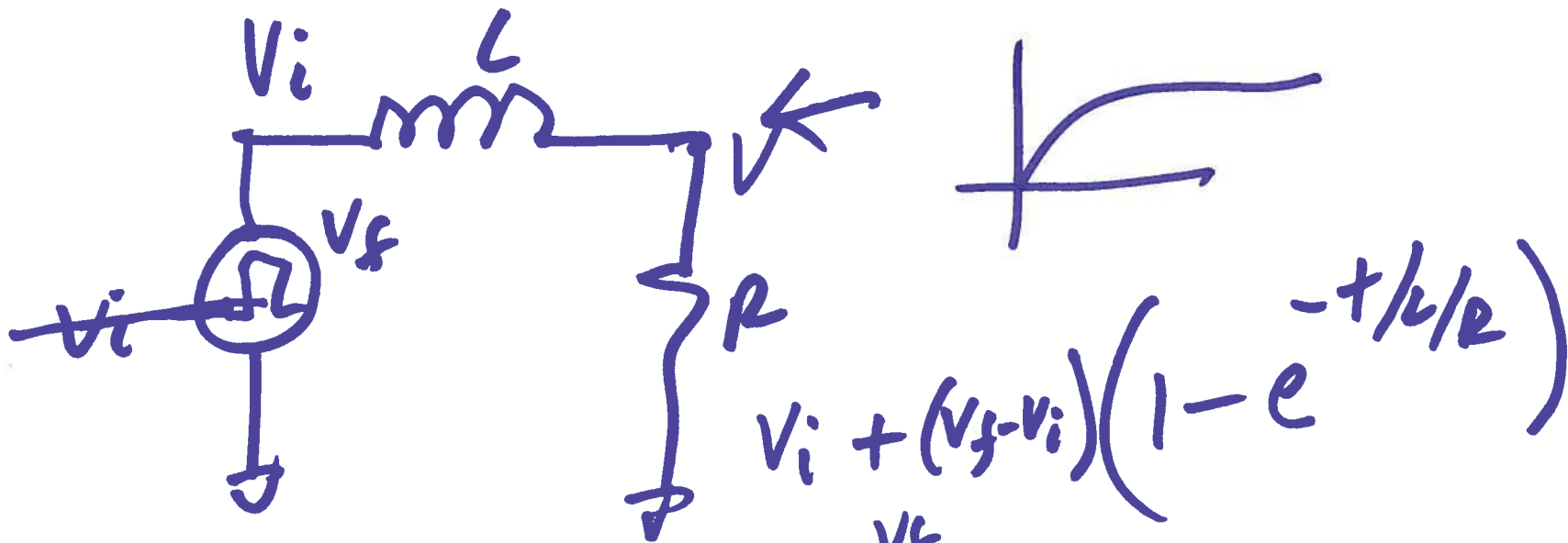

10)