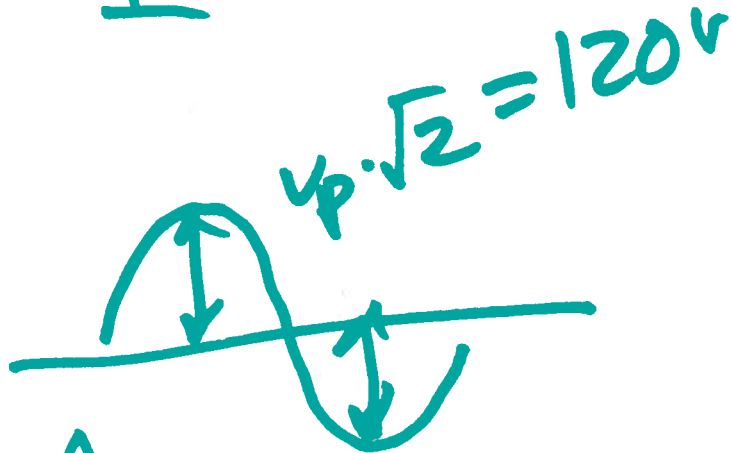


EE 220

# Circuits I

Lecture 19

$\sim 5 \text{ mA}$



$$\frac{120 \text{ V}}{20 \Omega} = 6 \text{ mA}$$



ideal  
don't

capacitors & inductors  
dissipate power  
they store energy

11

$$\frac{1}{C}$$

$$CV = Q$$

$$V = \frac{1}{C} \int i \cdot dt$$

$$P(t) = i(t) \cdot V(t)$$

$$i = C \cdot \frac{dV}{dt}$$

$$P(t) = V(t) \cdot C \cdot \frac{dV(t)}{dt}$$

$$E = \int P(t) \cdot dt = C \int_0^V V(t) dV(t)$$

$$E_{\text{Energy}} = C \cdot \frac{1}{2} (V - 0)^2$$


$$E = \frac{1}{2} CV^2$$

2)

$$\begin{aligned} P &= V \cdot I \\ &= \frac{V^2}{R} \\ &= I^2 \cdot R \end{aligned}$$


Power = Watts =  $\frac{J}{s}$

ENERGY = Joules

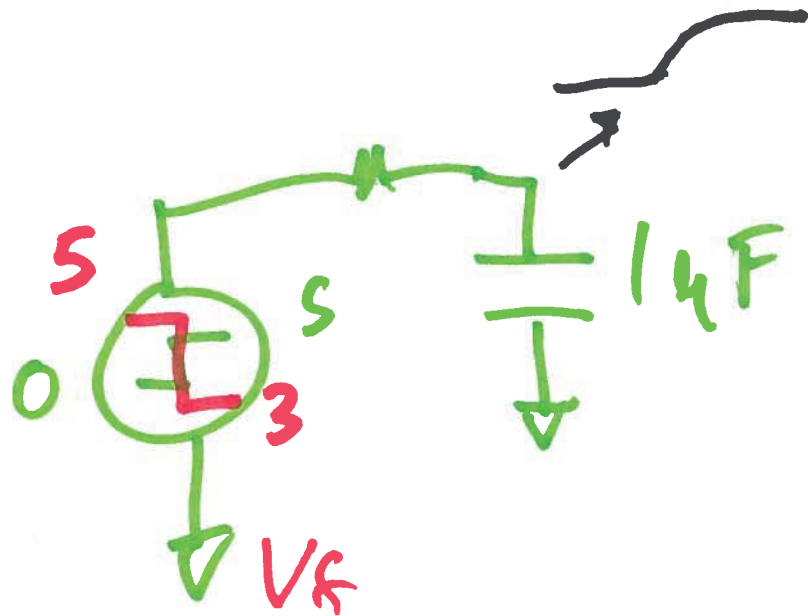

CALCULATE ENERGY stored in C
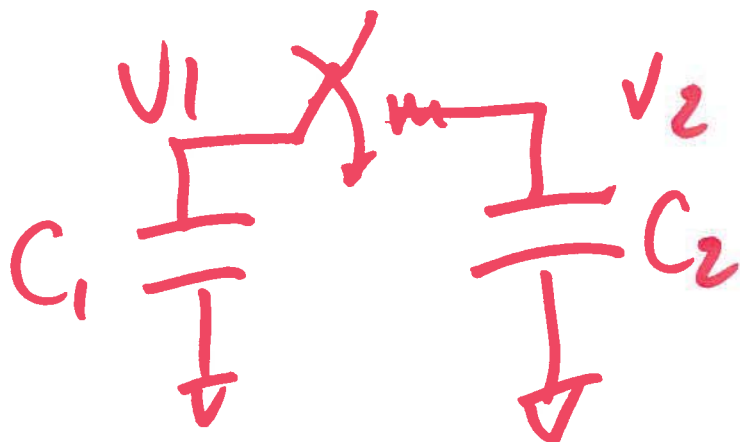
$$E = \frac{1}{2} 14F \cdot 5^2 = \underline{\underline{12.54J}}$$



$$E_d = \frac{1}{2} 14F \cdot 2^2 = 24J$$

$$C_1 V_1 + V_2 C_2 = V_f (C_1 + C_2)$$

$$P \approx C_L V_{DD}^2 \cdot f$$

3)

$$i(t) = \frac{1}{L} \int v(t) dt$$

$$p(t) = i(t) \cdot v(t)$$

$$v(t) = L \cdot \frac{di(t)}{dt}$$

$$p(t) = L \cdot i(t) \cdot \frac{di(t)}{dt}$$


$$\Sigma = \int p(t) \cdot dt = L \cdot \int_0^I i(t) \cdot dt = \boxed{\frac{1}{2} L I^2 = \Sigma}$$

↑ energy

10A ↓  $\left\{ \begin{array}{l} 1 \\ 3 \\ 10 \mu\text{H} \end{array} \right.$

$$\begin{aligned} \Sigma &= \frac{1}{2} 10\mu (10\mu\text{A})^2 \\ &= \frac{1}{2} \cdot 10^{-6} \cdot 10^{-6} \cdot 10^2 \cdot 10^{-6} \end{aligned}$$
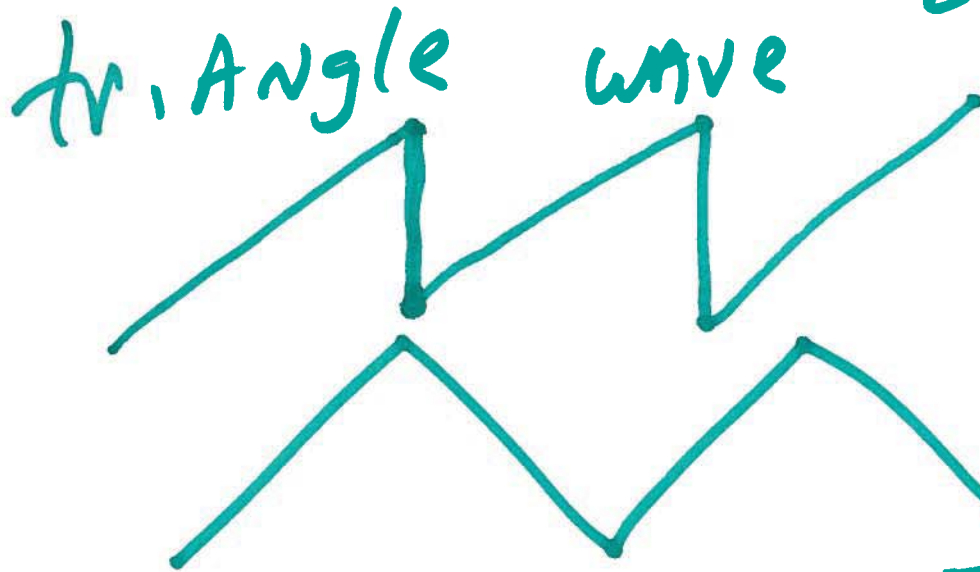
$$= \frac{1}{2} \text{NJ} = \frac{1}{2} \cdot 10^{-9} \text{J}$$



$\frac{\text{Volts}}{\text{distance field}}$  = Electric field

s/e,  $\frac{\text{V}}{\text{cm}}$



$$V = \int E \cdot dl$$



CMOSedu.com

# Integrators



$$I = C \frac{dV}{dt}$$

$$\frac{dV}{dt} = \frac{I}{C}$$

switch closes

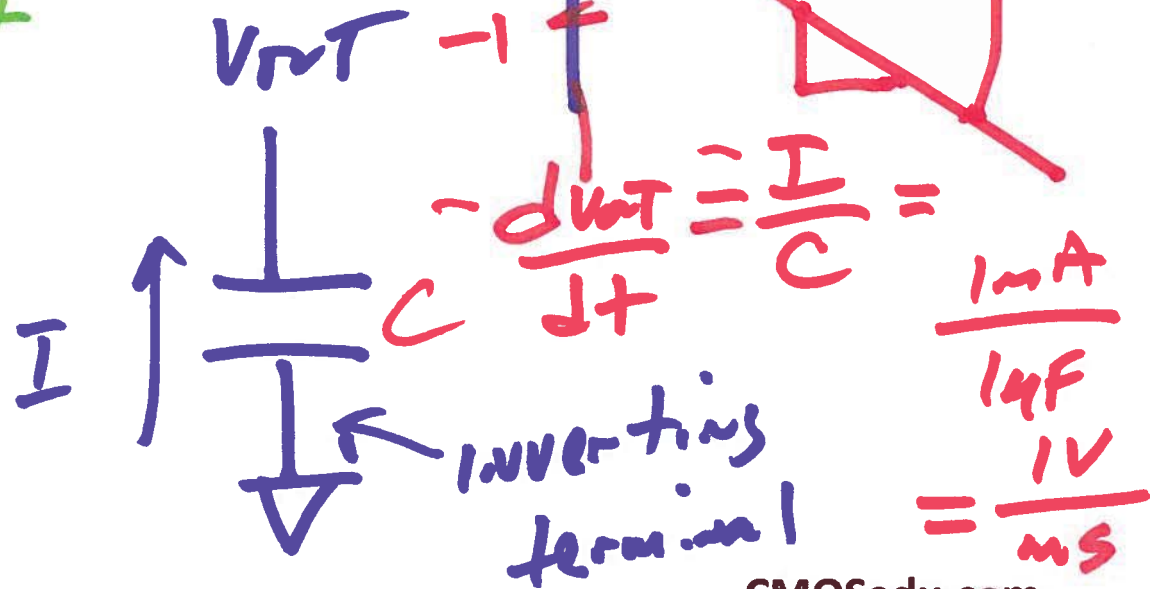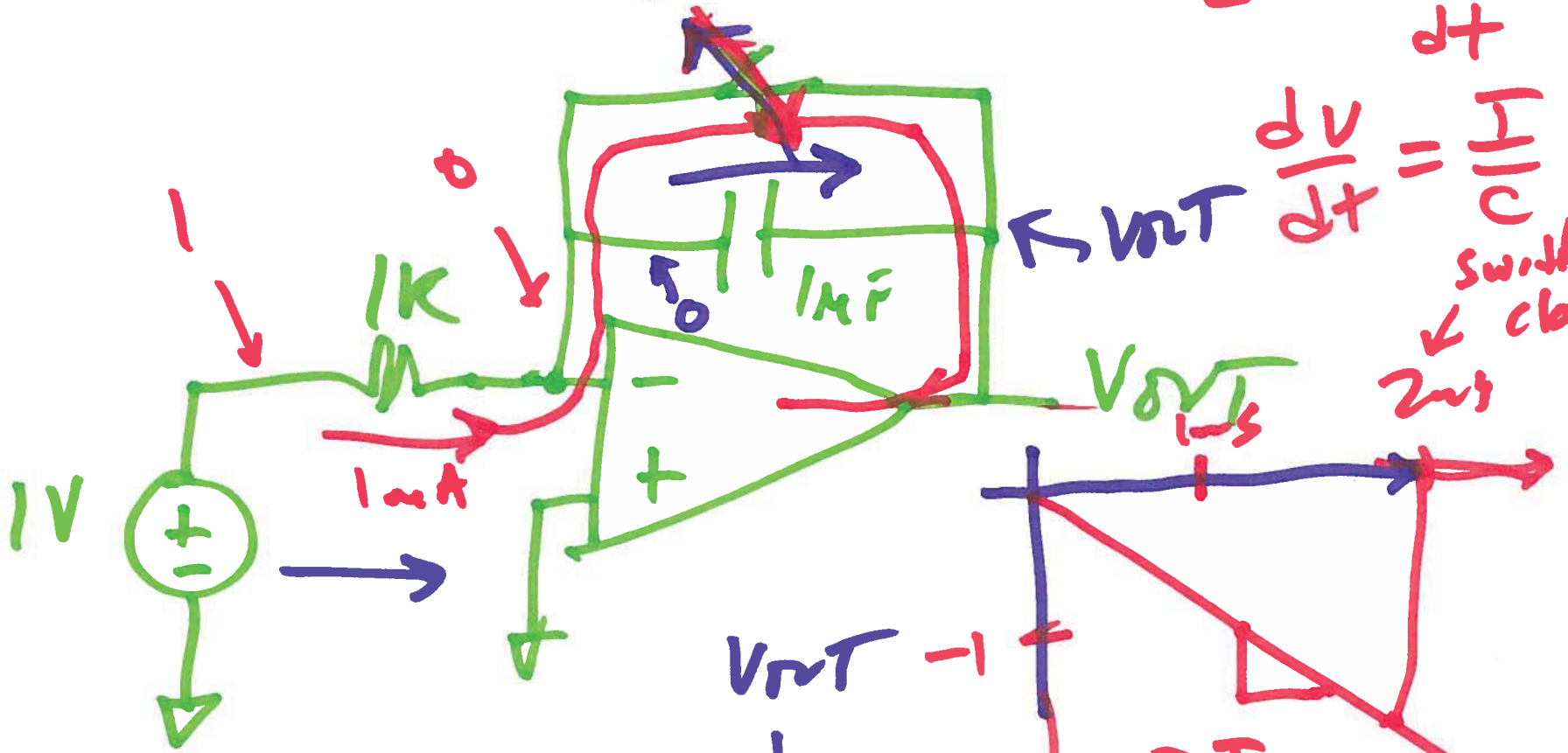

b)

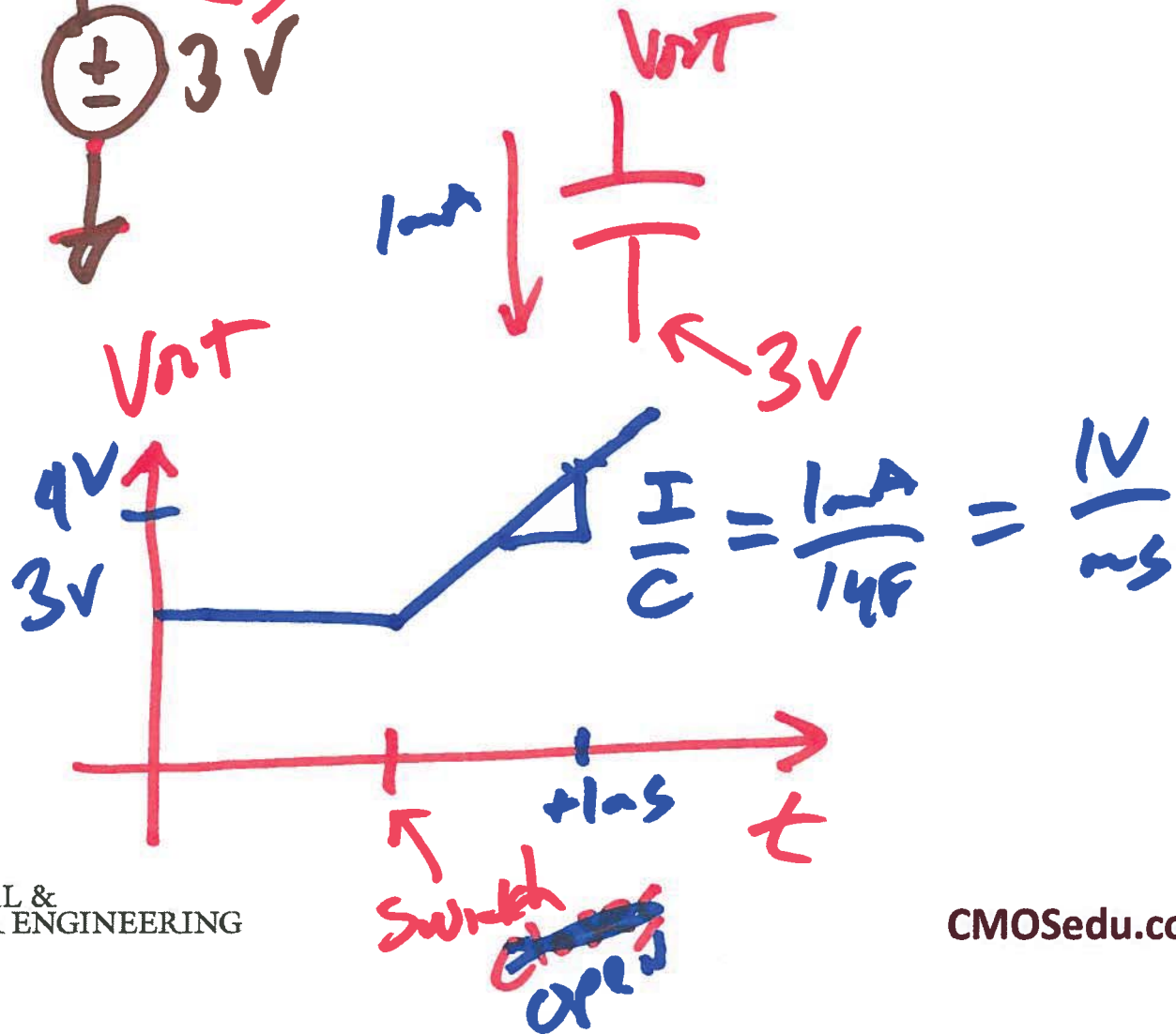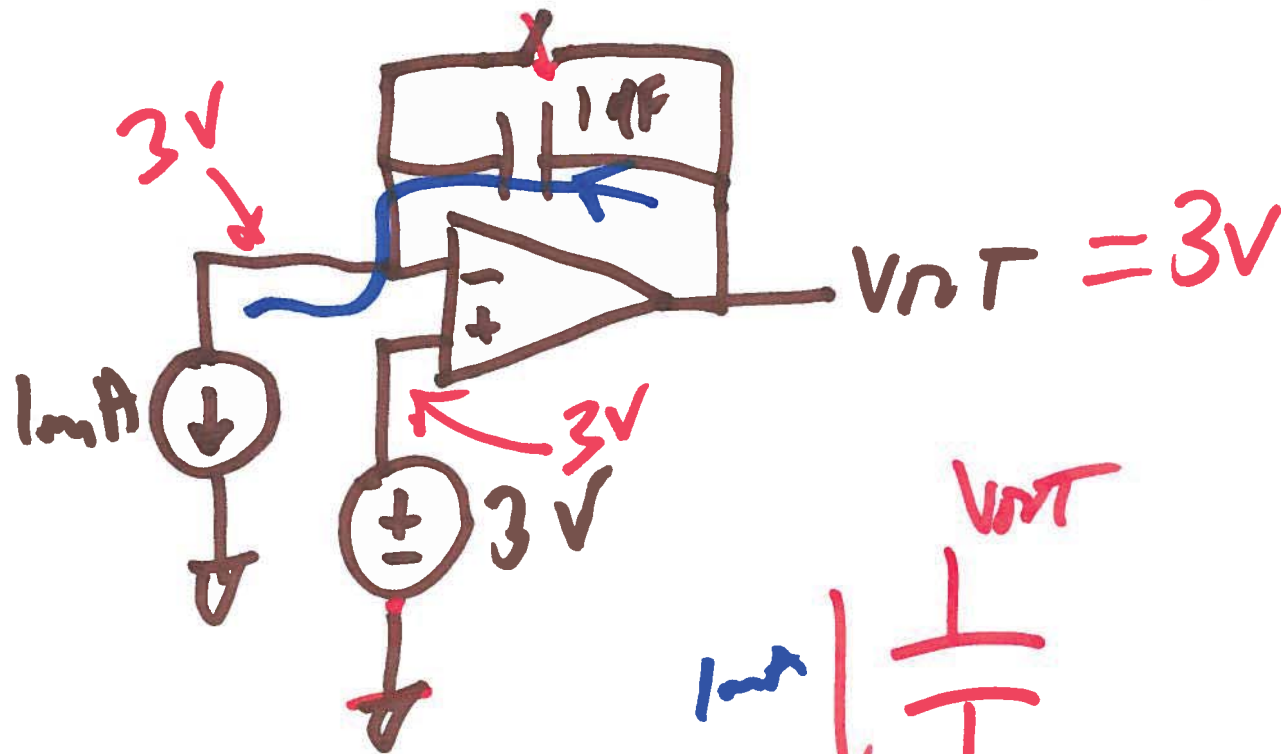

1)