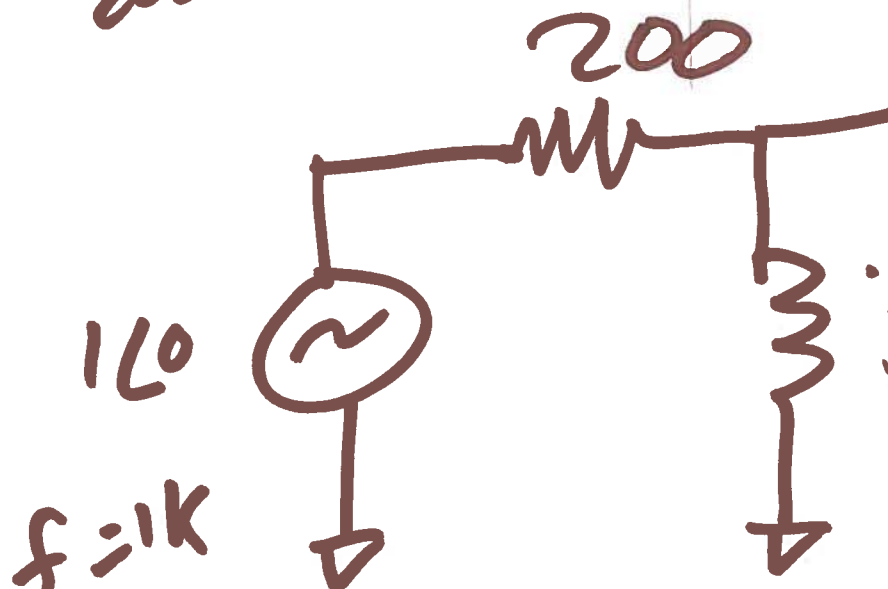


# EE 220

$$\sqrt{200^2 + 251^2} = 321 \text{ Circuits } |$$

$$\tan^{-1} \frac{251}{200} = 51.5^\circ$$

## Lecture 23



$$j \cdot 2\pi \cdot 10^3 \cdot 40 \cdot 10^{-6} = j \cdot 251$$

$$V_T = \frac{160 \cdot 0 + j251}{200 + j251}$$

$$|0 + j251| = 251$$

$$\angle \uparrow = 90^\circ = \tan^{-1} \frac{251}{0} = 90$$

1)

$$\text{RAD} \cdot \frac{360}{2\pi} \quad v_{out} = \frac{160 \cdot 251 \angle 90}{321 \angle 51.5}$$

$$\text{RAD} \cdot \frac{180}{\pi} = \text{deg.}$$

$$= \frac{1.251}{321} \angle 0 + 90 - 51.5$$

$$v_{out} = 0.782 \cdot$$

$$0.782 \angle 38.5^\circ$$


$$\sin(2\pi \cdot 1\text{kHz} \cdot t + 51.5)$$

$$\theta = \frac{360 \cdot t_d}{T}$$

$$t_d = \frac{38.5 \cdot}{360 \cdot 1\text{kHz}}$$

$$= \frac{360 \cdot t_d \cdot f}{2\pi}$$

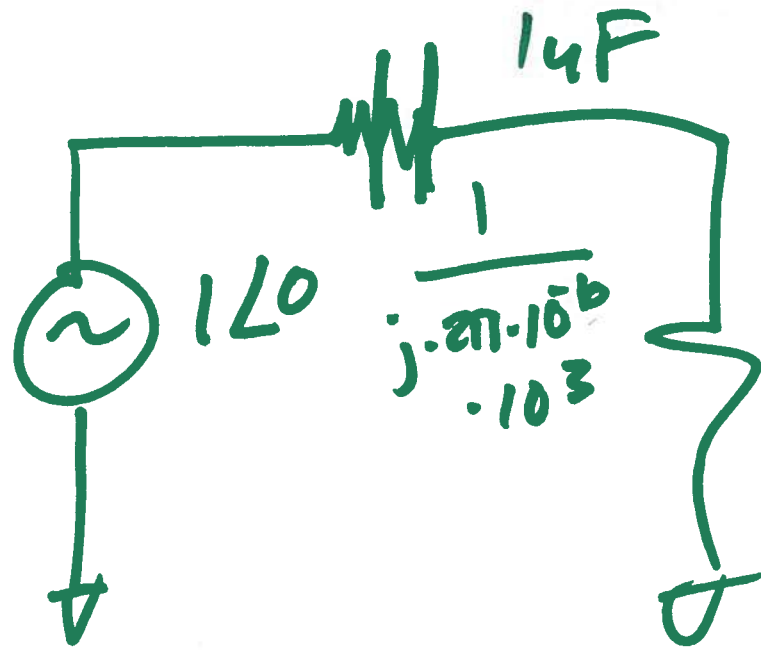v)  $t_d = \underline{\underline{0.11 \mu\text{s}}}$



$$\frac{1}{j2\pi f C}$$

200

RESISTANCE  
 $Z = R + jX$   
 ↑ impedance      ↑ Reactance

$$j\omega = S$$


$$\sigma + j\omega = S$$

$$Z_{in} = 100 \cdot \frac{200 + j \cdot 0}{200 + j(-159)}$$



$$= \frac{100 \cdot 200 \angle 0^\circ}{256 \angle -38.5^\circ}$$

$$= .781 \angle +38.5^\circ$$


$$200^2 + 159^2$$

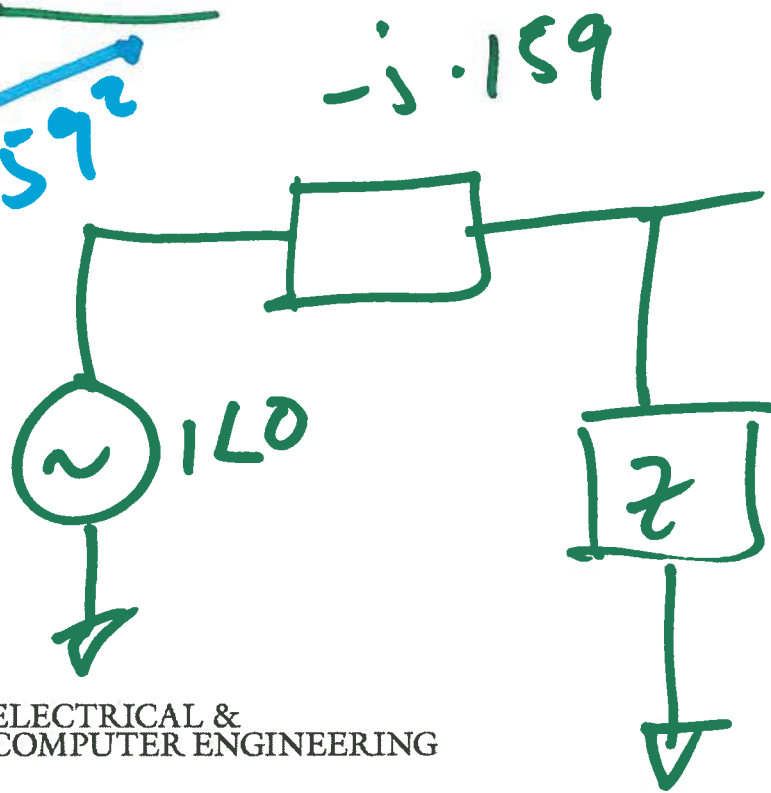

3)

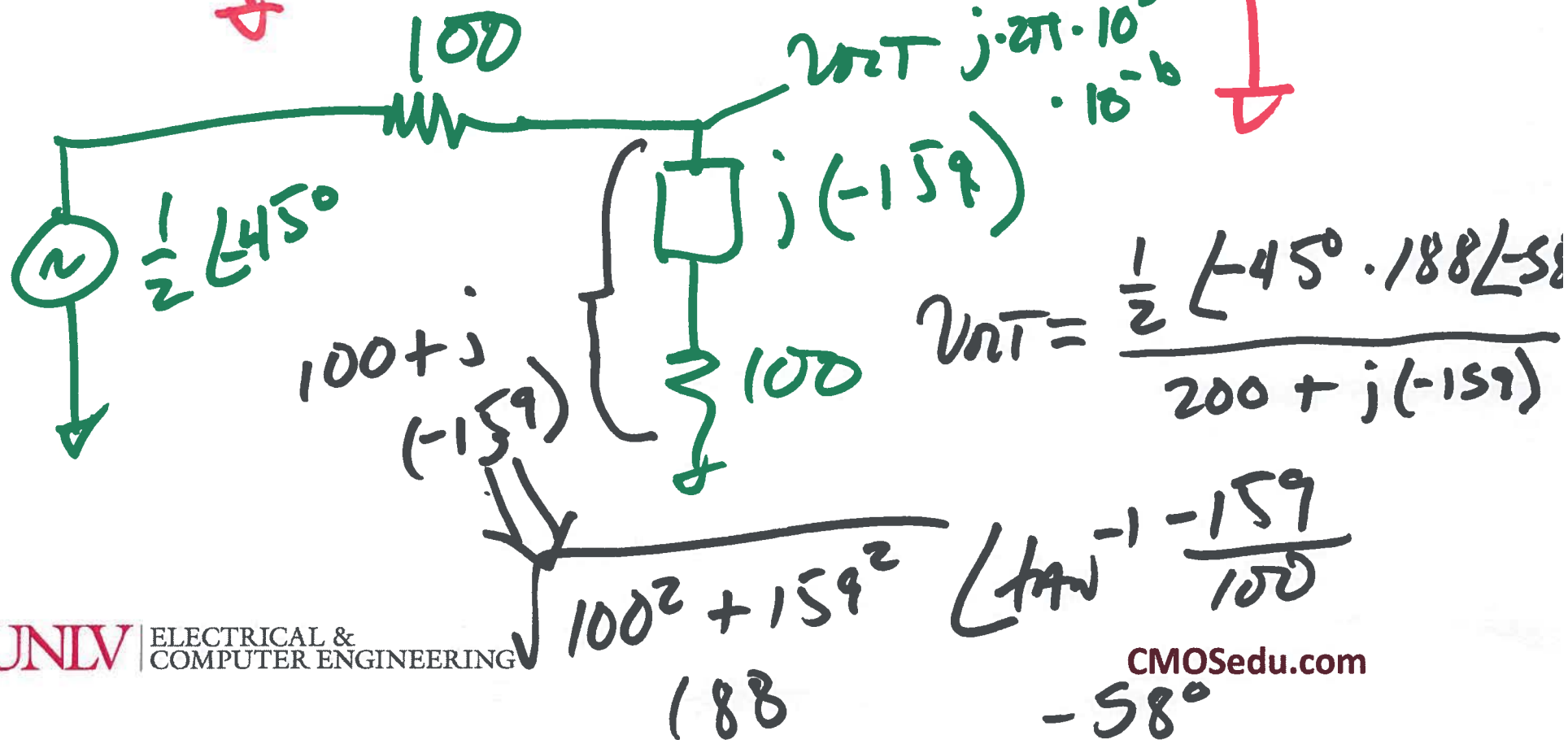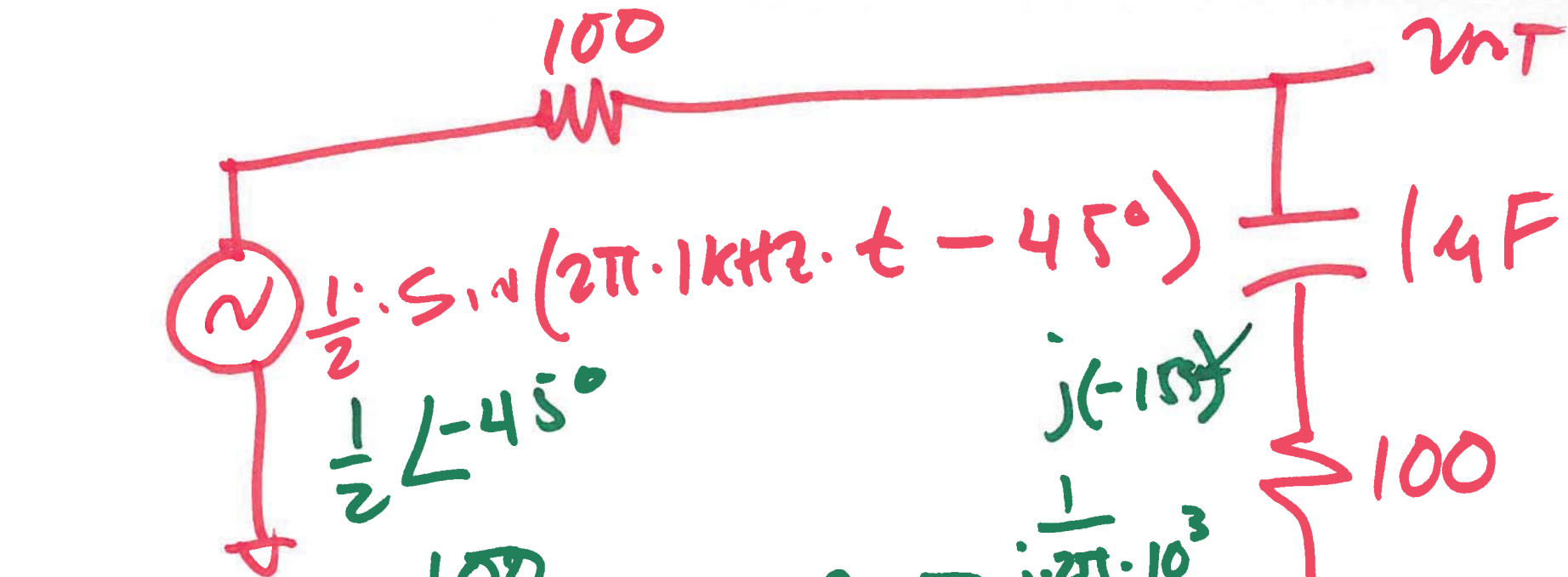

4)

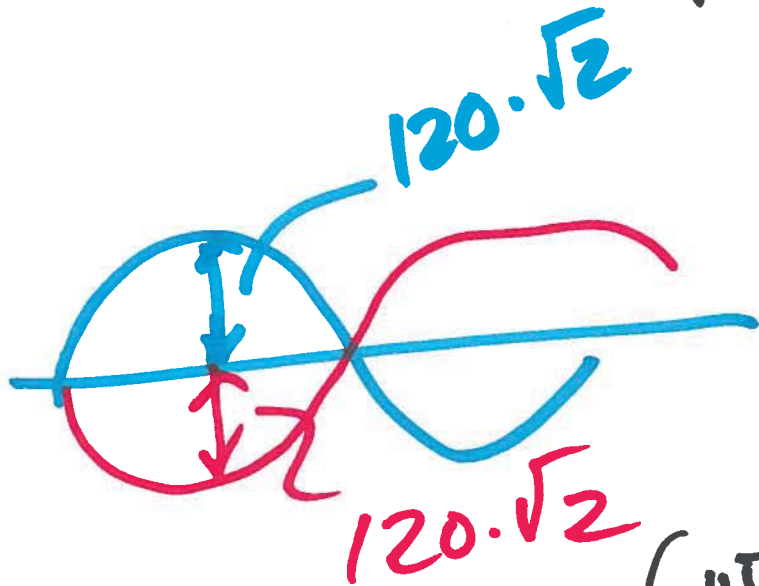

$$\sqrt{200^2 + (159)^2} = 255.5$$

$$\tan^{-1} \frac{-159}{200} = -38.5^\circ$$

$$V_{out} = \frac{\frac{1}{2} \angle 45^\circ \cdot 188 \angle -58^\circ}{256 \angle -38.5^\circ}$$

$$= \frac{(-45) + (-58)}{-(-38.5)} = .367 \angle -64.5^\circ$$


$$V_{out} = .367 \angle -64.5^\circ$$

$$t_d = \frac{64.5}{360} \cdot 1 \text{ms}$$


$$v_{out} = .367 \sin(2\pi \cdot 1 \text{kHz} \cdot t - 64.5^\circ)$$

$$= .179 \text{ms}$$

5)

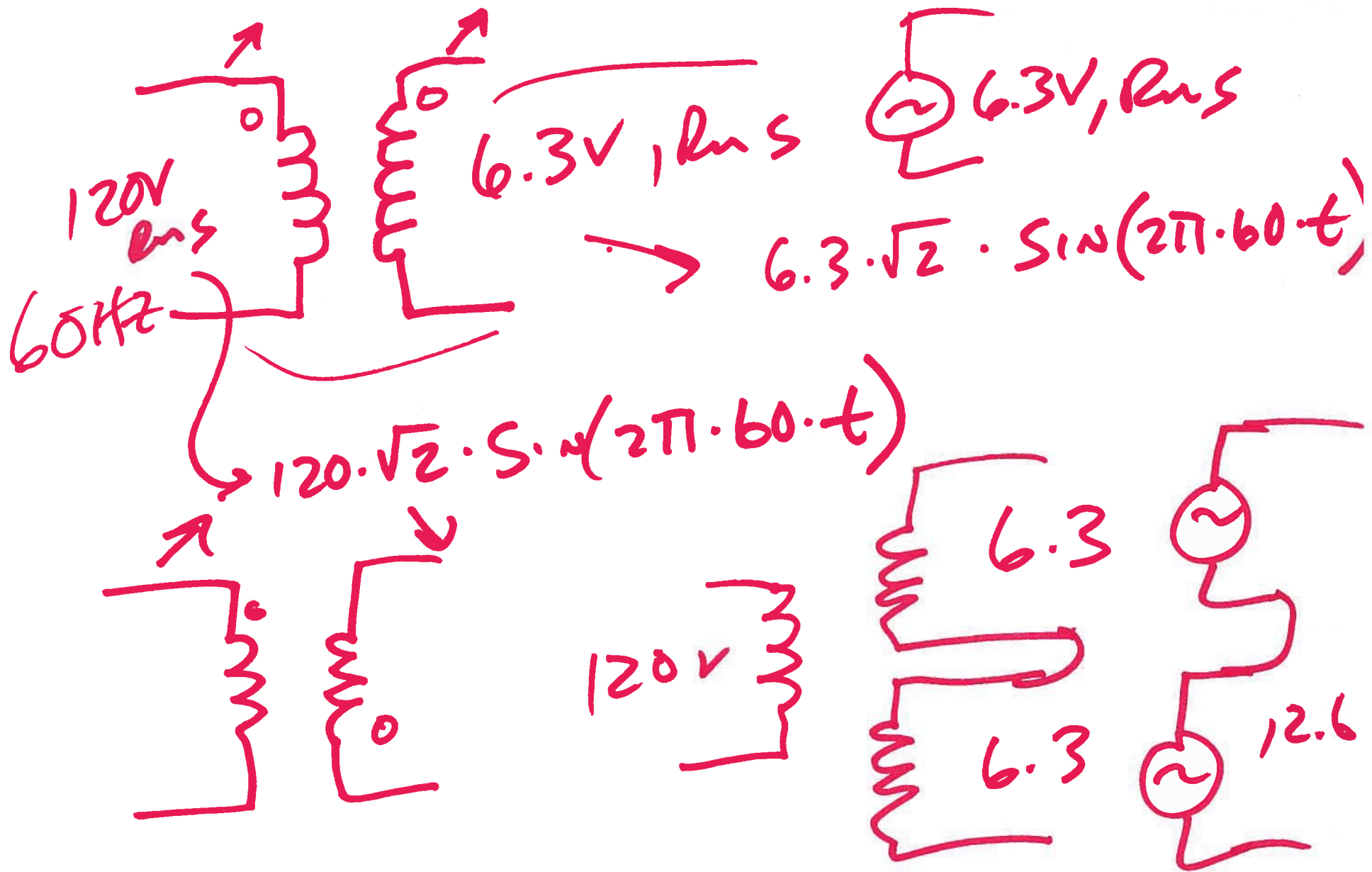

6)

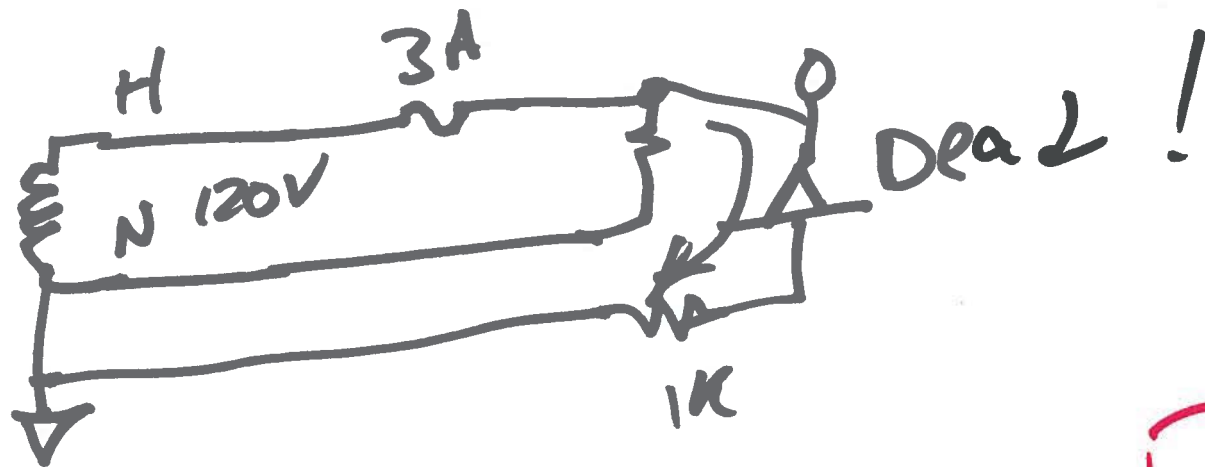

isolation transformer

