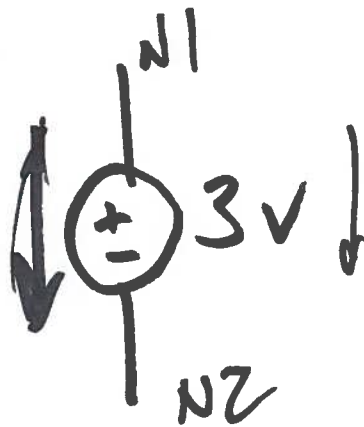


EE 220

Circuits I


Lecture 3



V1 N1 N2 DC 3



V1 N2 N1 DC 3

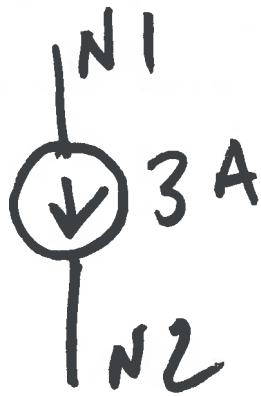

IX

N1

N2

DC

3




IY

N2

N1

DC

3

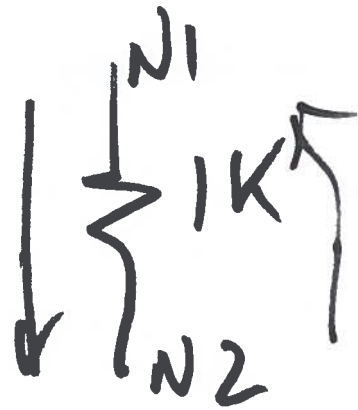

⊙ $R7$

$N1$


$N2$

$1K$

⊙ $R7$

$N2$ $N1$

$1K$

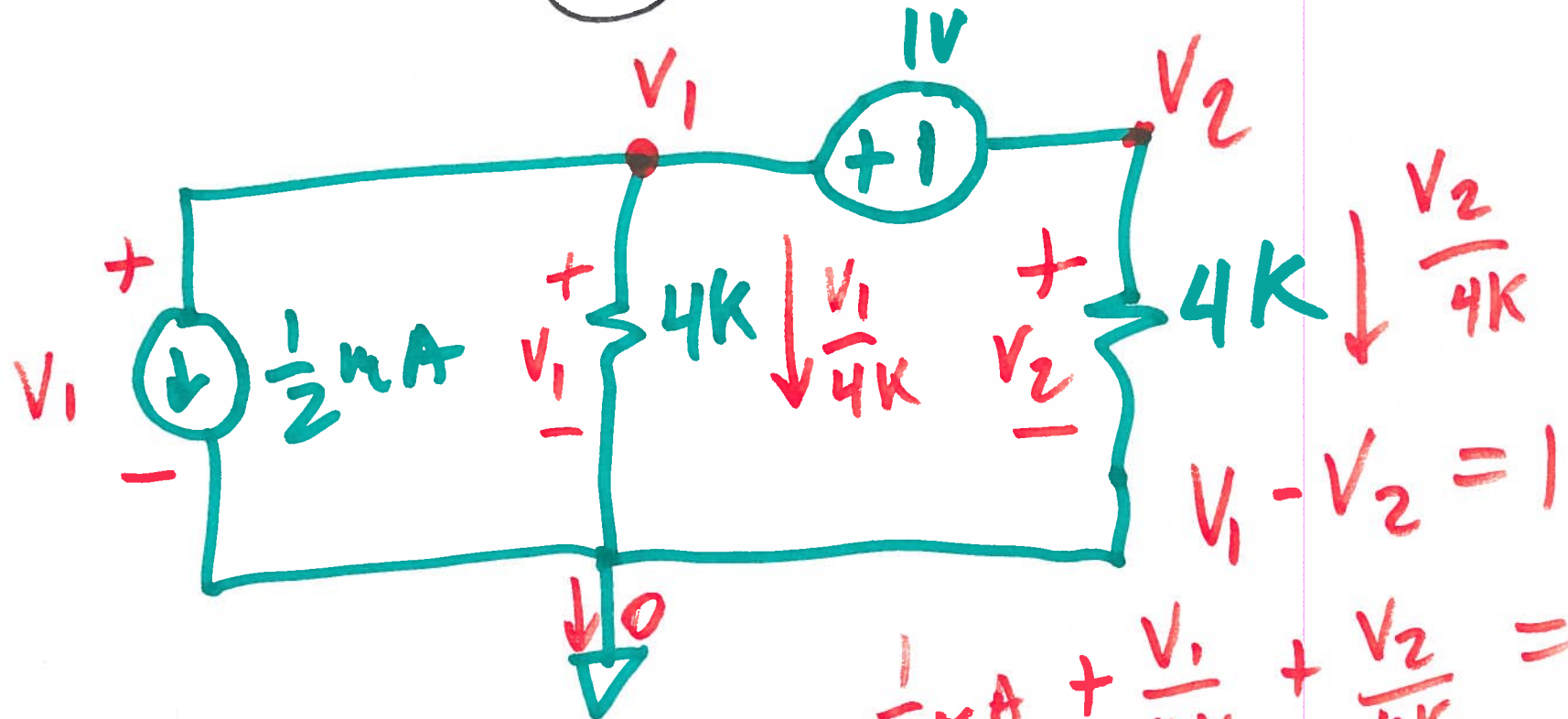

$$V_1 - V_2 = 1$$

$$KCL \quad \frac{1}{2}mA + \frac{V_1}{4K} + \frac{V_2}{4K} = 0$$

$$\frac{3 \text{ mA}}{4} = \frac{3}{4} \mu\text{A} \cdot 10^{-3}$$

$$= \frac{3}{4} \cdot 10^{-3}$$

$$\frac{1}{10^3} = 10^{-3}$$

$$\frac{V_2}{2\text{K}} = \frac{3 \text{ mA}}{4}$$

$$4V_2 = -2\text{K} \cdot 3 \text{ mA}$$

$V_1 = 1 + V_2$
 $4\text{K} \left(\frac{1}{2} \text{ mA} + \frac{1+V_2}{4\text{K}} + \frac{V_2}{4\text{K}} \right) = 0$

$$\frac{1 \text{ mA}}{2} + \frac{1+V_2}{4\text{K}} + \frac{V_2}{4\text{K}}$$

$$\frac{1 \text{ mA}}{2} + \frac{1}{4} \text{ mA} + \frac{V_2}{4\text{K}} + \frac{V_2}{4\text{K}} = 0$$


$$\frac{3}{4} \text{ mA} + \frac{V_2}{2\text{K}} = 0$$

$$\frac{(5+x)}{(3+x)} = \frac{7a}{x}$$

$$\frac{x(5+x)}{(3+x)} = a$$

Voltage divider

Attenuator

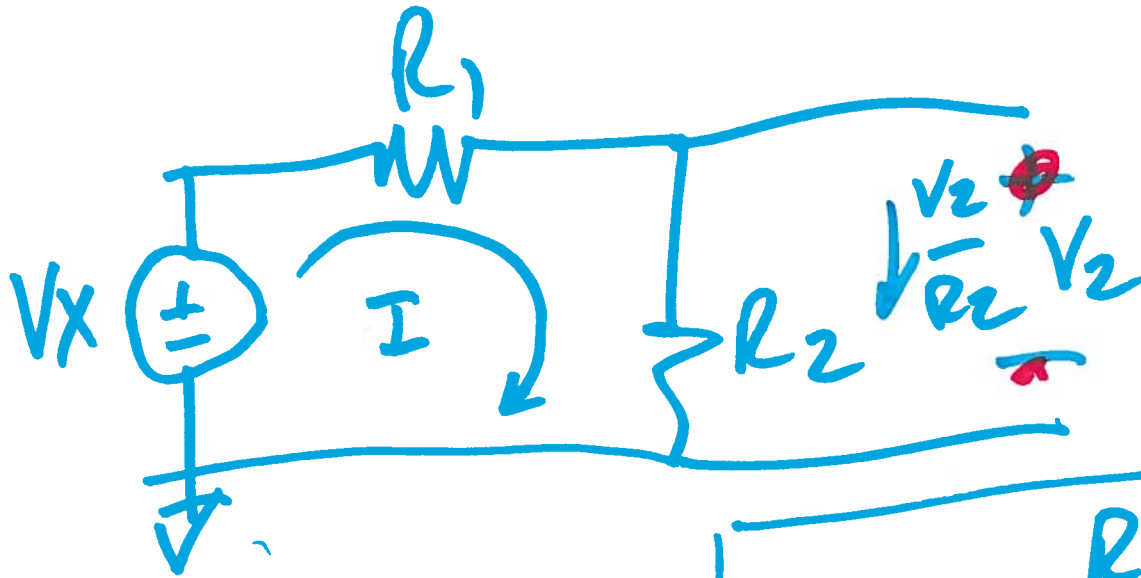


$$I = \frac{V_x}{R_1 + R_2} = \frac{V_2}{R_2}$$

$$V_2 = \frac{R_2}{R_1 + R_2} \cdot V_x$$

Memorize

$$V_2 = I \cdot R_2$$

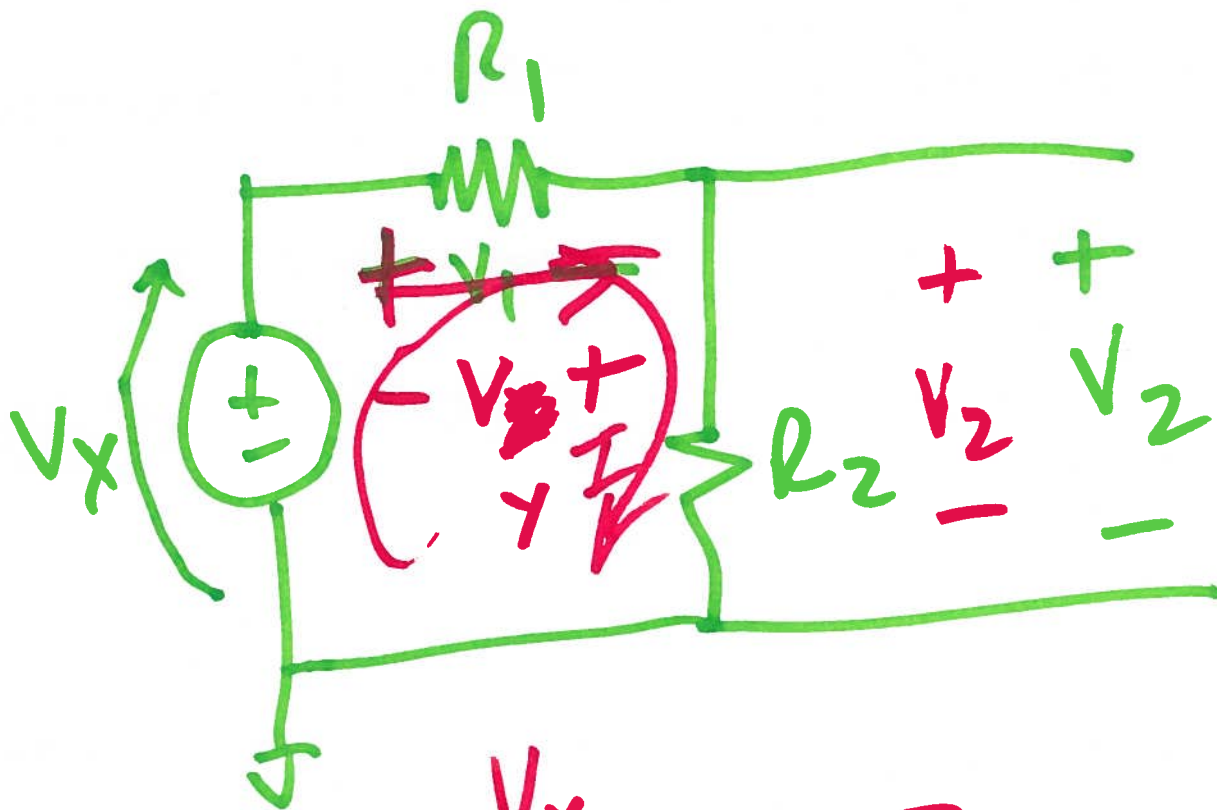

KVL

$$V_x - V_1 - V_2 = 0$$

$$V_x + V_y - V_2 = 0$$


$$V_1 = -V_y$$

$$\frac{V_x}{R_1 + R_2} = I$$


$$V_1 = I \cdot R_1$$
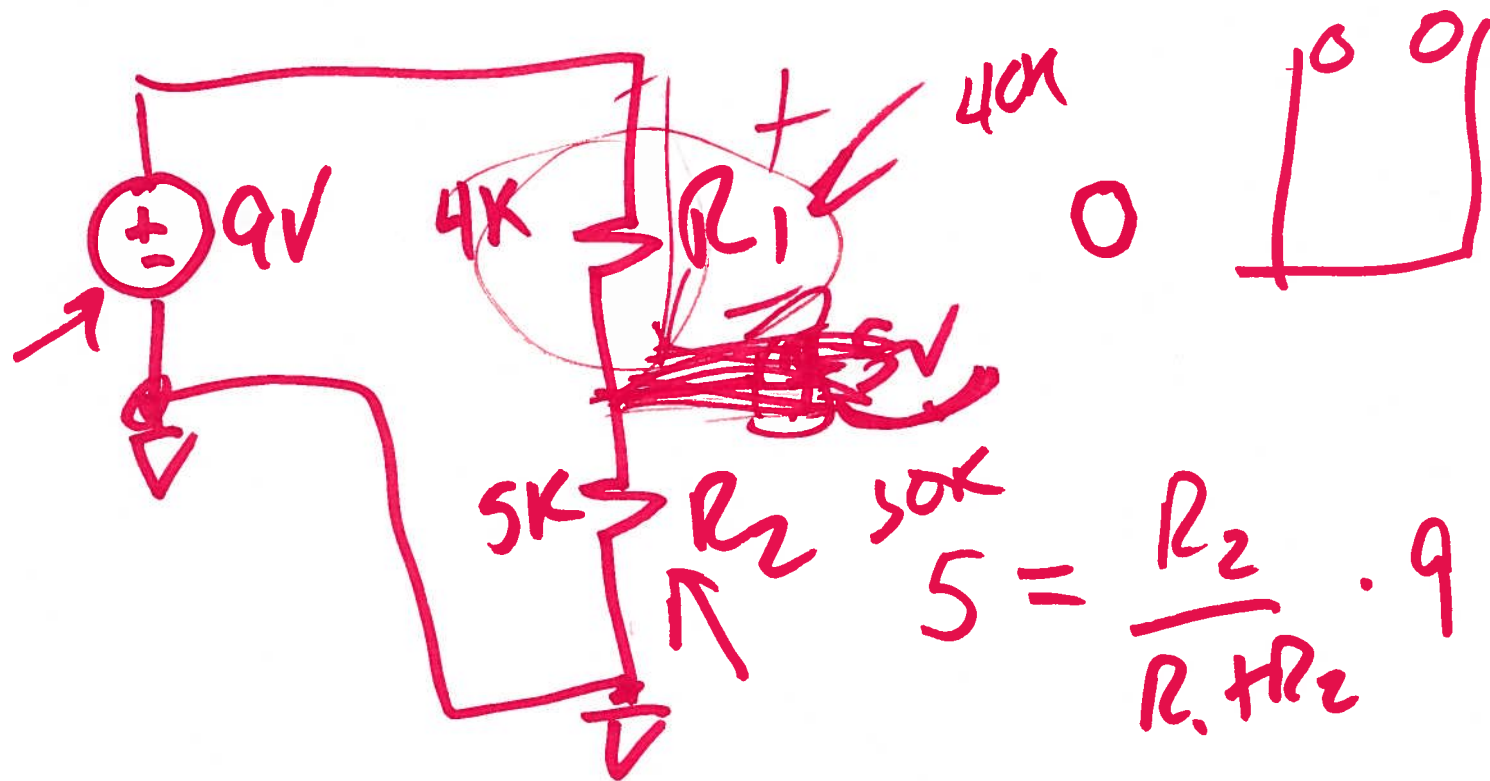
$$V_1 = V_x \cdot \frac{R_1}{R_1 + R_2}$$






$$5 = \frac{R_2}{R_1 + R_2} \cdot 9$$

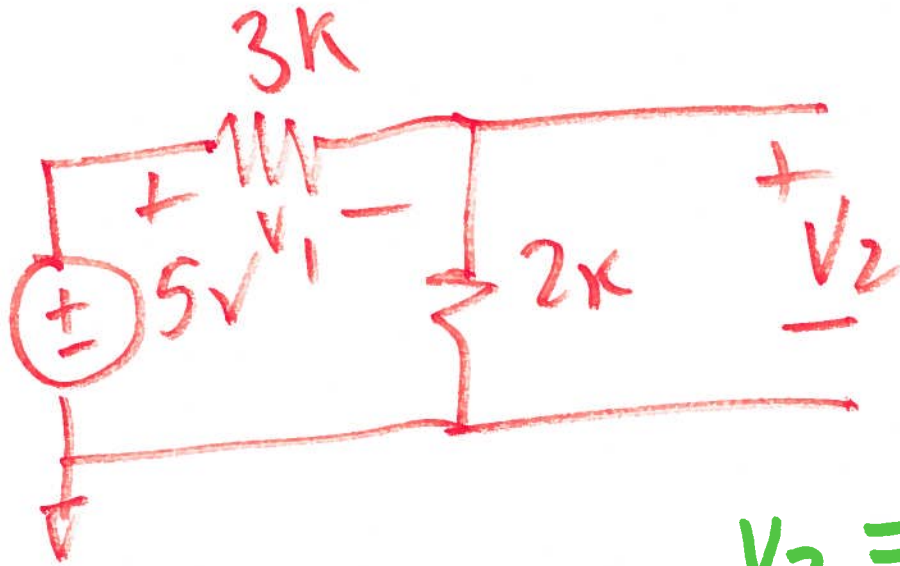


$$V_2 = \frac{2k}{2k + 3k} \cdot 5V = 2V$$
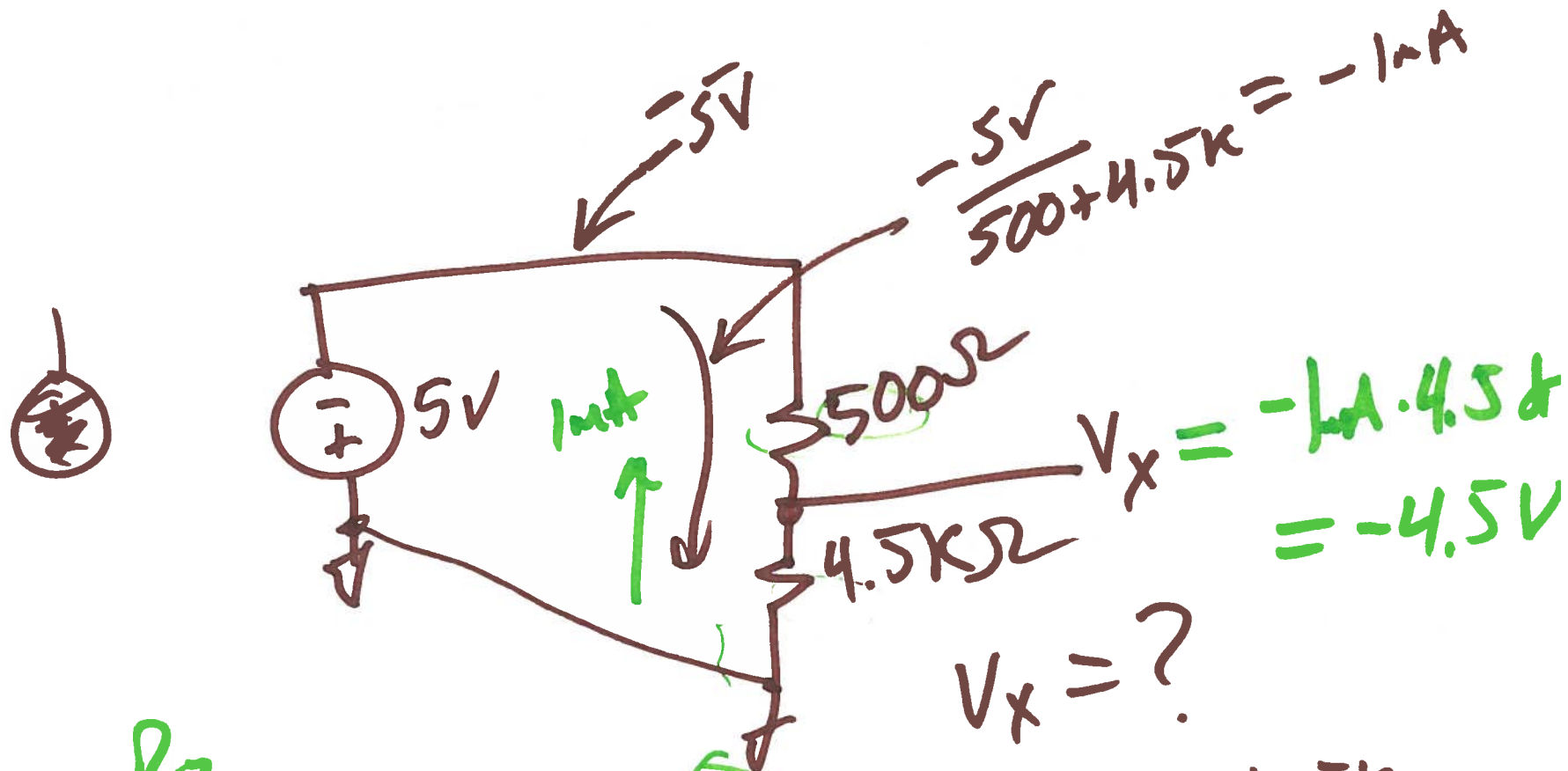
$$V_1 = \frac{3k}{2k + 3k} \cdot 5V = 3V$$



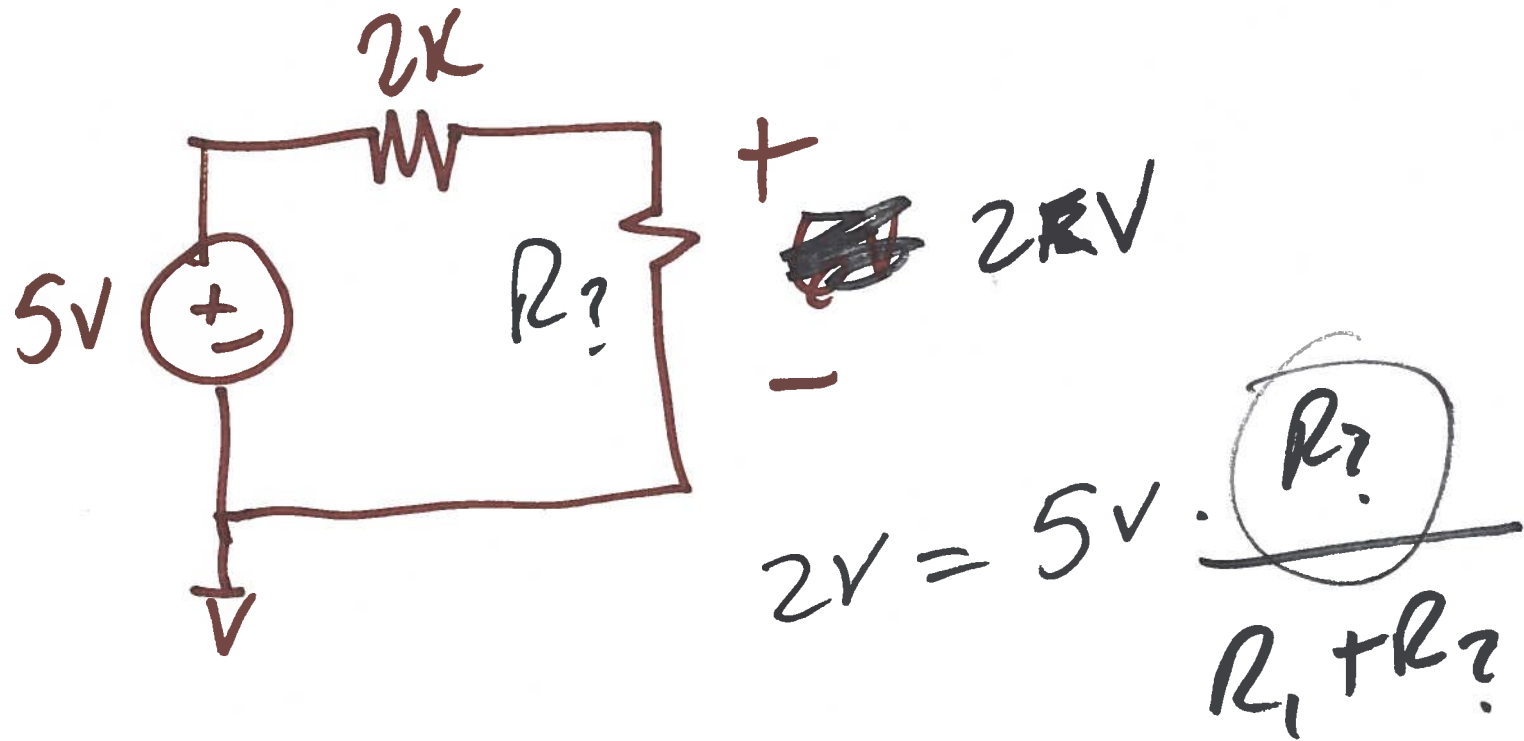
V_B
 R_2
 R_1
 V_A
 $V_A = V_B \frac{R_1}{R_1 + R_2}$
 $V_x = -5V \cdot \frac{4.5k}{4.5k + 500\Omega} = -4.5V$




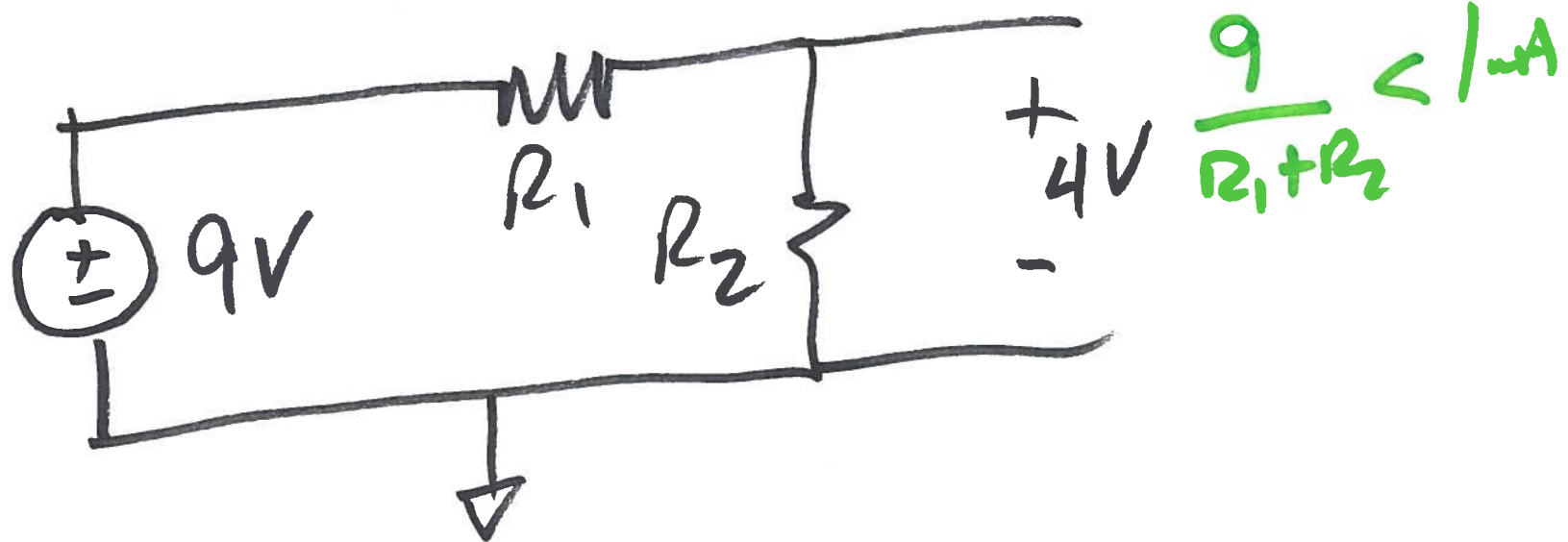11)


Design_{9V}
The battery must supply
 $< 1\mu A$ ←

Design A circuit to
generate 4V. $4 = 9 \cdot \frac{R_2}{R_1 + R_2}$




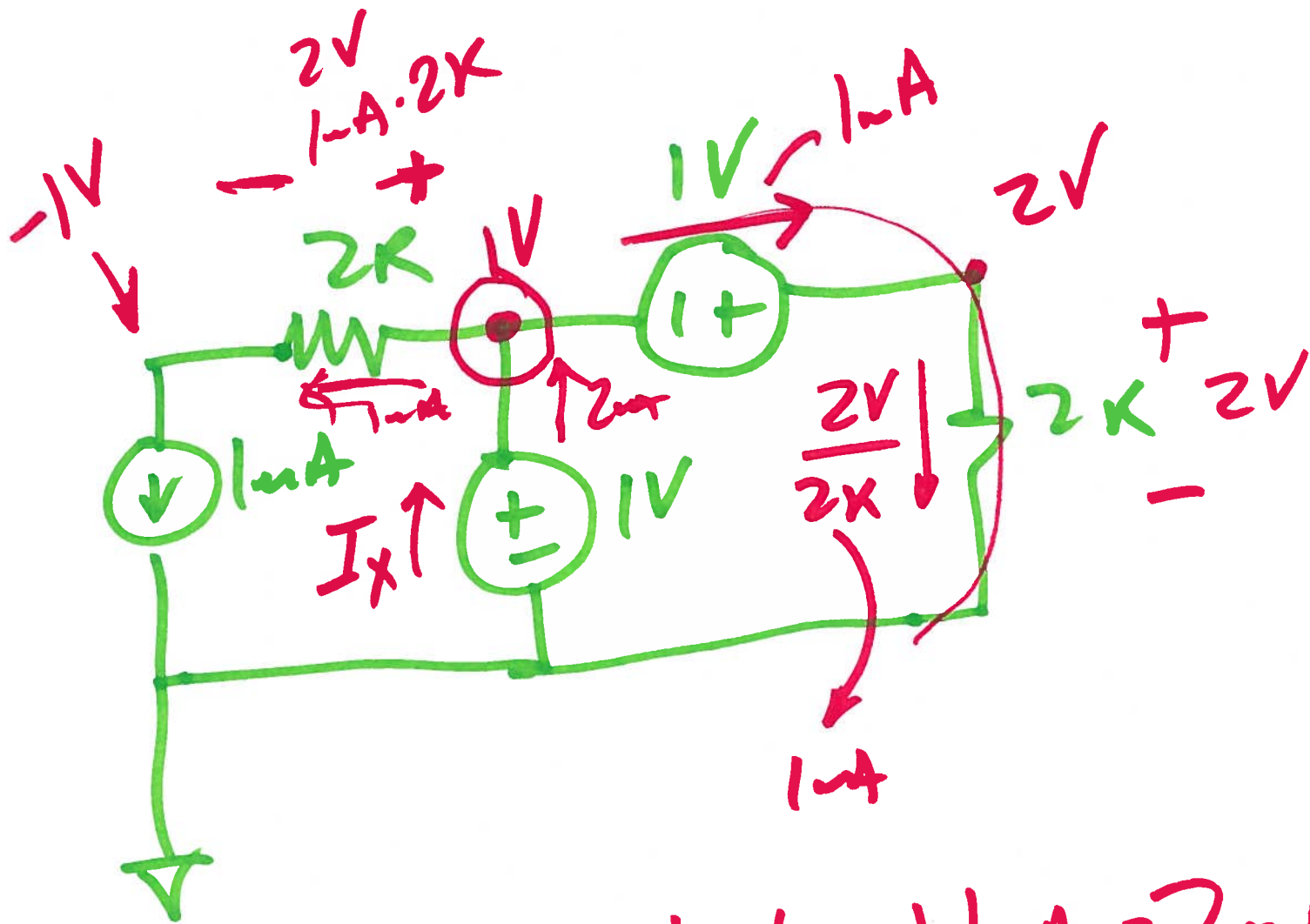
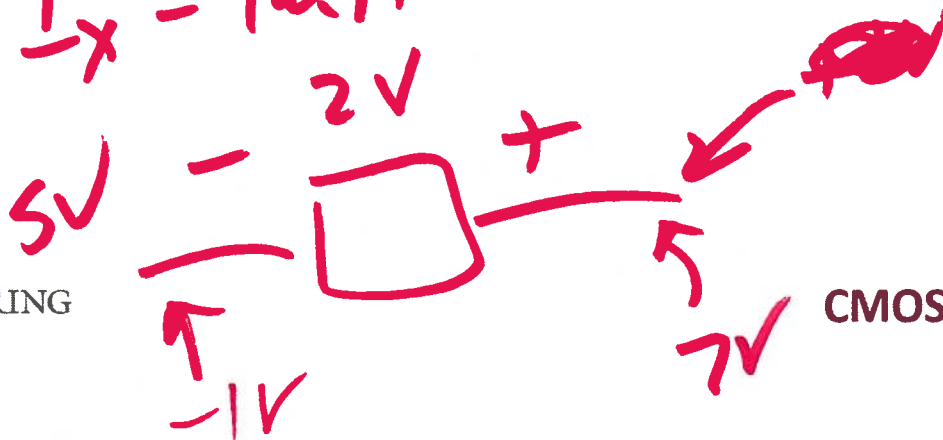
$$I_x = 1\text{mA} + 1\text{mA} = 2\text{mA}$$



Current divider

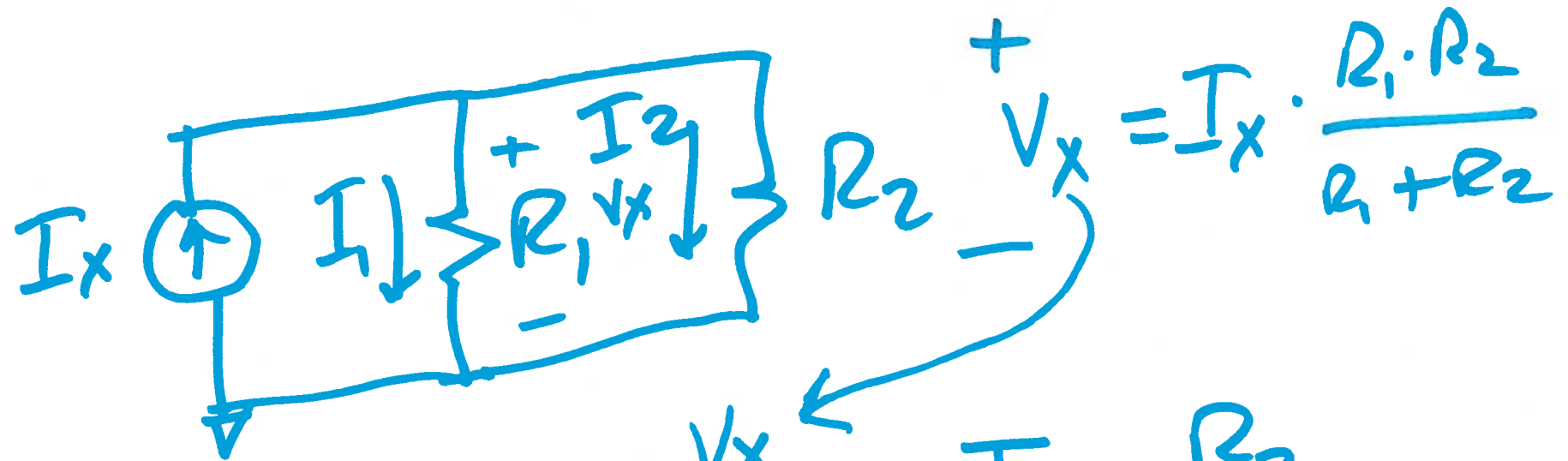


$$I_1 = \frac{V_x}{R_1} = I_x \cdot \frac{R_2}{R_1 + R_2}$$

current through R_1

$$I_2 = I_x \cdot \frac{R_1}{R_1 + R_2}$$
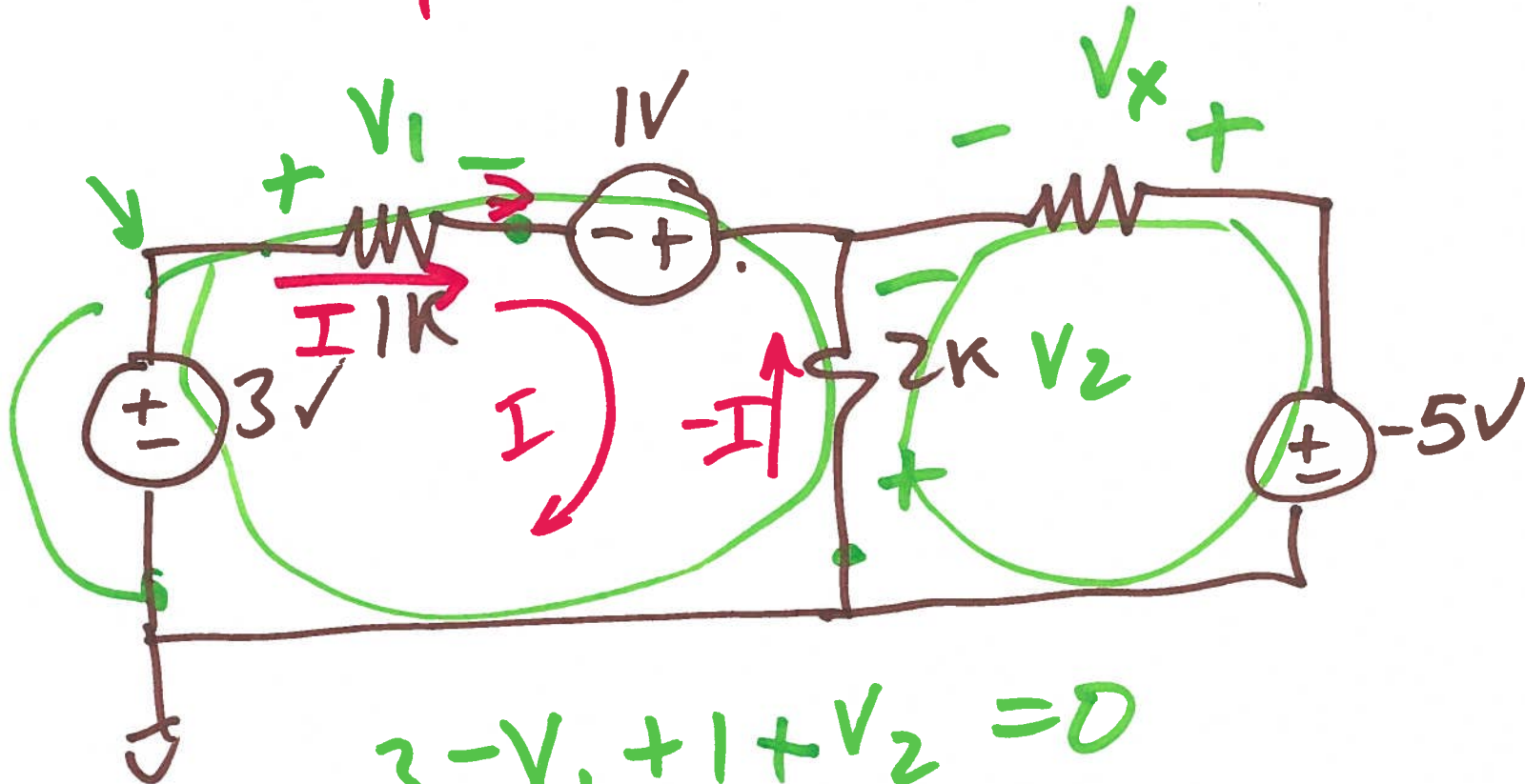
$$V_1 = I \cdot 1K \quad V_2 = -I \cdot 2K$$



$$3 - V_1 + 1 + V_2 = 0$$

$$-V_2 + V_x - (-5) = 0$$