


Lecture 4

$$I = \frac{V}{R}$$

@

EE 220



Circuits I

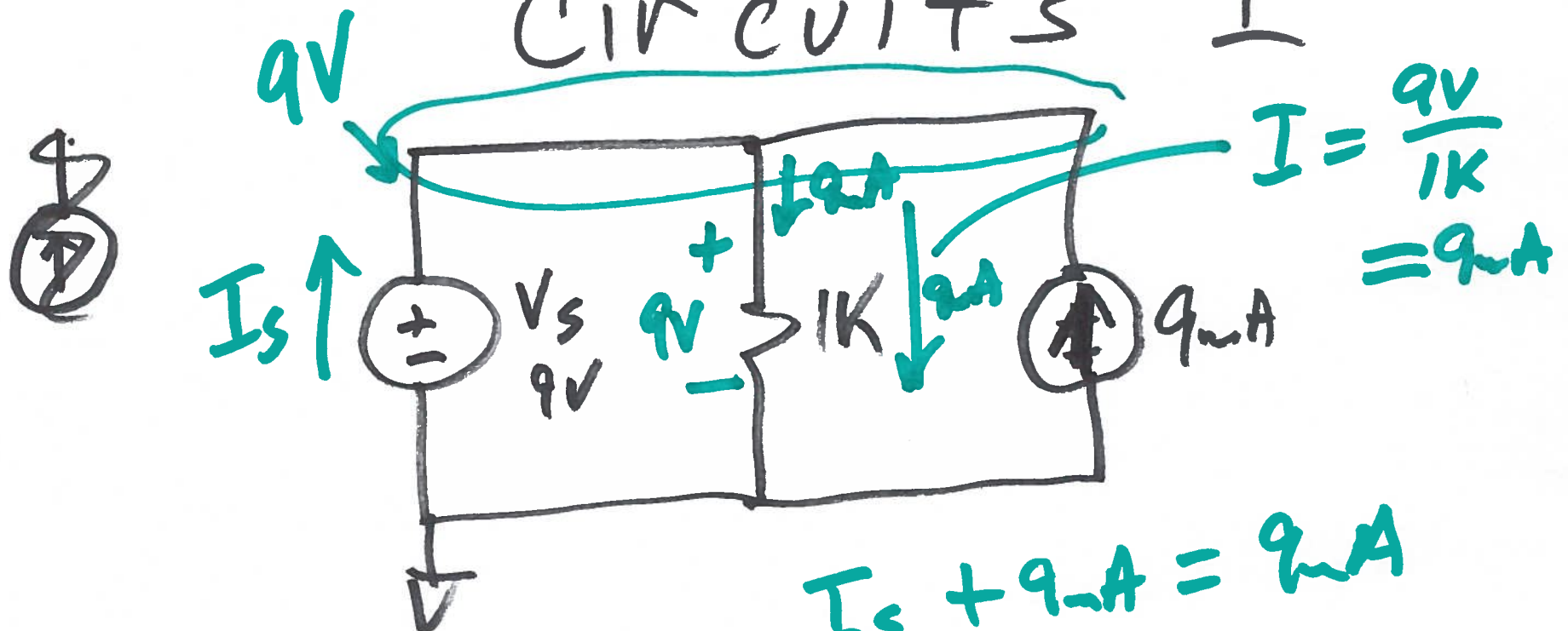

$$I_s + 9mA = 9mA$$


$$I_s = 0$$

1)

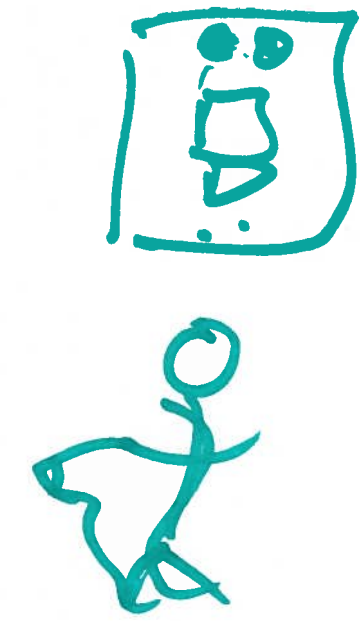
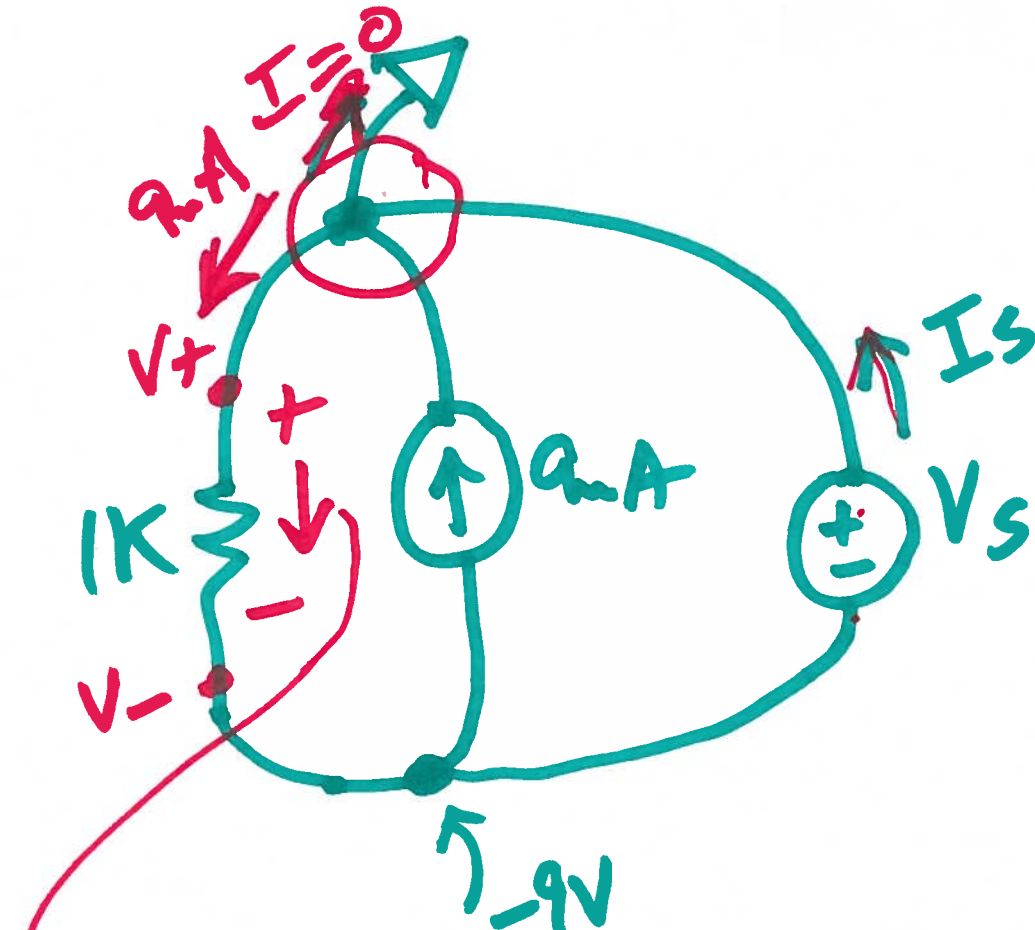


$$I = \frac{V_+ - V_-}{1K} = \frac{0 - (-9)}{1K} = 9mA$$

$$0 + 9mA = 9mA + I_s$$

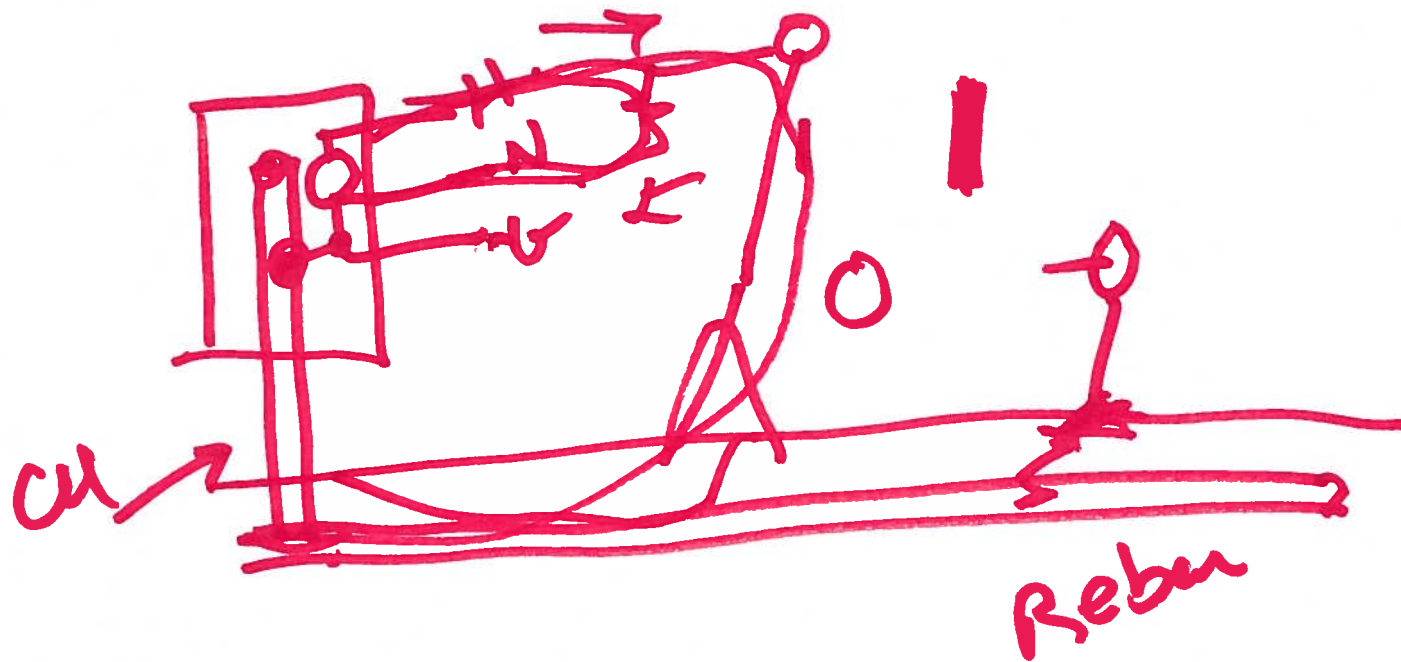



3)

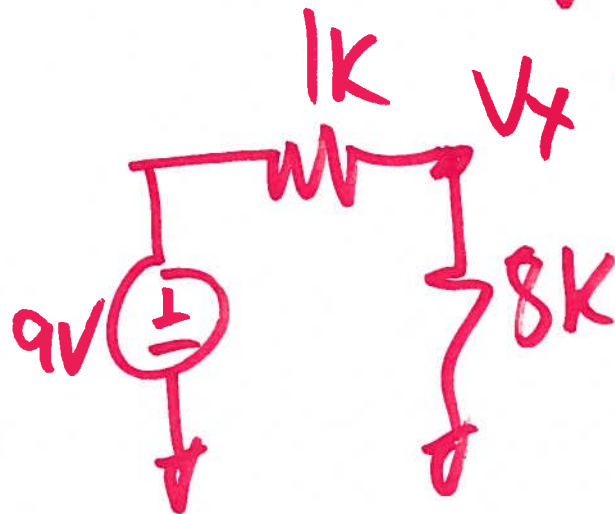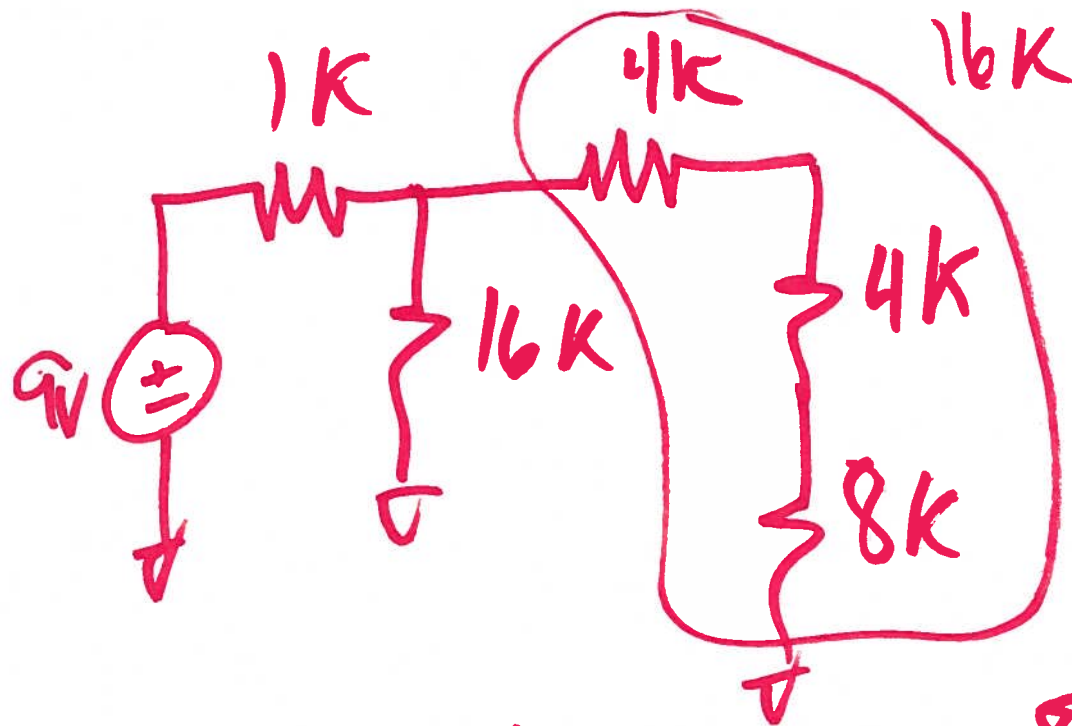


$$V_x = \frac{8k}{1k + 8k} \cdot 9V = \underline{\underline{8V}}$$

Show your work for credit!

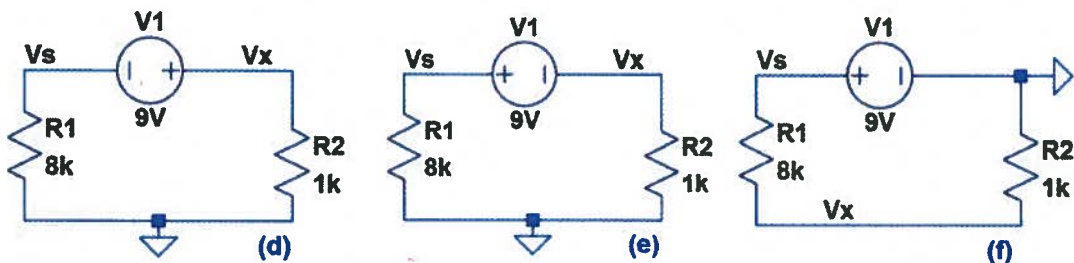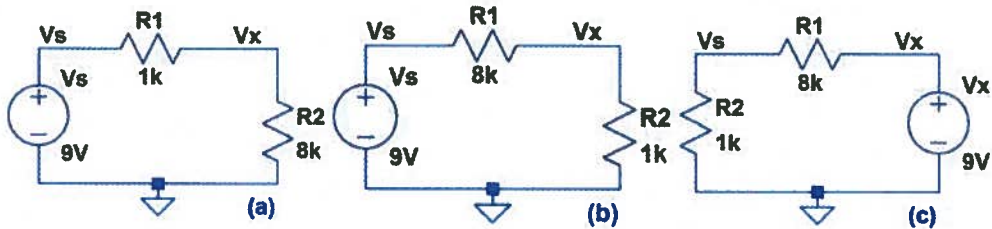
- Find the voltages V_x and V_s in each of the following circuits. Verify your hand calculations using LTspice. (6 points)



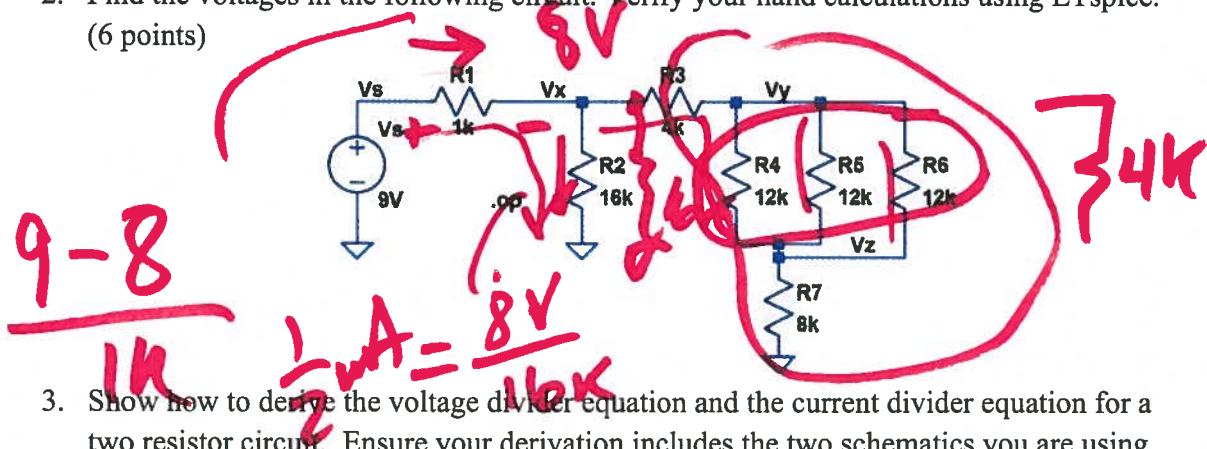
- Find the voltages in the following circuit. Verify your hand calculations using LTspice. (6 points)



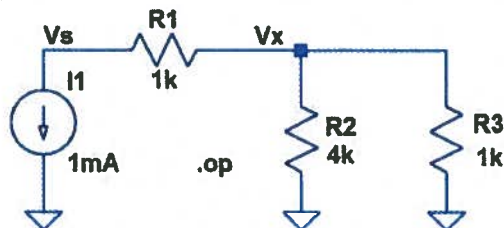
- Show how to derive the voltage divider equation and the current divider equation for a two resistor circuit. Ensure your derivation includes the two schematics you are using. Provide an example for each derivation. (4 points)
- Calculate V_s , V_x , and the current that flows in R_2 and R_3 . Verify your hand calculations using LTspice. (4 points)



5)

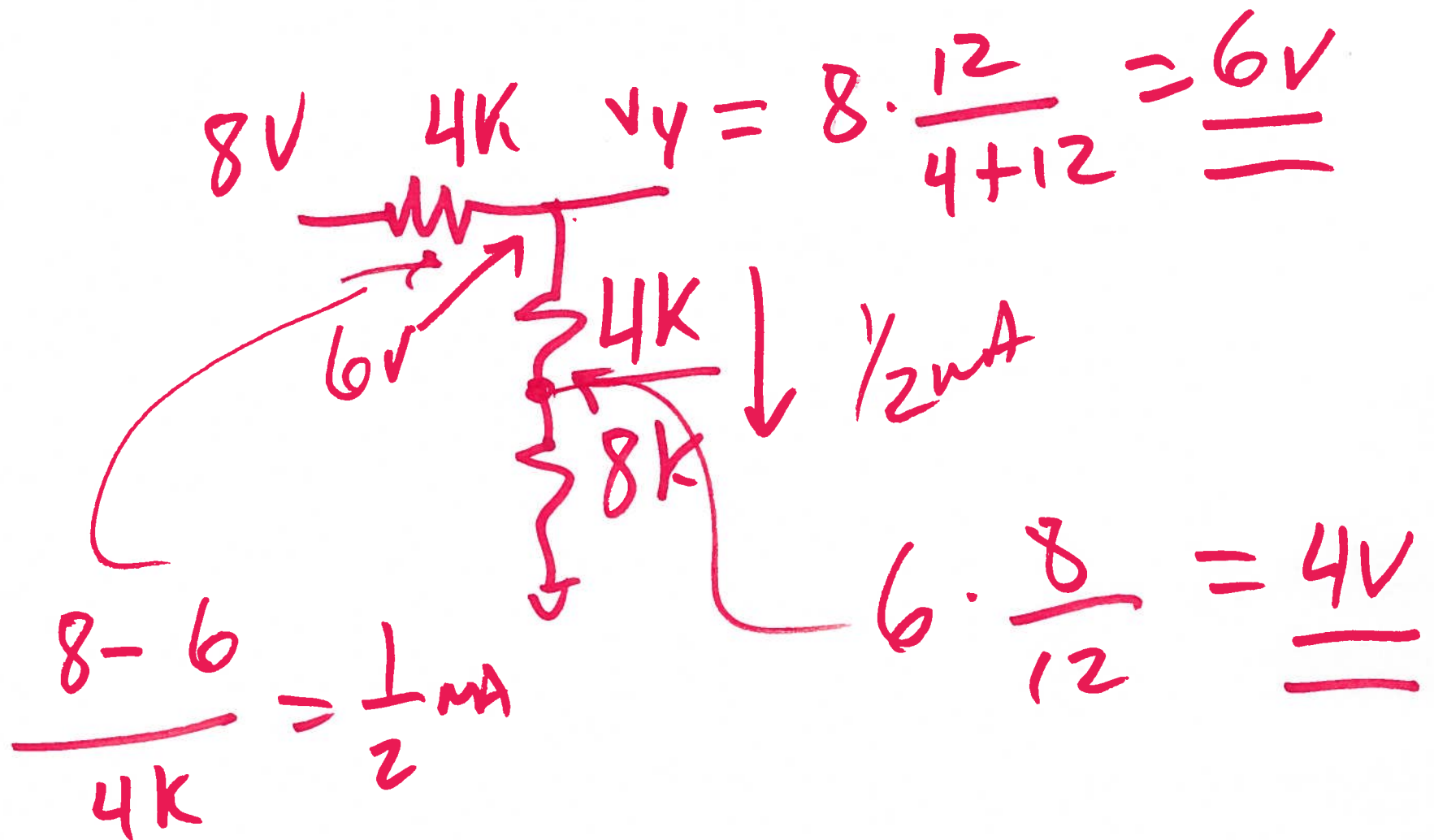

6)

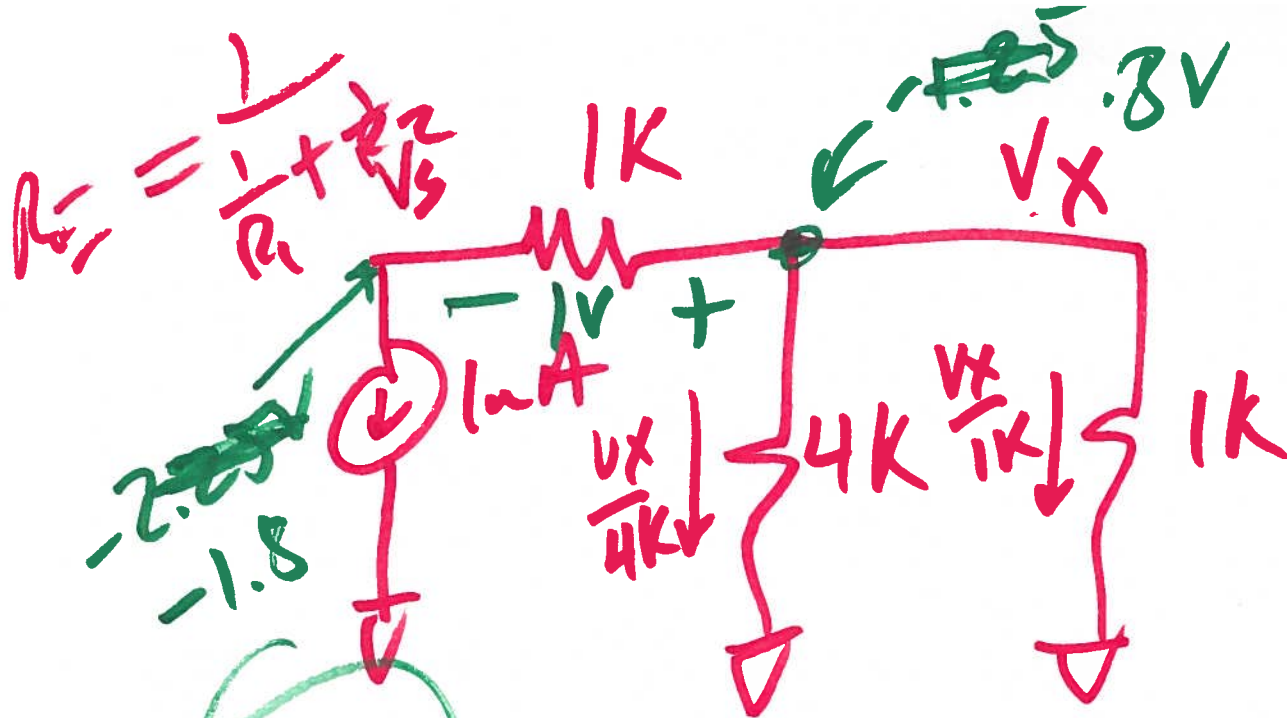

$$\frac{1}{R_E} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$1k \parallel 4k = \frac{1k \cdot 4k}{1k + 4k} = .8k$$

$$\frac{1}{1k + 4k} = \frac{1}{1k \parallel 4k} + \frac{V_x}{4k} + \frac{V_x}{1k} = 0$$


$$\frac{1}{1k + 4k} = -\frac{1}{.8k} = -\frac{10}{8} = -1\frac{2}{8} = -1\frac{1}{4} - 1mA$$

$$V_x = \frac{-1mA}{\left(\frac{1}{4k} + \frac{1}{1k}\right)} = \frac{-1mA}{\frac{1}{.4k} + \frac{1}{1k}}$$



$$V_x = \frac{-1mA \cdot \frac{1k \cdot 4k}{1k + 4k}}{\frac{1}{4k} + \frac{1}{1k}} = \frac{-1mA \cdot .4k}{\frac{1}{4k} + \frac{1}{1k}}$$


~>

Superposition

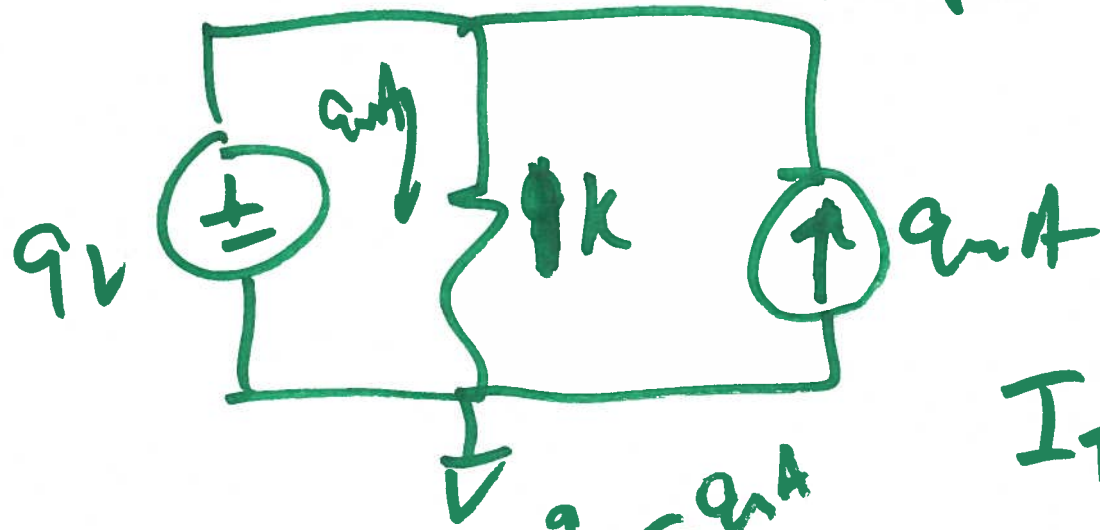

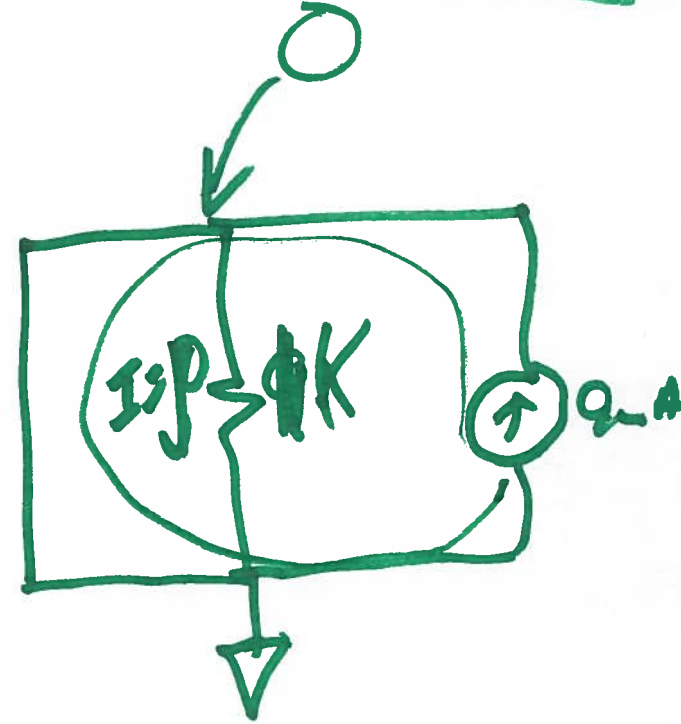
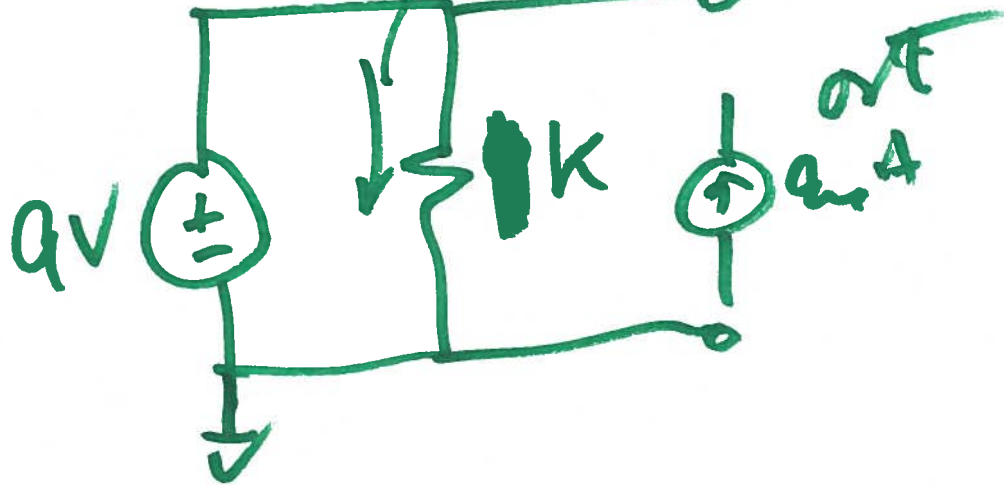
$$I_T = q.A + 0 = \underline{\underline{q.A}}$$




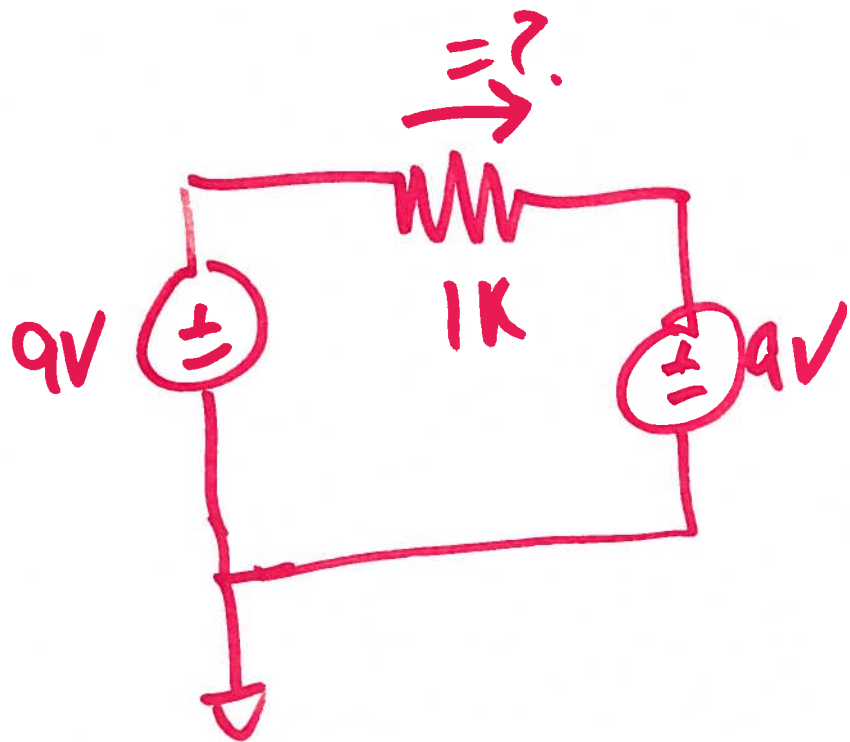

$$I_T = 9\mu A + (-9\mu A) = 0$$


$$I = \frac{0 - 9}{1K} = -9\mu A$$

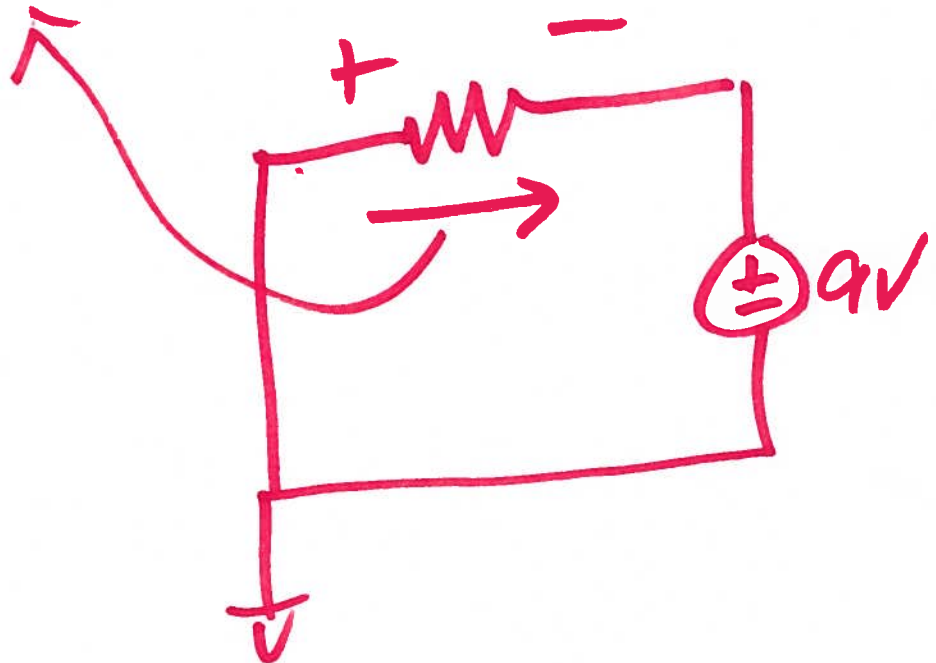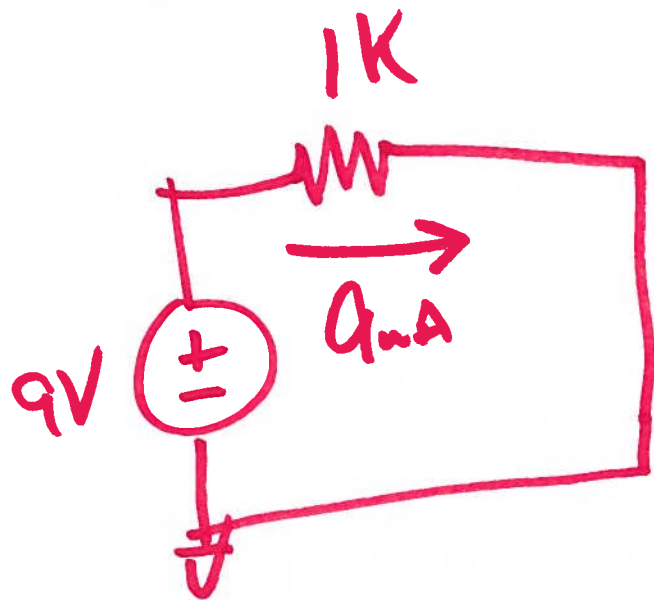


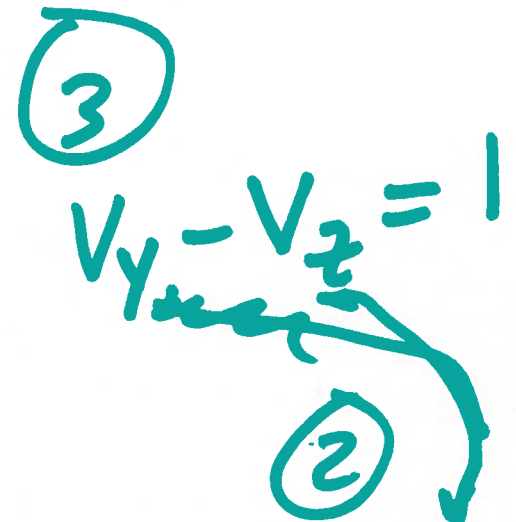


$$\frac{V_y - V_x}{1K} = \frac{0 - V_z}{1K}$$
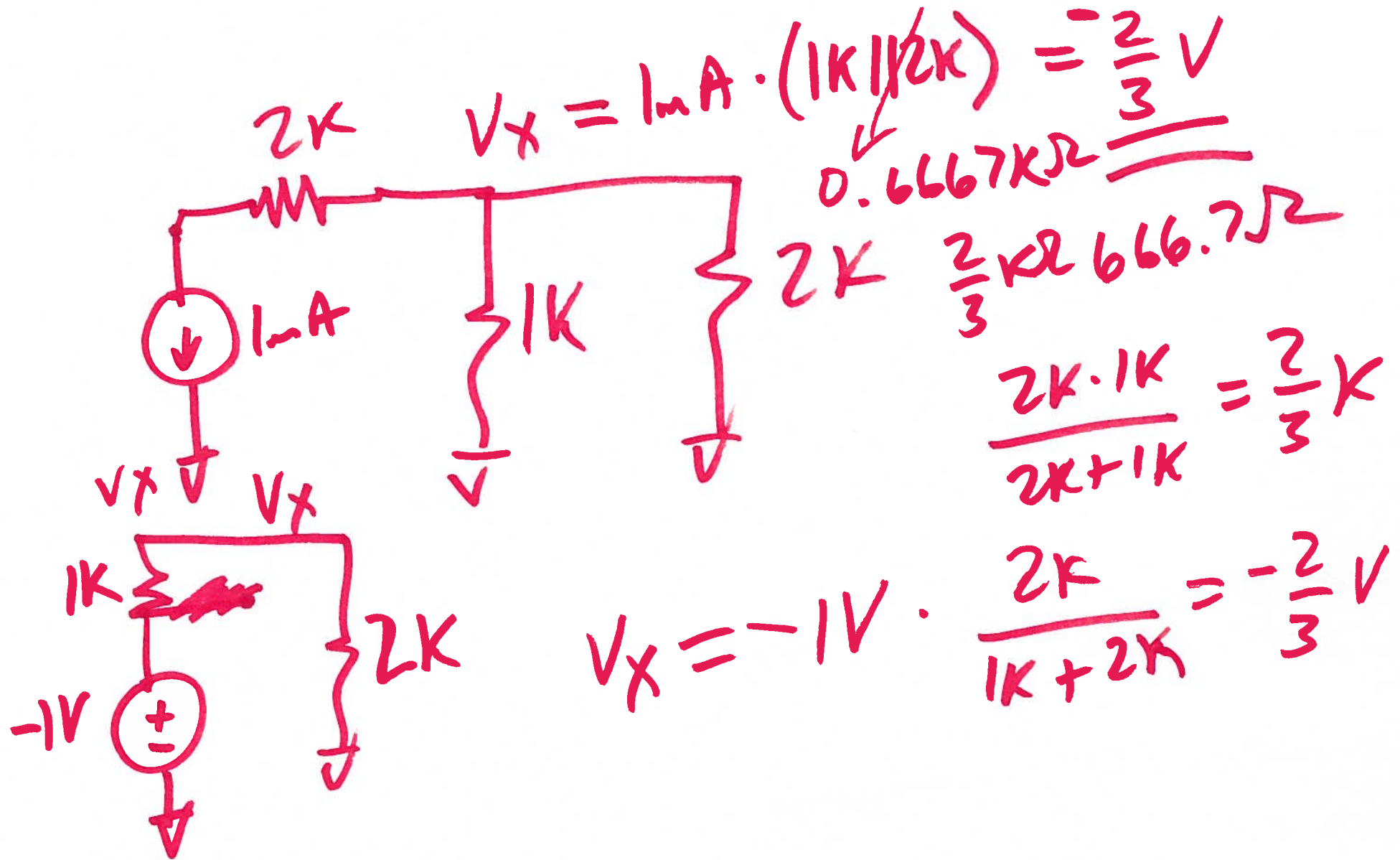
$$1\text{mA} + \frac{V_x + 1}{1\text{K}} = \frac{V_y - V_x}{1\text{K}}$$



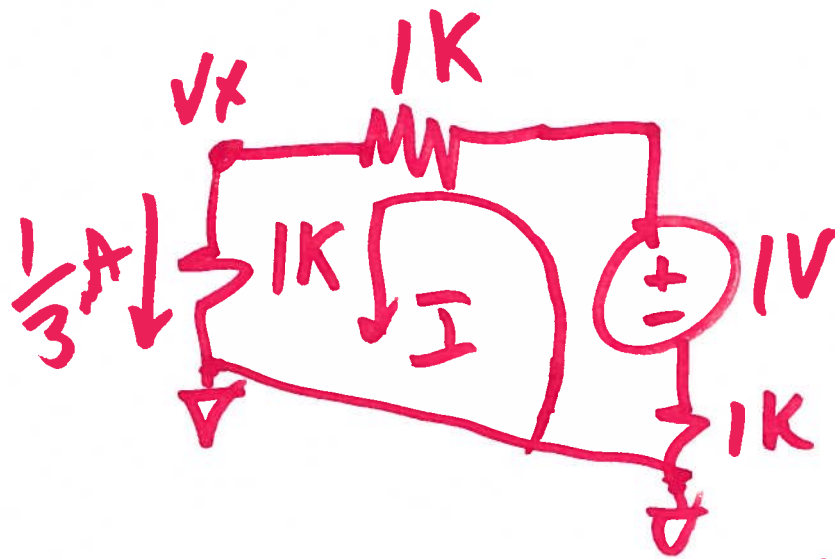



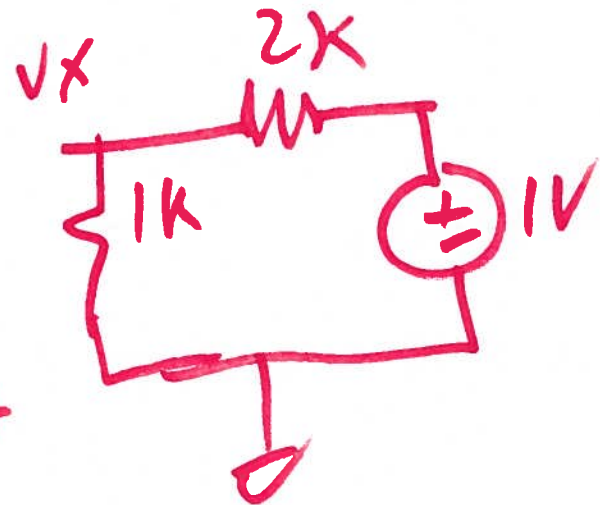
$$V_x = 1V \cdot \frac{1K}{2K+1K} = \underline{\underline{\frac{1}{3}V}}$$



$$\frac{1V}{3K} = I = \frac{1}{3}mA$$

$$V_x = \frac{1}{3}mA \cdot 1K = \underline{\underline{\frac{1}{3}V}}$$
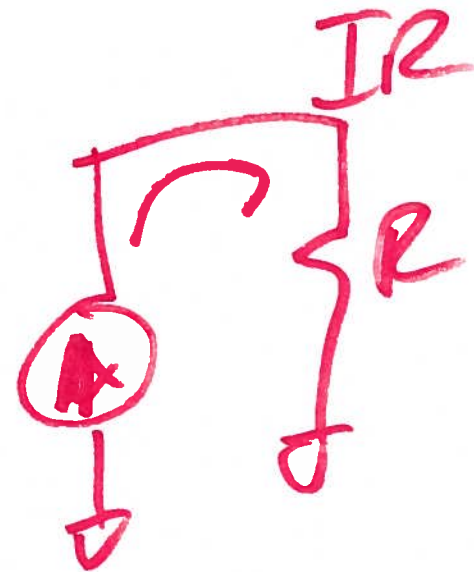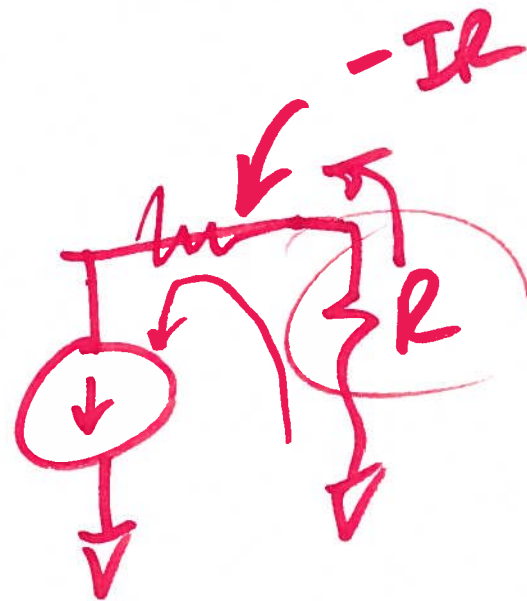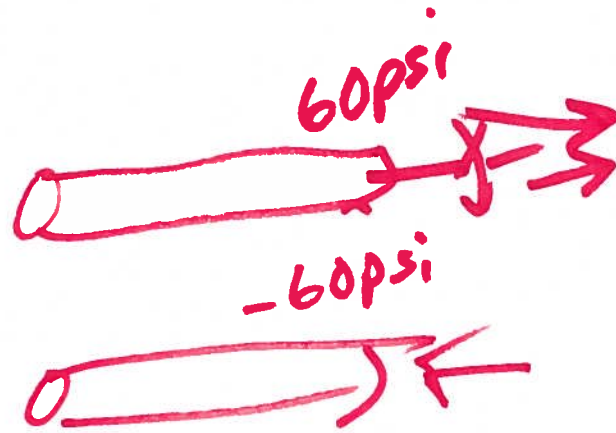
$$-\frac{2}{3} - \frac{2}{3} + \frac{1}{3} = \underline{\underline{-1V}}$$



Power.

Resistor

$$P = I \cdot V$$

power

$$I = \frac{V_s}{R_1 + R_2}$$

$$V_{R_2} = \frac{R_2}{R_1 + R_2} V_s$$

$$R_1 = R_2$$

$$\left(\frac{V_s}{R_1 + R_2} \cdot R_2 \right) = P$$

