
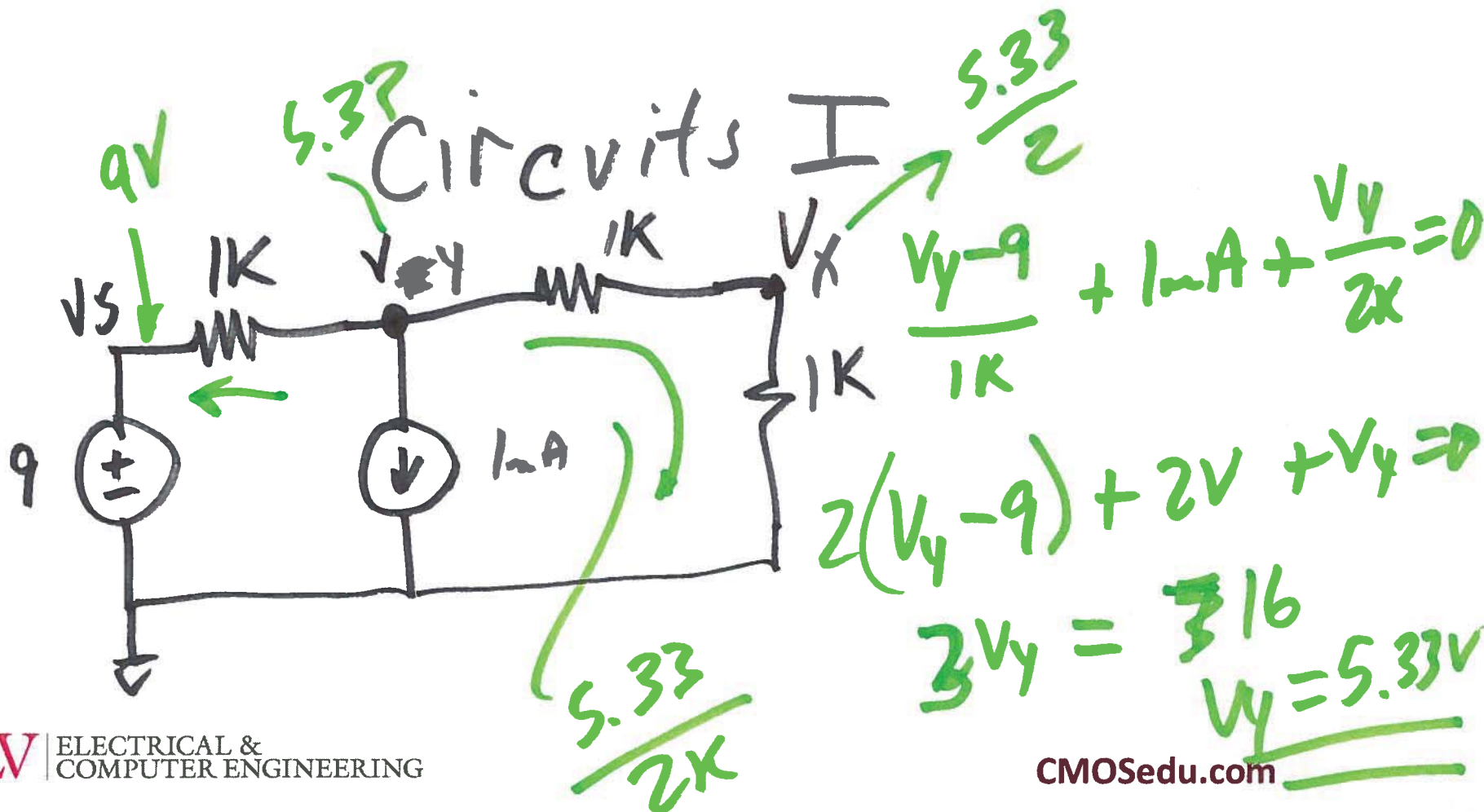


EE 220

Lecture 5

$$V_x = V_y \cdot \frac{1}{2}$$

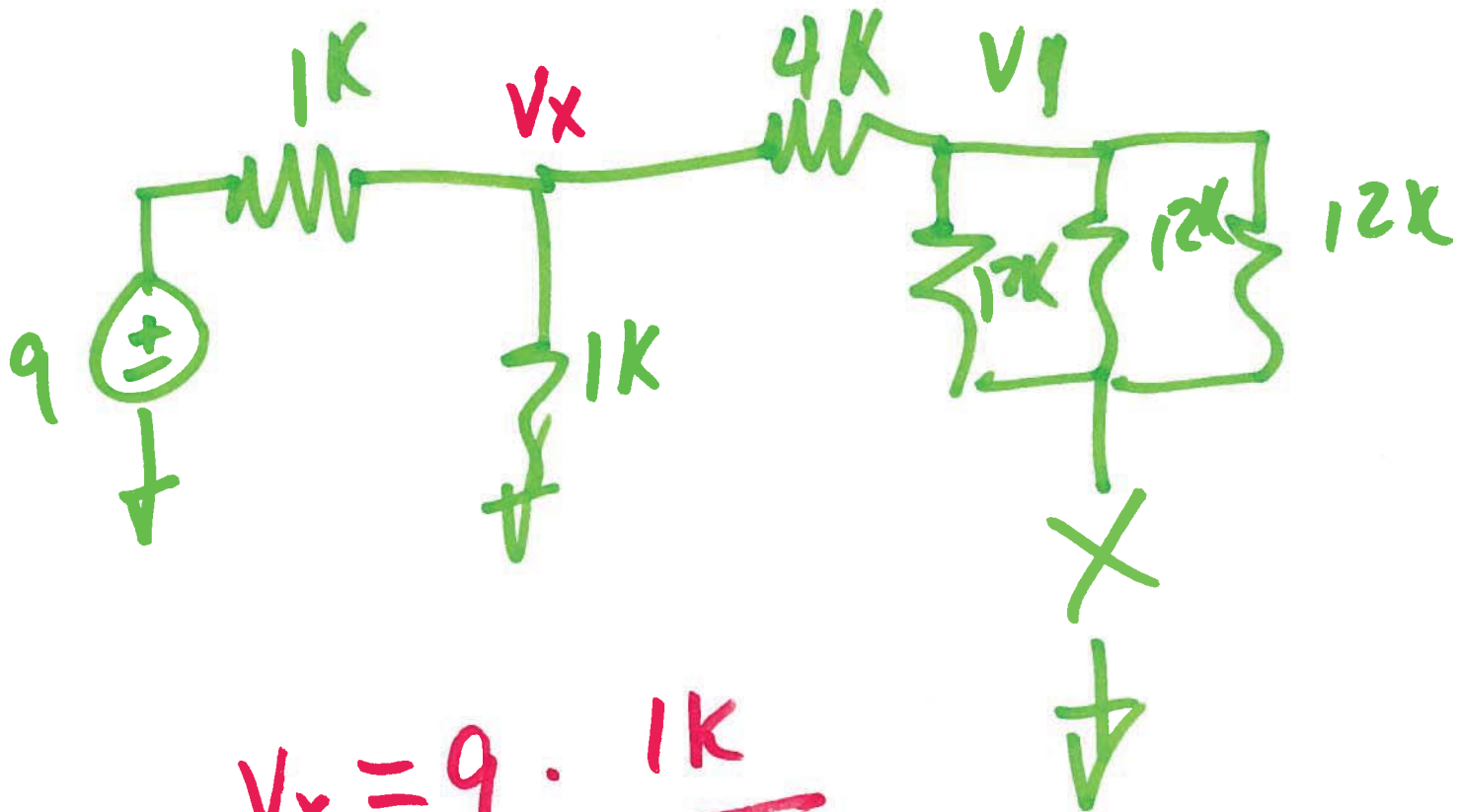





$$V_x = 9 \cdot \frac{1k}{1k + 1k}$$

$$= \underline{\underline{4.5V}}$$

$$\frac{1k \cdot 1k}{1k + 1k}$$

$$\frac{2 \cdot 10^6}{2 \cdot 10^3}$$


$$= 500 \Omega$$

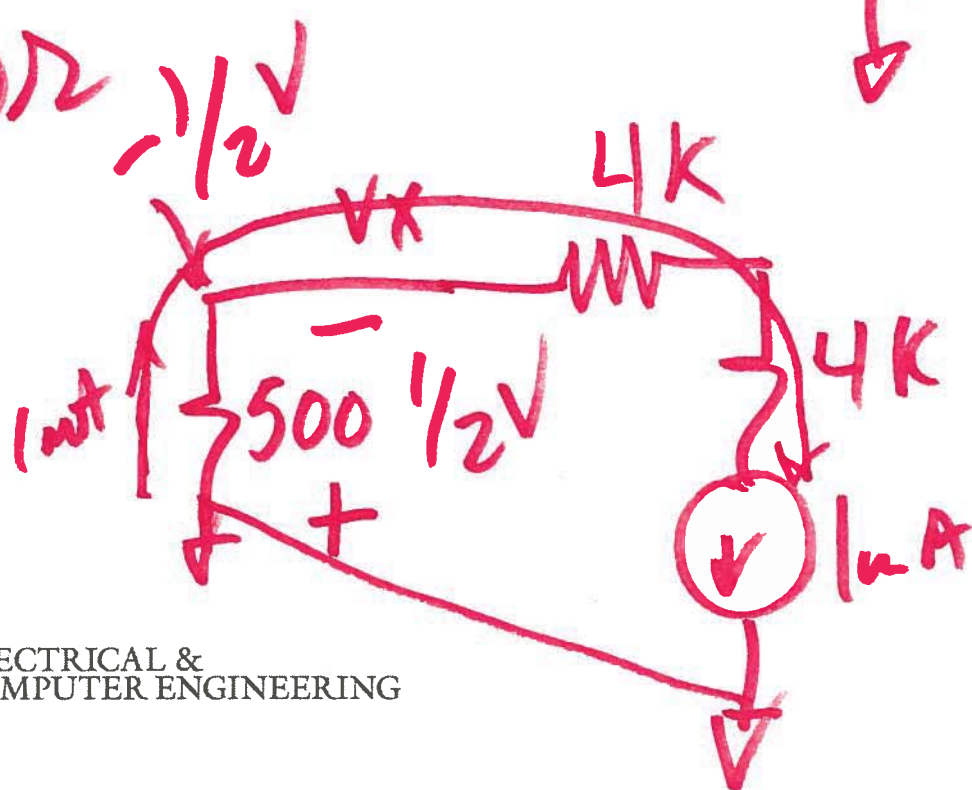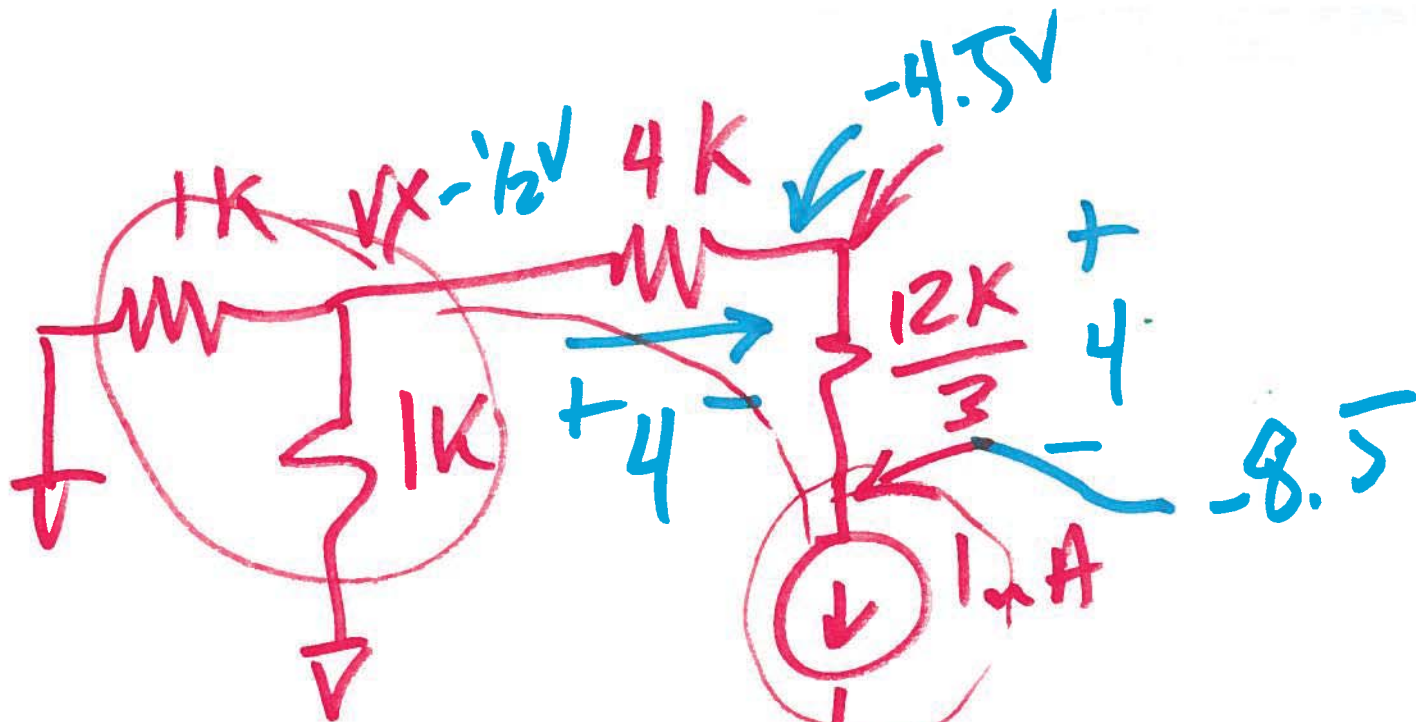

$$\uparrow \downarrow \begin{matrix} + \\ - \end{matrix} v = -I \cdot R$$

$$\downarrow \uparrow \begin{matrix} + \\ - \end{matrix} v = I \cdot R$$

3)

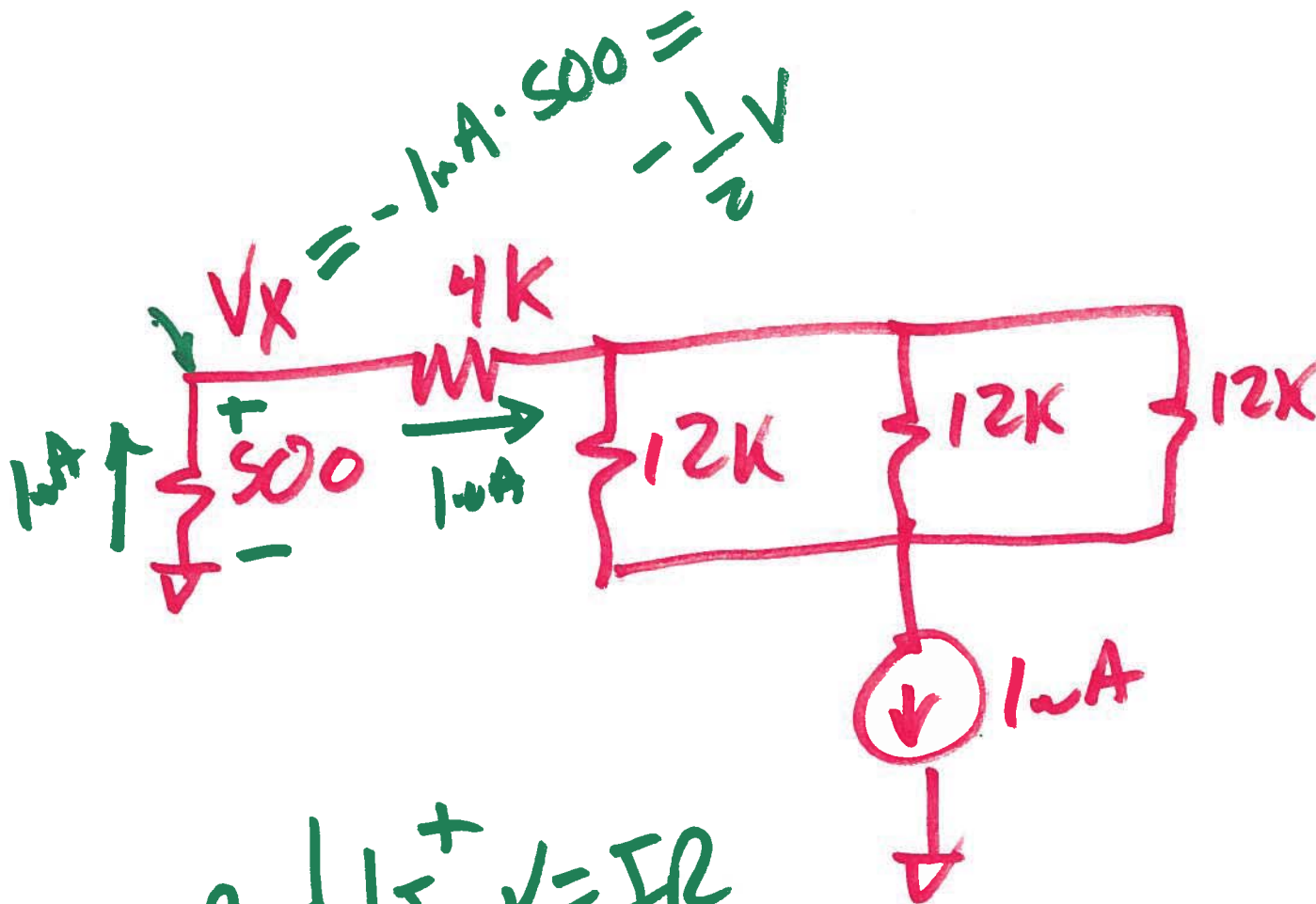

$$R \downarrow I^+ \quad V = IR$$


$$V_2 = 3V$$

$$+ 3 - 0$$

$$V_x = -1\mu A \cdot 500 = -\frac{1}{2}V$$

4)

Mesh Analysis

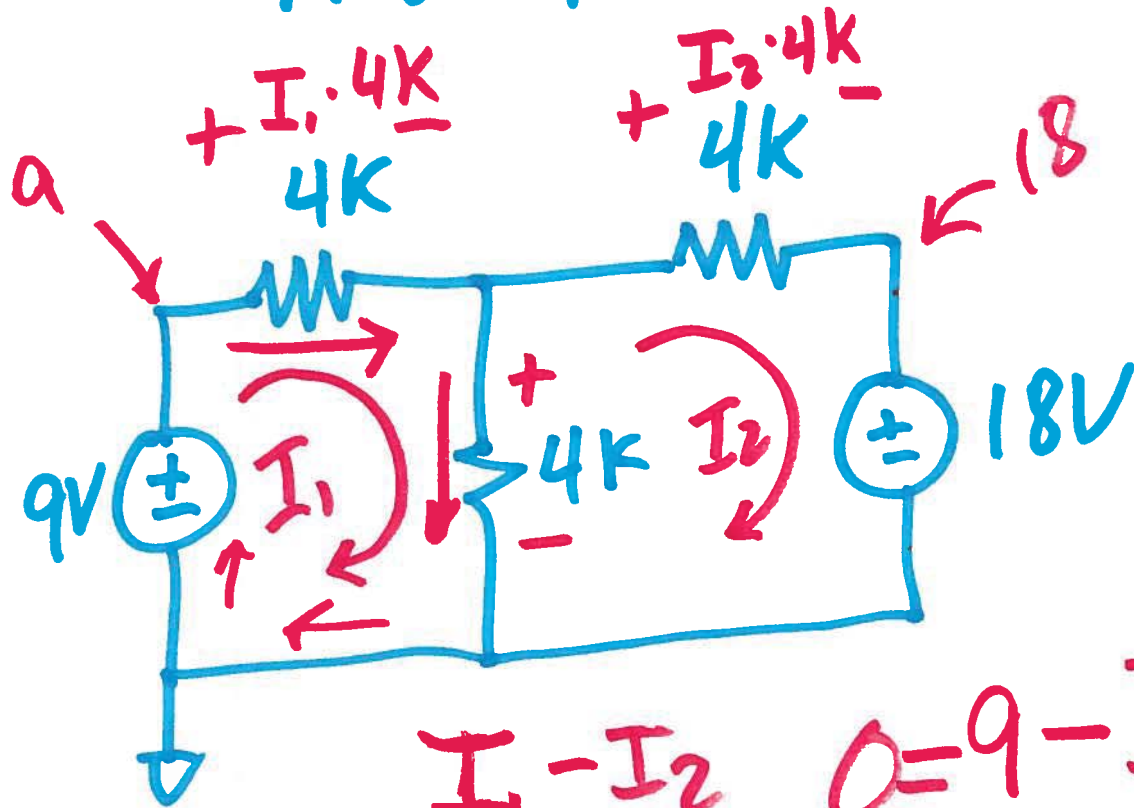

$$I_1 - I_2 \quad 0 = 9 - I_1 \cdot 4k - (I_1 - I_2) \cdot 4k$$

$$I_2 = 2I_1 - \frac{9}{4} \text{ mA}$$

\swarrow
2.25 mA

$$0 = \frac{9}{4} \text{ mA} - 2I_1 + I_2$$

5)

$$I_1 - 2I_2 - \frac{18}{4k} = 0$$

$$I_1 - 2\left(2I_1 - \frac{9}{4} \text{mA}\right) - \frac{18}{4k} = 0$$


$$I_1 - 4I_1 + \cancel{\frac{18}{4}} - \frac{18}{4k} = 0$$


$$-3I_1 = 0$$

$$I_1 = 0$$

$$I_2 = 2I_1 - 2.25 \text{mA}$$


$$I_2 = -2.25 \text{mA}$$

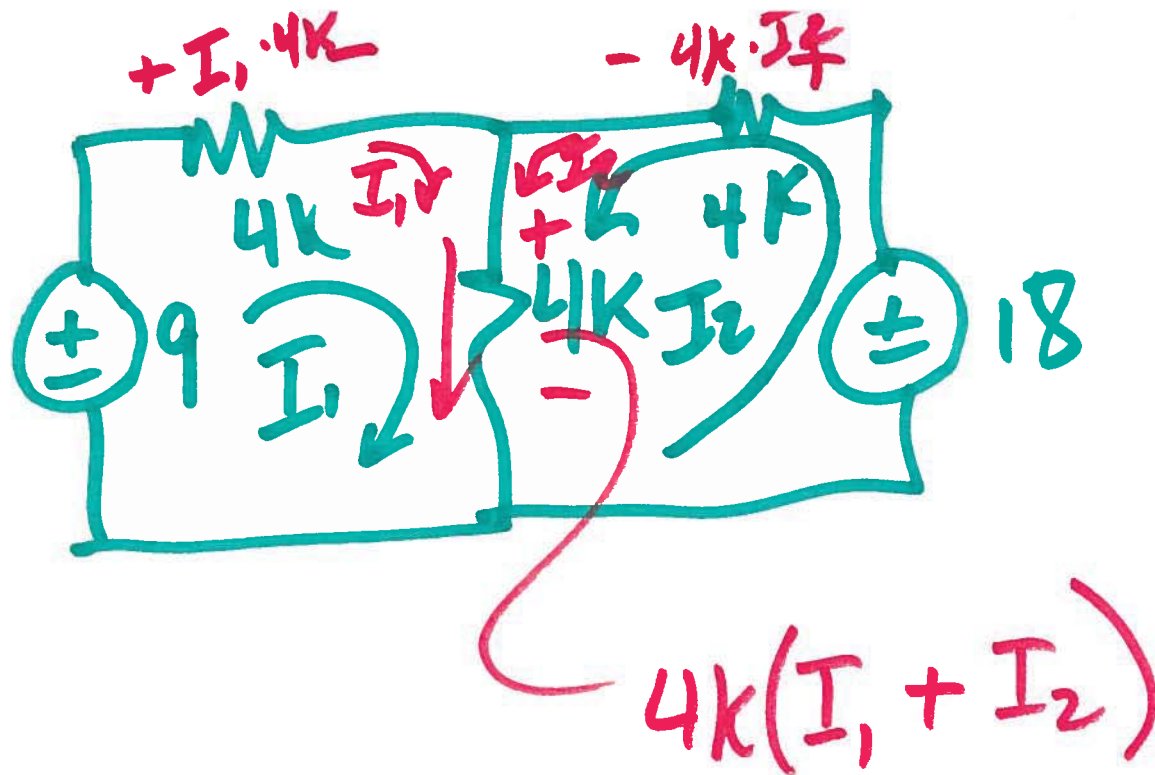


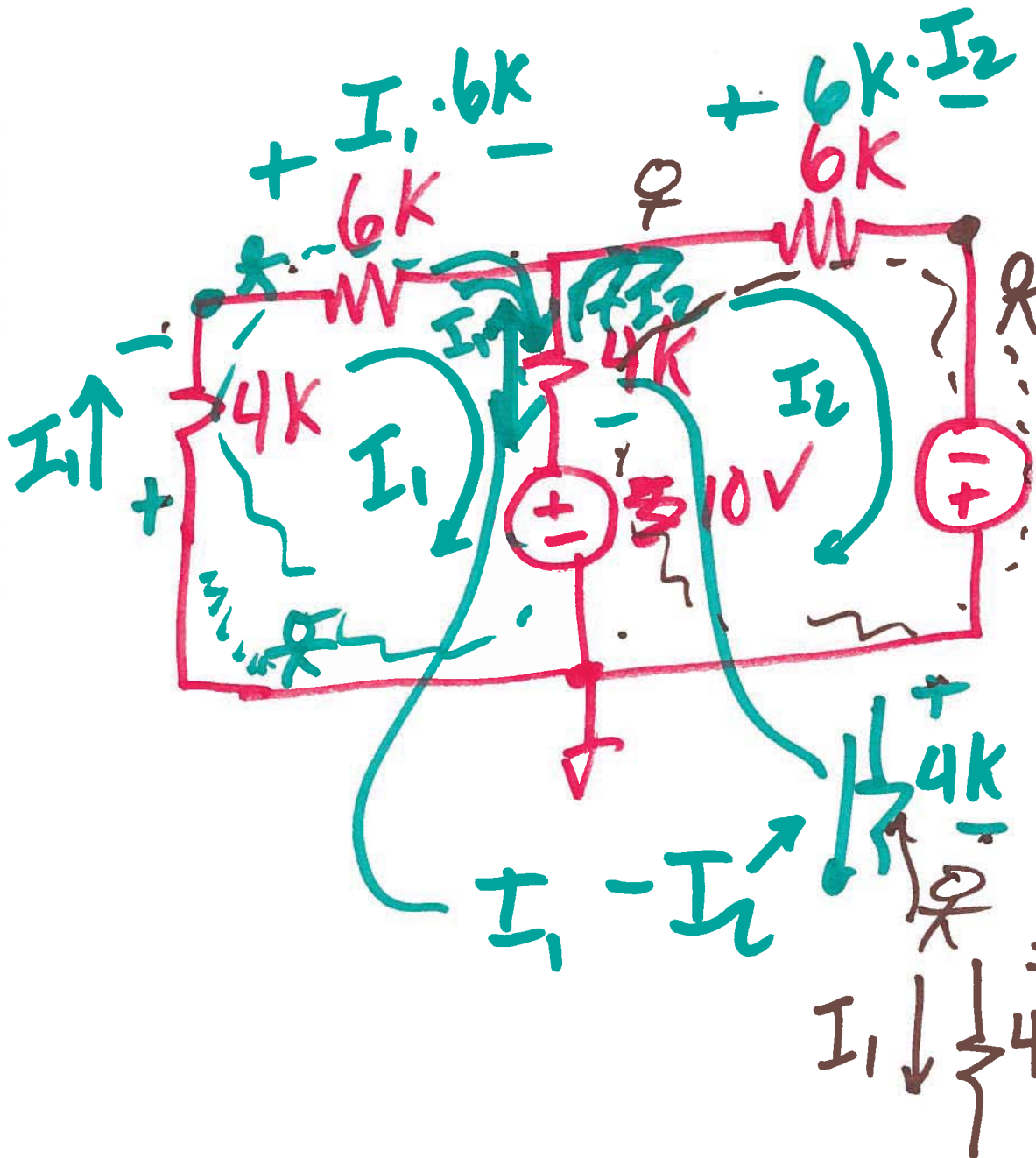

$$\begin{aligned}
 & -I_1 \cdot 6k - (I_1 - I_2) \cdot 4k \\
 & -10V - I_1 \cdot 4k \\
 & = 0
 \end{aligned}$$

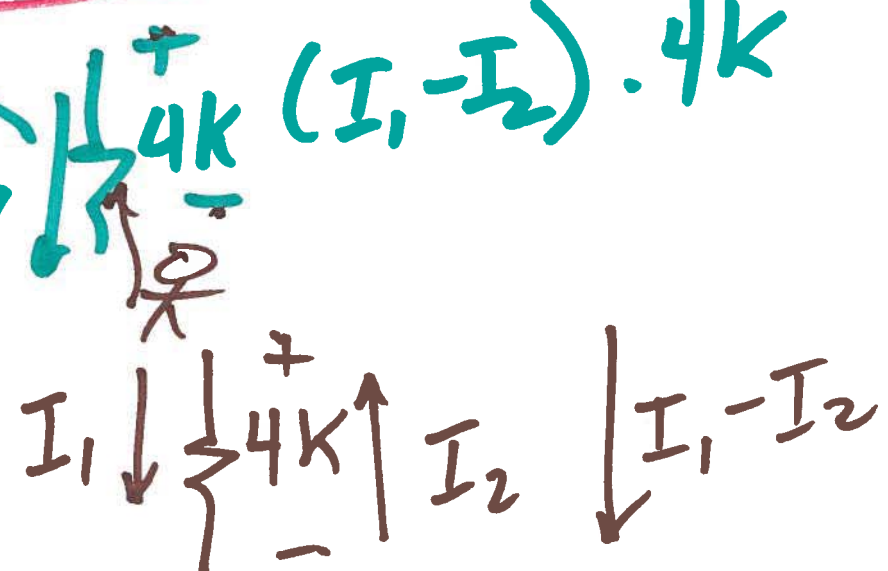
$$\begin{aligned}
 & 3 + 10 + (I_1 - I_2) \cdot 4k \\
 & - 6k I_2 = 0
 \end{aligned}$$



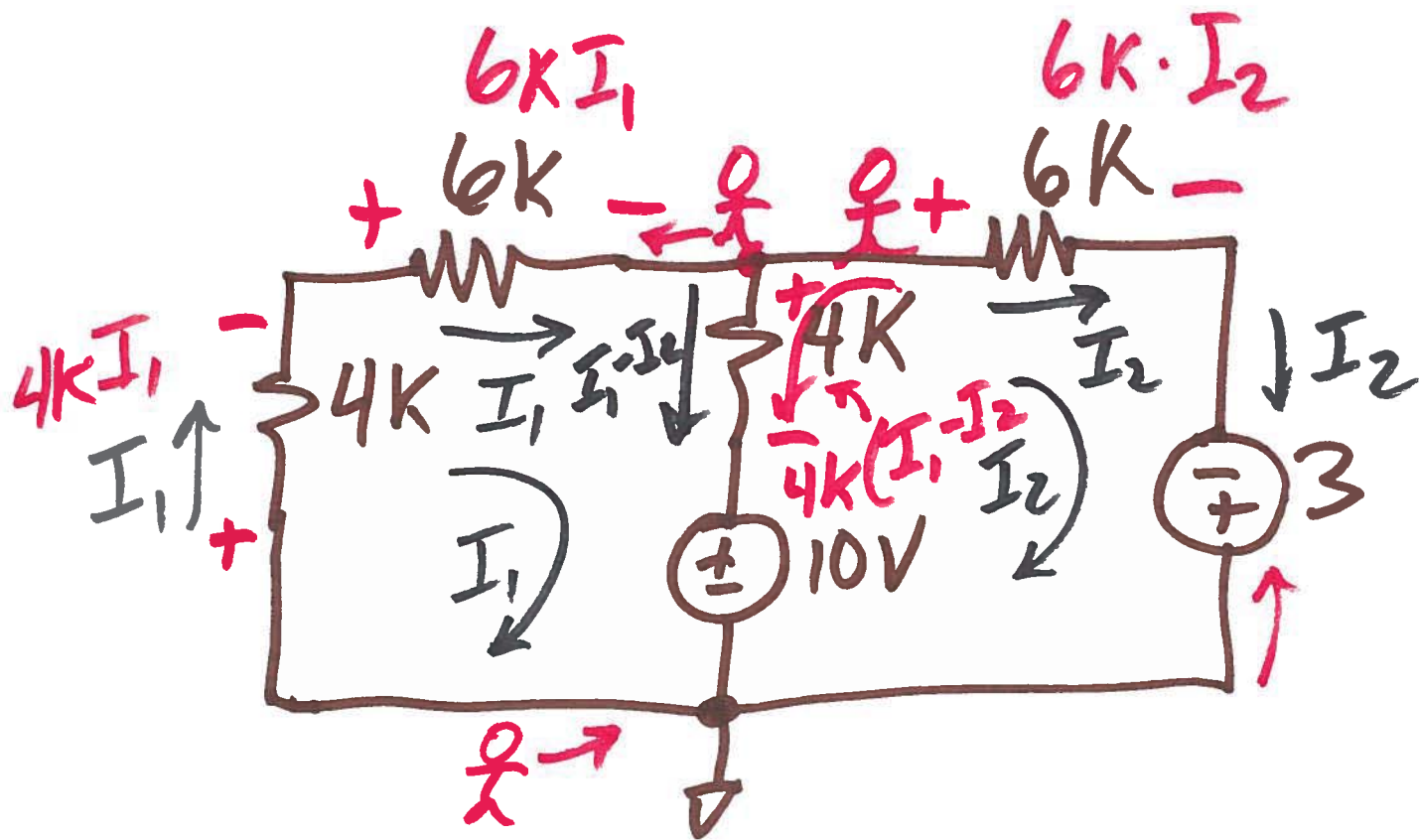

$$6kI_1 + 4kI_1 + 10 + 4k(I_1 - I_2) = 0$$

$$-4k(I_1 - I_2) - 10 - 3 + 6kI_2 = 0$$

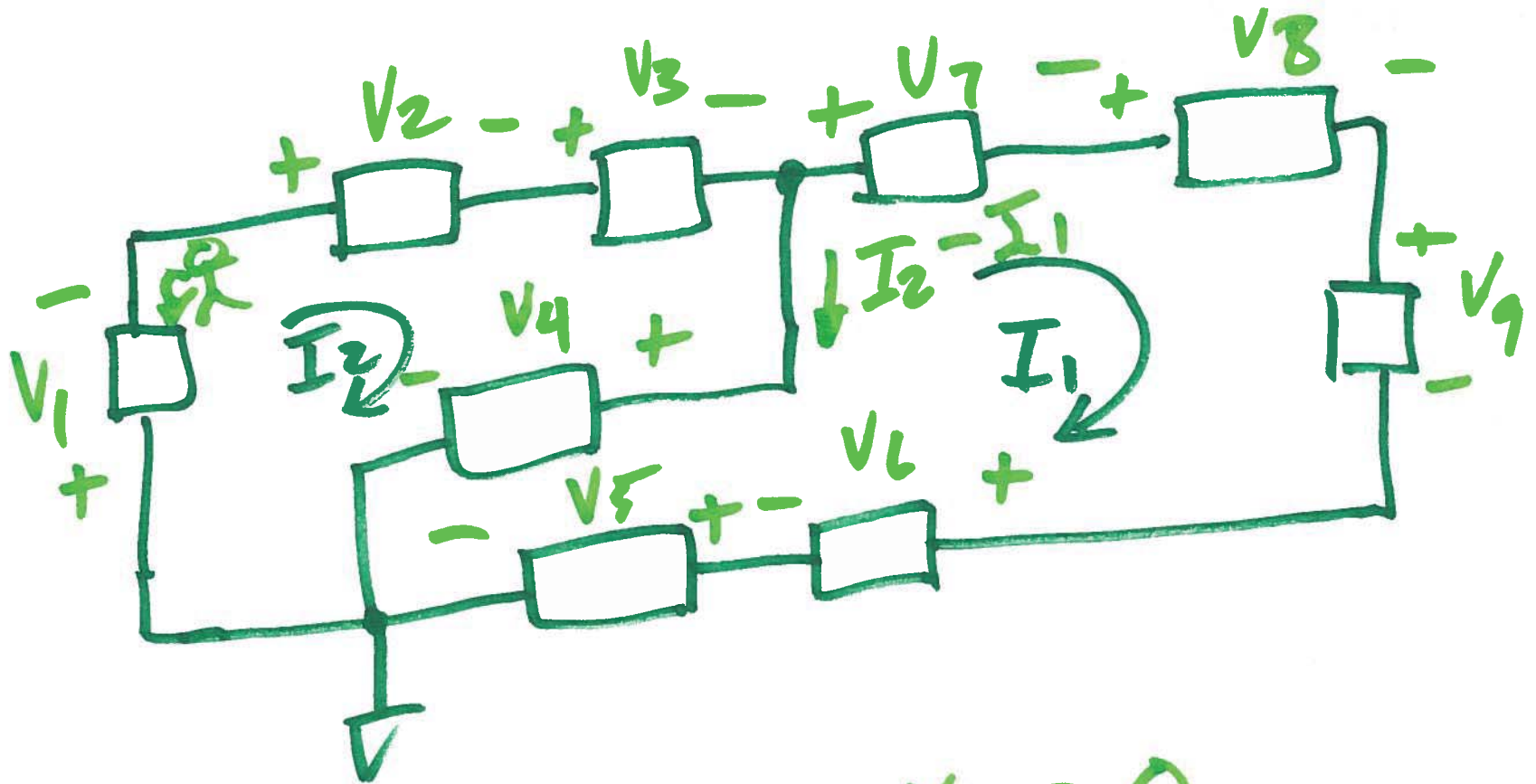

$$V_1 + V_4 + V_3 + V_2 = 0$$

$$V_1 + V_5 + V_6 + V_9 + V_8 + V_7 + V_3 + V_2 = 0$$

