
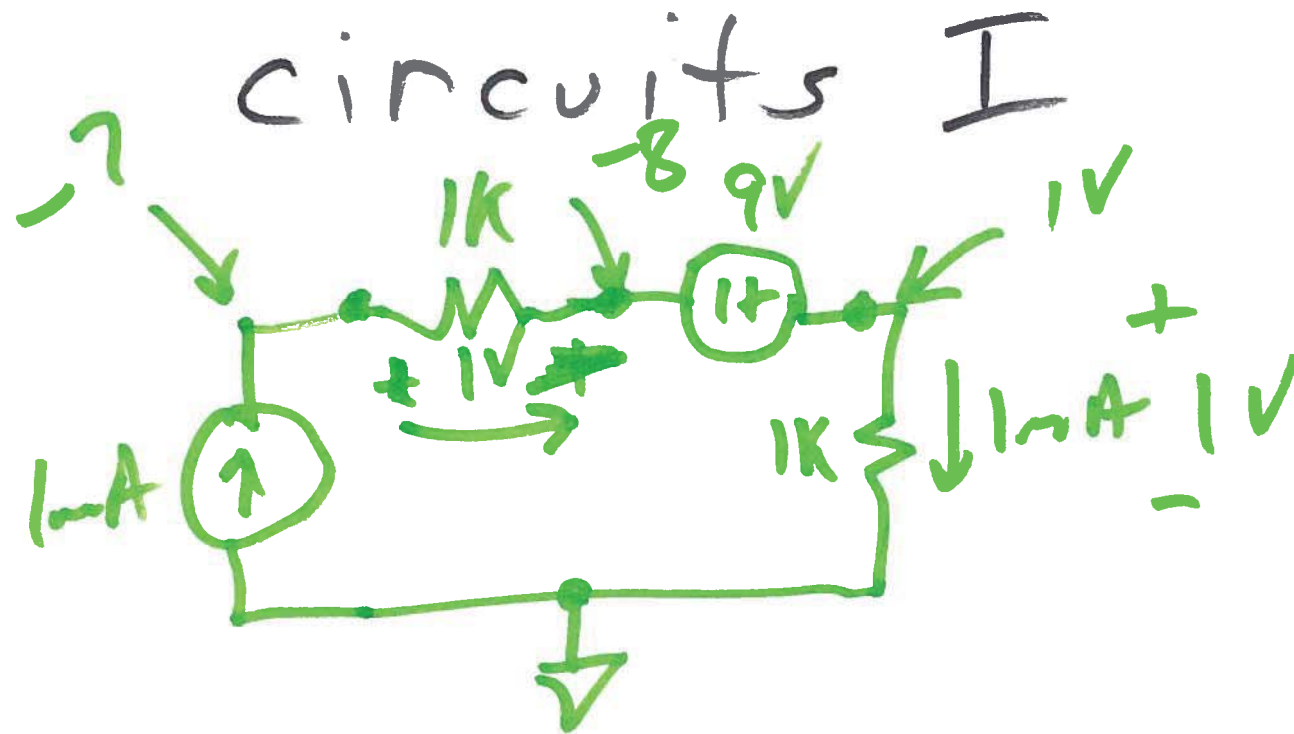


EE 220



Lecture 6  $1 - (-8) = 9$

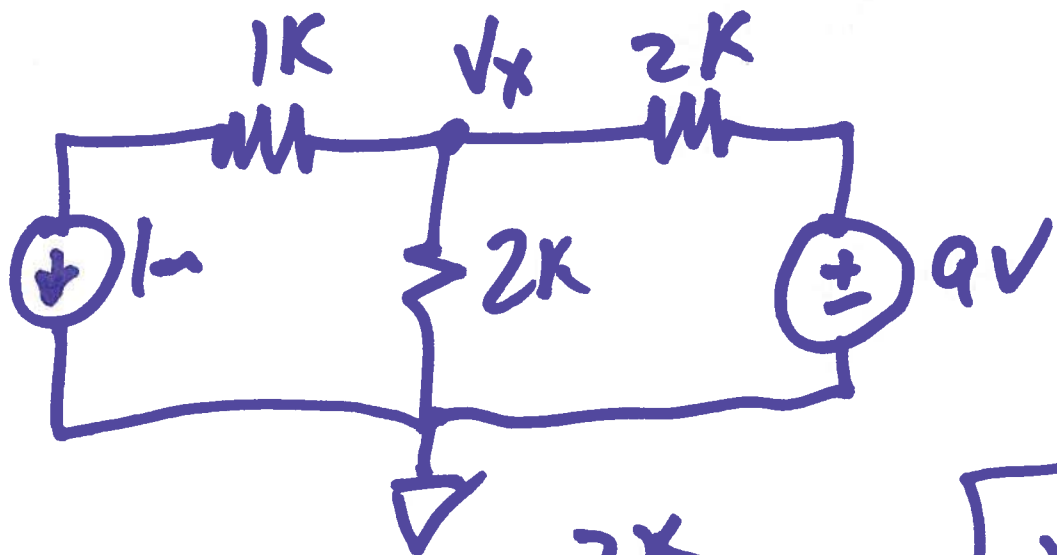




$4.5\text{V} = V_x$

$V_x = 3.5\text{V}$

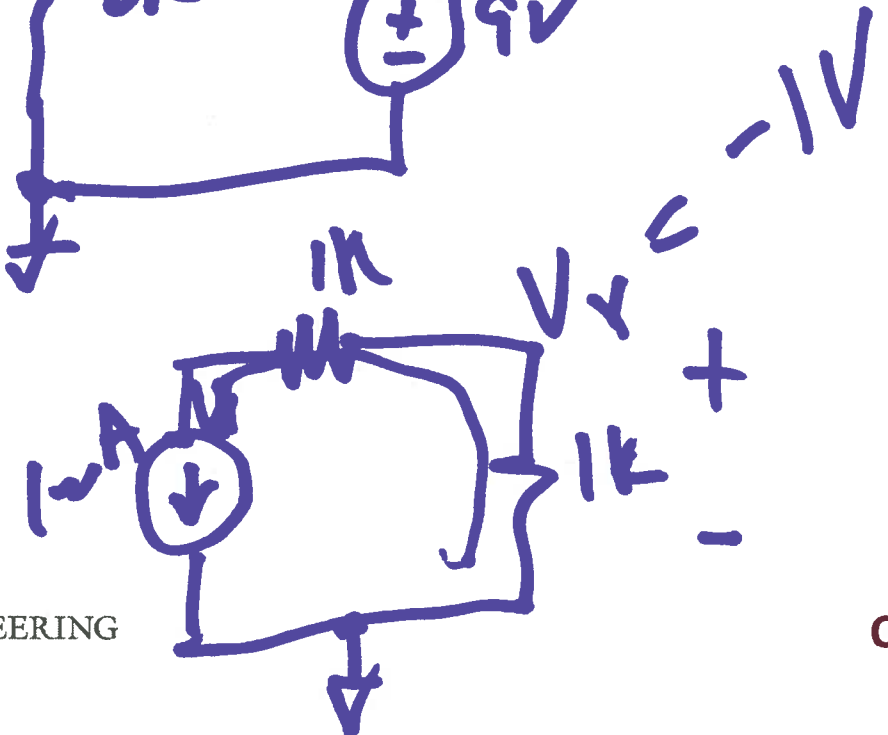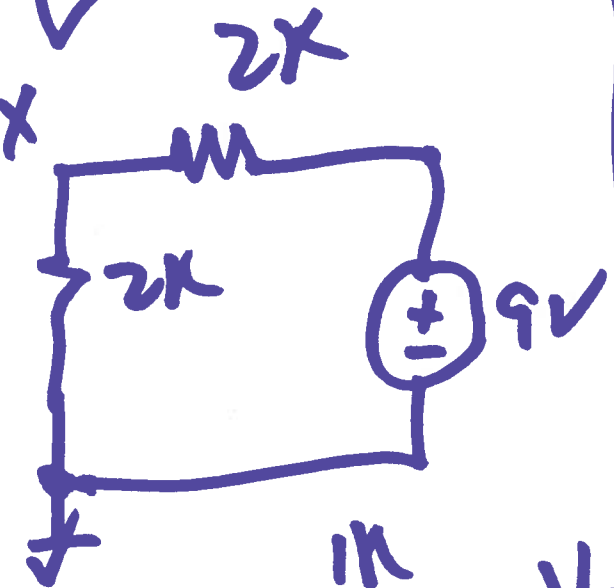

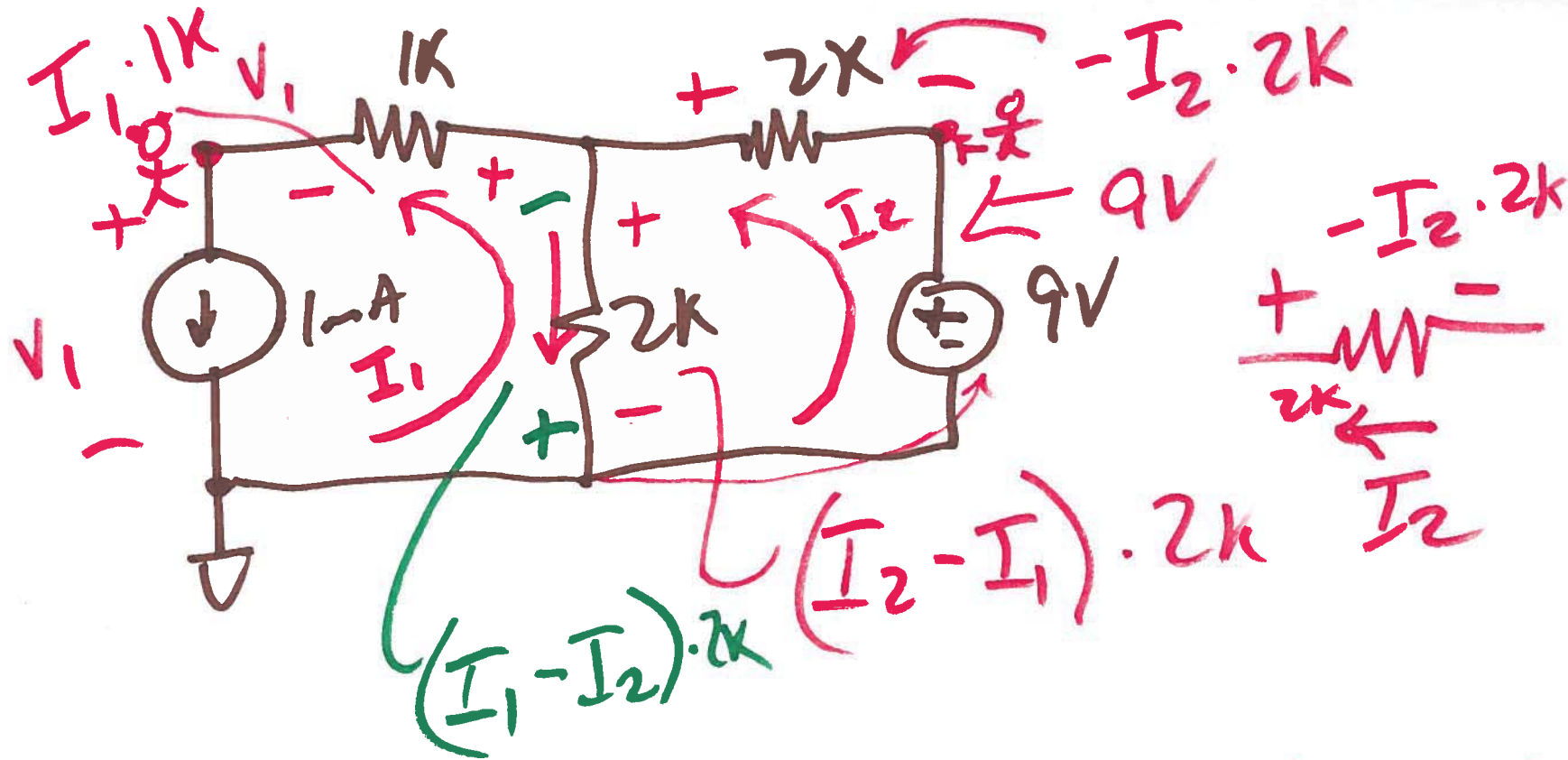


$$-V_1 + (I_2 - I_1)2\text{k} - I_1 \cdot 1\text{k} = 0$$

$$-(-I_2 \cdot 2\text{k}) - (I_2 - I_1) \cdot 2\text{k} + 9 = 0$$

$$I_1 = 1\text{mA}$$

3)

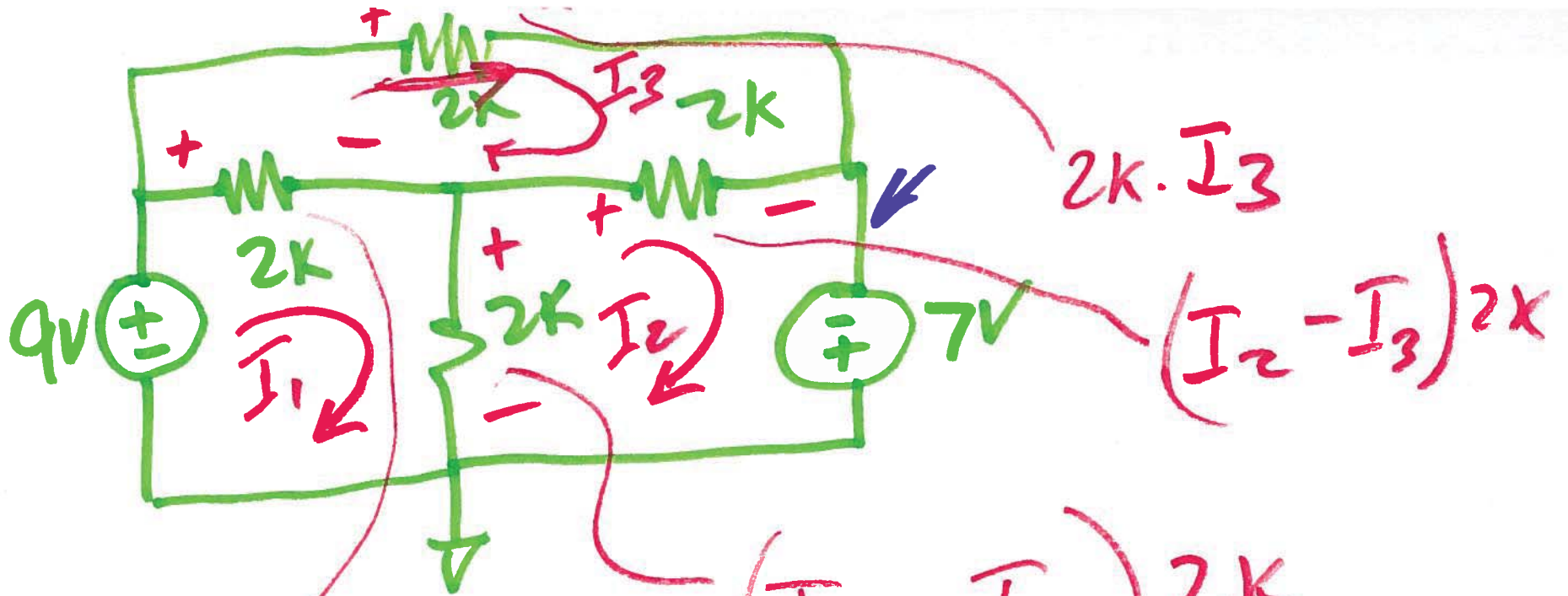

~~$I_1 \cdot 2k$~~

$(I_1 - I_3) \cdot 2k$

$$0 = 9 - (I_1 - I_3) \cdot 2k - (I_1 - I_2) \cdot 2k$$

$$0 = -7 + (I_2 - I_3) \cdot 2k - (I_1 - I_2) \cdot 2k$$

$$0 = (I_1 - I_3) \cdot 2k - I_3 \cdot 2k + (I_2 - I_3) \cdot 2k$$

$$0 = 9 - 4kI_1 + 2kI_2 + 2kI_3$$

$$0 = -7 - 2kI_1 + 4kI_2 - 2kI_3$$

$$0 = 0 + 2kI_1 + 2kI_2 - 6kI_3$$

= 0

$$-7 - 2kI_1$$

$$+ 4kI_2$$

$$-\frac{2}{3}kI_1 - \frac{2}{3}kI_2$$

$$I_3 = \frac{1}{3}I_1 + \frac{1}{3}I_2$$

$$0 = 9 - 4kI_1 + 2kI_2 + \frac{2}{3}kI_1$$

$$0 = 9 - 3\frac{1}{2}kI_1 + 2\frac{2}{3}kI_2 + \frac{2}{3}kI_2$$

$$0 = -7 - 2kI_1 + 3\frac{1}{2}kI_2$$

4)

$$0 = 27 - 10kI_1 + 8kI_2$$

$$\left( 0 = -21 - 8kI_1 + 10kI_2 \right) \frac{8}{10}$$

$$0 = \frac{-168}{10} - \frac{64k}{10}I_1 + 8kI_2$$

$$\begin{array}{r} 27 \\ 16.8 \\ \hline 43.8 \end{array}$$

$$0 = 27 + \frac{168}{10} \left( -10k + \frac{64k}{10} \right) I_1$$


$$I_1 = \frac{43.8}{3.6} \text{ mA}$$

$$0 = 43.8 - 3.6kI_1$$


b)



# THEVENIN'S THEOREM

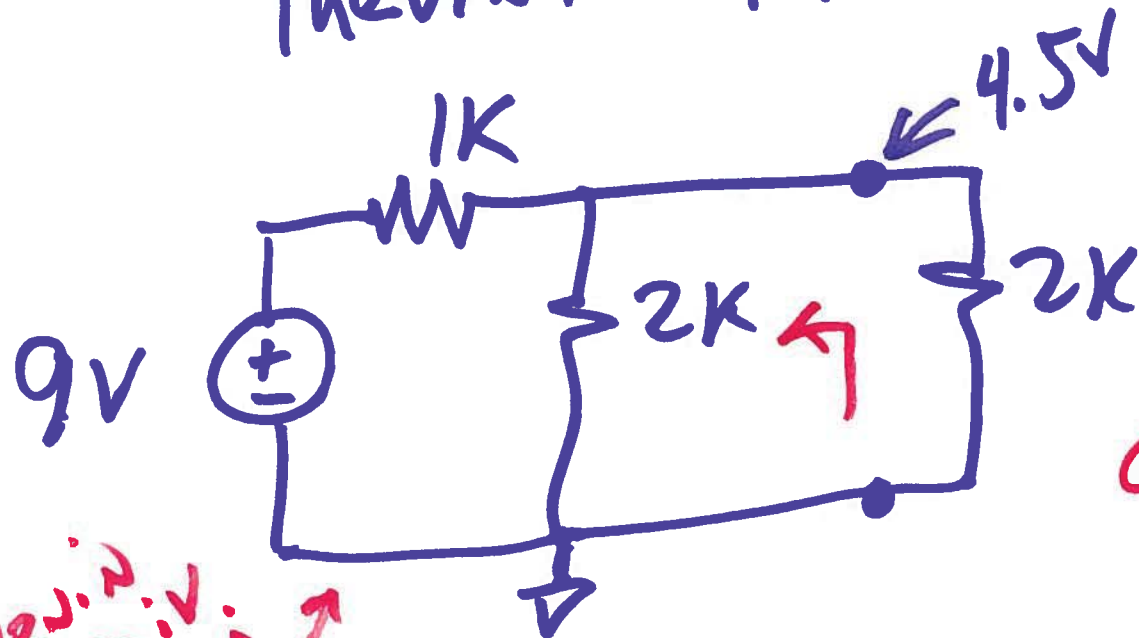

THEVENIN'S V.  
EX OF

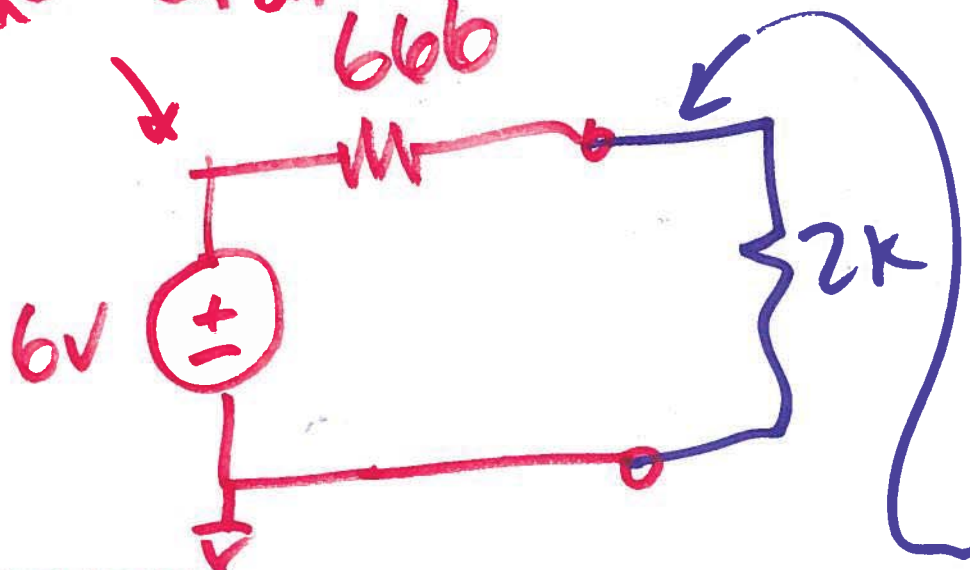


open circuit  
voltage

$$V_{oc} = 6V = V_{TH}$$

$$R_{TH} = 666\Omega$$

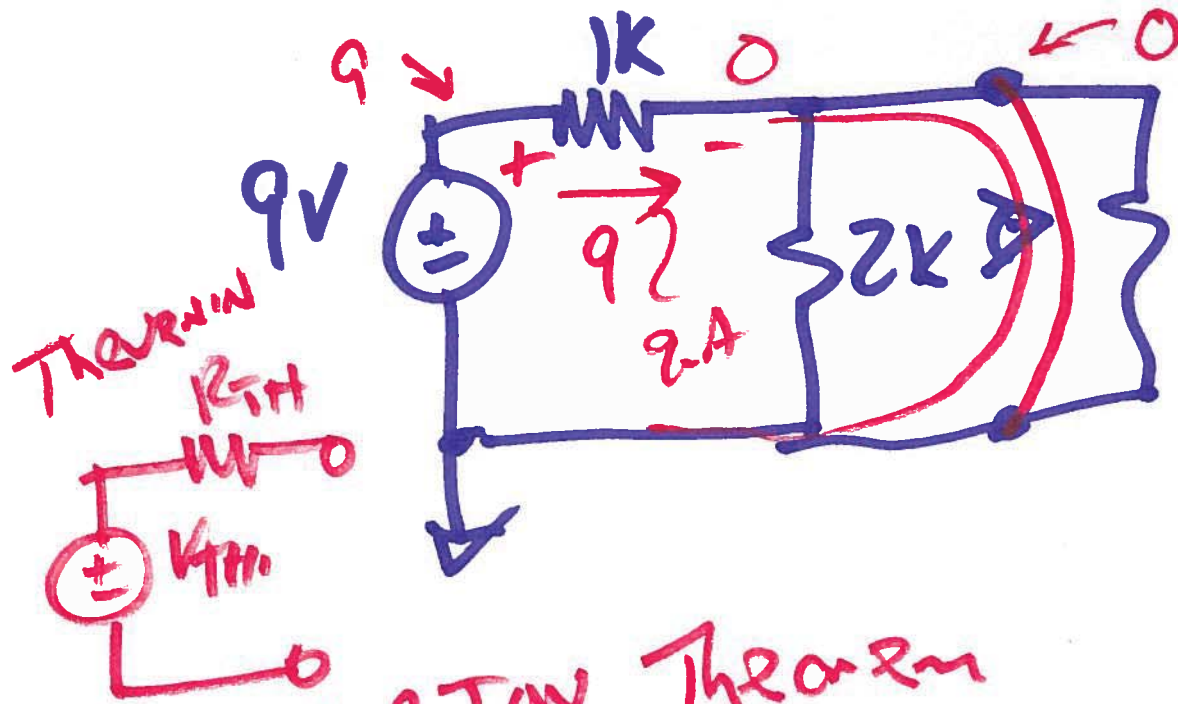
$$6V \cdot \frac{2k}{2k + 666} = \frac{12}{2666} = 4.5V$$




$$V_{oc} = V_{TH} = 6V$$

$$I_{sc} = \frac{9}{1k} = 9mA$$

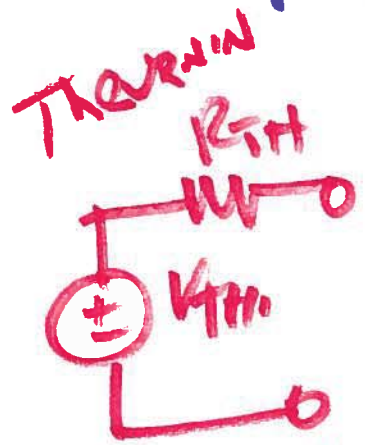
$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{6}{9mA} = 666\Omega$$



NORTON Theorem

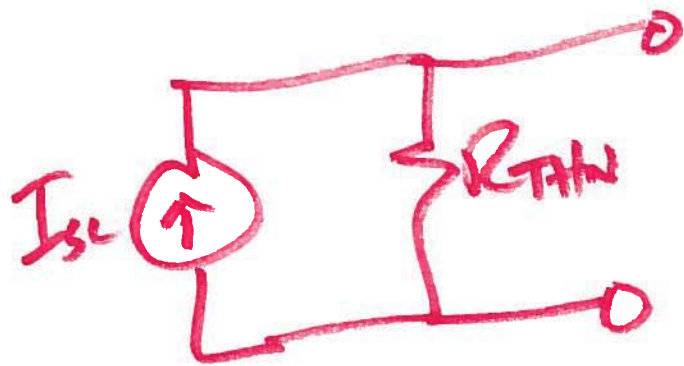


$$R_{TH} \cdot I_{sc} = V_{TH}$$

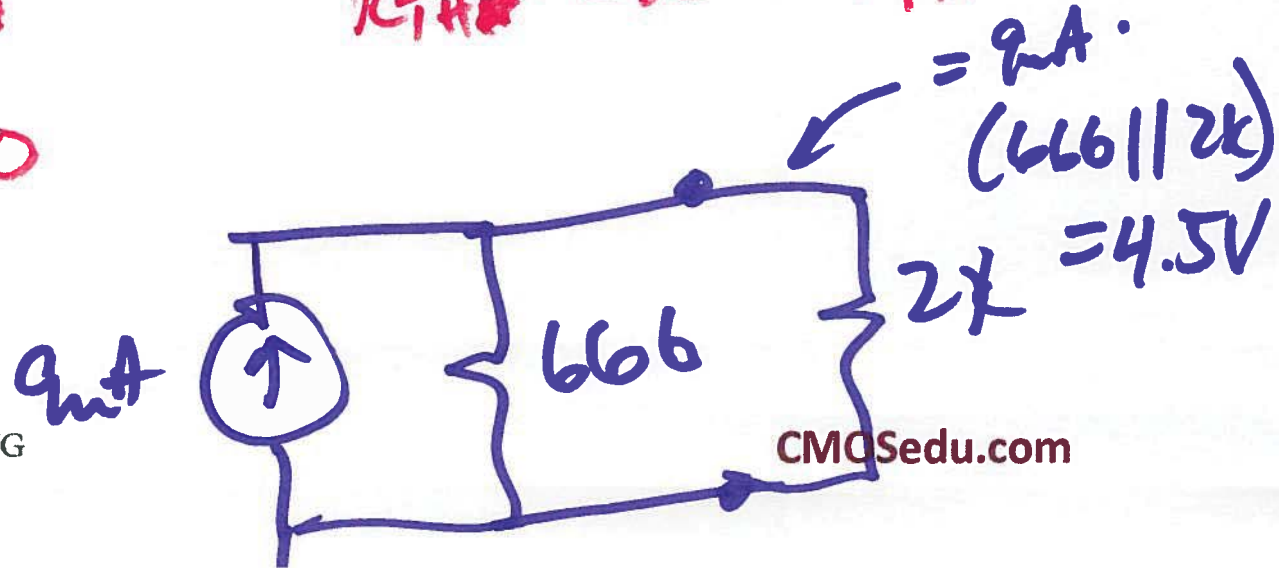

8)



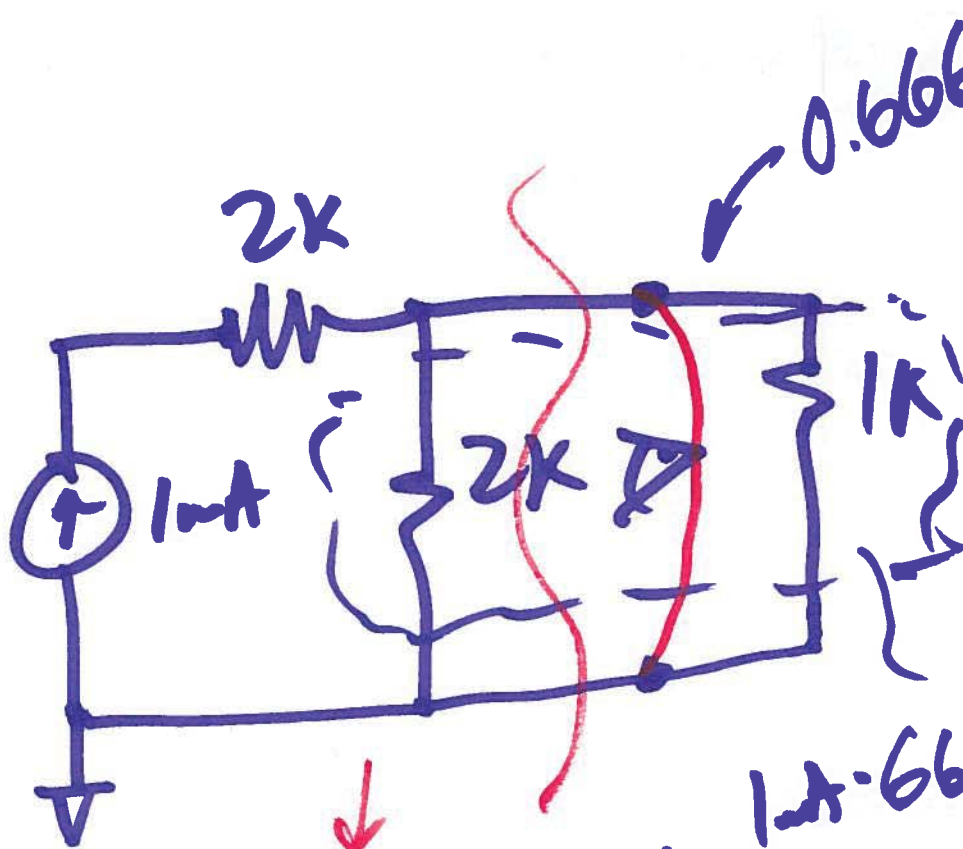


$V_{oc} = V_{TH} = 2V$

$R_{TH} = 2K$


$I_{SC} = 1mA$

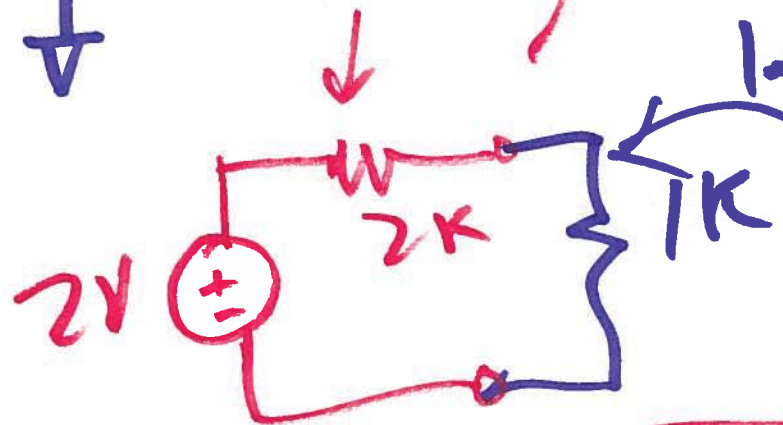$R_{TH} = \frac{V_{TH}}{I_{SC}} = \frac{2V}{1mA} = 2K$



$1mA \cdot 666\Omega$

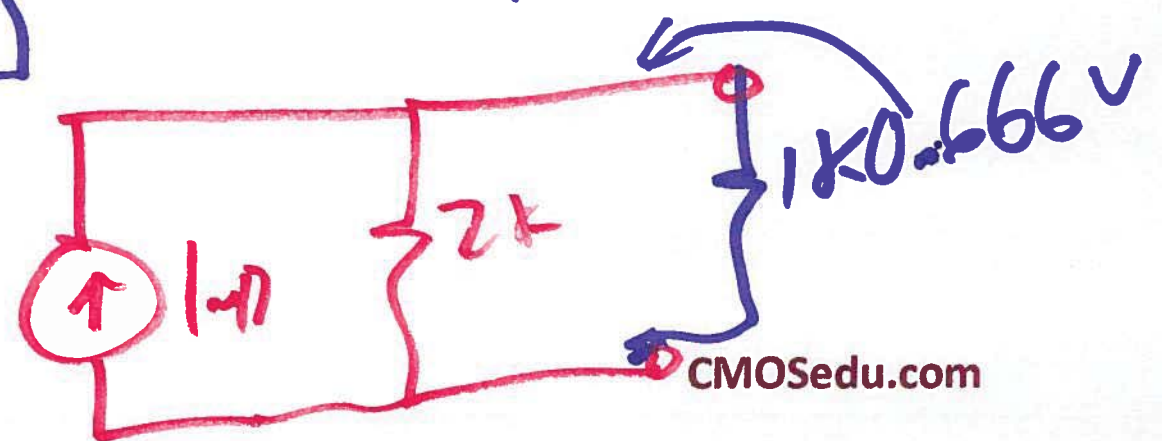$2V \cdot \frac{1K}{1K+2K} = \frac{2V}{3} = 666mV$



9)