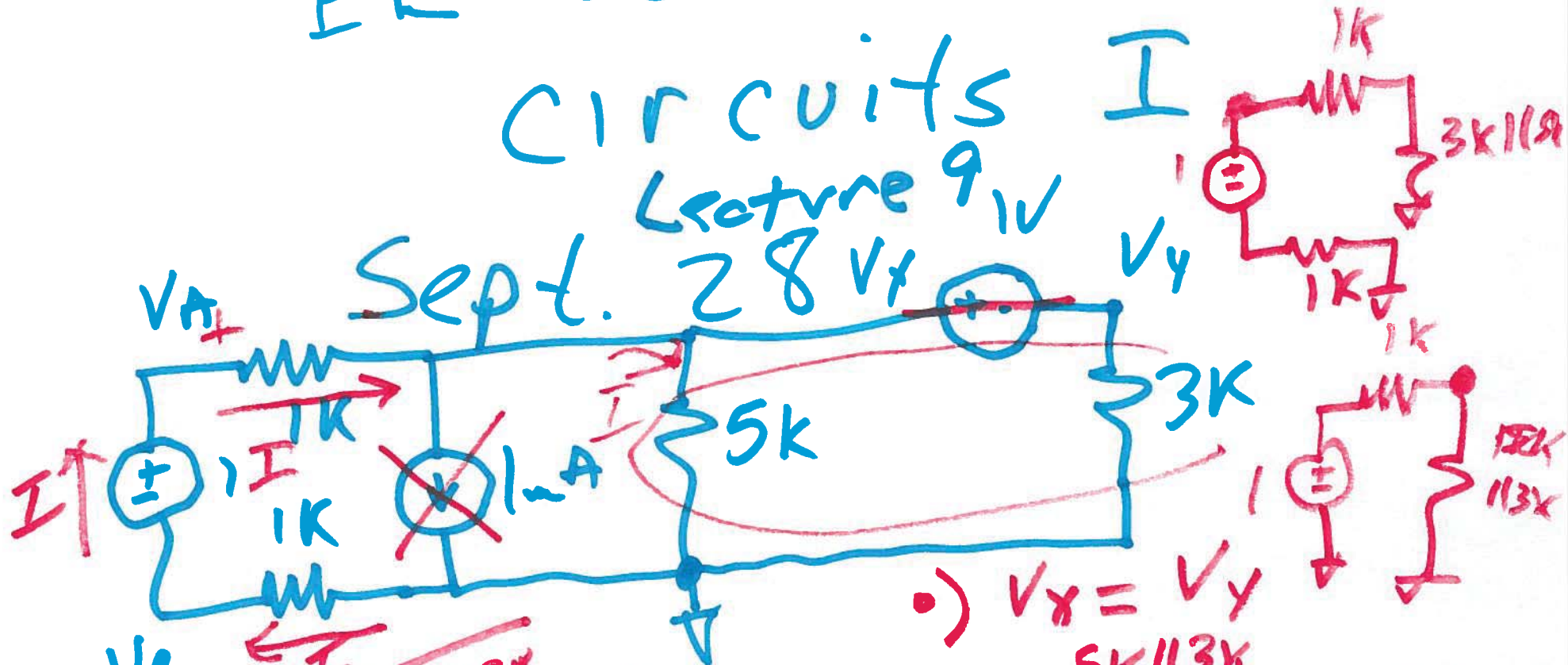


EE 220

Circuits I


Lecture 9

Sept. 28



$$I = \frac{1}{1k + 1k + 5k \parallel 3k}$$

$$V_x = I \cdot 5k \parallel 3k$$



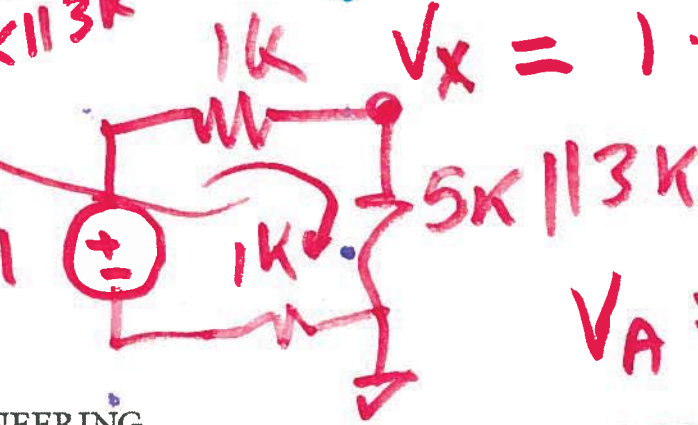


$$V_x = 1 \cdot \frac{5k \parallel 3k}{5k \parallel 3k + 1k + 1k}$$

$$V_x = V_y = \frac{5k \parallel 3k}{5k \parallel 3k + 1k + 1k}$$

$$V_A = I \cdot (1k + 3k \parallel 5k)$$


$$V_B = V_A - 1$$

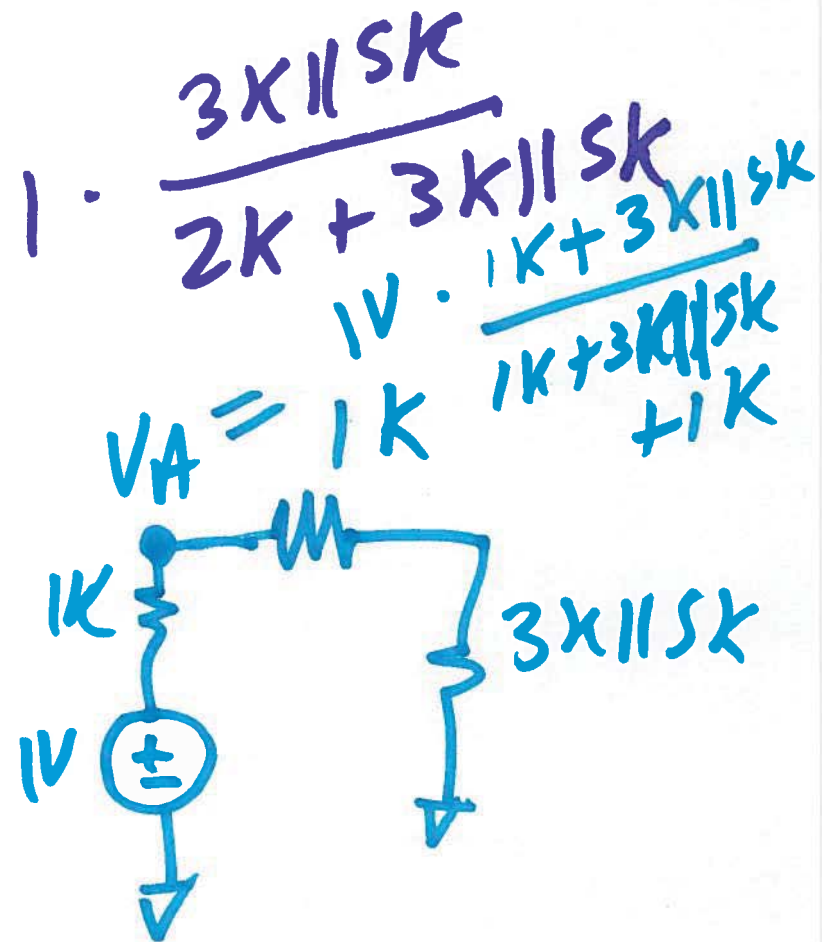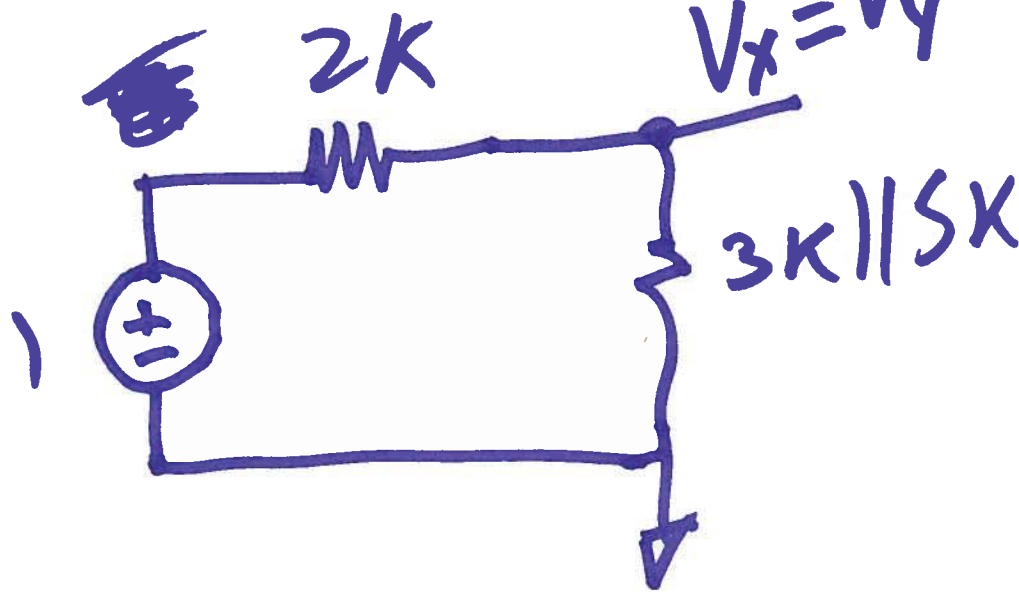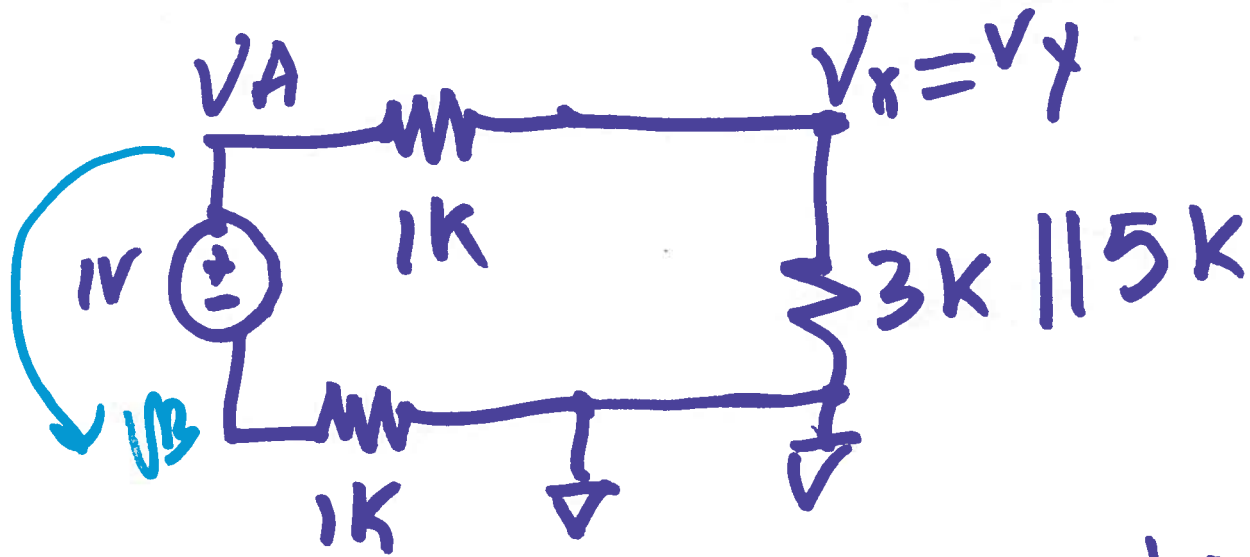


$$V_X = V_Y = 1 \cdot \frac{3k \parallel 5k}{2k + 3k \parallel 5k}$$

$$V_A = 1k = 4V \cdot \frac{1k + 3k \parallel 5k}{1k + 3k \parallel 5k + 1k}$$

$$V_B = V_A - 1$$

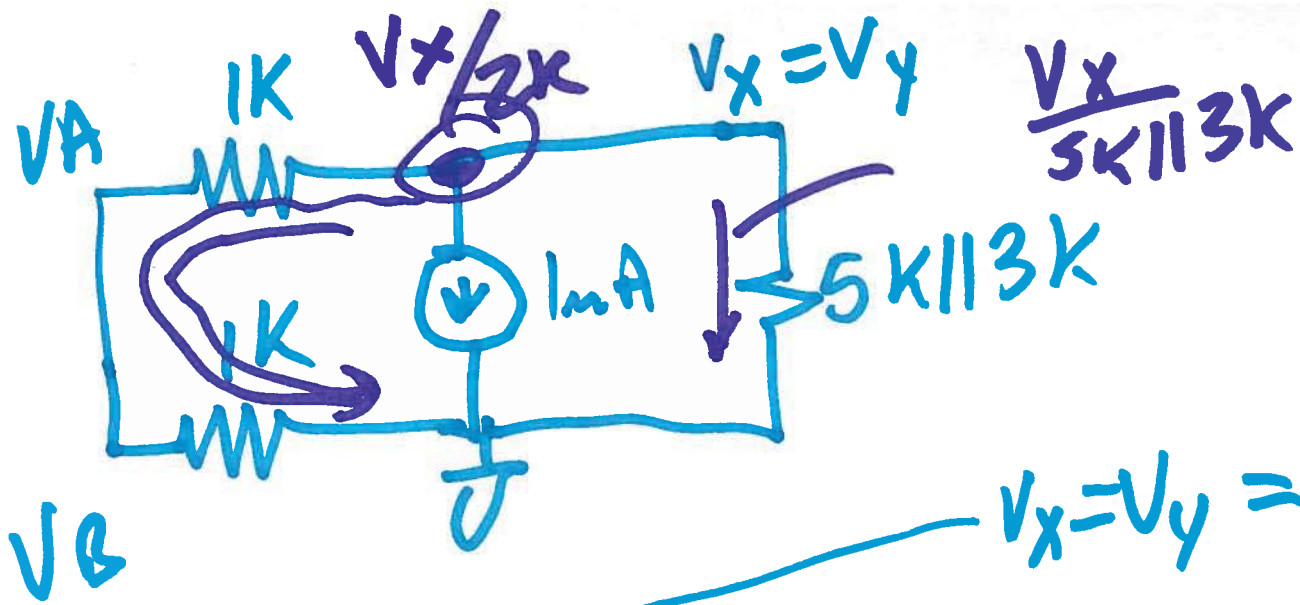
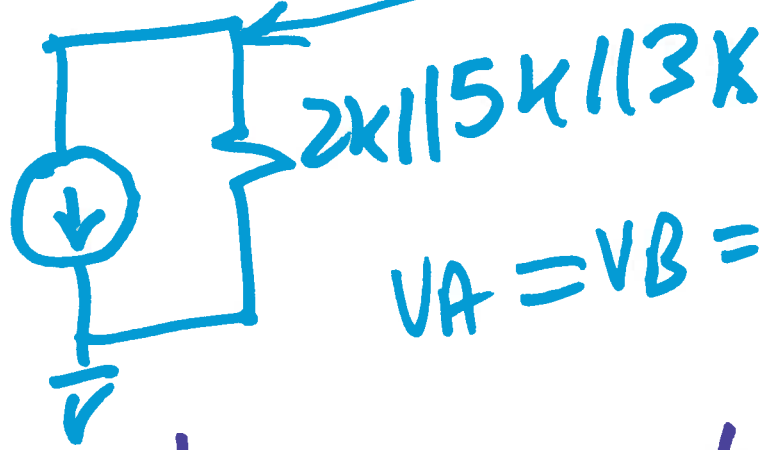
$$V_x = V_y = -1\text{mA} \cdot (2\text{K} \parallel 5\text{K} \parallel 3\text{K})$$




$$V_A = V_B = V_x \cdot \frac{1\text{K}}{1\text{K} + 1\text{K}} = \frac{V_x}{2}$$


$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} \quad 1\text{mA} + \frac{V_x}{2\text{K}} + \frac{V_x}{5\text{K} \parallel 3\text{K}} = 0$$

$$R_T = \frac{1}{\frac{1}{2} + \frac{1}{1}} \quad V_x = \frac{-1\text{mA}}{\frac{1}{2\text{K}} + \frac{1}{5\text{K} \parallel 3\text{K}}} = -1\text{mA} \cdot \frac{2\text{K} \parallel 5\text{K} \parallel 3\text{K}}{2\text{K}}$$

2)

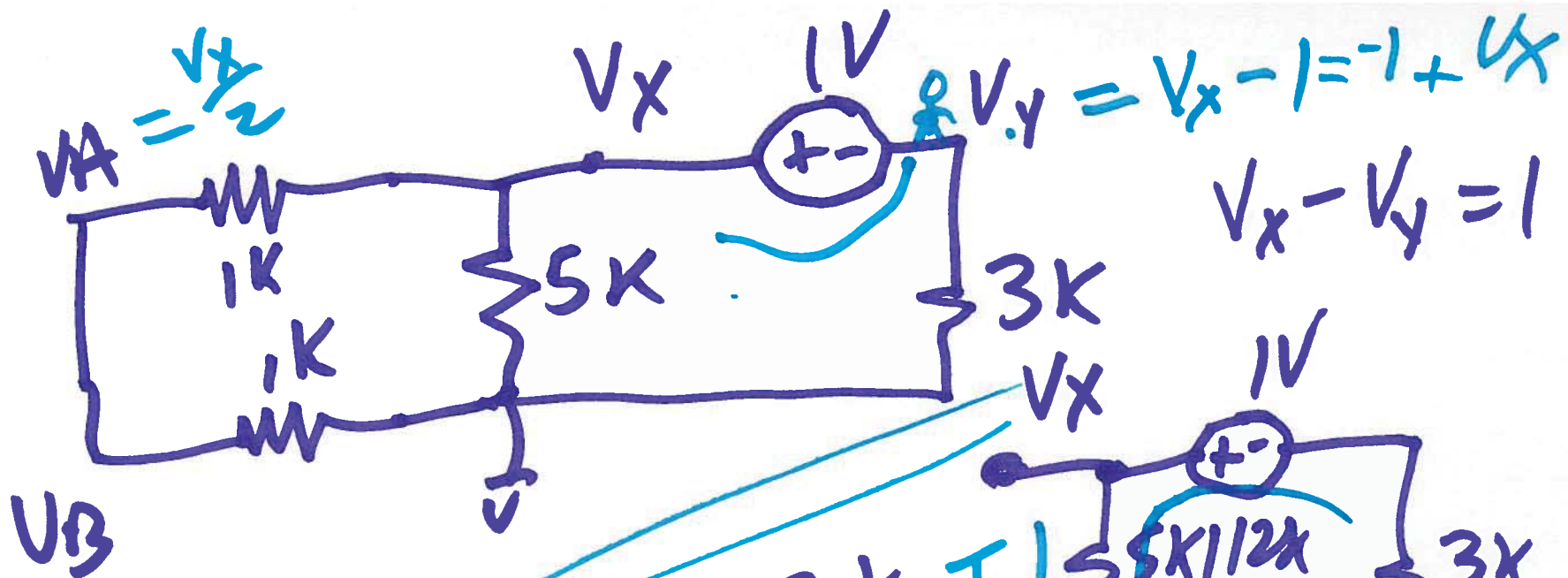

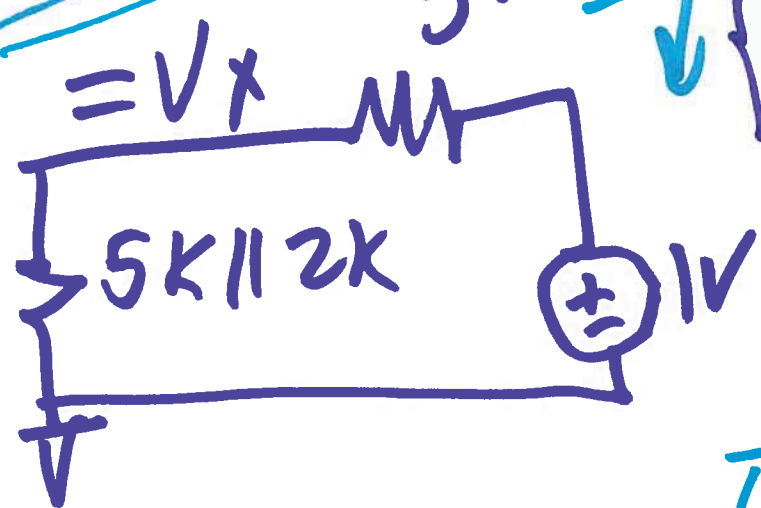
$$1 \cdot \frac{5k \parallel 2k}{5k \parallel 2k + 3k}$$



$$I = \frac{1V}{5k \parallel 2k + 3k}$$

$$V_x = I \cdot 5k \parallel 2k$$

a)

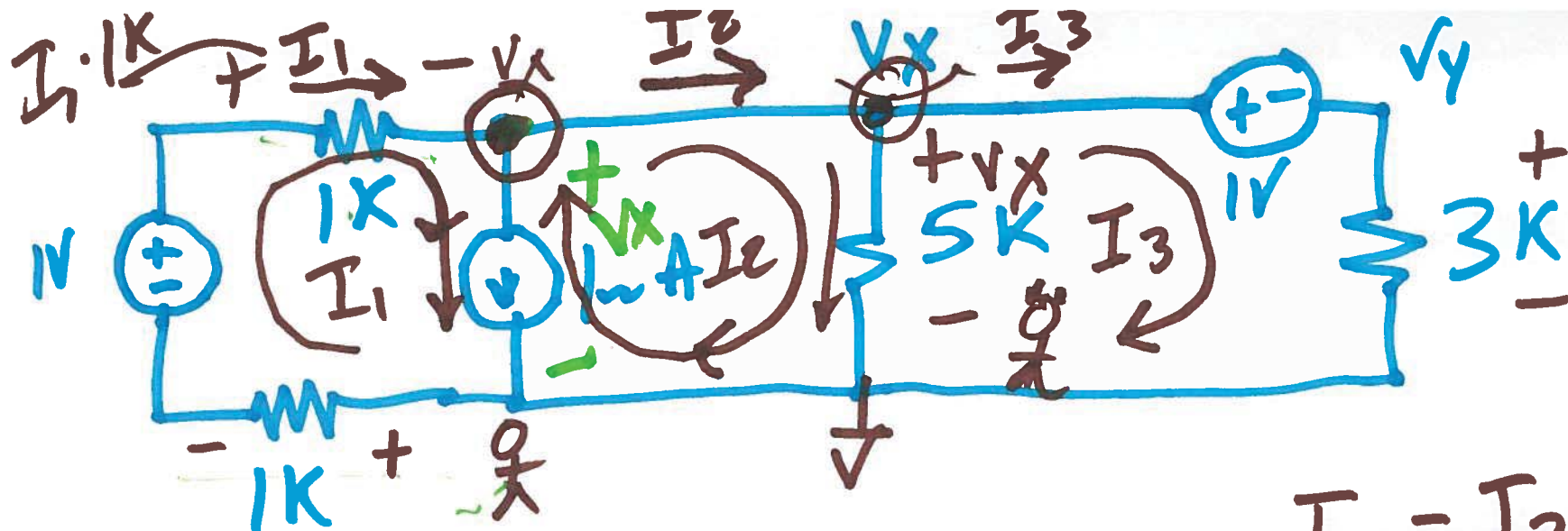

$$I_2 = I_3 + \frac{V_x}{5k}$$

$$V_y = V_x - 1$$

$$I_1 = I_2 + 1mA$$


$$I_3 = \frac{V_y}{3k}$$

$$\frac{V_x}{5k} = I_2 - I_3$$

$$V_x = 5k(I_2 - I_3) \quad 1k \cdot I_1 + 1 - I_1 \cdot 1k - V_x = 0$$

$$V_x - 1 - I_3 \cdot 3k = 0$$

5)

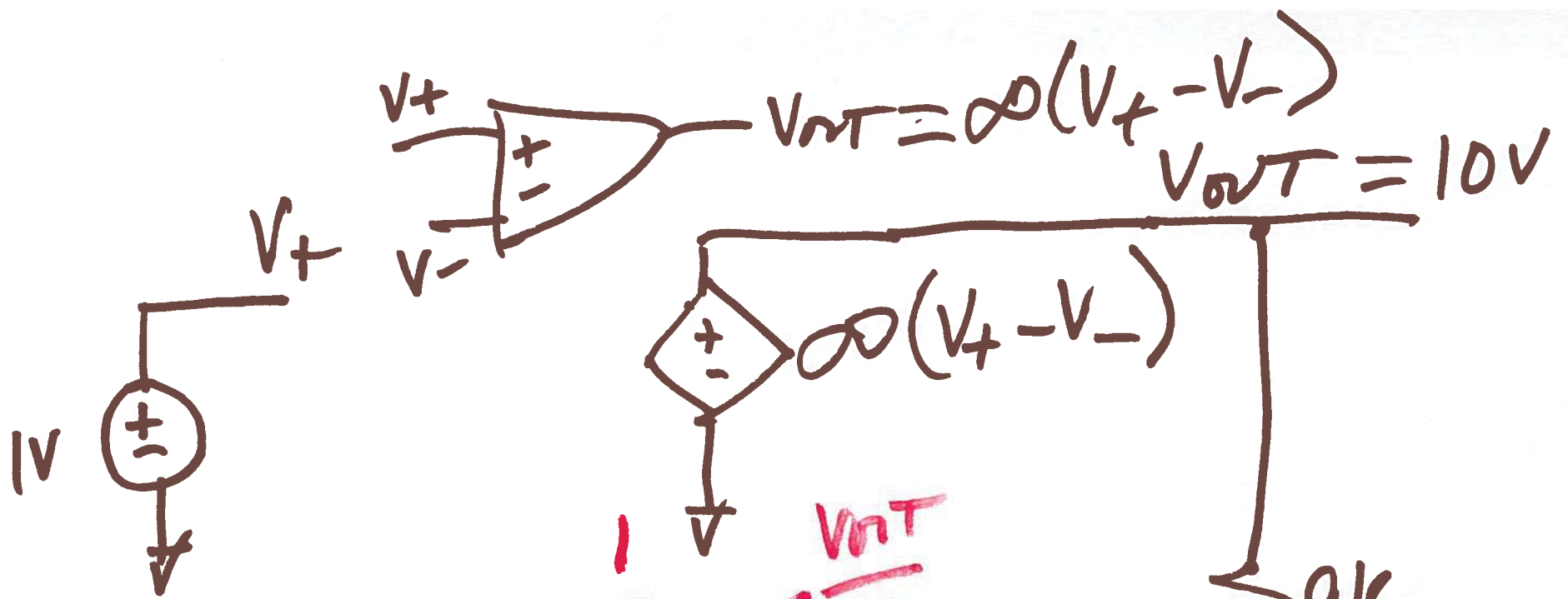

$V_{out} = \infty(V_+ - V_-)$
 $V_{out} = \frac{V_{out}}{10}$

$V_{out} = \infty - \frac{V_{out} \cdot \infty}{10}$

$V_{out} \left(1 + \frac{\infty}{10}\right) = \infty$

$V_- = V_{out} \cdot \frac{1k}{1k + 9k} = \frac{V_{out}}{10}$

$V_{out} = \frac{\infty}{1 + \frac{\infty}{10}} = \frac{1}{\frac{1}{\infty} + \frac{1}{10}} = 10$

b)