


Study Session I final

EE 220

Circuits I

$$V_x = 5V$$

$$V_y = 9, V_s = 9V$$

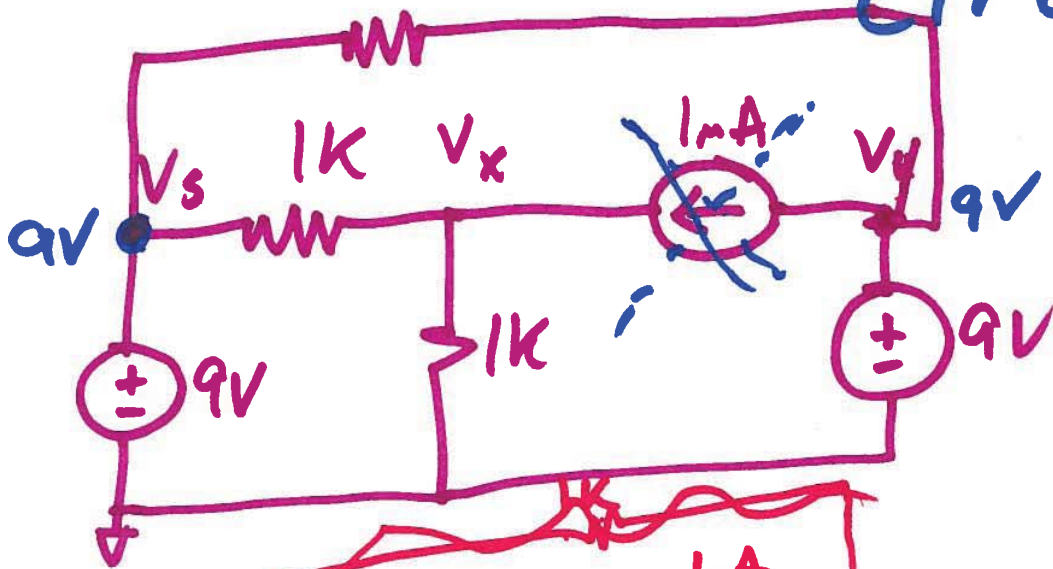

reverse

$$V_x = 4.5V$$

$$V_y = 9V$$

$$V_s = 9V$$





short 9V sources

$$V_s = 0$$

$$V_y = 0$$

$$V_x = \frac{1}{2}V$$

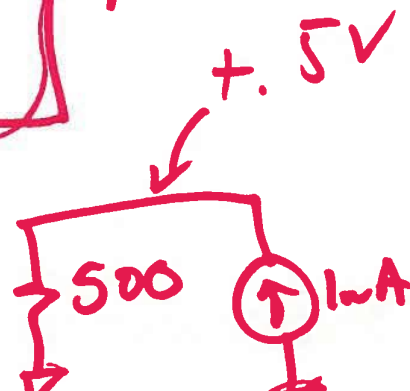

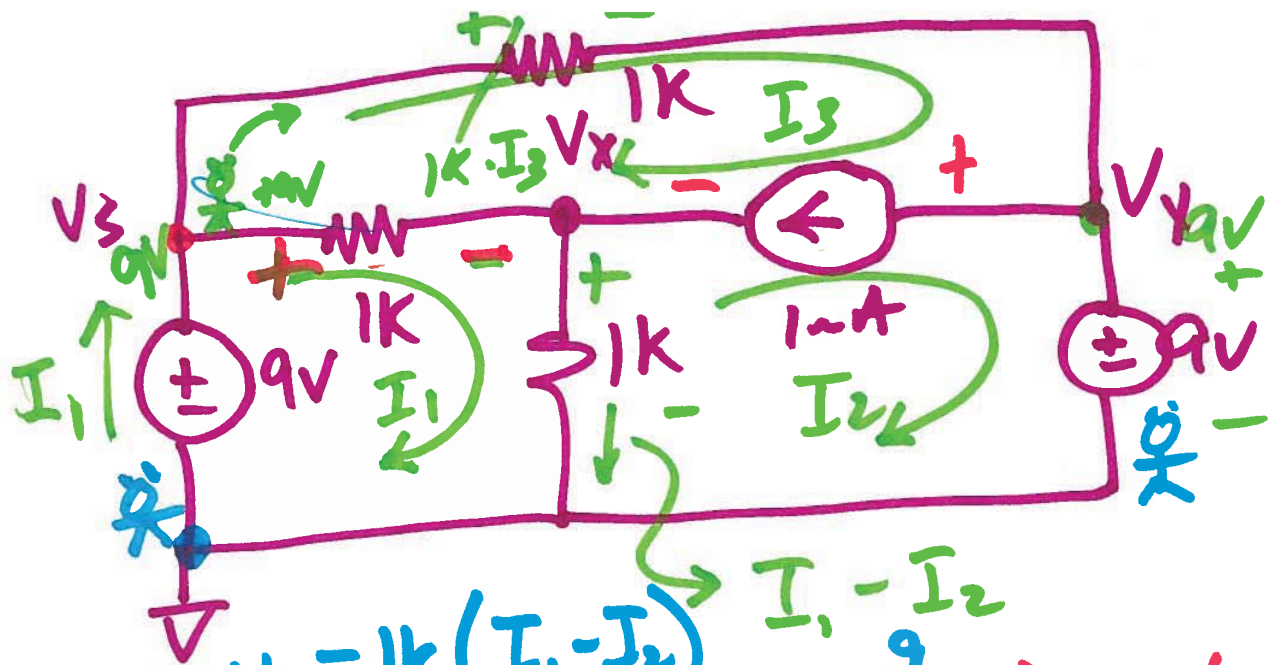

$$I_3 - I_2 = 1 \text{mA}$$

$$9 - 1k \cdot I_3 - 9 = 0$$

$$I_3 = 0$$

$$V_x = 1k(I_1 - I_2)$$

$$-I_3 \cdot 1k - (V_y - V_x) + (I_1 - I_3) \cdot 1k = 0$$

$$I_3 - I_2 = 1 \text{mA}$$

$$9V - (I_1 - I_2) \cdot 1k - (I_1 - I_2) \cdot 1k = 0$$

$$-9V - (V_y - V_x) - (I_1 - I_3) \cdot 1k = 0$$

$$0 \quad (-I_1 + I_3) \cdot 1k + 0$$

$$9 - V_x = 0$$

$$I_3 - I_2 = 1 \text{ mA}$$

$$-I_3 \cdot 1k - (9 - V_X) + 1k(I_1 - I_2) + (I_1 - I_3) \cdot 1k = 0$$

$$-I_1 \cdot 1k + I_3 \cdot 1k + 9 - V_X + 1k(I_1 - I_2) = 0$$

$$I_3 - I_2 = 1 \text{ mA}$$

$$-I_3 \cdot 1k - 9 + 1k \cdot I_1 - 1kI_2 + 1k \cdot I_1 - 1kI_3 = 0$$

$$-I_1 \cdot 1k + I_3 \cdot 1k + 9 - 1k \cdot I_1 + 1kI_2 = 0$$

$$\rightarrow I_3 - I_2 = 1 \text{ A}, \quad I_3 = 1 \text{ A} + I_2$$

$$I_3 = 0$$

$$2kI_1 - 1kI_2 - 2kI_3 = 9$$

$$-2kI_1 + 1kI_2 + 1kI_3 = -9$$

$$2k \cdot I_1 - 1kI_2 - 2 - 2kI_2 = 9$$


$$-2kI_1 + 1kI_2 + 1 + 1kI_2 = -9$$

$$2kI_1 - 3kI_2 = 11$$

$$-2kI_1 + 2kI_2 = -10$$

$$-1kI_2 = 1$$

$$I_2 = -1 \text{ A}$$

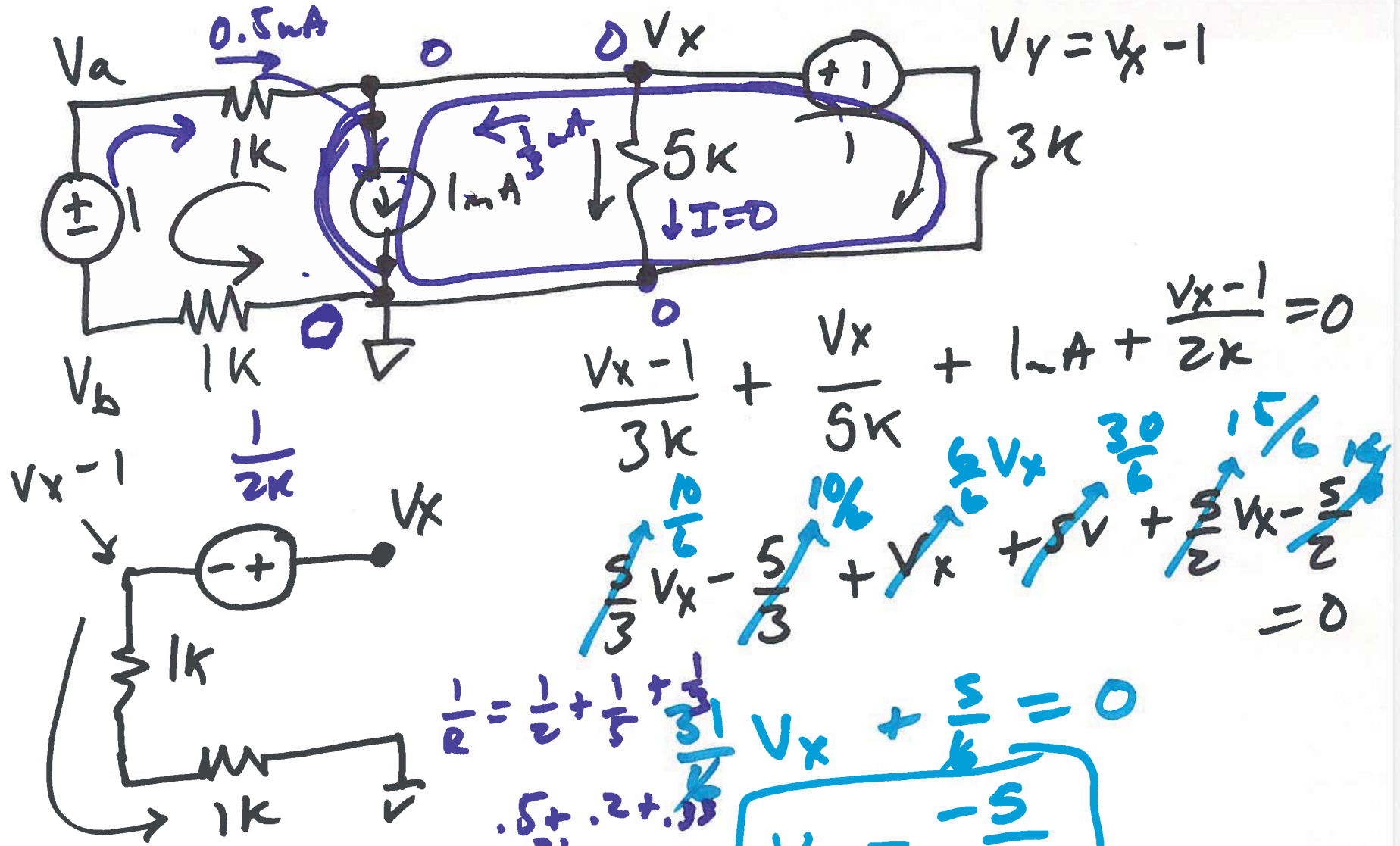

$$R_{TH} = 2k \parallel 5k \parallel 3k$$


$$= \frac{31}{30} k \approx 1k$$

$$I_{SC} = 0.833 \mu A$$

$$V_x = -\frac{5}{31}$$

$$V_{TH} =$$

CMOSedu.com

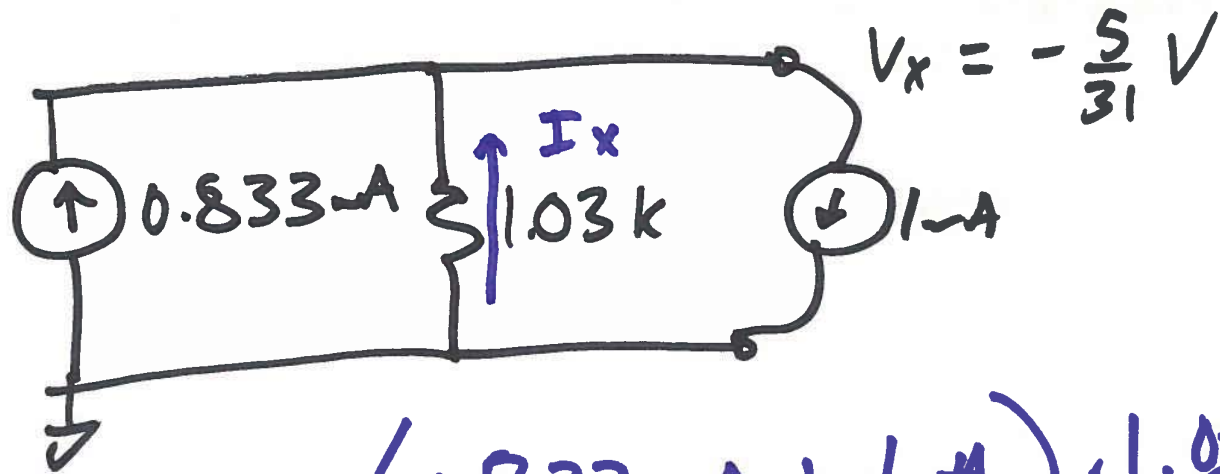

$$0.833 \text{ mA} + I_x = 1 \text{ mA}$$


$$I_x = 1 \text{ mA} - 0.833$$


$$\left(-0.833 \text{ mA} + 1 \text{ mA} \right) \cdot 1.03 \text{ k}$$

$$V_x = -I_x \cdot 1.03 \text{ k}$$

$$= -0.167 \text{ mA} \cdot 1.03 \text{ k}$$

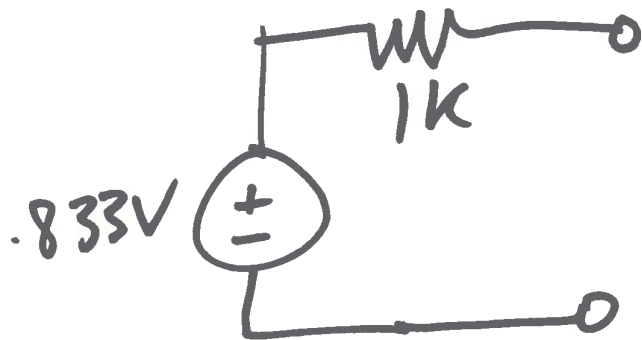
$$= \underline{\underline{-\frac{5}{31} \text{ V}}}$$




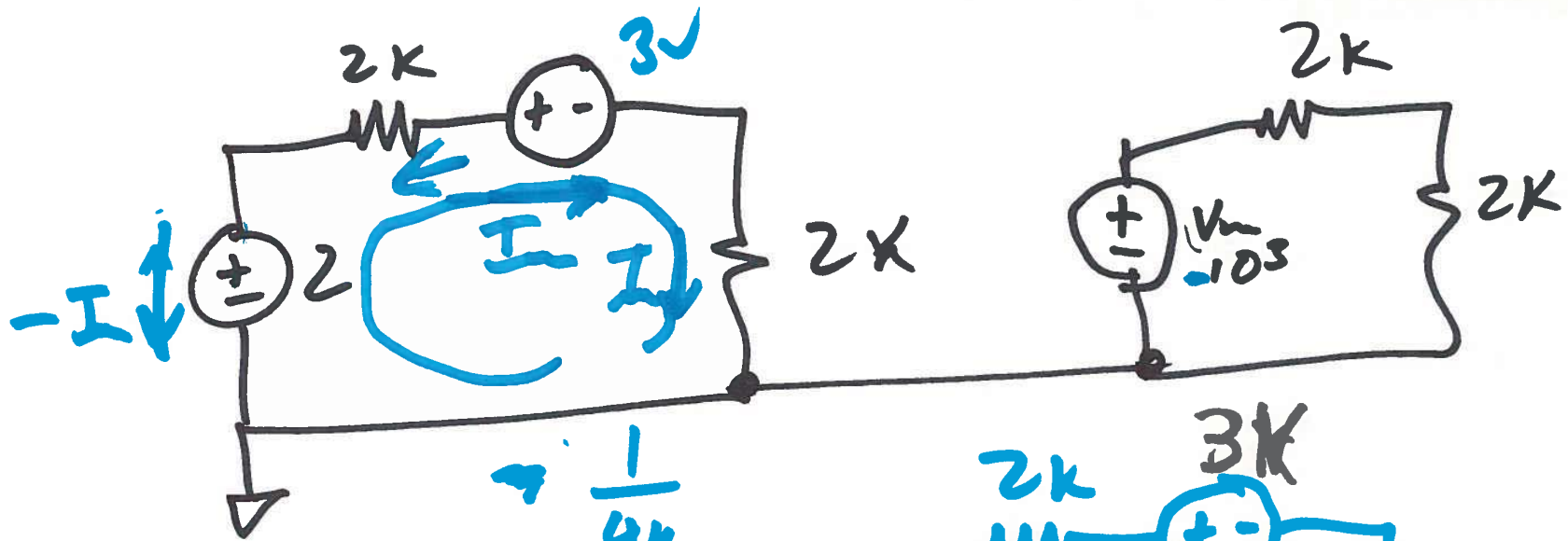


$\rightarrow \frac{1}{4k}$


$-\frac{1}{4k}$

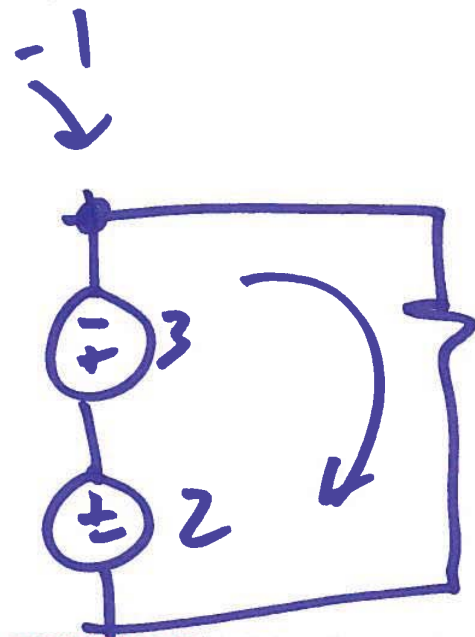

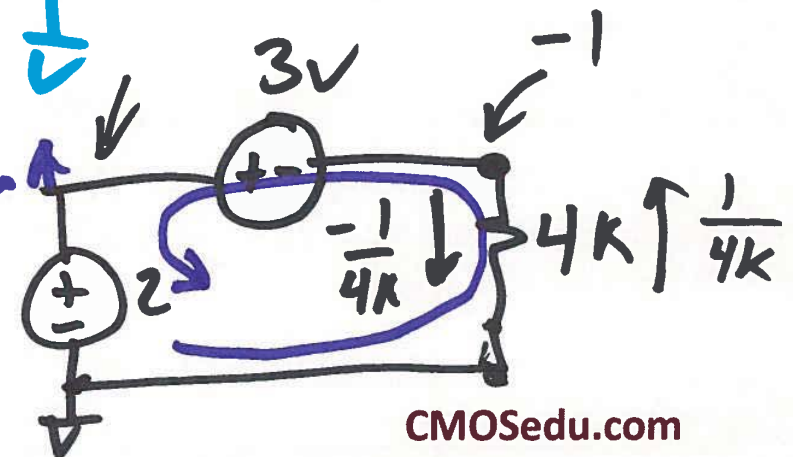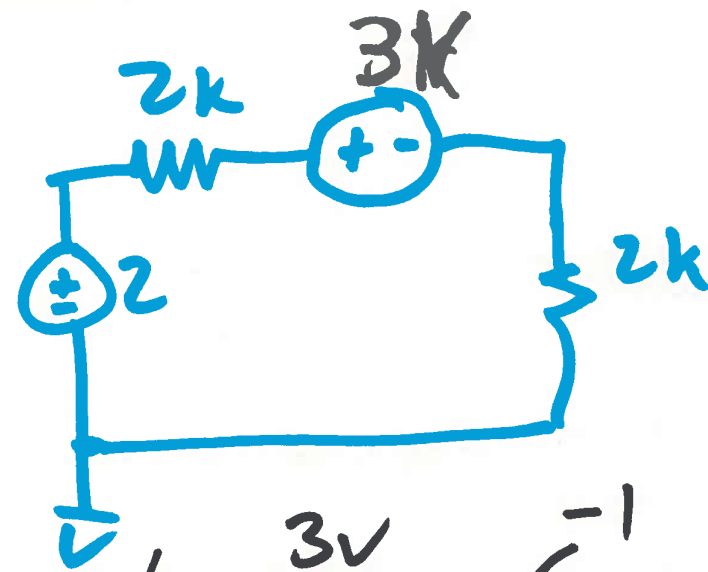$4k \downarrow \begin{matrix} + & - & 1 & - & 0 \\ & & 4k & & \end{matrix}$
 $= -\frac{1}{4}$



(b)

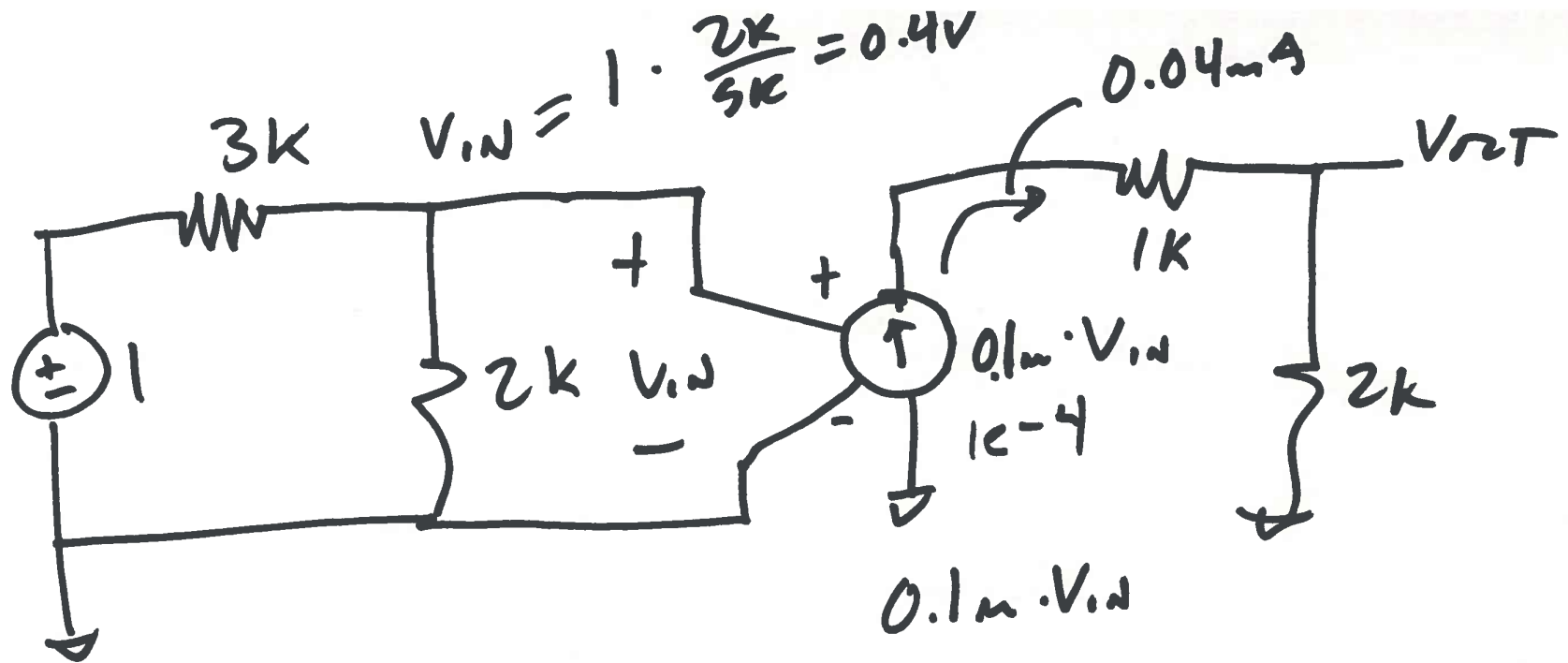

$$\begin{aligned}
 V_{out} &= 0.04mA \cdot 2k \\
 &= 0.08V \\
 &= \underline{\underline{80mV}}
 \end{aligned}$$

7)