
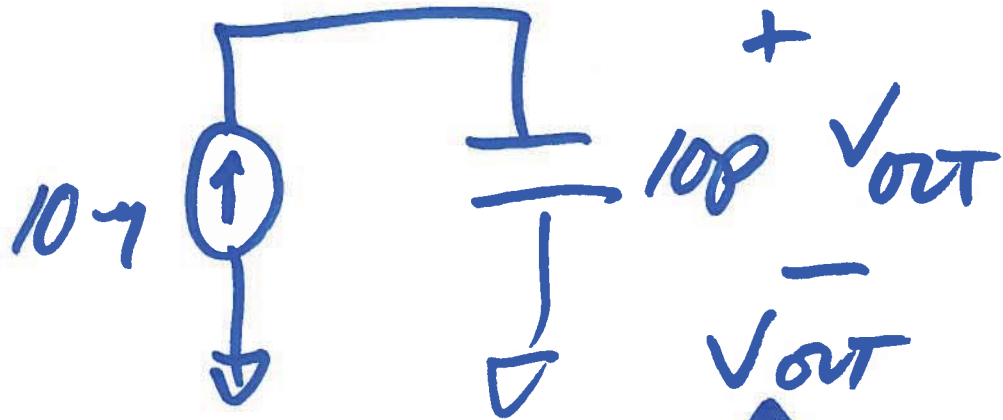


EE 220 Circuits II

Study Session III

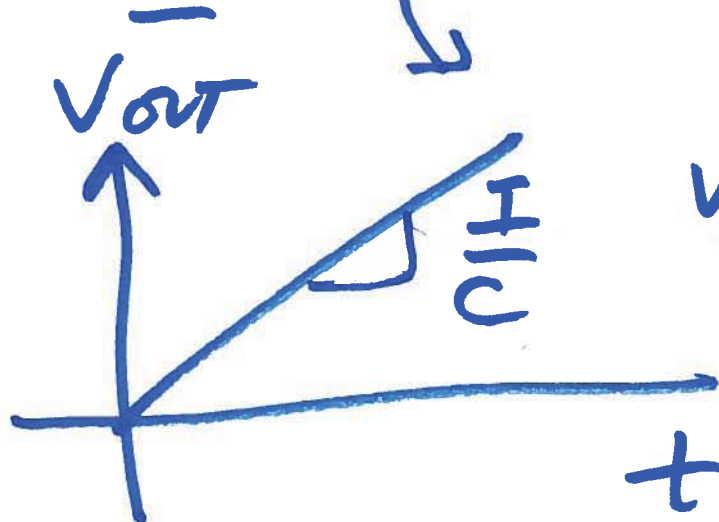

$$V = \frac{1}{C} \int i \cdot dt$$
$$I = C \frac{dV_{out}}{dt}$$





$$V_{out} = \frac{1}{C} \int_0^t I \cdot dt$$

$$V_{out} = \frac{10\text{mA}}{100} \cdot t$$

1)

C/I

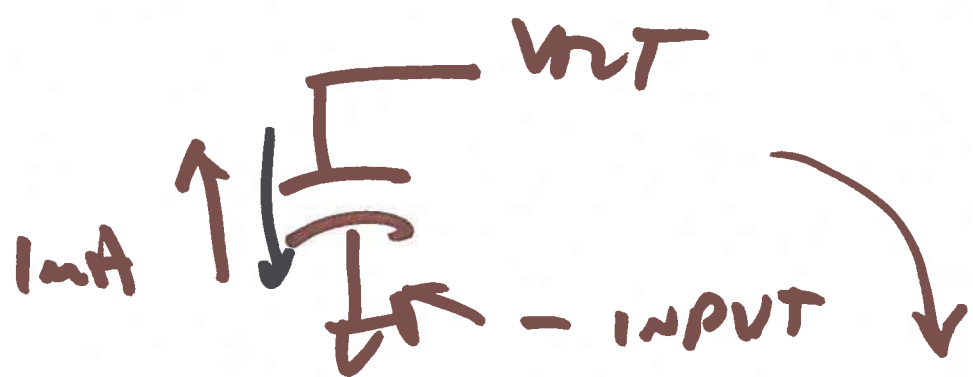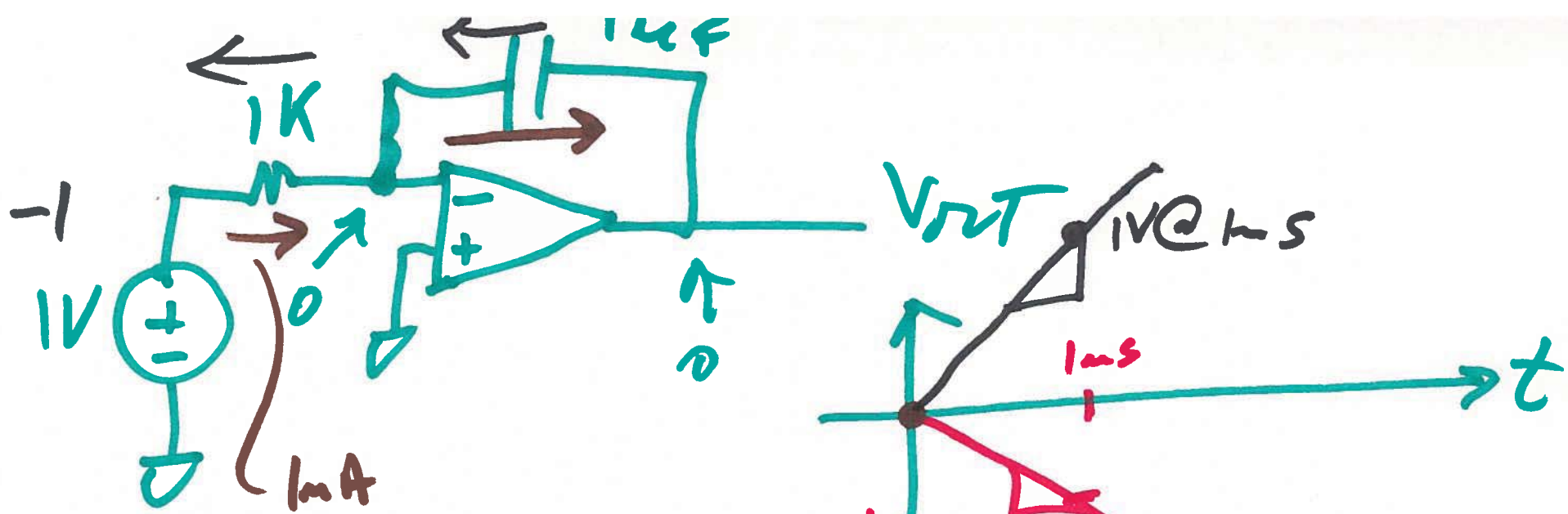


$$V_{out} = \frac{1}{C} \int_0^t -1mA dt$$

$$I \downarrow \frac{1}{C} \uparrow v \rightarrow \frac{1}{C} \int i \cdot dt = v$$

$$-i = C \frac{dv}{dt} \quad \frac{-1V}{ms} = 10^{-6} \frac{C}{V} \cdot t$$

2)

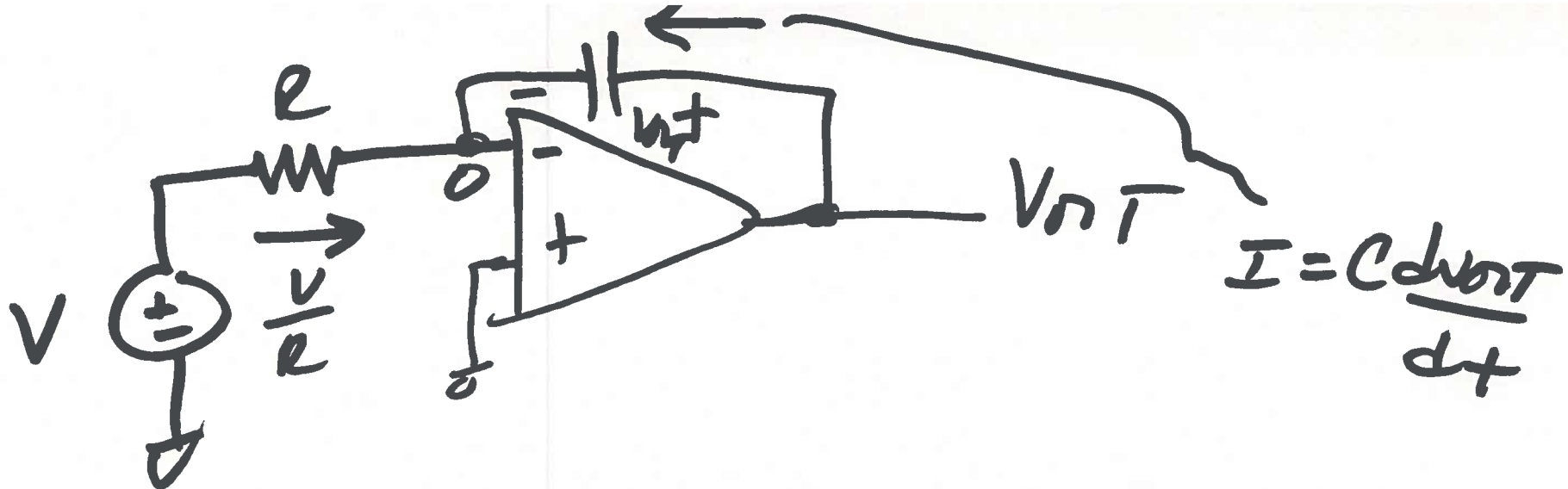


$$I \quad \frac{V}{R} + C \frac{dV_{out}}{dt} = 0$$

$$V_{out} = -\frac{(V/R)}{C} \cdot t$$

$$\left(\begin{aligned} C \frac{dV_{out}}{dt} &= -\frac{V}{R} \\ dV_{out} &= -\frac{V}{R} \cdot dt \end{aligned} \right)$$

3)

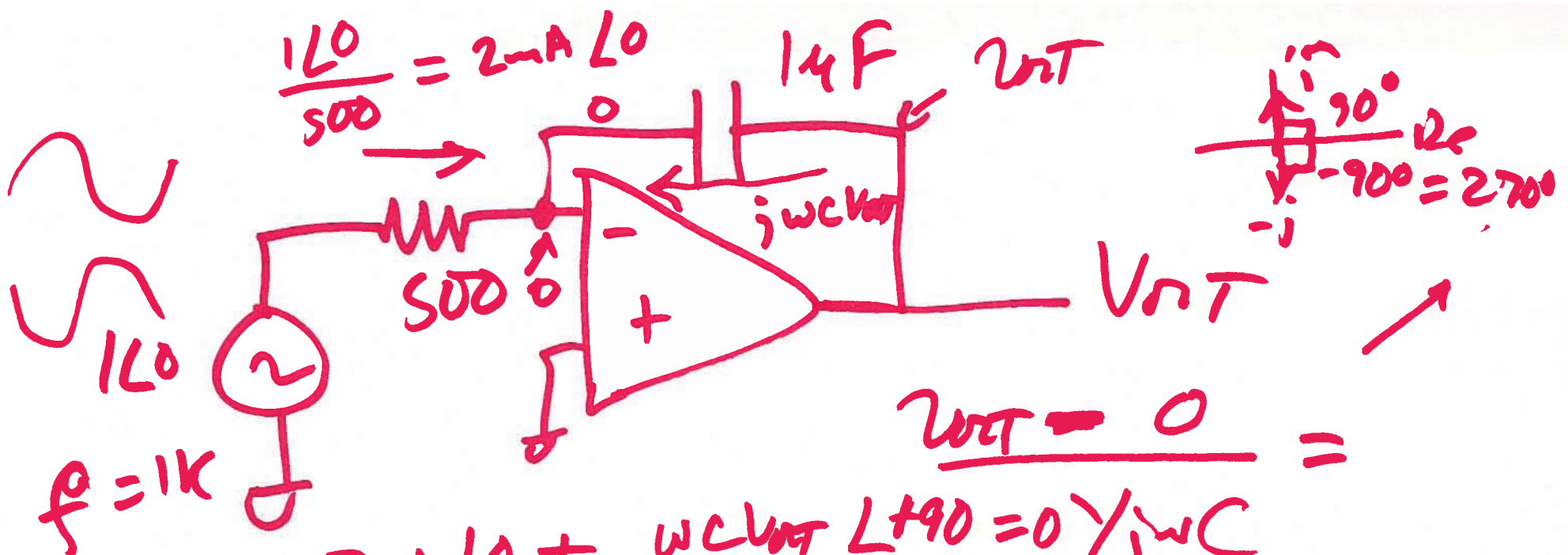

$$2mA L0 + \omega C V_{out} L+90 = 0 / j\omega C$$


$$2mA L0 = -j\omega C V_{out} = \omega C V_{out} L-90^\circ$$

$$2mA L0^\circ + \omega C V_{out} L90 = 0$$

$$2mA L0^\circ = -\omega C V_{out} L90^\circ$$

$$= \omega C V_{out} L-90^\circ$$

4)

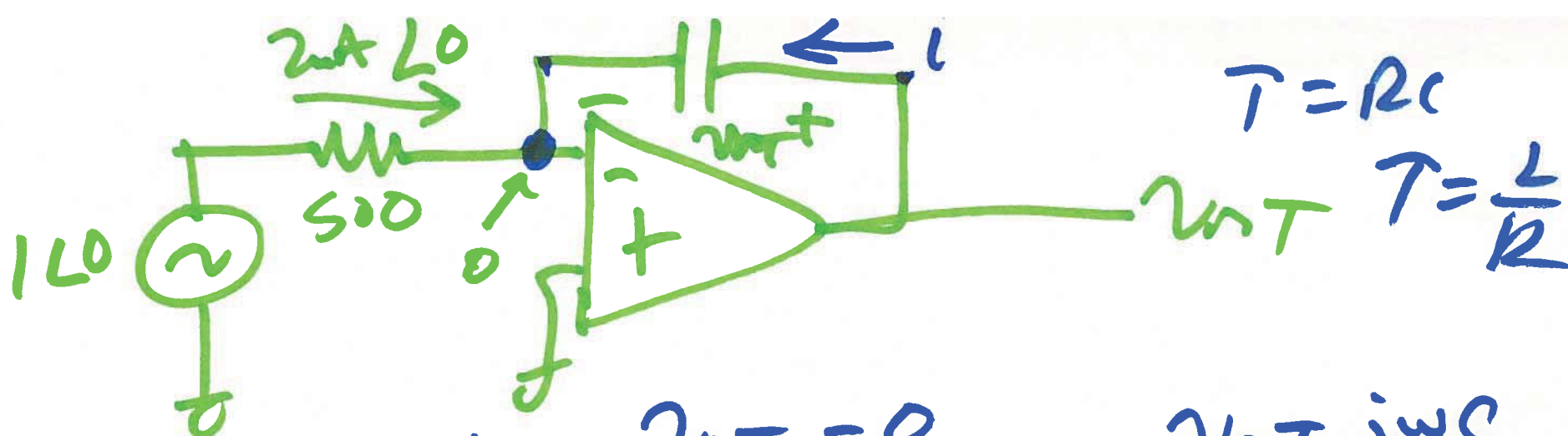

$$i = \frac{v_{in} - 0}{R} = v_{in} \cdot j\omega C$$

$$2mA \angle 0^\circ + 6.28 \cdot 10^{-3} \angle 90^\circ \frac{1}{j\omega C} = 0$$

$$2mA \angle 0^\circ = 6.28 \cdot 10^{-3} \angle 90^\circ$$

$$2mA \angle 0^\circ = v_{in} \cdot 6.28 \cdot 10^{-3} \angle 270^\circ$$

$$v_{in} = \frac{2 \cdot 10^{-3} \angle 0^\circ}{6.28 \cdot 10^{-3} \angle 270^\circ} = \frac{2}{6.28} \angle -270^\circ$$

$$= \frac{2}{6.28} \angle 90^\circ$$

$$= 318 \angle 90^\circ$$

5)


$$V_{in} = 1V \cdot \sin 2\pi \cdot 10^3 \cdot t$$

$$V_{out} = 0.318 \sin(2\pi \cdot 10^3 \cdot t + 90^\circ)$$

$$\theta = \frac{t_d}{T} \cdot 360$$




$$90^\circ = \frac{t_d}{1\mu s} \cdot 360$$

$$\frac{1\mu s}{4} = t_d = 250ns$$

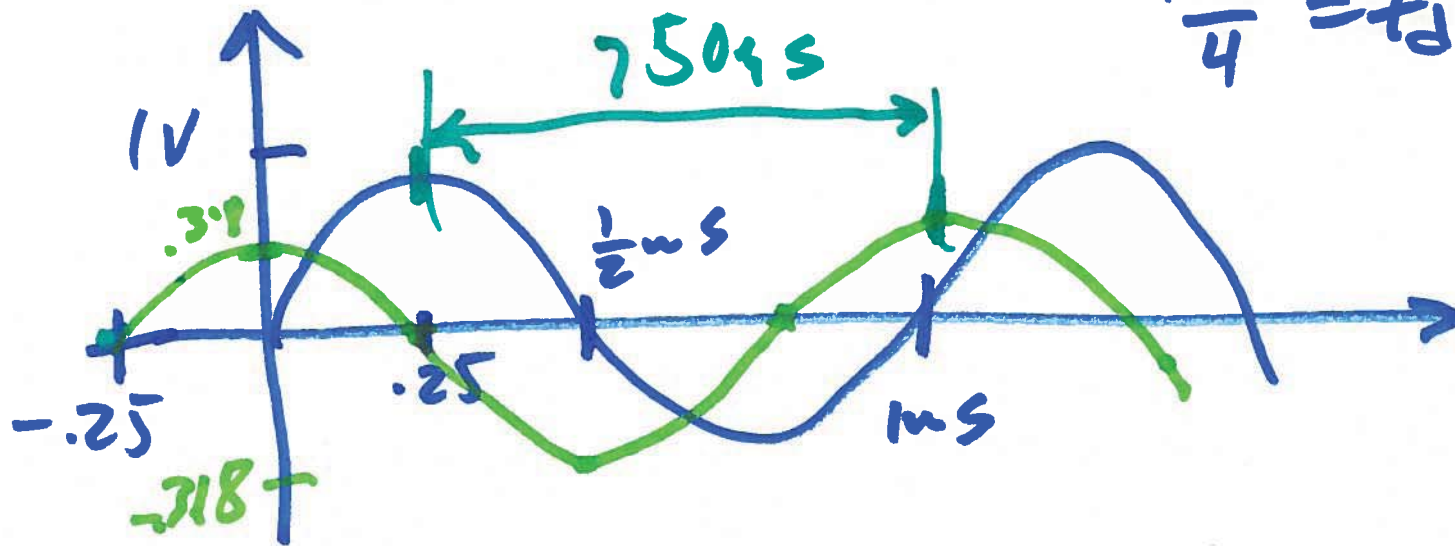

b)

Plot Frequency Response of

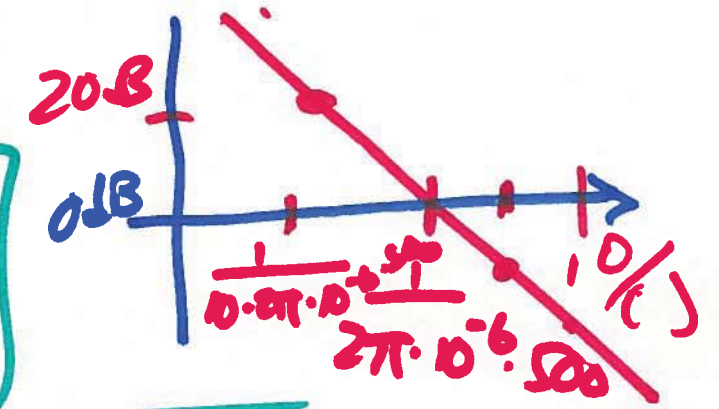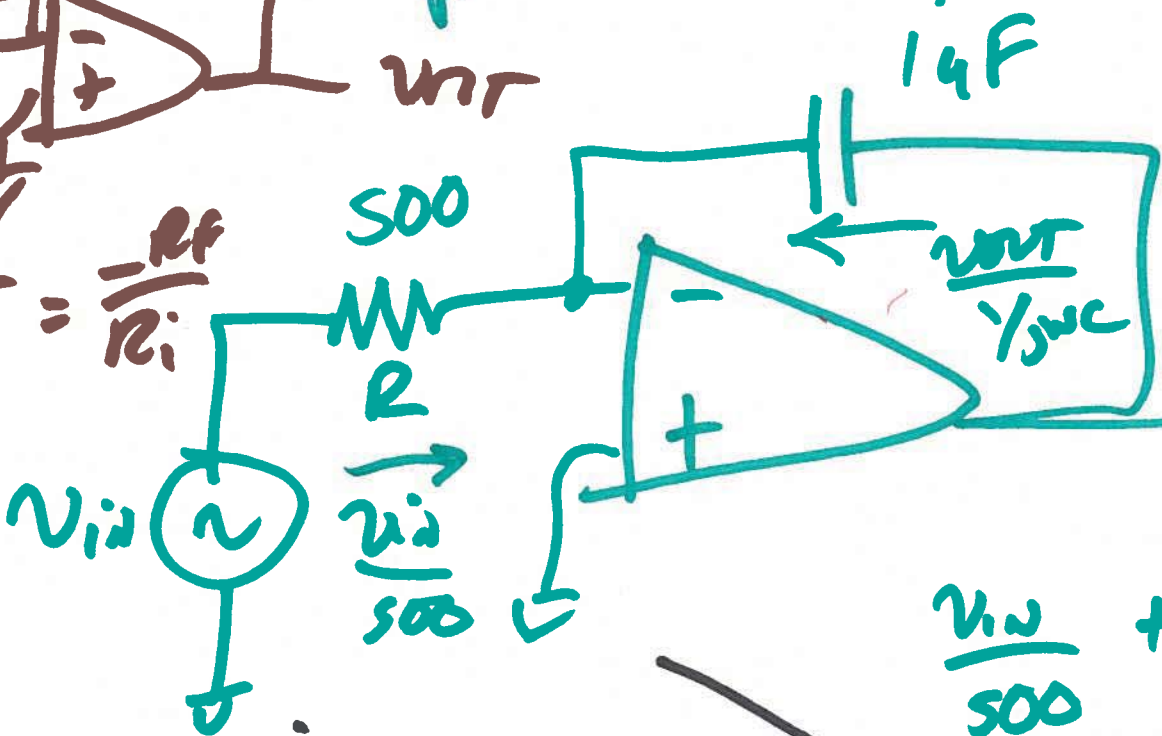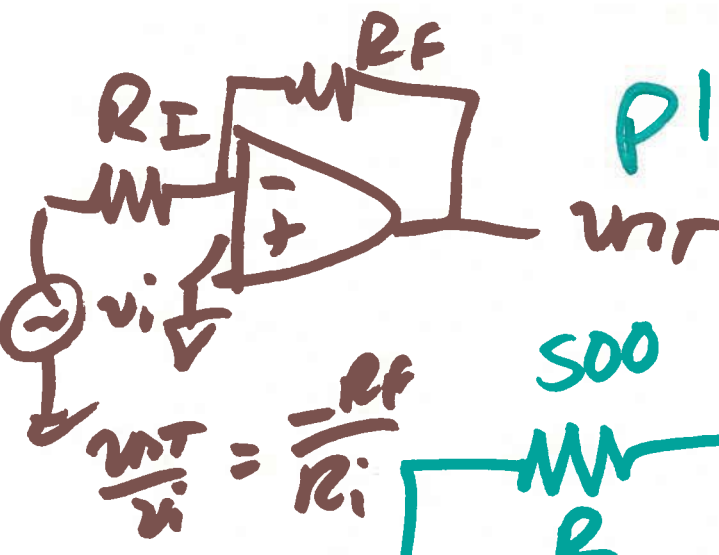

$$\frac{v_o}{500} + \frac{v_o T}{j\omega C_f} = 0$$

$$\frac{v_o T}{v_i} = \frac{j}{2\pi \cdot 10^{-6} \cdot 500 \cdot f}$$

$$\frac{v_o T}{v_i} = - \frac{j\omega C_f}{500}$$

$$\left| \frac{v_o T}{v_i} \right| = \frac{1}{2\pi \cdot 10^{-6} \cdot 500} \cdot \frac{1}{f} = \frac{1}{2\pi \cdot 10^{-6} \cdot 500} \cdot \frac{1}{f} = \frac{1}{j \cdot \pi f \cdot 10^{-6} \cdot 500}$$

$$\angle \frac{v_o T}{v_i} = 90^\circ$$


7)

$$v_{in} = 2 \sin(2\pi \cdot 30 \cdot t)$$

$$v_{out} = 20 \cdot \sin(2\pi \cdot 30 \cdot t + 90)$$

$$-\frac{44}{23} + 2$$

$$-\frac{44}{23} + 2k \cdot I_x$$

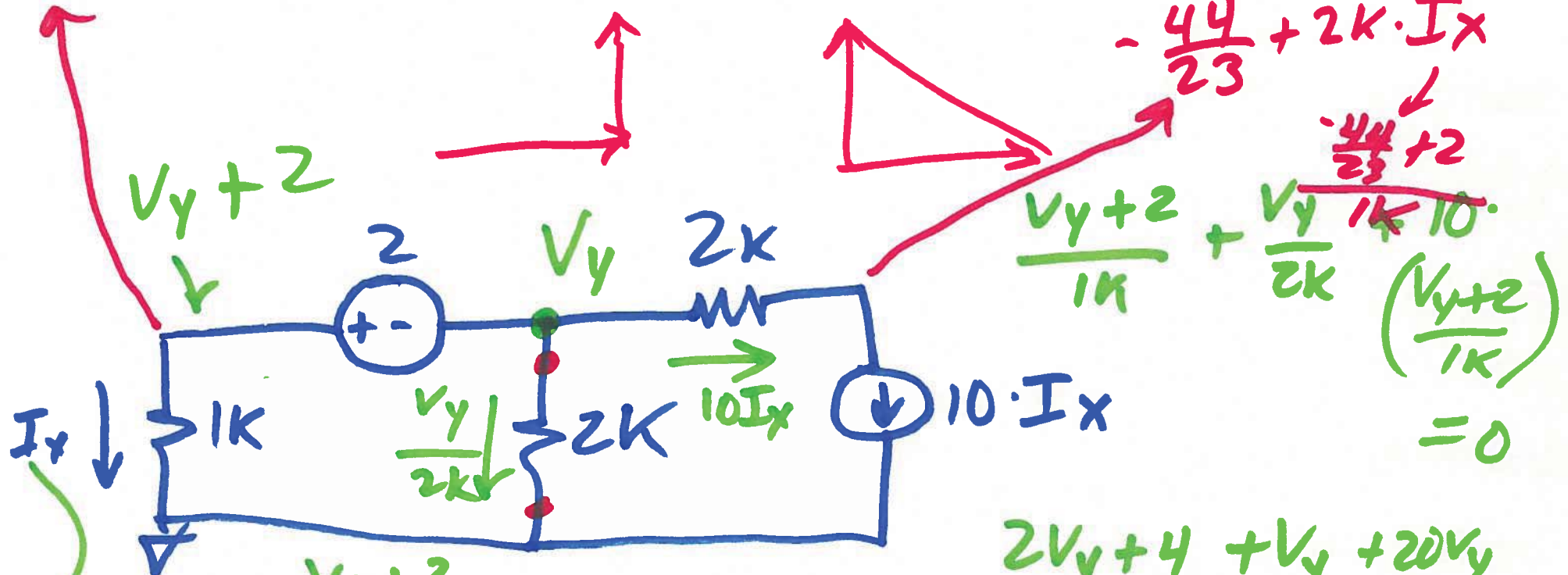


$$\frac{v_y + 2}{1k} + \frac{v_y}{2k} - 10 \cdot \left(\frac{v_y + 2}{1k}\right) = 0$$

$$2v_y + 4 + v_y + 20v_y + 40 = 0$$

$$23v_y = -44$$

$$v_y = -\frac{44}{23}$$


8)

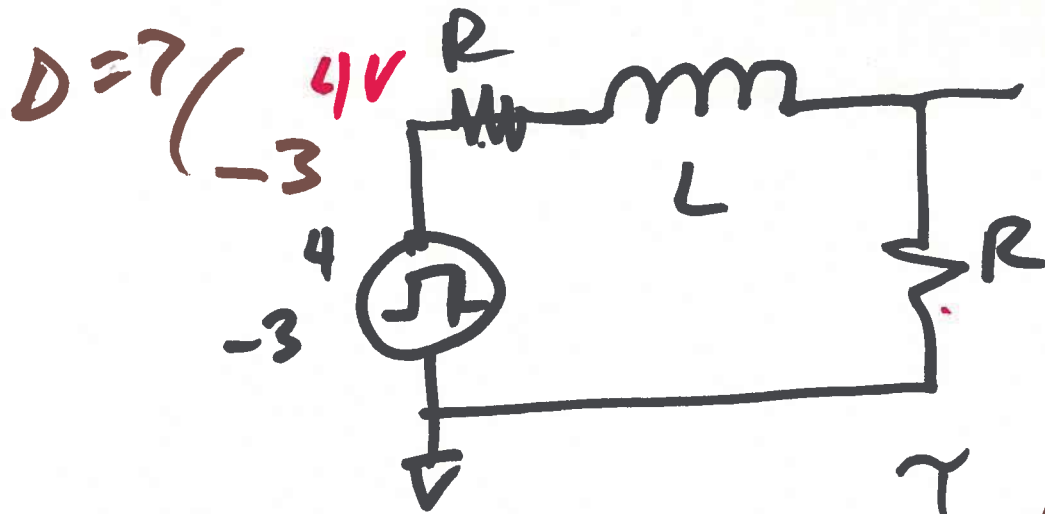


$20\mu T$ $2V$ -1.5 $\Delta = 3.5$

$$V_f + (V_i - V_f) e^{-t/\tau}$$

$T \gg \frac{L}{2R} = \tau$

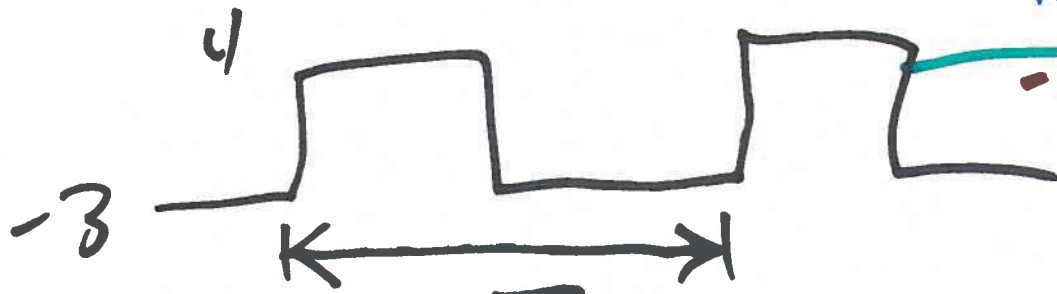


$$f = \frac{1}{T}$$

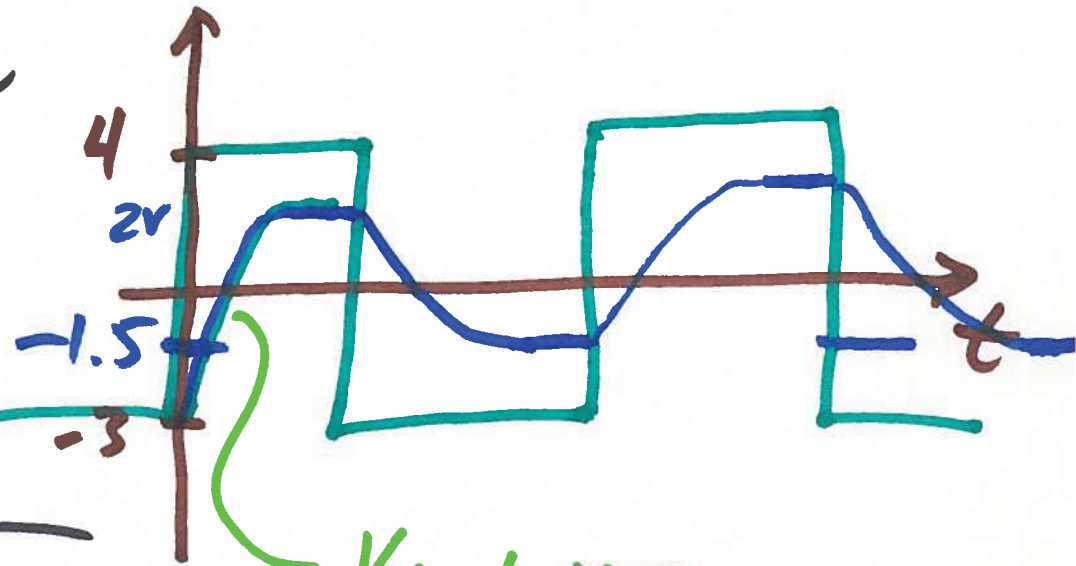

$V_f + \dots$

$$V_i + V_f (1 - e^{-t/\tau})$$

9)

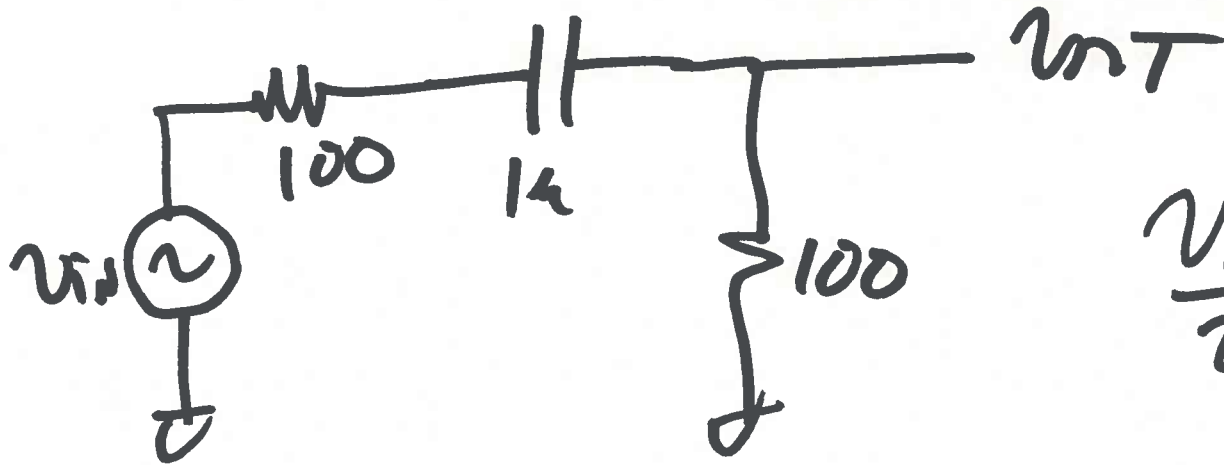


$$\frac{u_{VT}}{u_s} = \frac{100}{200 + \frac{1}{j\omega \cdot 10^{-6}}}$$

$$\frac{u_{VT}}{u_s} = \frac{0 + j \cdot \omega \cdot 100 \cdot 10^{-6}}{1 + j\omega \cdot 200 \cdot 10^{-6}} = \frac{0 + j \frac{f}{1.59k}}{1 + j \frac{f}{796}}$$

$$\left| \frac{u_{VT}}{u_s} \right| = \frac{\frac{f}{1.59k}}{\sqrt{1 + \left(\frac{f}{796}\right)^2}} \quad \angle \frac{u_{VT}}{u_s} = 90 - \tan^{-1} \frac{f}{796}$$


$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{f}{1.59k} \sqrt{1 + \left(\frac{f}{796} \right)^2}$$
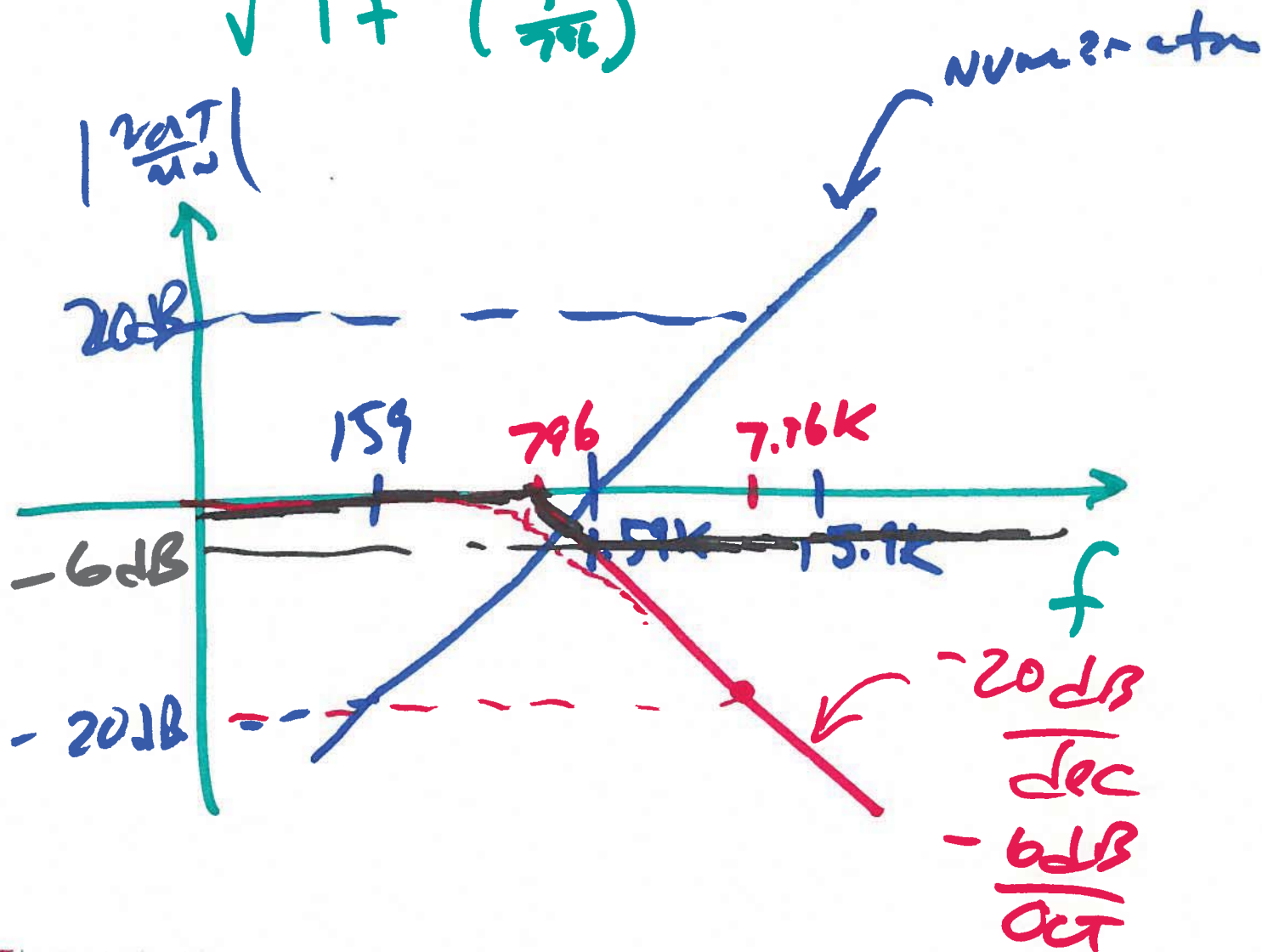
$$20 \log \frac{1}{\sqrt{2}} = -3 \text{ dB}$$




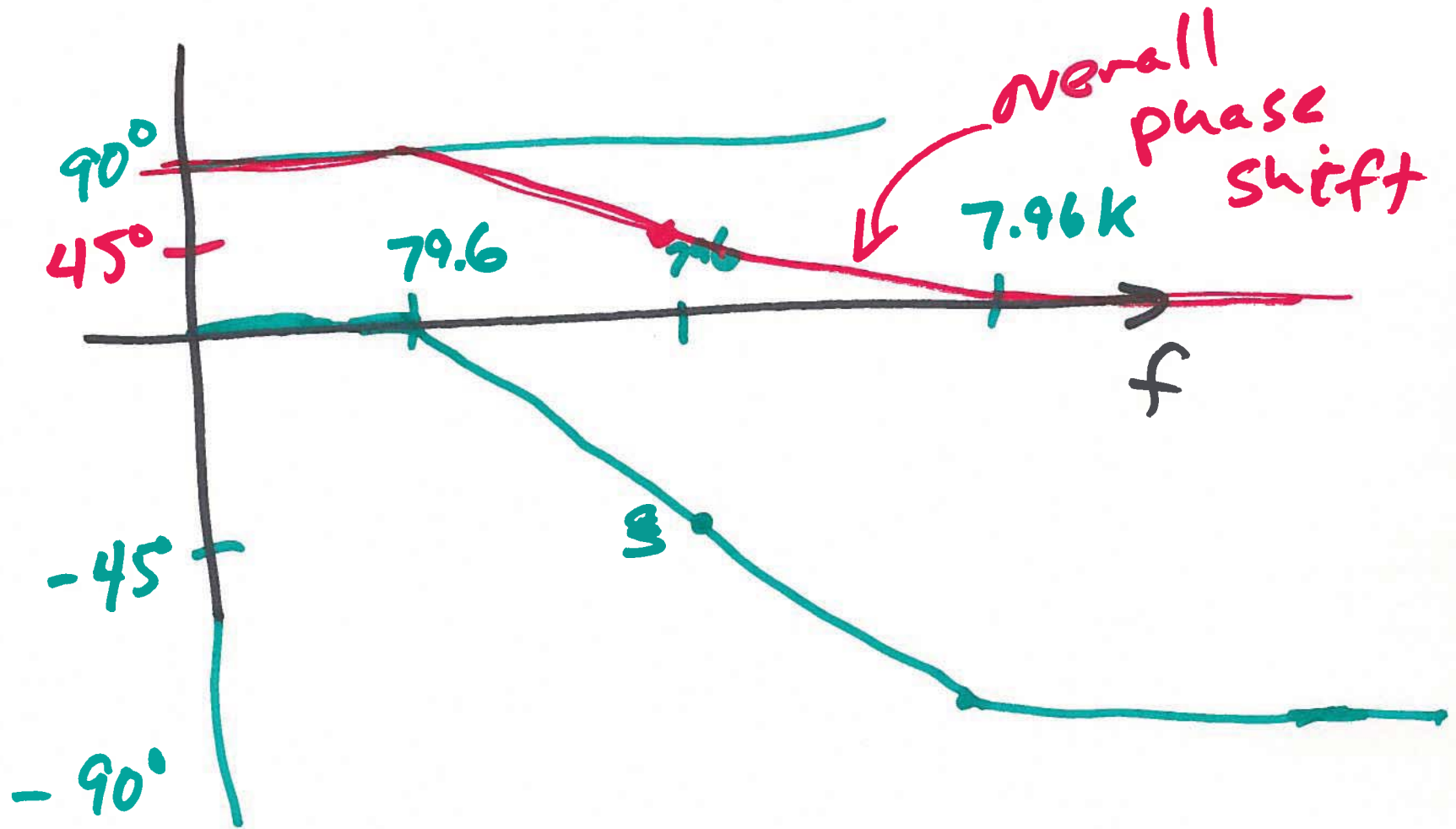11)

$$\angle \frac{V_{out}}{V_{in}} = 90 + \left(-\tan^{-1} \frac{f}{796} \right)$$



12)

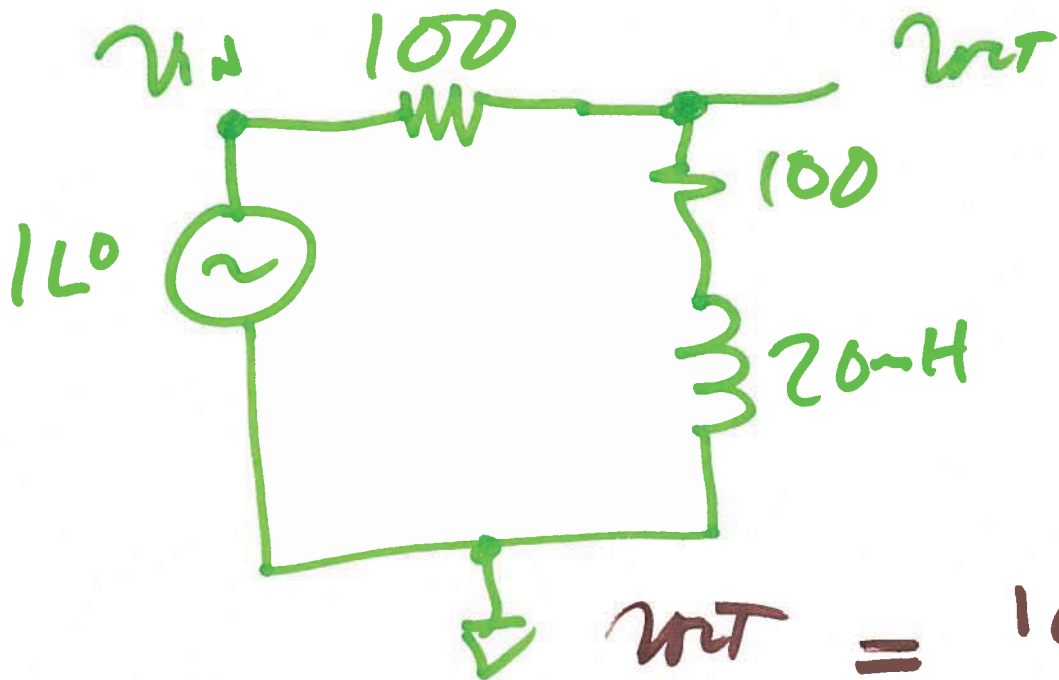

$$\frac{v_{nT}}{v_n} = \frac{100 + j\omega 20\text{mH}}{200 + j\omega 20\text{mH}}$$

$j\omega L$

$$\frac{v_{nT}}{v_n} = \frac{100}{200} \cdot \frac{1 + j\omega \frac{20\text{mH}}{100}}{1 + j\omega \frac{20\text{mH}}{200}}$$

$$\frac{1}{2\pi \cdot \frac{20\text{mH}}{100}} = 796$$

$$\frac{1}{2\pi \cdot \frac{20\text{mH}}{200}} = \cancel{796} \cdot 2 = 1.59\text{k}$$

$$= \frac{1}{2} \cdot \frac{1 + j \frac{f}{796}}{1 + j \frac{f}{1.59\text{k}}}$$


13)


$$\left| \frac{v_{out}}{v_{in}} \right| = 20 \log \frac{1}{2} + 20 \log \sqrt{1 + \left(\frac{f}{796} \right)^2}$$

-6dB ←

$$- 20 \log \sqrt{1 + \left(\frac{f}{1.59k} \right)^2}$$
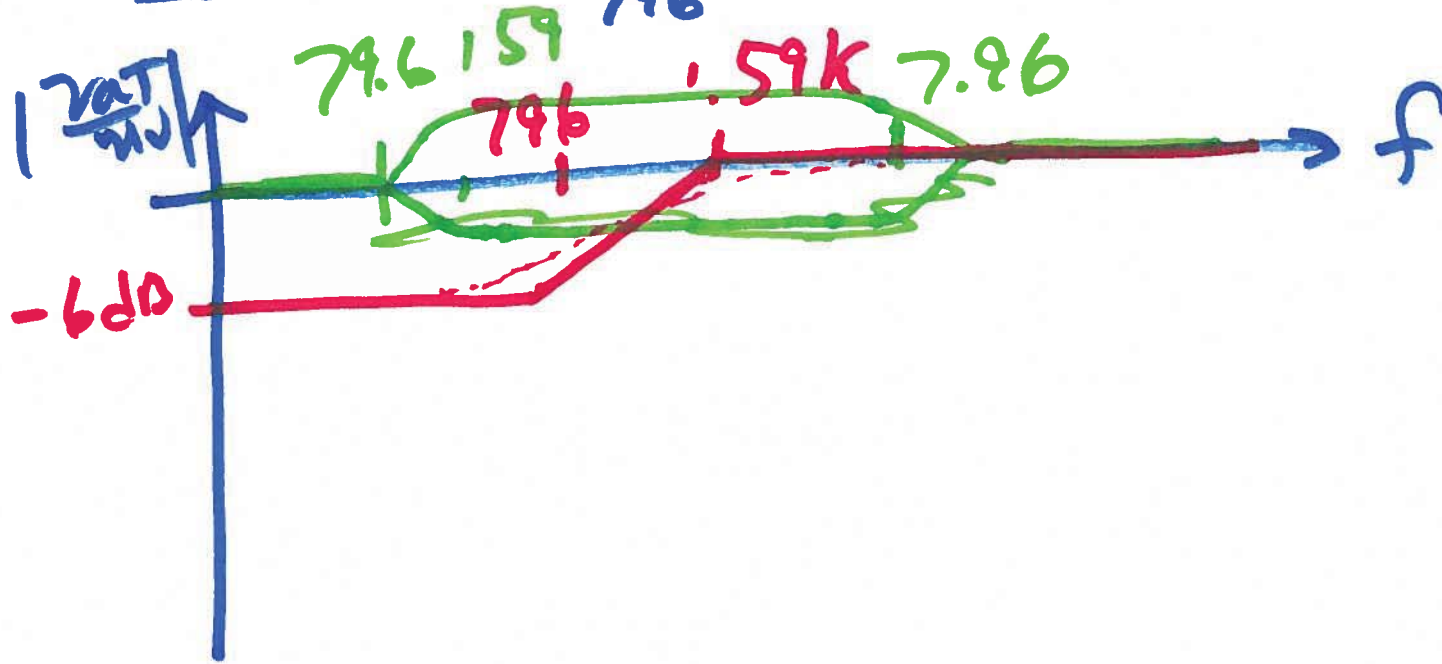
$$20 + \tan^{-1} \frac{f}{796} - \tan^{-1} \frac{f}{1.59k}$$



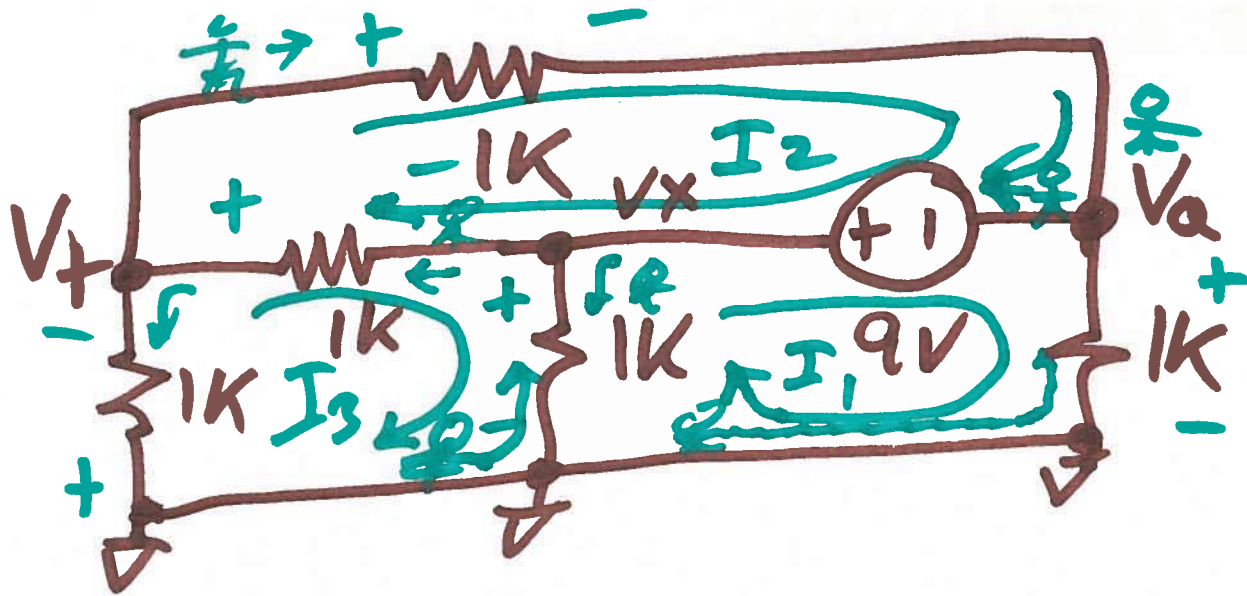

$$9V - 1k(I_3 - I_1) + 1k \cdot I_1 = 0$$

$$9V + 1k(I_3 - I_2) - I_2 \cdot 1k = 0$$

$$1k(I_3 - I_1) + 1k(I_3 - I_2) + 1k \cdot I_3 = 0$$