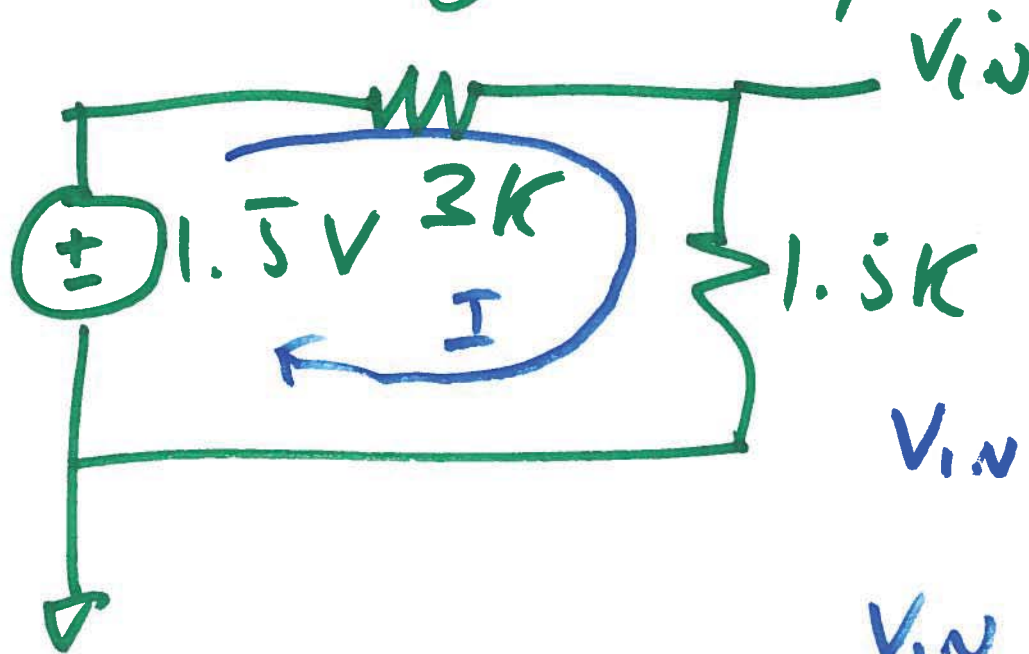


EE 220 circuits 1

~~###~~ Lecture 12

OCT. 9, 2017



$$I = \frac{1.5}{3k + 1.5k}$$

$$V_{IN} = I \cdot 1.5k$$

$$V_{IN} = 1.5 \cdot \frac{1.5k}{3k + 1.5k}$$

$$V_{IN} = 0.5V$$


1)

$0.0001 = 1e^{-4} = 0.1e^{-3} = 0.1m = 100 \mu$



1E4

$R_{TH} = \infty$
 $V_{OC} = \infty$

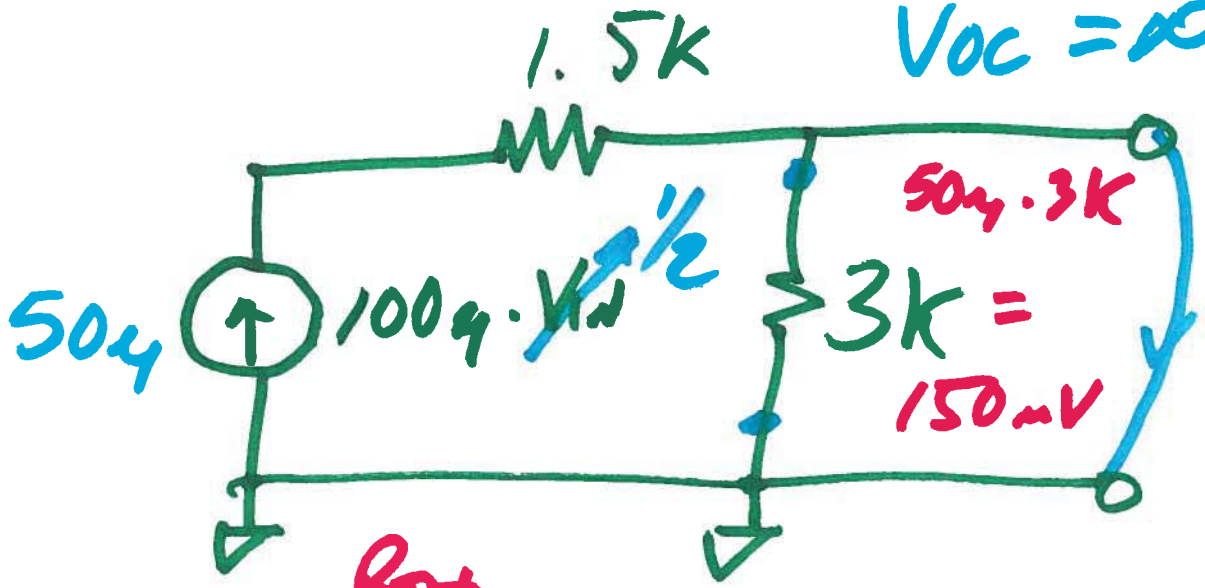$I_{sc} = \frac{V_{oc}}{R_{TH}}$
 $= \frac{\infty}{\infty}$



$I_{sc} = 50 \mu A$

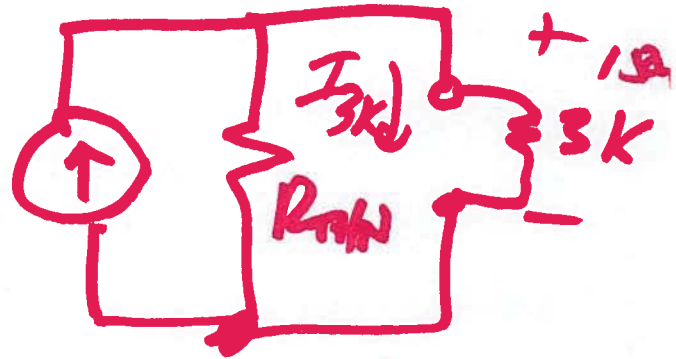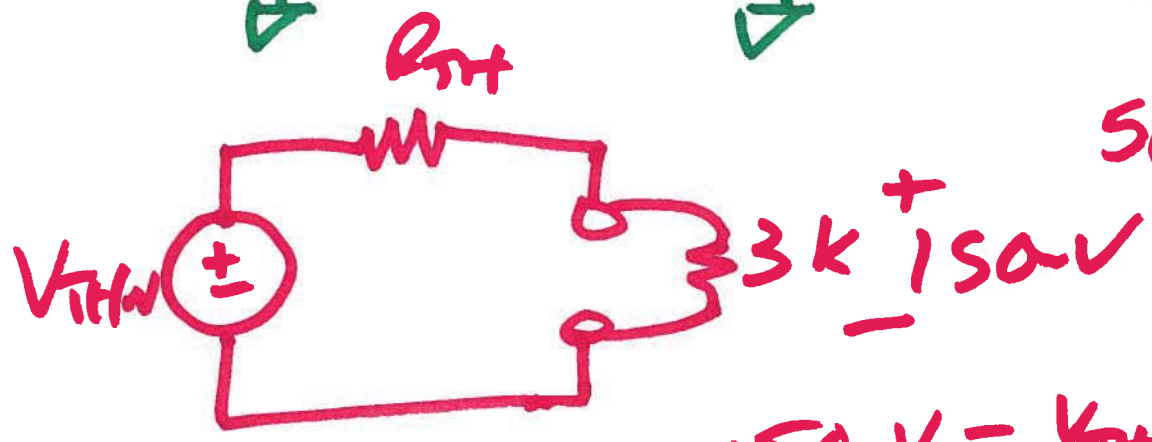

$150 \mu V = V_{TH} \cdot \frac{3K}{3K + R_{TH}}$

$I_{3K} = 50 \mu A \cdot \frac{R_{TH}}{R_{TH} + 3K}$

2)

$$\frac{150\mu\text{V}}{3\text{K}} = I_{3\text{K}} = 50\mu\text{A} \cdot \frac{R_{\text{TH}}}{R_{\text{TH}} + 3\text{K}}$$

$$\frac{150 \cdot 10^{-3}}{3 \cdot 10^3}$$

$$50\mu\text{A} \cdot R_{\text{TH}} + 150\mu\text{V} = 50\mu\text{A} \cdot R_{\text{TH}} + 150\mu\text{V}$$

$$\frac{150 \cdot 10^{-6}}{3 \cdot 10^0}$$

$$150\mu\text{V} = V_{\text{TH}} \cdot \frac{3\text{K}}{3\text{K} + R_{\text{TH}}}$$

$$\frac{150\mu\text{V}}{3\text{K}}$$

$$= 50\mu\text{A}$$


$$150\mu\text{V}(3\text{K} + R_{\text{TH}}) = V_{\text{TH}} \cdot 3\text{K}$$

$$3\text{K} + R_{\text{TH}} = V_{\text{TH}} \cdot \frac{3\text{K}}{150\mu\text{V}}$$

$$3\text{K} + R_{\text{TH}} = \frac{V_{\text{TH}}}{50\mu\text{A}}$$

$$R_{\text{TH}} = \frac{V_{\text{TH}}}{50\mu\text{A}} - 3\text{K}$$

3)

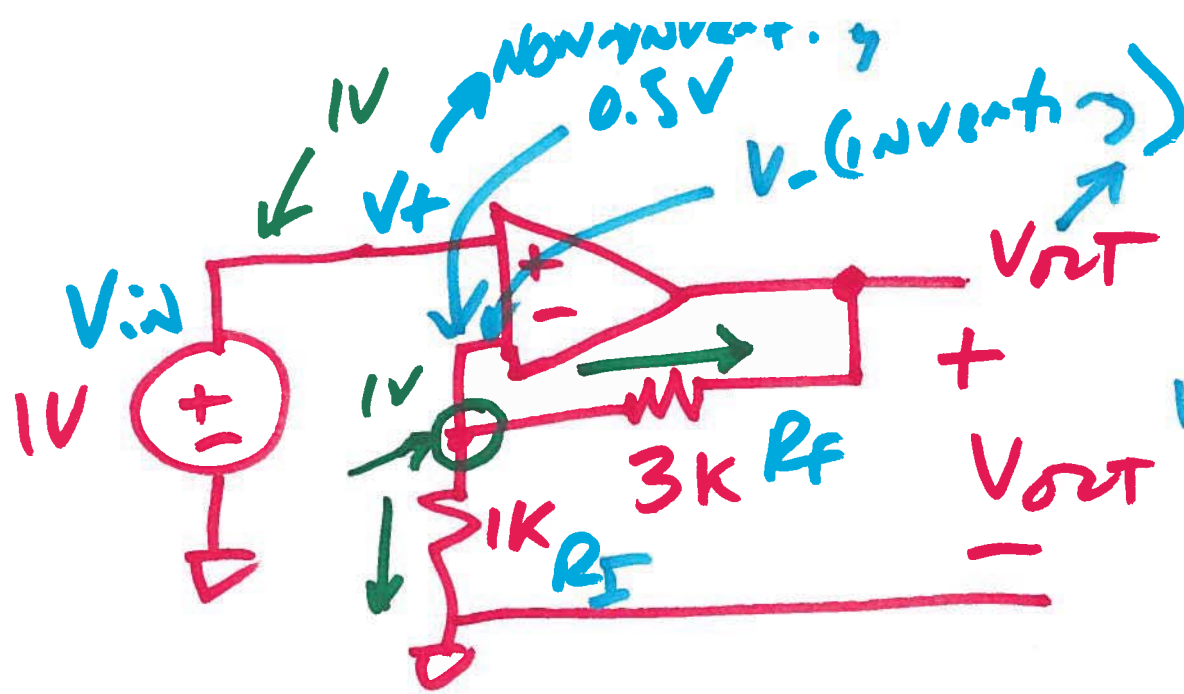

$$V_{out} = A_v (V_+ - V_-)$$

$$V_{out} = \infty \cdot \left(1 - \frac{1}{\beta}\right)$$

$$\frac{V_{out}}{V_{in}} = \frac{R_f + R_i}{R_i}$$

$$= 1 + \frac{R_f}{R_i}$$

$$\frac{V_{in}}{R_i} + \frac{1 - V_{out}}{3k R_f} = 0$$

$$3V + 1V - V_{out} = 0$$


$V_{out} = 4V$

NON-INVERTING

Memorize these

4)

NON-INVERTING

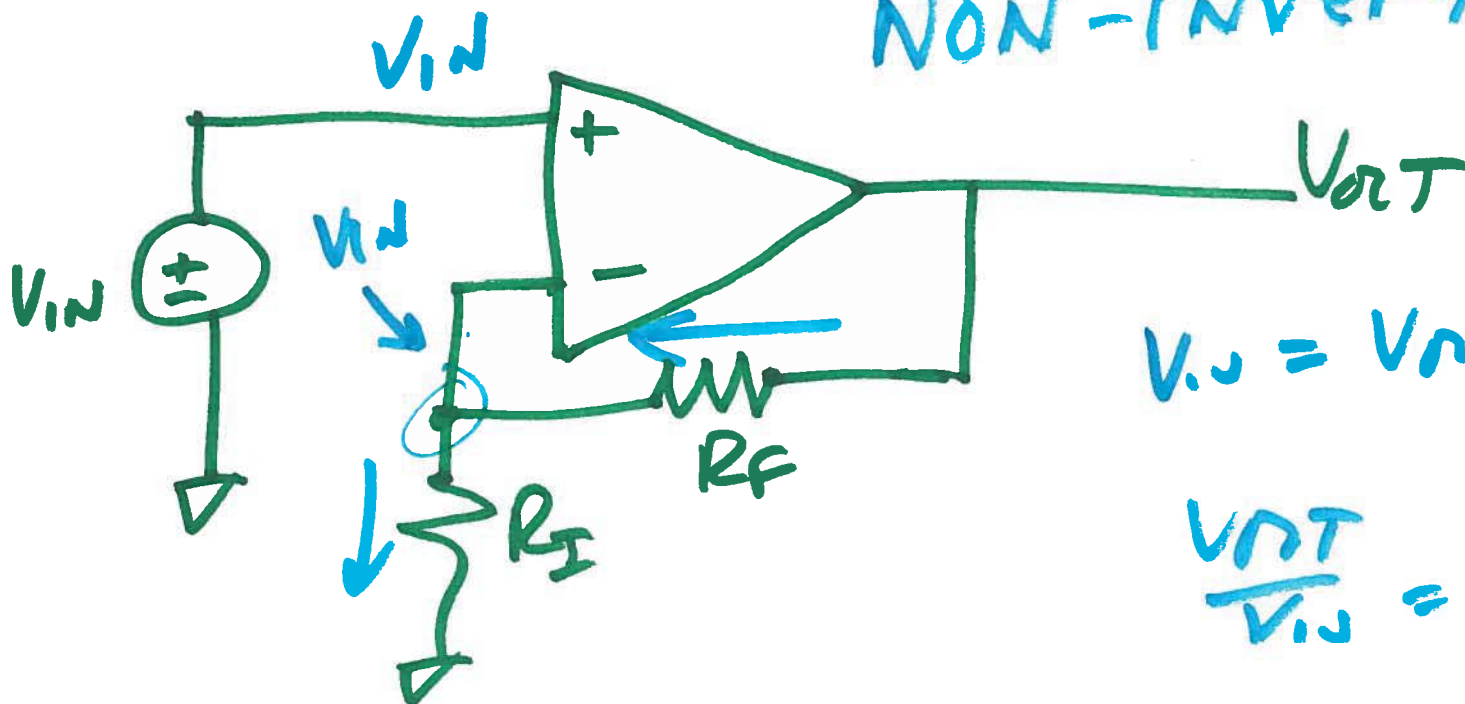

$$V_{in} = V_{out} \cdot \frac{R_I}{R_I + R_F}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_I + R_F}{R_I}$$


$$= 1 + \frac{R_F}{R_I}$$

$$\frac{V_{in}}{R_I} = \frac{V_{out} - V_{in}}{R_F}$$

$$V_{in} \left(\frac{1}{R_I} + \frac{1}{R_F} \right) = \frac{V_{out}}{R_F} \Rightarrow \frac{V_{out}}{V_{in}} = \underline{\underline{1 + \frac{R_F}{R_I}}}$$

5)

NON-ideal op-amp

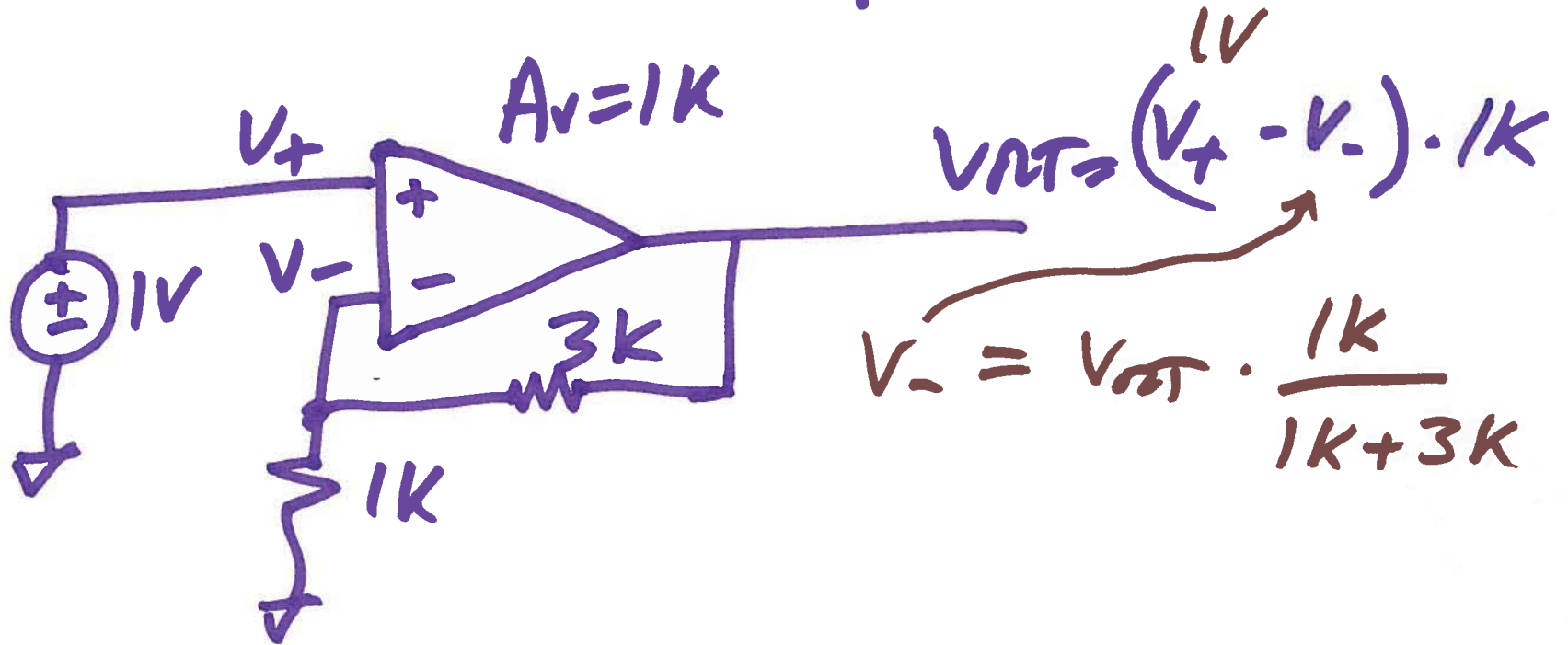


$$V_{VT} = (V_+ - V_-) \cdot 1k$$

$$V_- = V_{out} \cdot \frac{1k}{1k + 3k}$$

$$V_{VT} = \left(1 - V_{out} \cdot \frac{1k}{1k + 3k}\right) \cdot 1k$$


Inverting

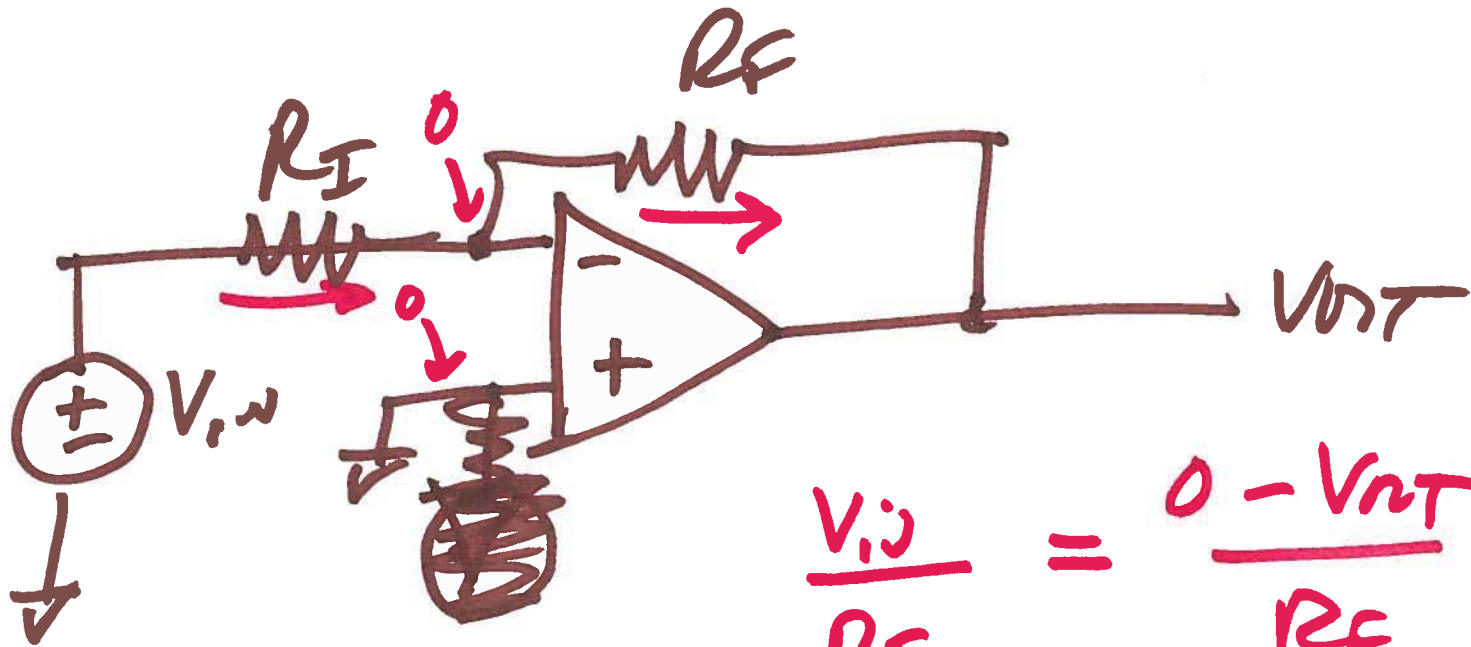

$$\frac{V_{in}}{R_I} = \frac{0 - V_{out}}{R_F}$$

$$\frac{V_{out}}{V_{in}} = -\frac{R_F}{R_I}$$

1)

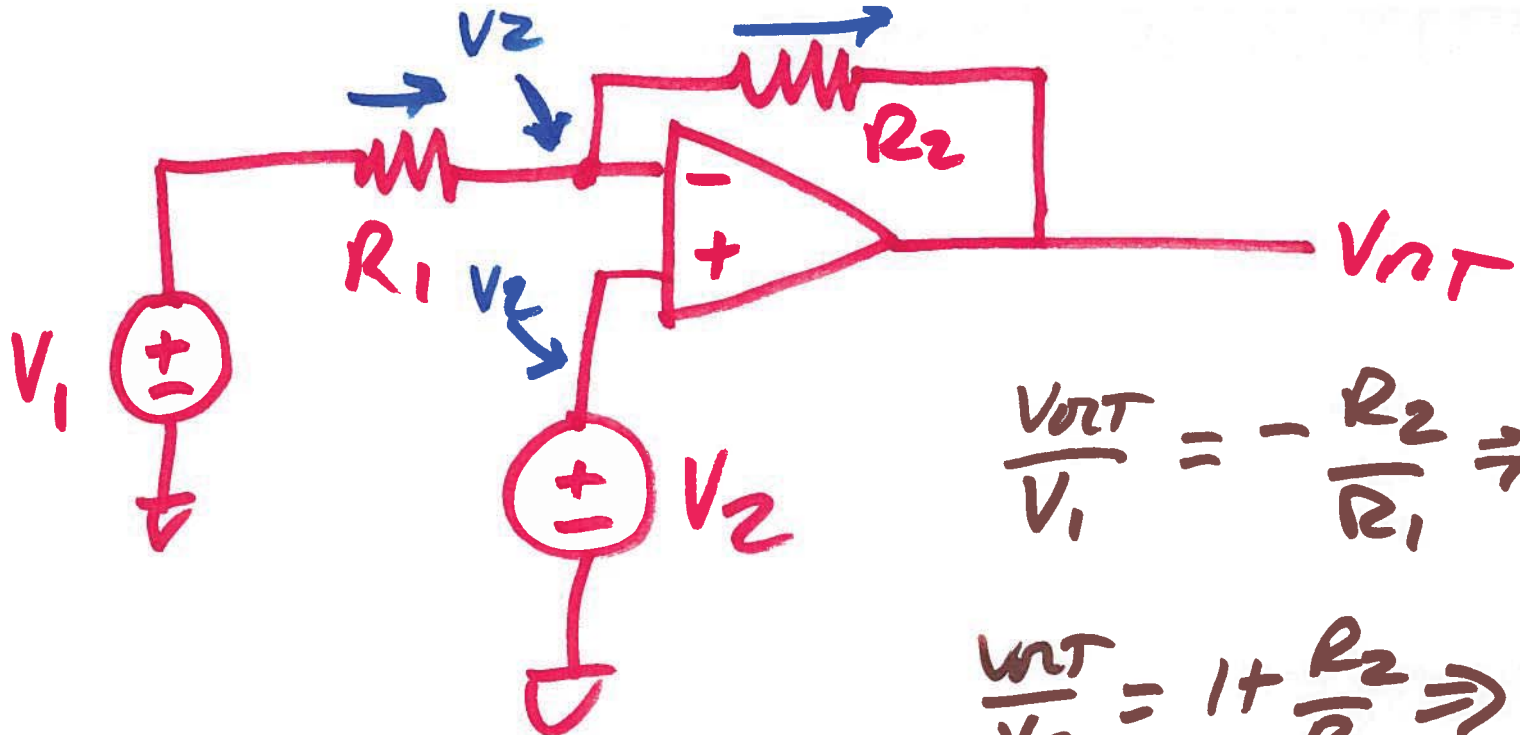

$$\frac{V_{out}}{V_1} = -\frac{R_2}{R_1} \Rightarrow V_{out} = -\frac{R_2}{R_1} \cdot V_1$$

$$\frac{V_{out}}{V_2} = 1 + \frac{R_2}{R_1} \Rightarrow V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_2$$



$$\frac{V_1 - V_2}{R_1} = \frac{V_2 - V_{out}}{R_2}$$

$$V_{out} = -\frac{R_2}{R_1} \cdot V_1 + \left(1 + \frac{R_2}{R_1}\right) V_2$$

$$\frac{R_2}{R_1} V_1 - \frac{R_2}{R_1} V_2 = V_2 - V_{out}$$

8)

Voltage follower

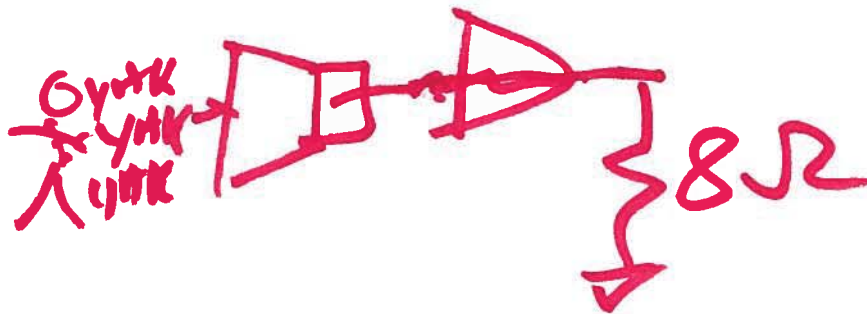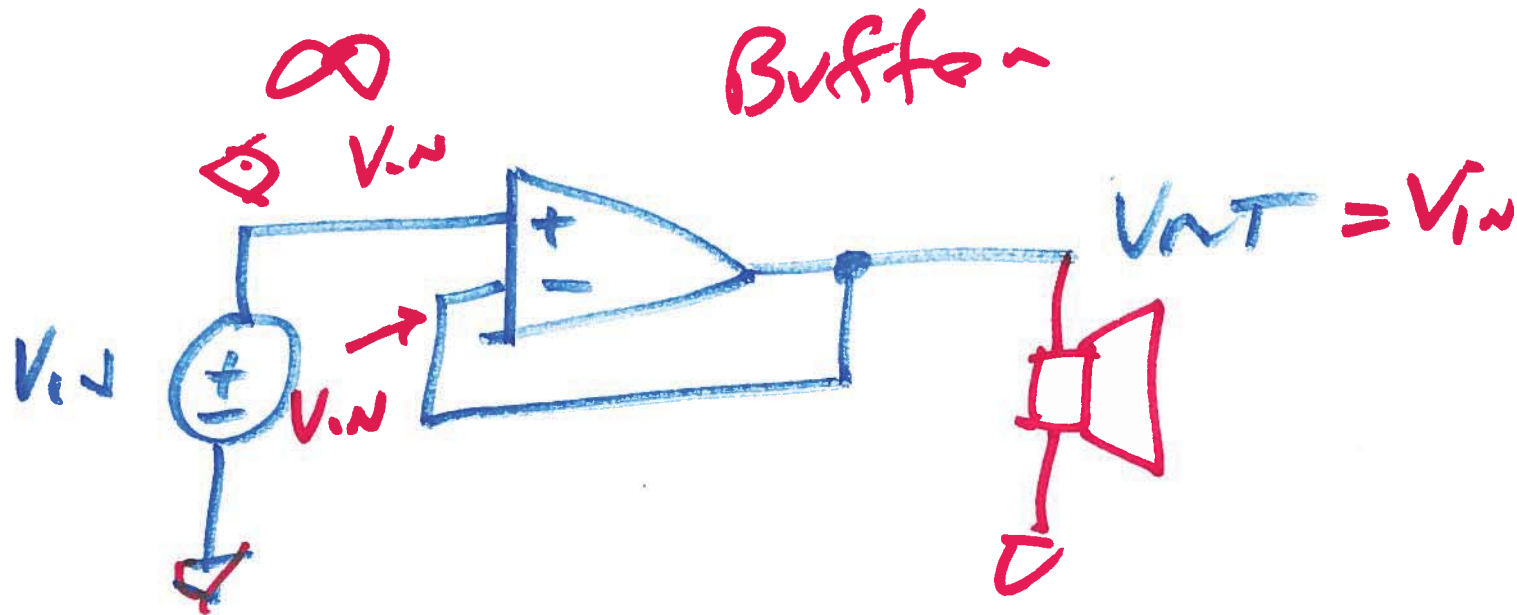

a)