

EE 220 Circuits 1

Lecture 16

OCTOBER 25, 2017


$$i(t) = \frac{1 \mu\text{A}}{1 \mu\text{s}} \cdot t = t$$

$$i = C \frac{dv}{dt}$$

$$V = \frac{1}{C} \int_0^t i dt$$

$$V = \frac{1}{10 \text{ pF}} \frac{1}{2} t^2$$
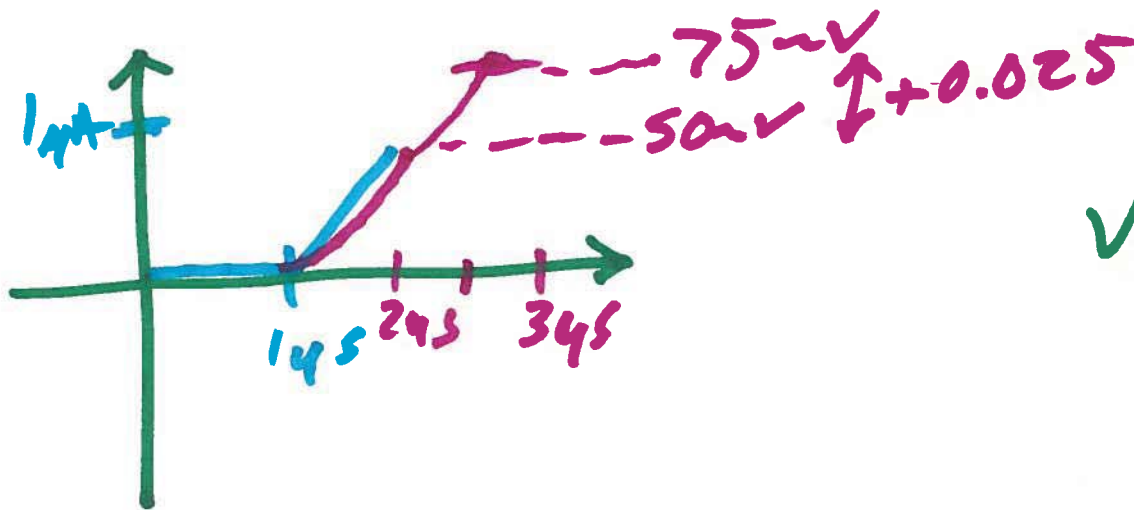
$$\frac{(145)^2}{20 \text{ pF}} = \frac{1}{20} = 0.05$$



$$i(t) = -\frac{24A}{14s} \cdot t + 14A$$

$$V(t) = \frac{1}{C} \int_{0, 24s}^{14s, 34s} (-2t + 14A) dt$$

$$= \frac{1}{10pF} [-t^2 + 14A \cdot t]$$


$$V(0) = 0$$

$$V\left(\frac{1}{2}4s\right) = \frac{1}{10pF} \left[-\left(0.5 \times 10^{-8}s\right)^2 + 10A \cdot 10^{-8} \cdot \frac{1}{2} \right]$$

$$\frac{1}{40} = \frac{1}{10} \left[-0.25 + \frac{1}{2} \right] = \frac{0.25}{10}$$
$$\frac{1}{40} = 0.025$$



Inductors (Henrys)

e

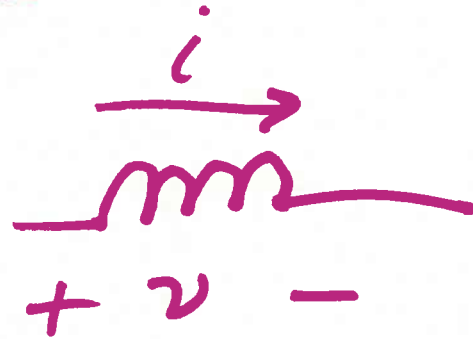


$$v(t) = L \cdot \frac{di(t)}{dt}$$
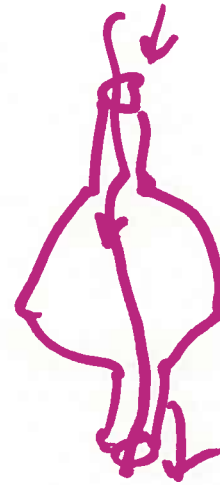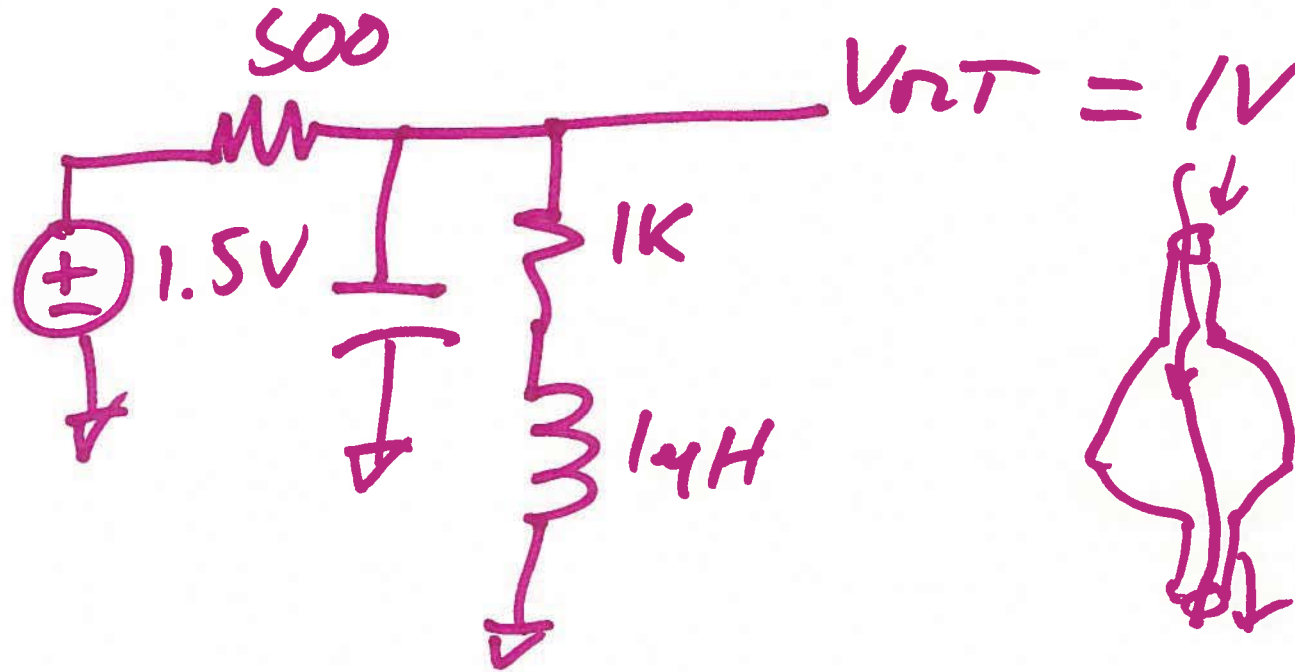
$$i(t) = \frac{1}{L} \int v(t) \cdot dt$$




Magnetic flux

3)

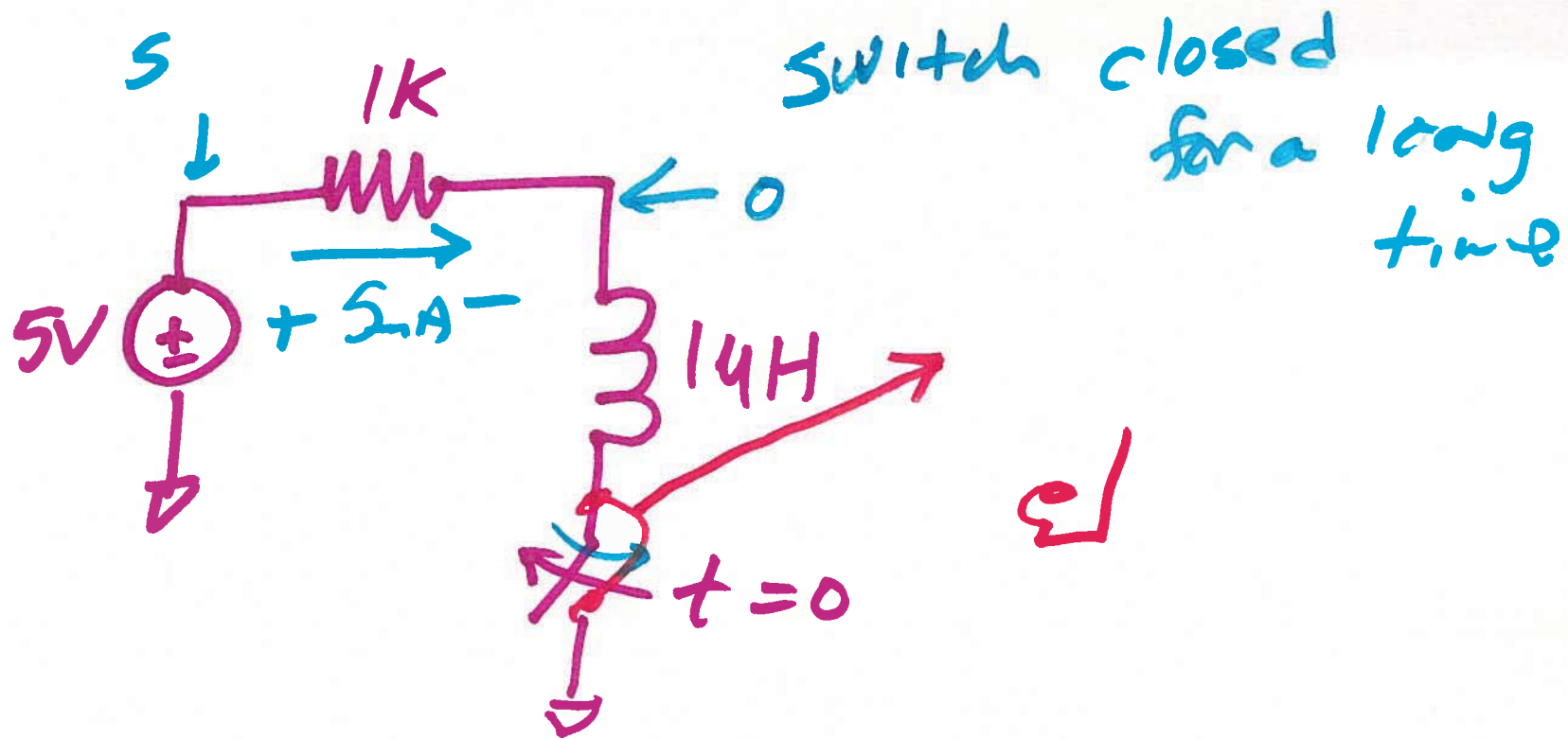

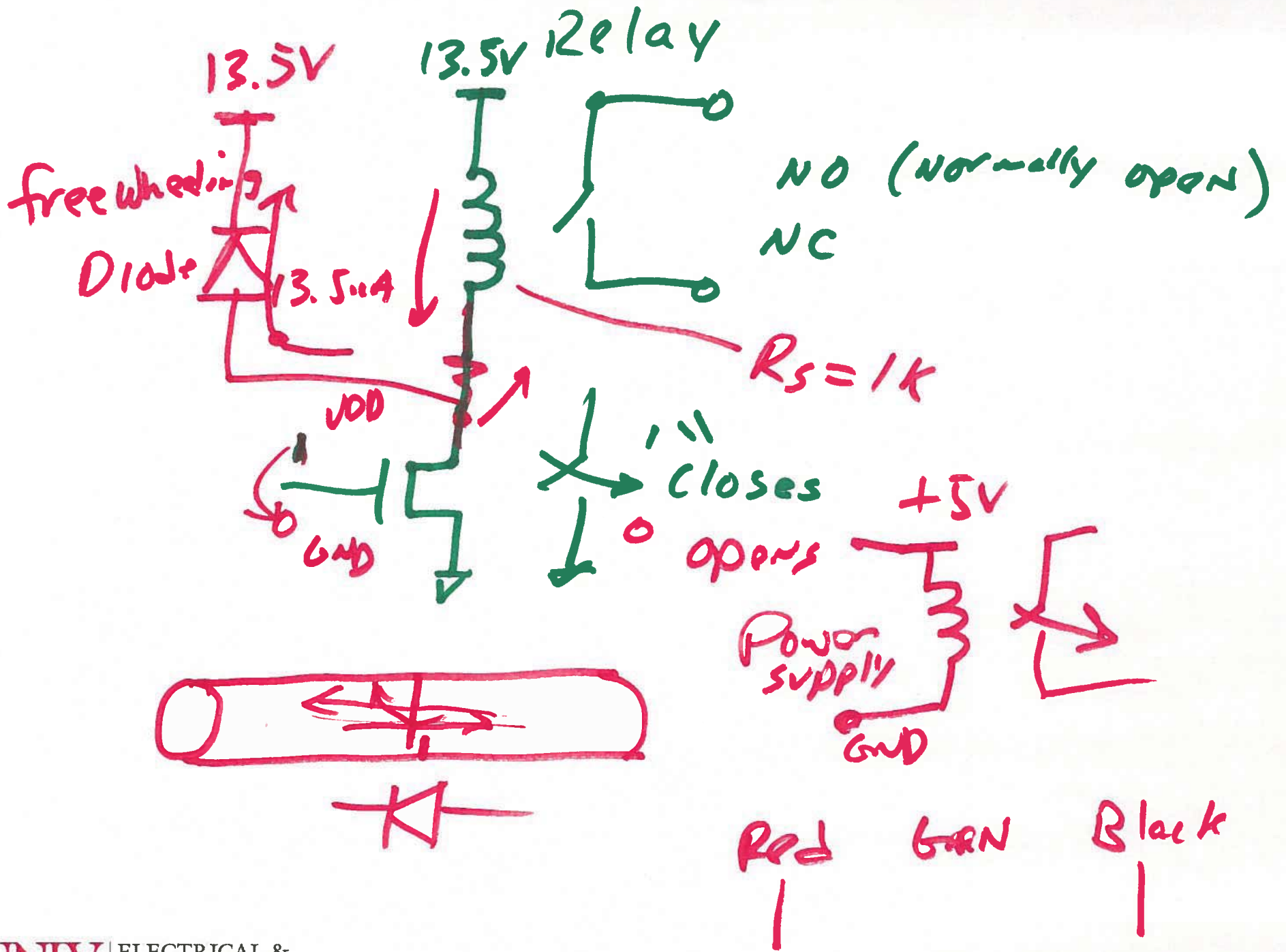
$$\frac{L}{R} = \frac{10^{-6}}{10^3} = \frac{14H}{1k} = \underline{\underline{10^{-9} \text{ ns}}}$$



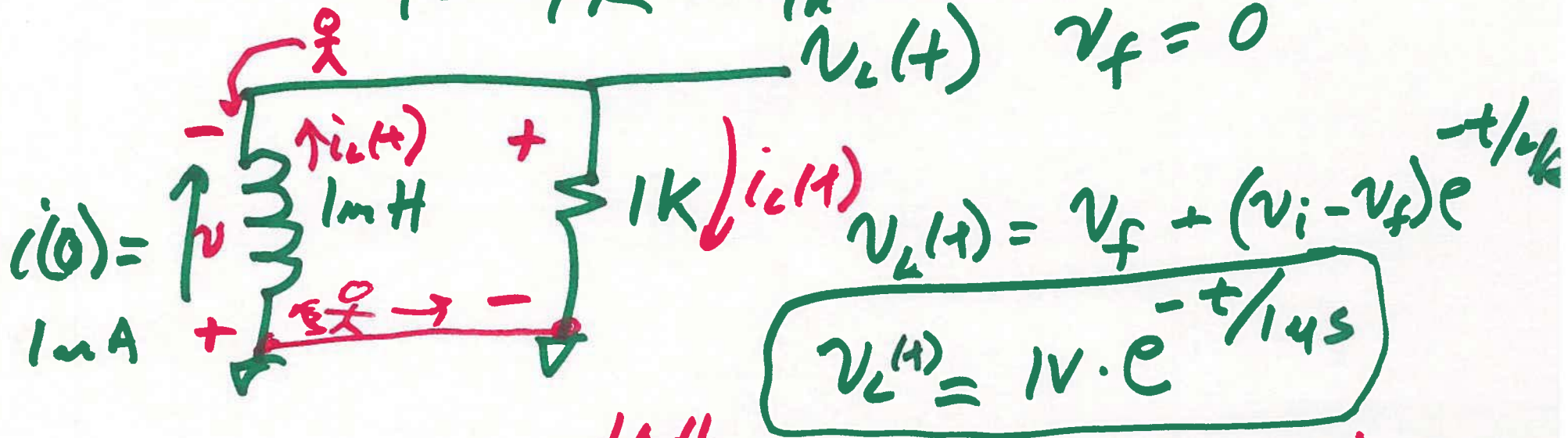5)

$$\tau = L/R = \frac{1mH}{1K} = 1\mu s \quad v_i = 1V \quad v_f = 0$$



$$1K \cdot i_L(t) + L \cdot \frac{di_L(t)}{dt} = 0$$

$$-1K \cdot i_L(t) = 1mH \cdot \frac{di_L(t)}{dt}$$

$$-t = \int_{i(0)}^{i_L(t)} -dt = \int_{1mA}^{i_L(t)} \frac{1\mu s}{i_L(t)} \cdot \frac{di_L(t)}{dt} = 1\mu s \cdot \ln \frac{i_L(t)}{1mA}$$

$$i_L(t) = 1mA \cdot e^{-t/1\mu s}$$

$$i_L(t) = i(0) \cdot e^{-t/1\mu s}$$

$$v = L \frac{di}{dt}$$

6)