

# EE 220 Circuits 1

November 1, 2017

Lecture 18



$$V = L \cdot \frac{di}{dt}$$

$$\frac{1.5}{500 \mu\text{H}} = \frac{di}{dt}$$

$$\downarrow$$

$$\frac{1.5}{\frac{1}{2} \times 10^{-3}} = 3,000$$

$$500 \mu = 0.5 \text{ m}$$

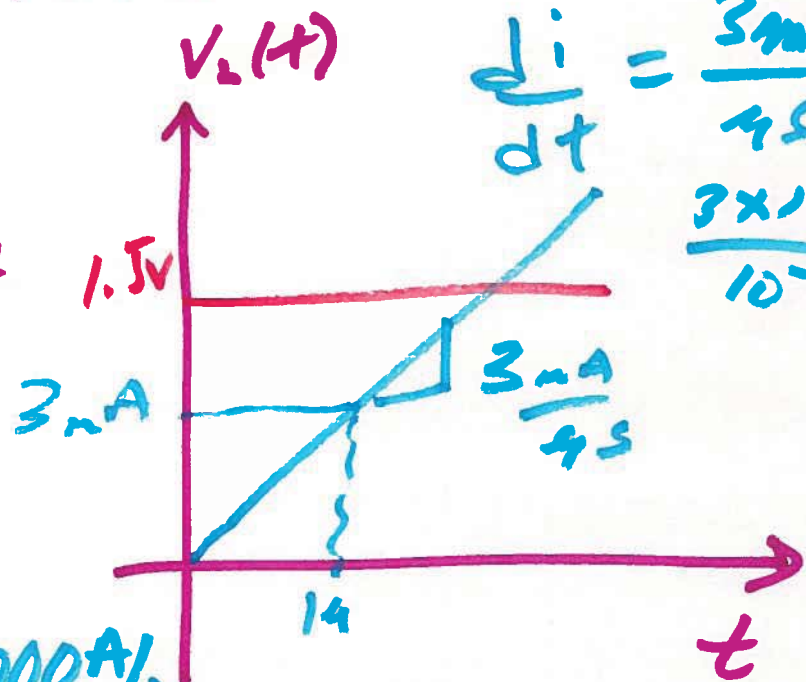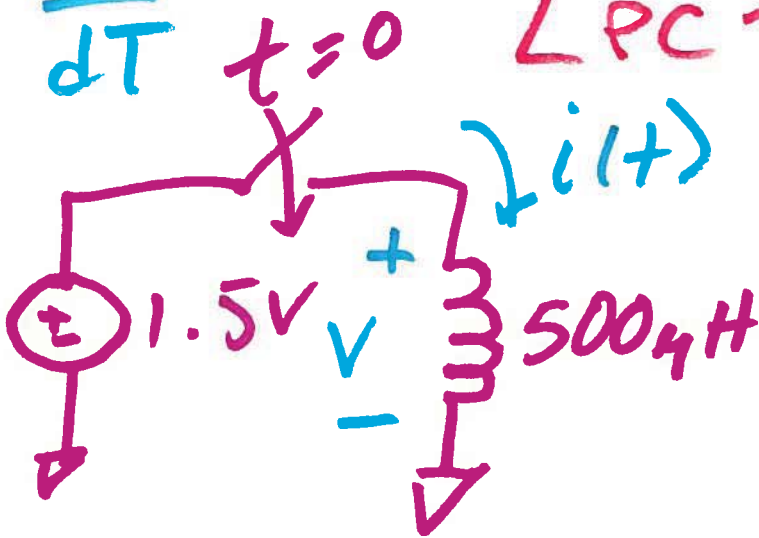

$$\frac{3,000}{11} = \frac{3 \text{ mA}}{45} = \frac{3 \times 10^{-3}}{10^{-2}}$$

$$\frac{di}{dt} = 3,000 \text{ A/s} = \frac{3 \text{ mA}}{45}$$

$$i(t) = 3 \text{ mA} \cdot t$$


1)

$I \Rightarrow DC$

$i \Rightarrow AC$  (time varying)

$V_{DS} = V_D - V_S \rightarrow DC$

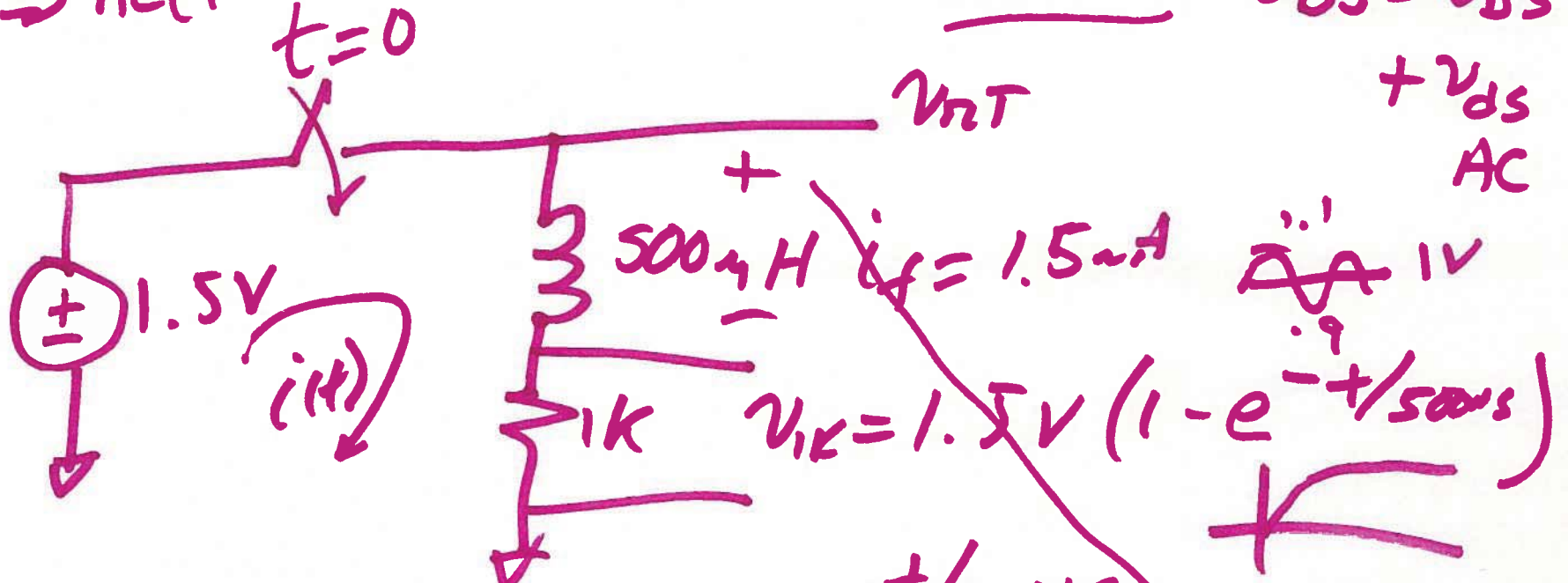
$v_{ds} = AC$   $i_i = 0$   $v_{DS} = V_{DS} + v_{ds}$




$$i(t) = i_f + (i_i - i_f)e^{-t/500\mu s}$$

$$= 1.5mA(1 - e^{-t/500\mu s})$$

$$1.5 - v_{1k} = 1.5e^{-t/500\mu s}$$

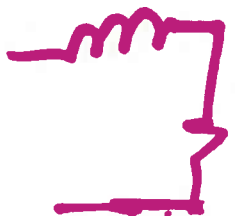

2)

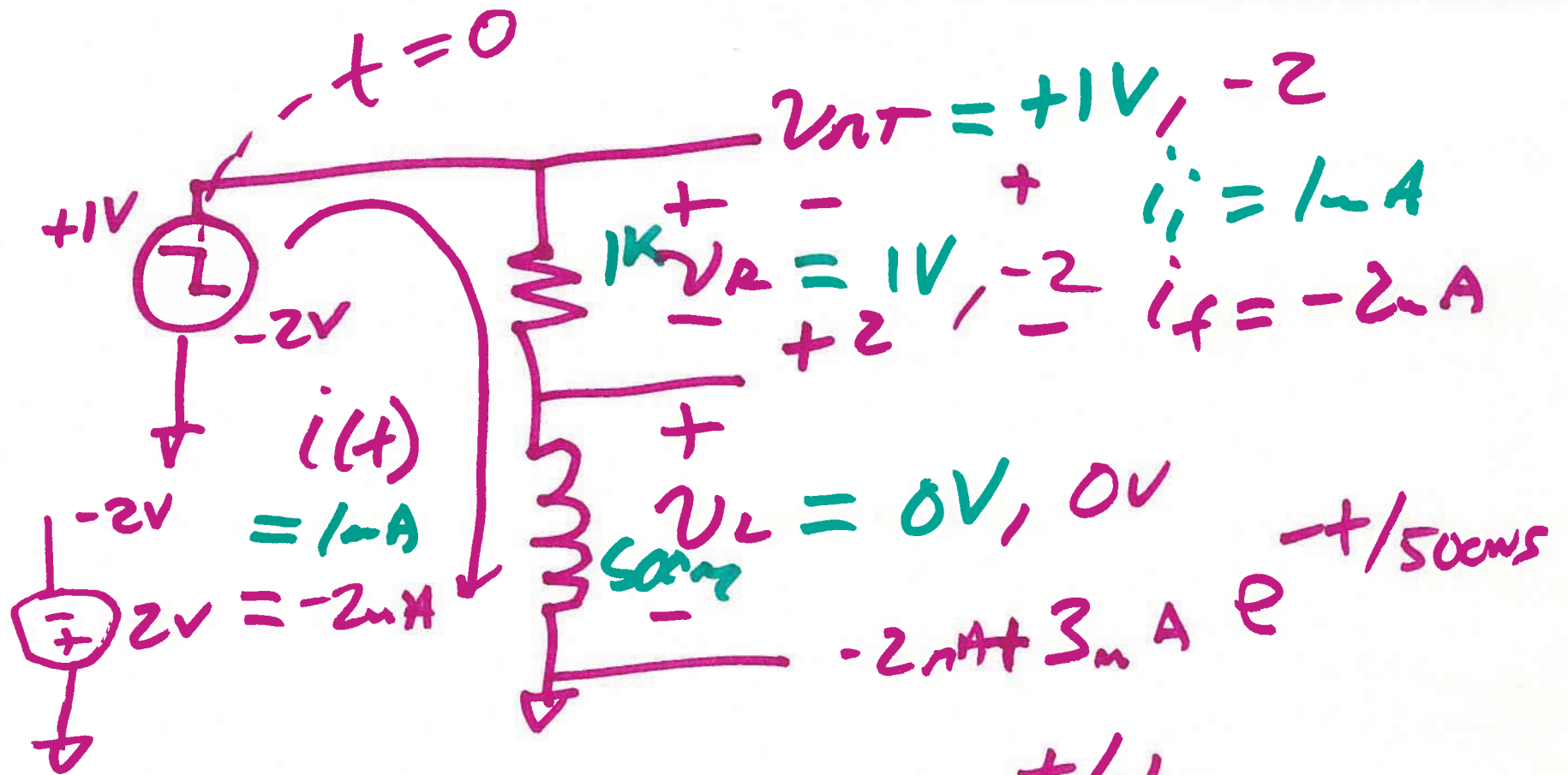

$$i(t) = i_f + (i_i - i_f) e^{-t/\tau}$$


$$= -2mA + (1mA - (-2mA)) e^{-t/4\tau}$$

$t > 0$

500ns



3)

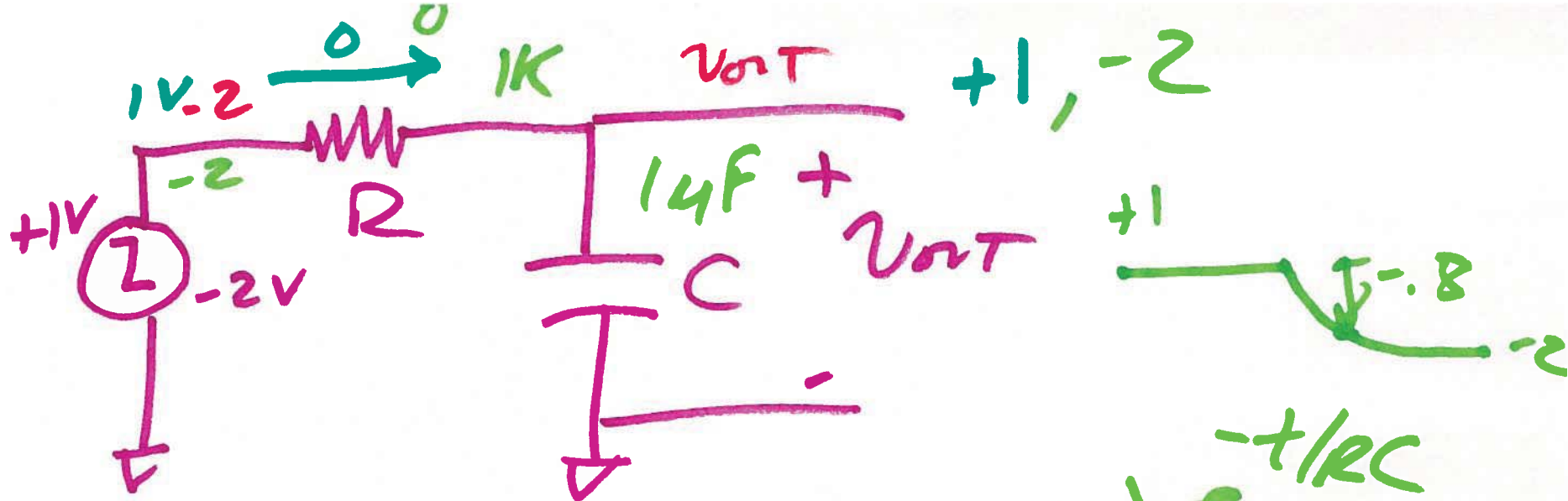

$$v_{out} = v_f + (v_i - v_f) e^{-t/RC}$$


$$-2 + (1 - (-2)) e^{-t/RC}$$

$$v_{out}(t) = -2 + 3e^{-t/1\mu s}$$

$$i = \frac{-2 - v_{out}}{1k} = \frac{-2 - (-2 + 3e^{-t/1\mu s})}{1k}$$

$$= -3mA e^{-t/1\mu s}$$

4)

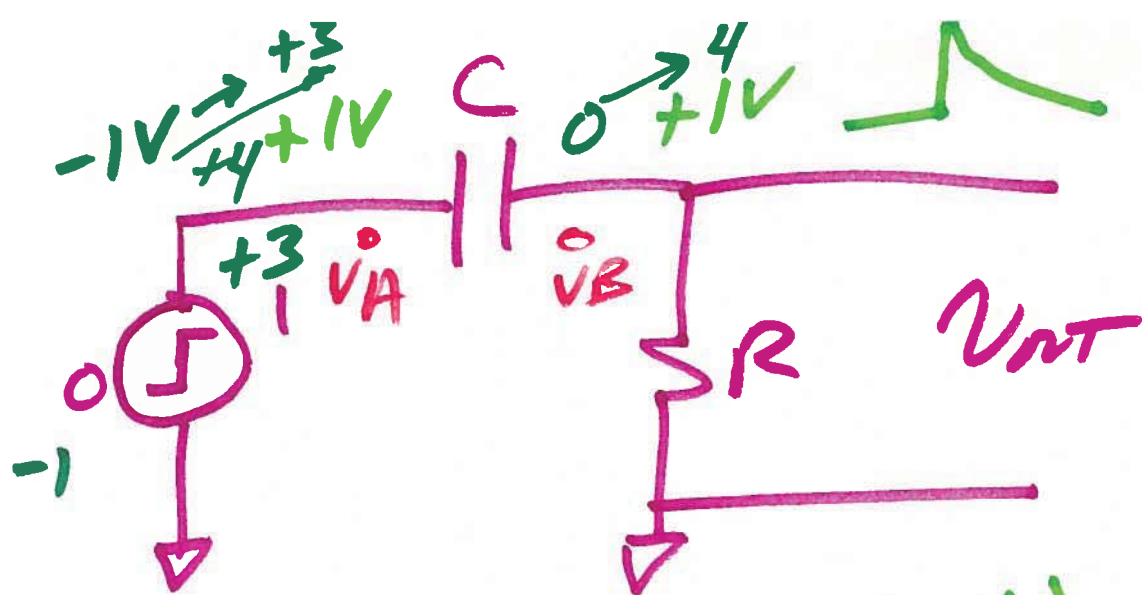

$$v_i = 1V$$

$$v_f = 0$$

$$v_{OUT}(t) = v_f + (v_i - v_f)e^{-t/RC}$$

$$v_{OUT} = 1e^{-t/RC}$$

$$v_{OUT} = 4 \cdot e^{-t/RC}$$

$$(V_A - V_B)C = Q$$

5)