
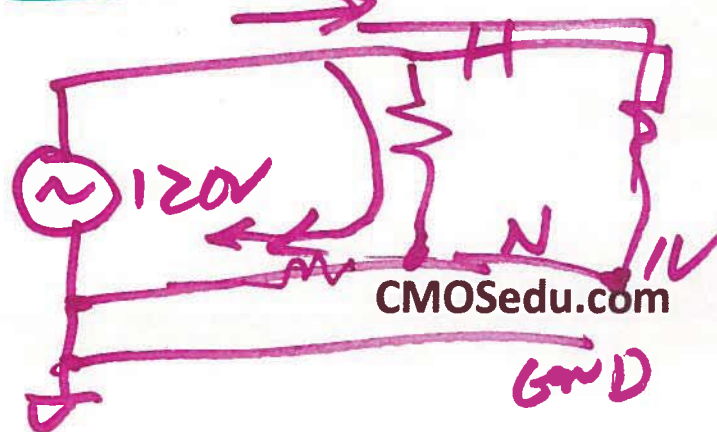
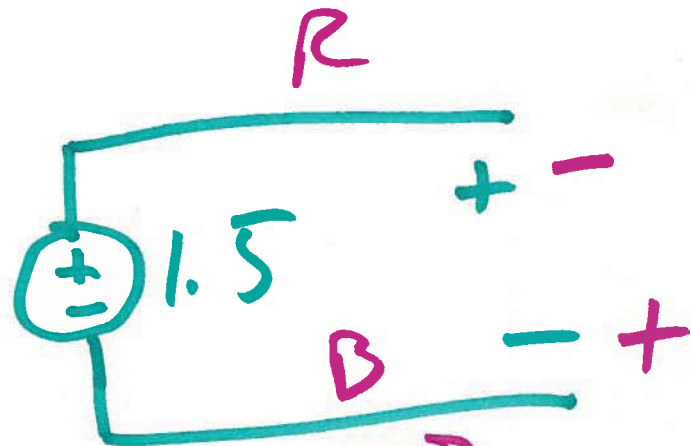


EE 220 Circuits I



NOV. 6, 2017

Lecture 19

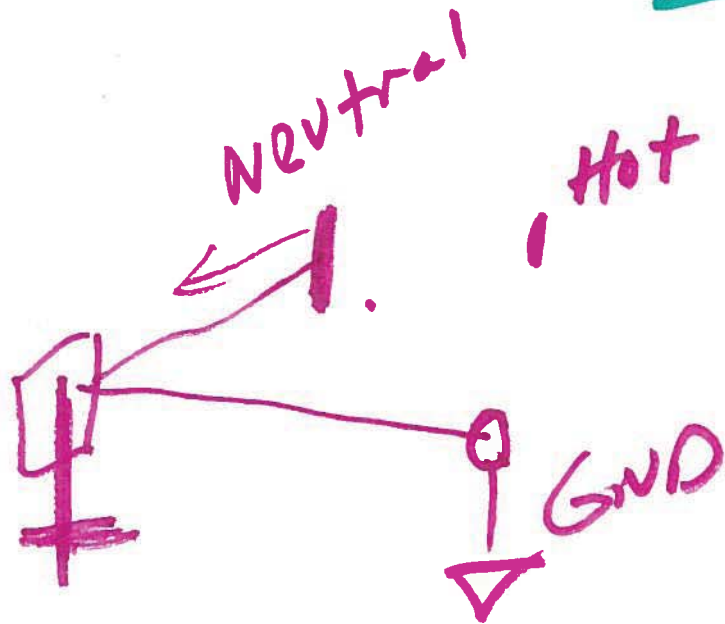

Energy ≠ Power

$$P = VI = I^2 \cdot R = \frac{V^2}{R}$$

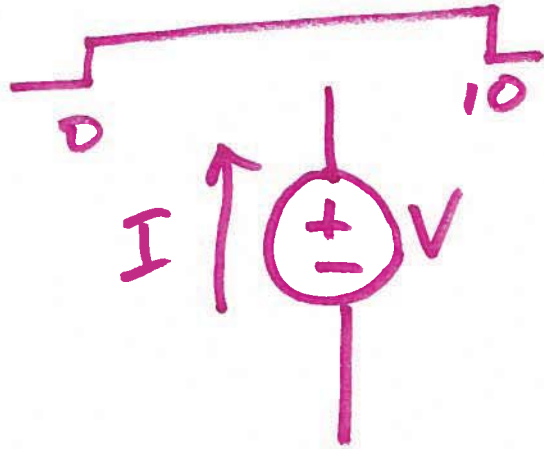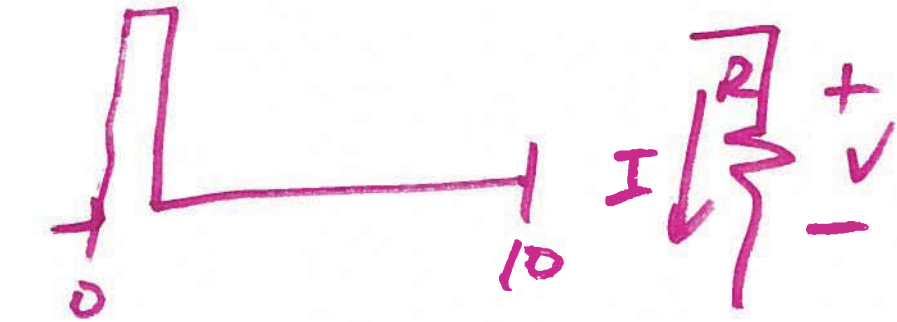

$$P = -I \cdot V$$

Neg. power indicates
supplying power

$$\text{power, WATTS} = \frac{\text{Energy, Joules}}{\text{time, seconds}}$$

$$1.5V \cdot \boxed{1.5 \text{ mA} \cdot \text{H}} = 2.25 \cdot 3600 \text{ Joules}$$

$$2.25 \text{ mW} \cdot \text{H}$$

2)

Ideal CAPACITOR & INDUCTOR


$\epsilon = 200 \cdot 12.5$ Joules don't dissipate power
 IF they store energy!



$$p(t) = v(t) \cdot i(t)$$

$$\epsilon = \int p(t) \cdot dt = \epsilon_{\text{ENERGY}}$$

$$i(t) = C \frac{dv(t)}{dt}$$

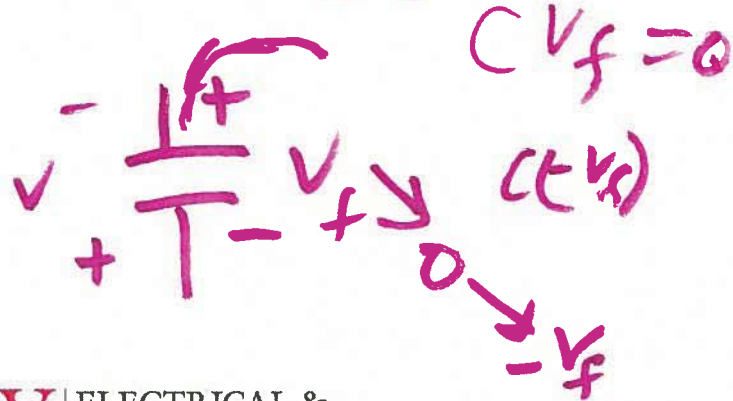


$$= \int_{0}^{V_f} v(t) \cdot C \cdot \frac{dv(t)}{dt} \cdot dt$$

$$= C \cdot \frac{1}{2} v^2 \Big|_0^{V_f} = \frac{1}{2} C V_f^2 = \epsilon$$

Inductor Energy Storage

$$p(t) = i(t) \cdot v(t)$$

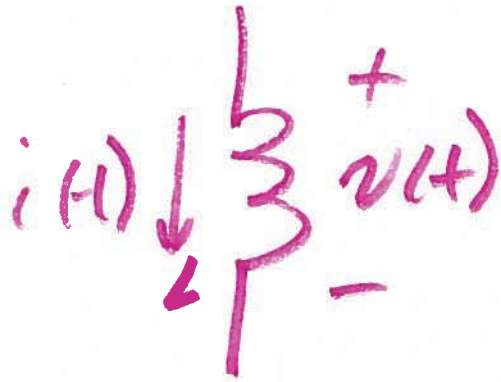


$$\mathcal{E} = \int p(t) \cdot dt$$

$$v(t) = L \cdot \frac{di(t)}{dt}$$


$$\mathcal{E} = L \int_0^I i(t) \cdot \frac{di(t)}{dt} \cdot dt$$

$$\mathcal{E} = \frac{1}{2} L I^2$$


$B_{15} = 100k$
Integrator

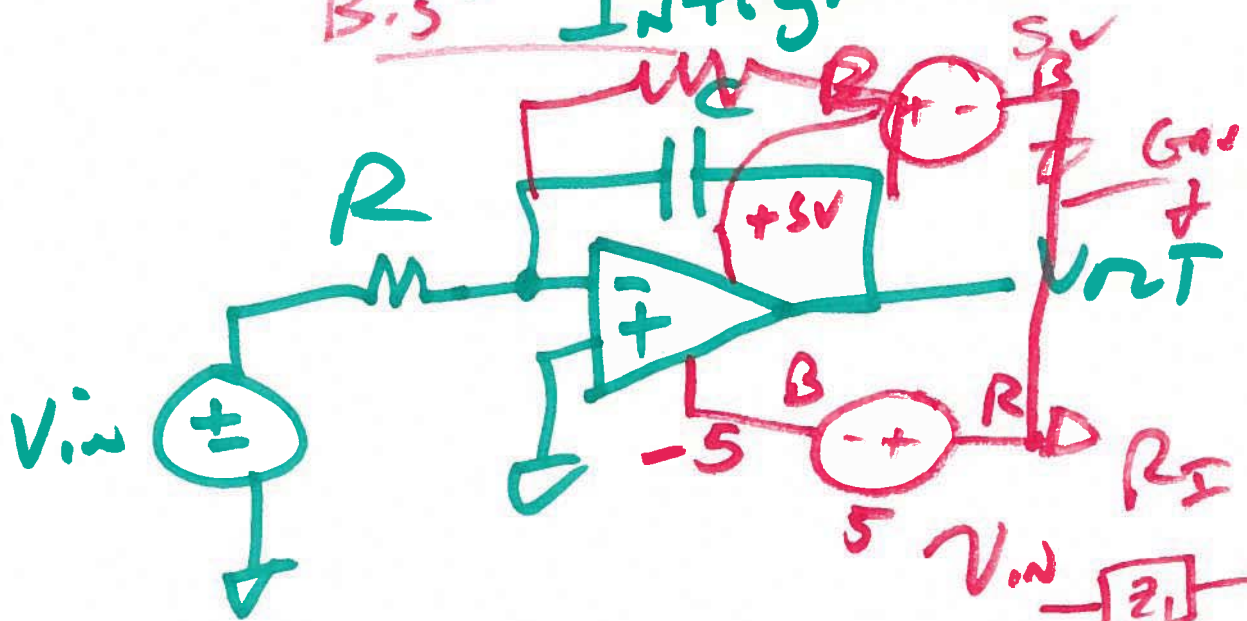

Inverting

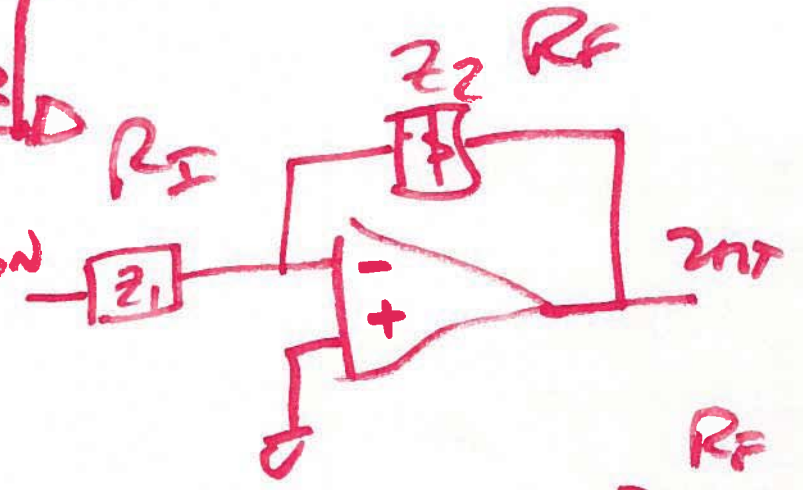

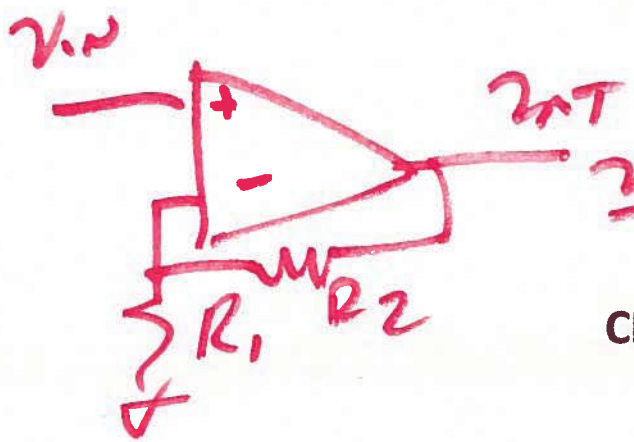
$$\frac{V_{out}}{V_{in}} = -\frac{Z_2}{Z_1}$$



$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1} = \frac{R_1 + R_2}{R_1}$$


5)

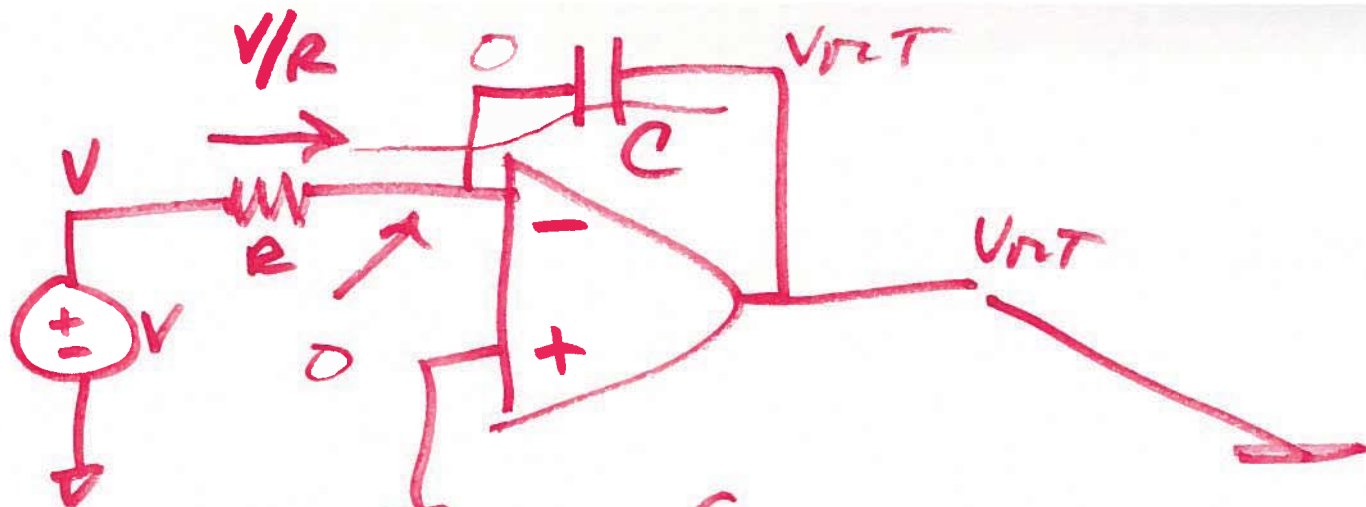

$$V_{out} = -\frac{1}{C} \int \frac{V}{R} \cdot dt$$

$$= -\frac{1}{RC} \int_0^+ V \cdot dt$$
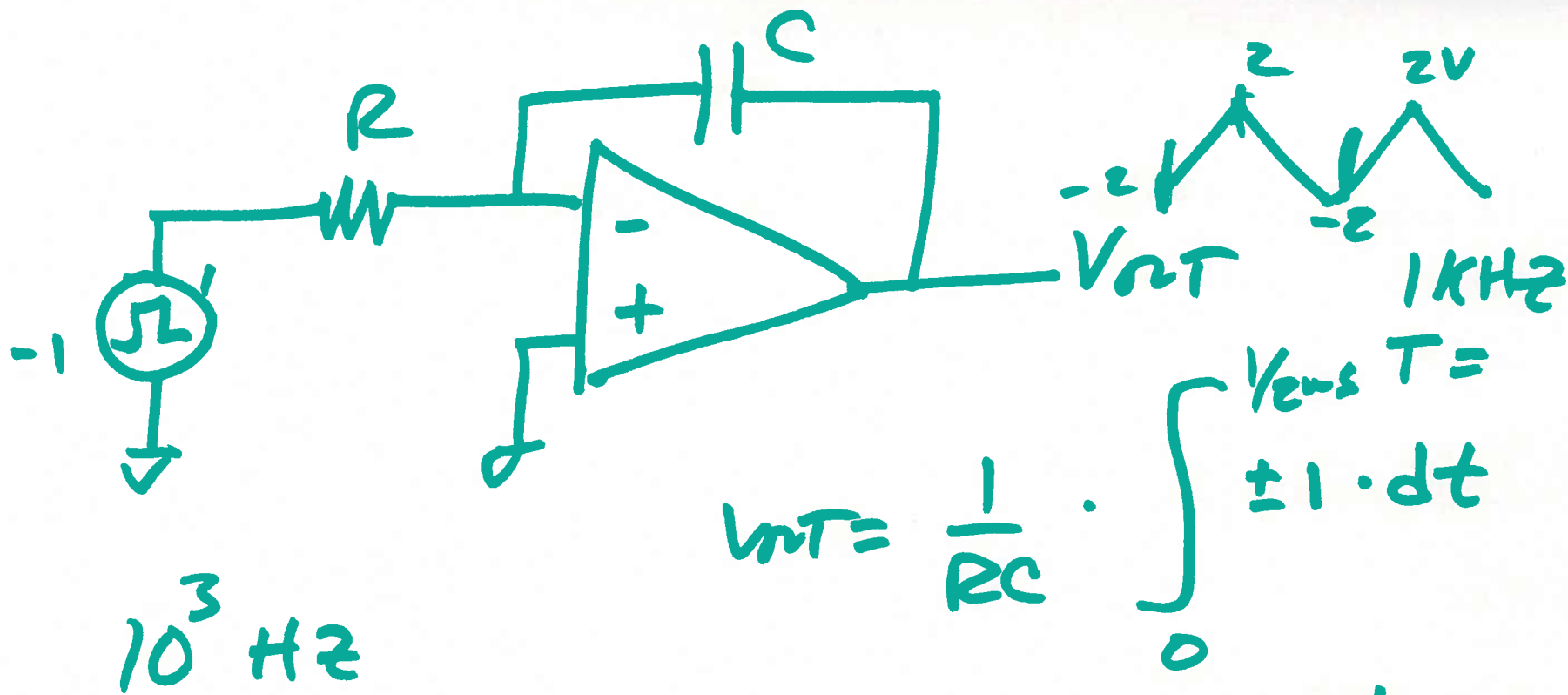
$$V_{out} = -\frac{1}{RC} \cdot V \cdot t$$



$T = \frac{1}{f} = 1\text{ms}$
 $\frac{1}{R \cdot 10^{-6}} \cdot \frac{1}{2} \text{ms} = 4 = \frac{1}{RC} \cdot \int_0^{1/2\text{ms}} 1 \cdot dt$

$\frac{0.5 \cdot 10^{-3}}{R} = 4$
 $R = \frac{0.5 \cdot 10^{-3}}{4} = 125$
 $C = 14 \text{ F}$

1)