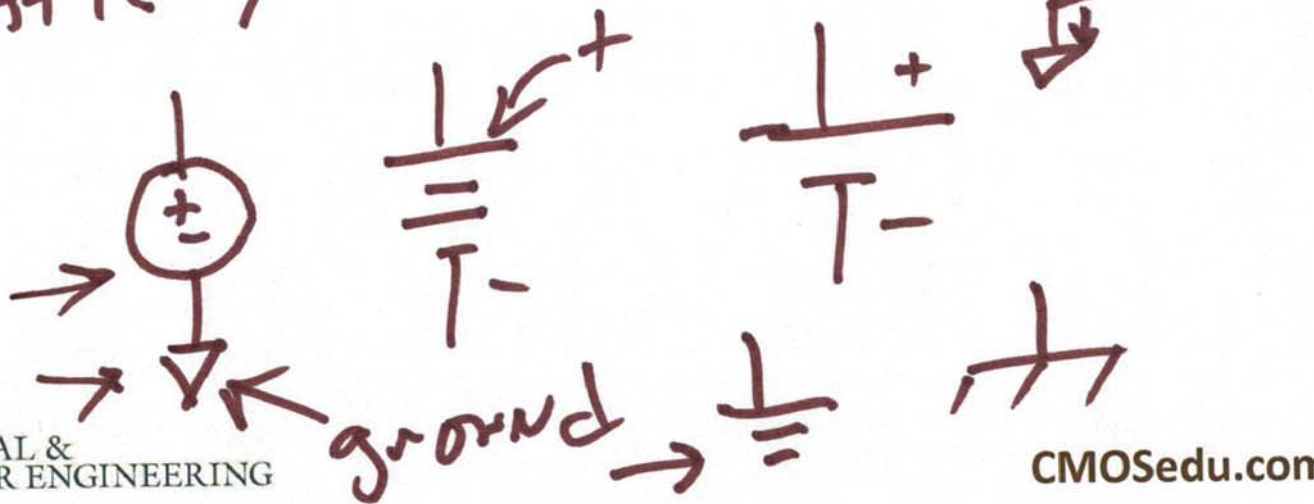


EE 220 Circuits I

August 28, 2017

Lecture 1


BATTERY



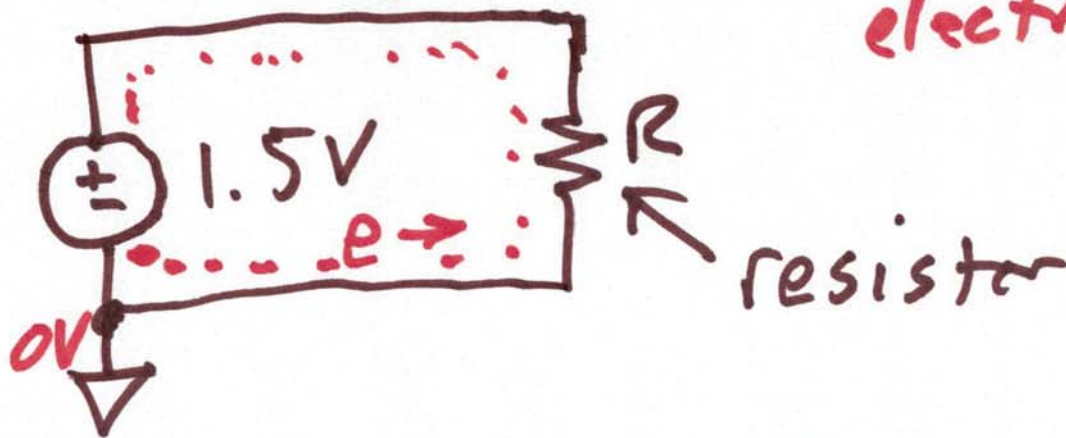
1)

BATTERY


$I = \text{current}$ is opposite
electron flow



resistor

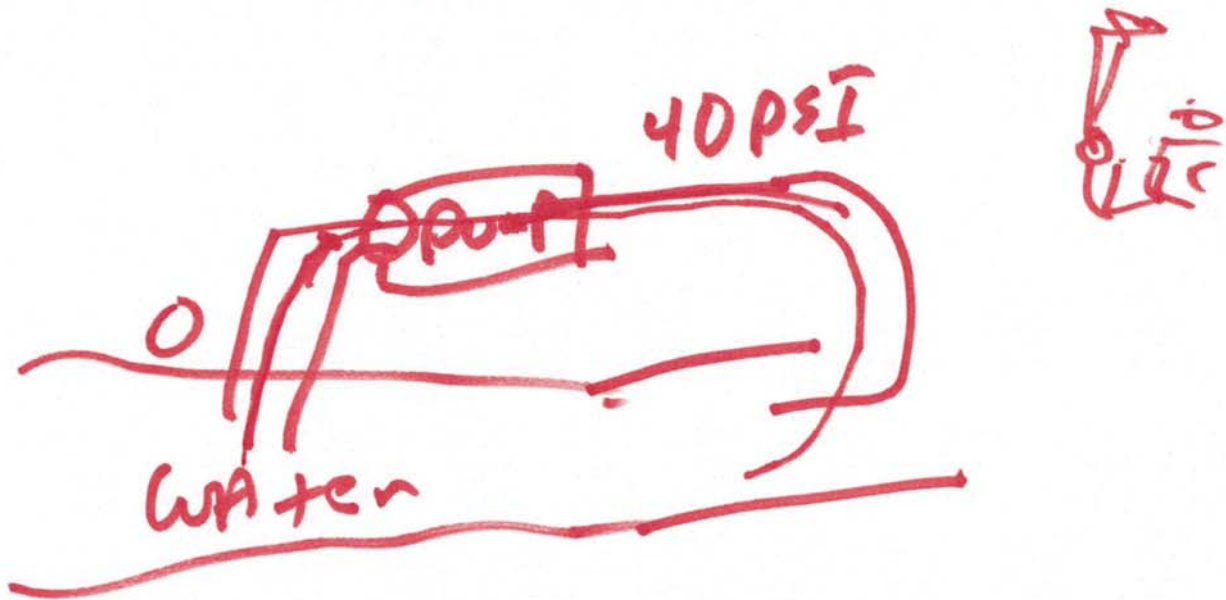

2)

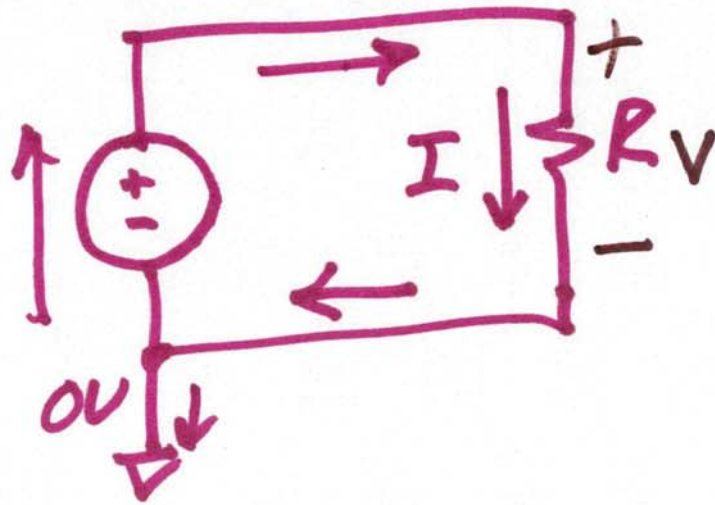

$R \rightarrow \infty$ (open)


$R \rightarrow 0$ (short)

Ohm's law

$$V = I \cdot R$$




open

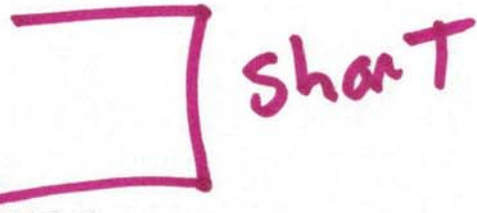

short

3)

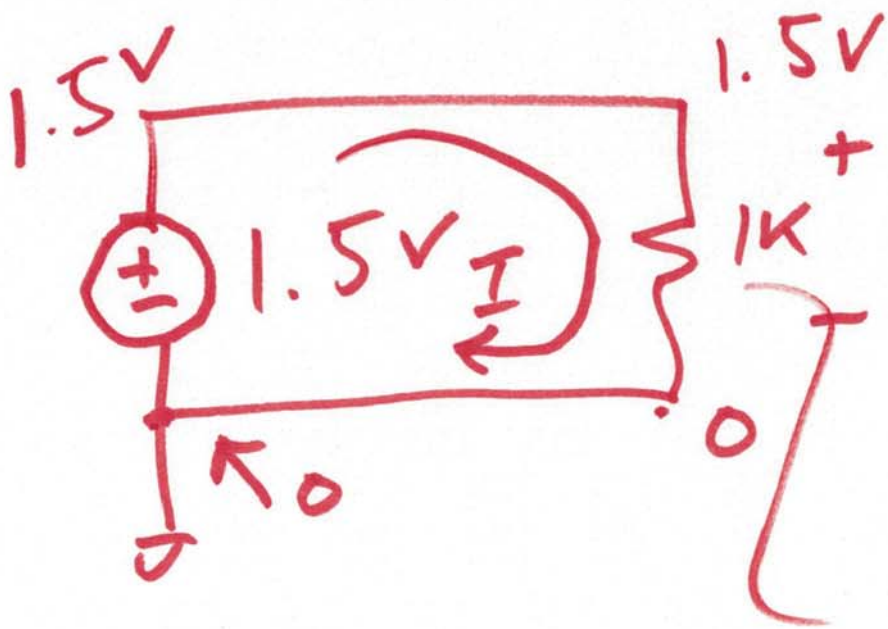

$$V = IR$$

$$I = ?$$

$$I = \frac{V}{R} = \frac{1.5}{1k} =$$

1,000 Ω

1.5 μA

unit of $1.5e-3$
resistance

ohms



current

↓
Amperes

"Columbs"




s

4)

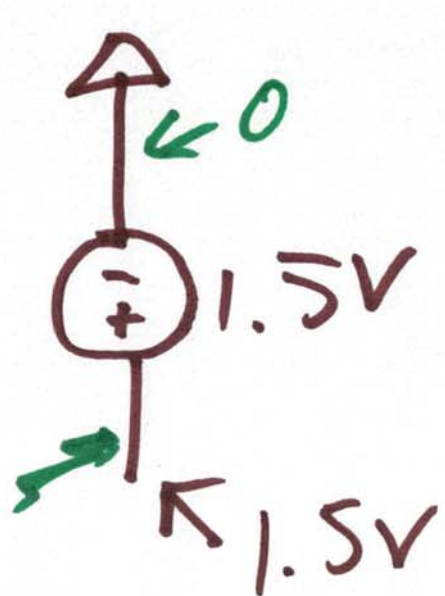
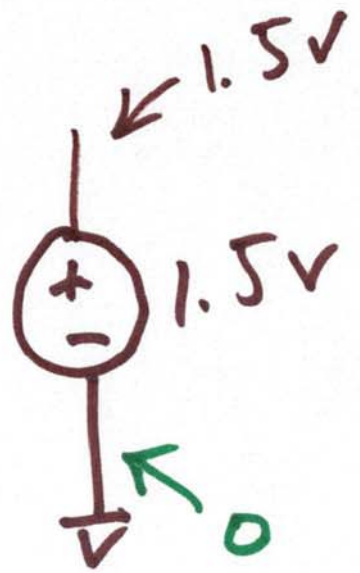


$$V = I \cdot R$$


$$I = 0$$

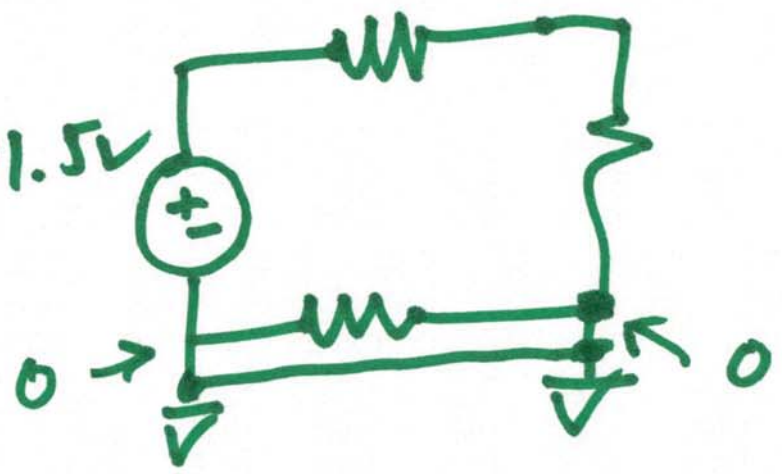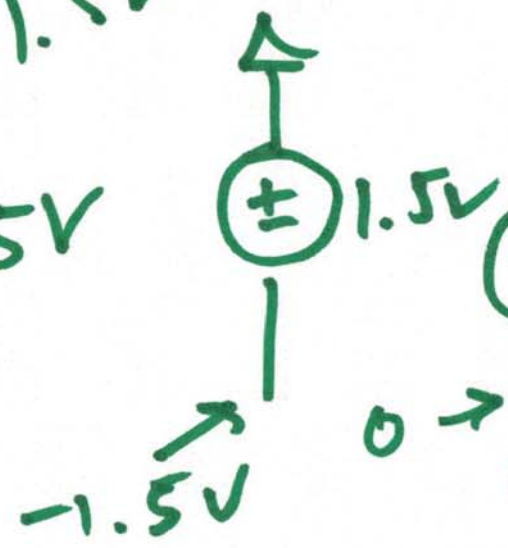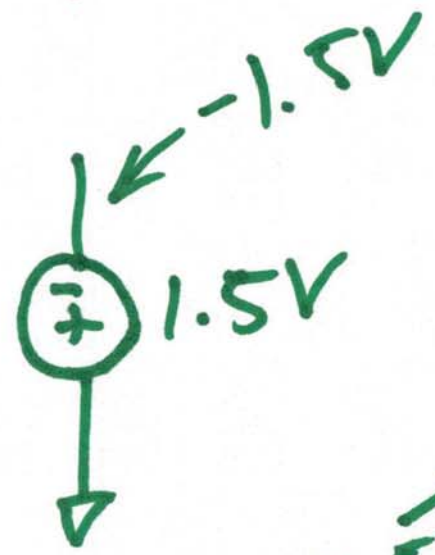

5)

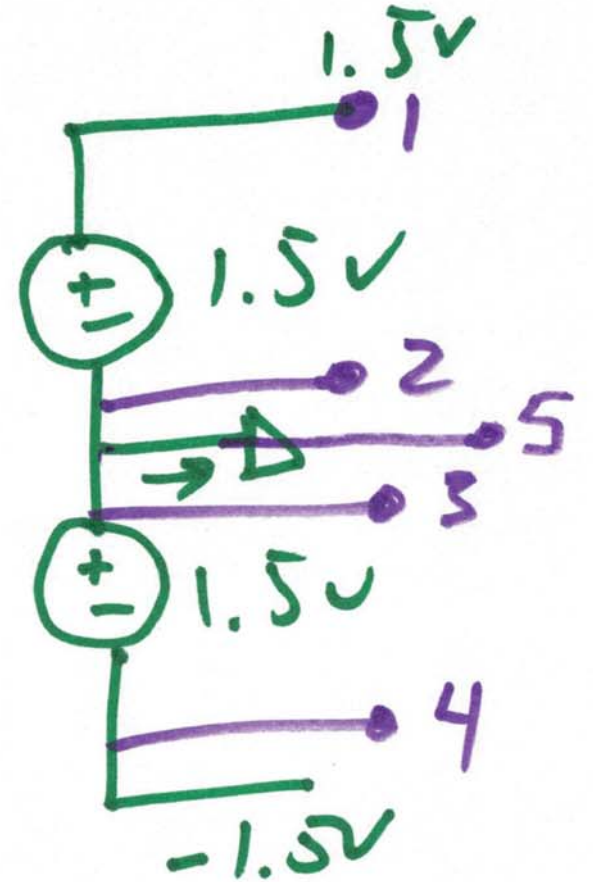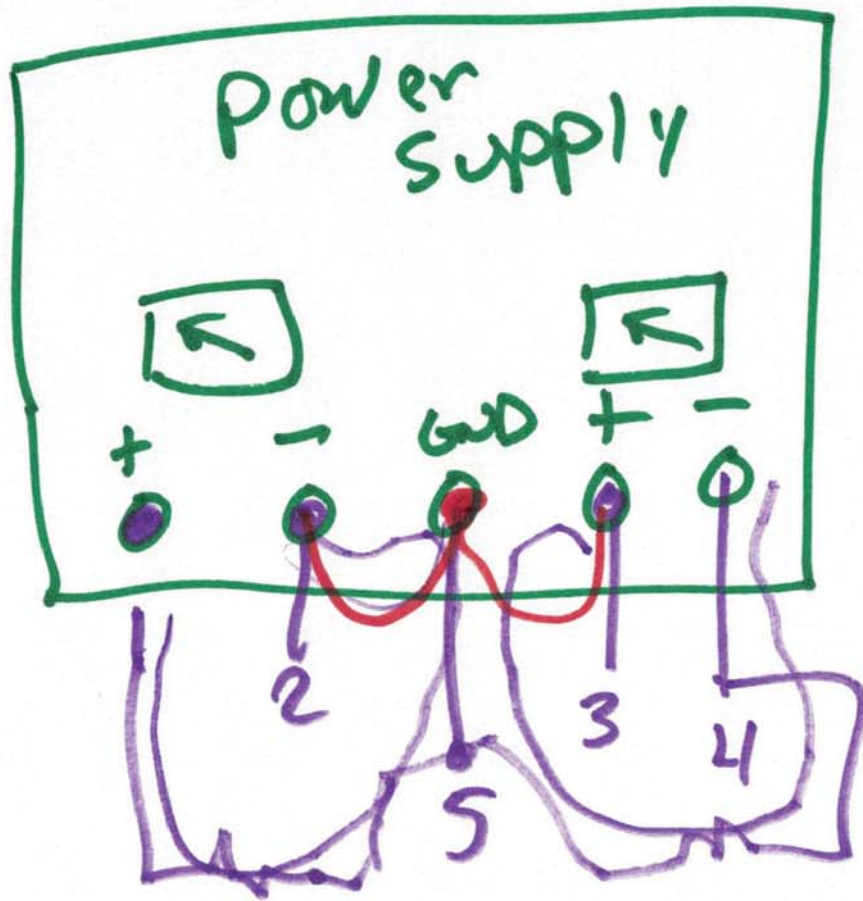

b)

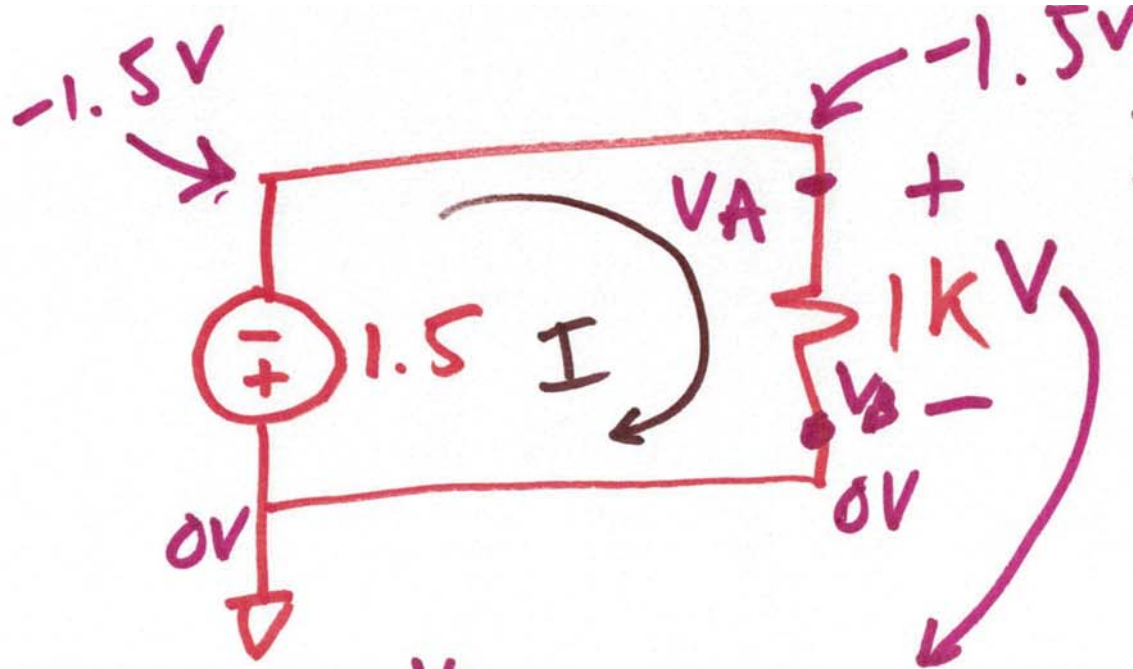

$$I = ?$$


$$V = I \cdot R$$

$$I = \frac{V}{R}$$

$$V = V_A - V_B$$

$$-1.5 - 0 = -1.5V$$


$$I = \frac{-1.5V}{1k} = -1.5\mu A$$

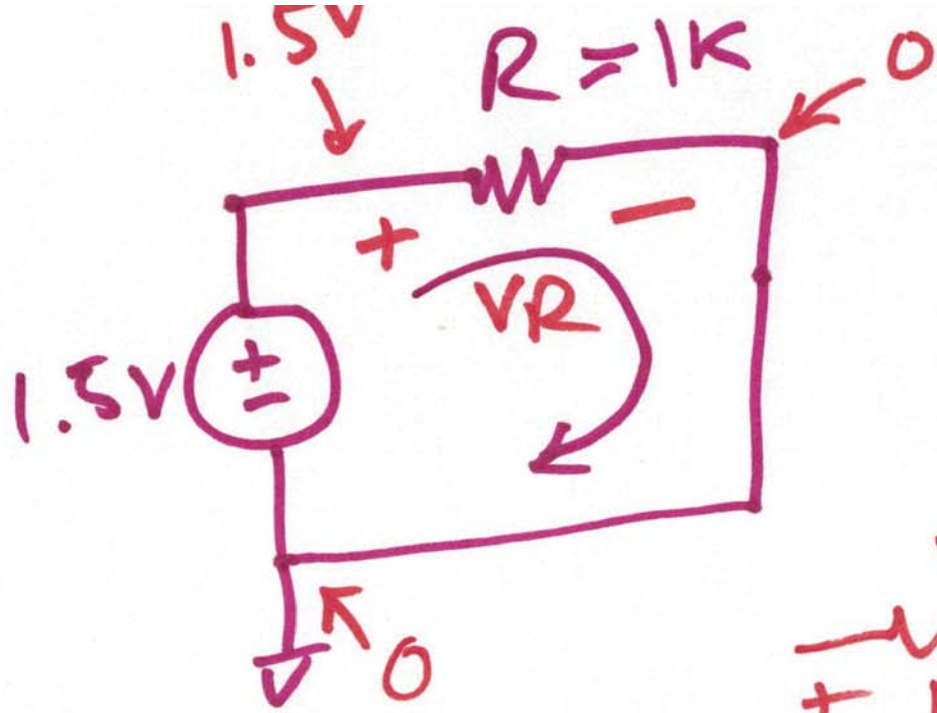

$$V = IR$$

$$V_R = 1.5 - 0 = 1.5V$$

$$I = \frac{1.5V}{1K} = 1.5\mu A$$

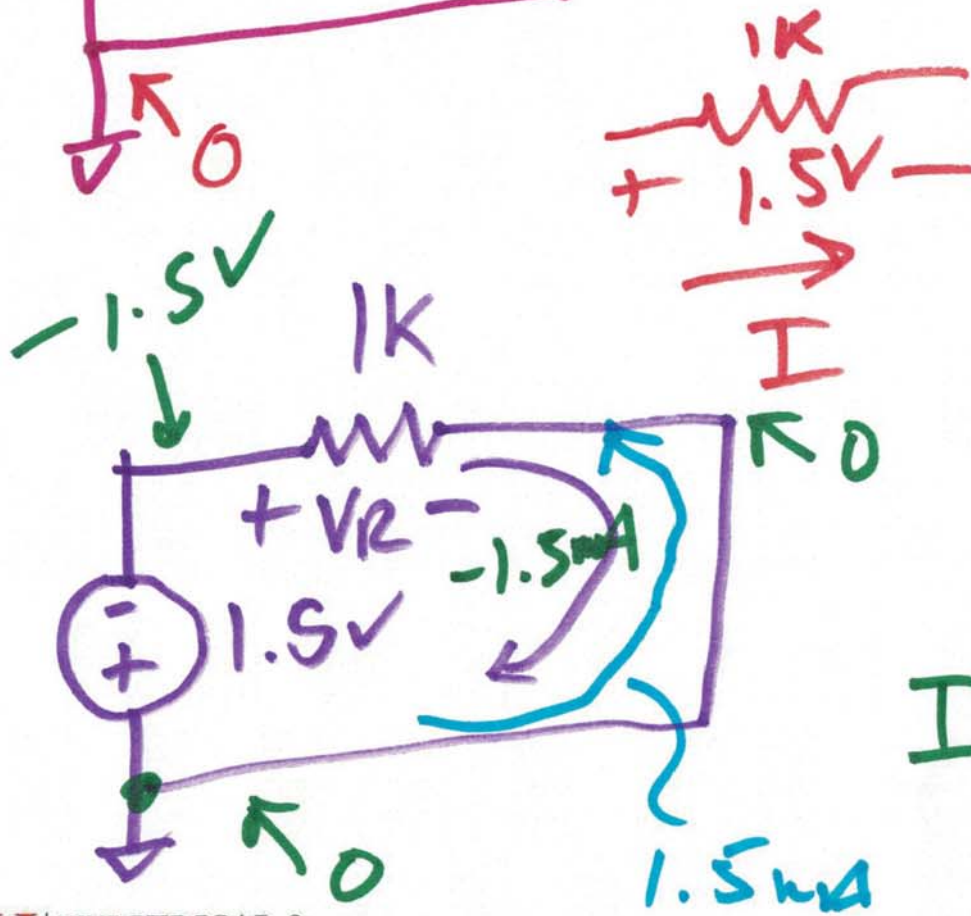


$$V_R = -1.5 - 0$$

$$= -1.5V$$

$$I = \frac{-1.5V}{1K}$$

$$= -1.5\mu A$$

8)

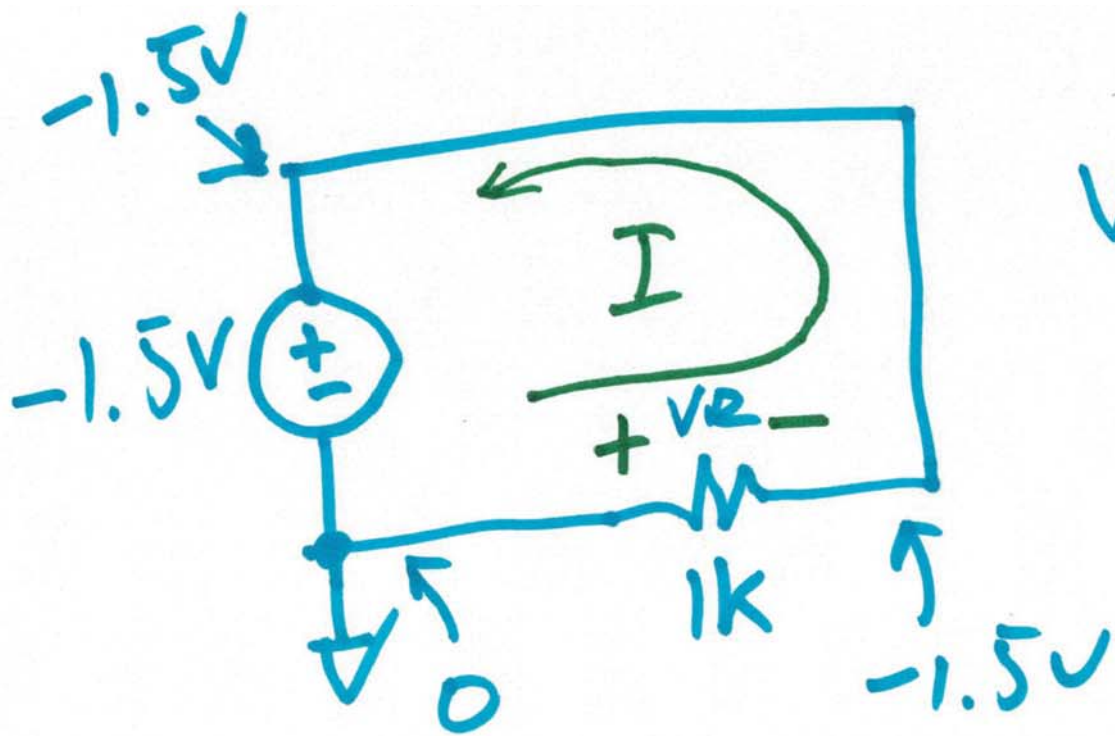

$$V_R = 0 - (-1.5V)$$

$$V_R = 1.5V$$

$$I = 1.5 \mu A$$

$$\frac{1.5}{1k\Omega} = I$$


$$I \downarrow \begin{matrix} + \\ | \\ R \\ | \\ - \end{matrix} V = IR$$

$$I \uparrow \begin{matrix} + \\ | \\ R \\ | \\ - \end{matrix} V = -I \cdot R$$

$$I \downarrow \begin{matrix} - \\ | \\ R \\ | \\ + \end{matrix} V' = -I \cdot R$$

$$I \uparrow \begin{matrix} - \\ | \\ R \\ | \\ + \end{matrix} V = I \cdot R$$

a)

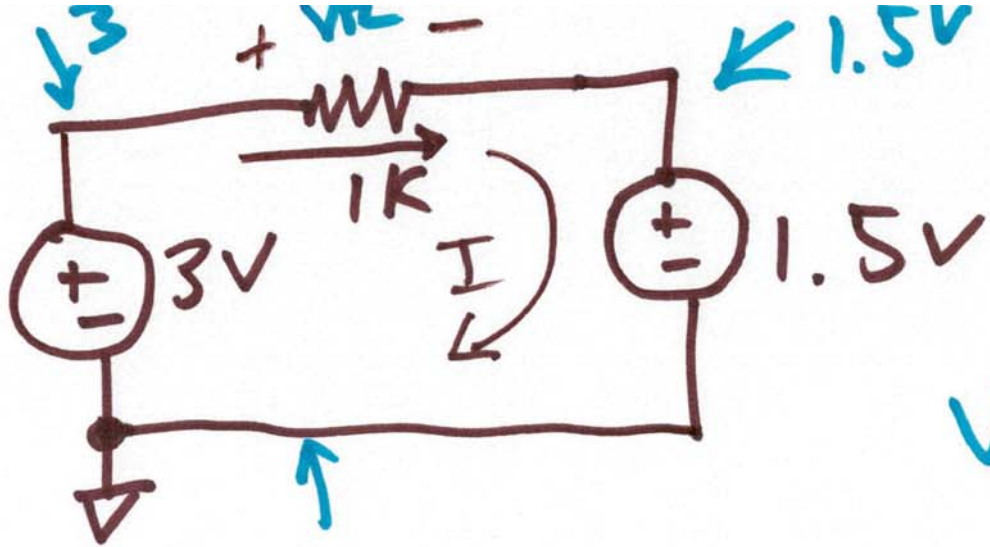


$$V = I \cdot R$$

$$V_R = 3 - 1.5 = \underline{\underline{1.5V}}$$


$$I = \frac{1.5}{1k} = 1.5 \mu A$$

$$V_R = 1.5 - 3 = -1.5V$$

$$I = \frac{-1.5}{1k} = -1.5 \mu A$$

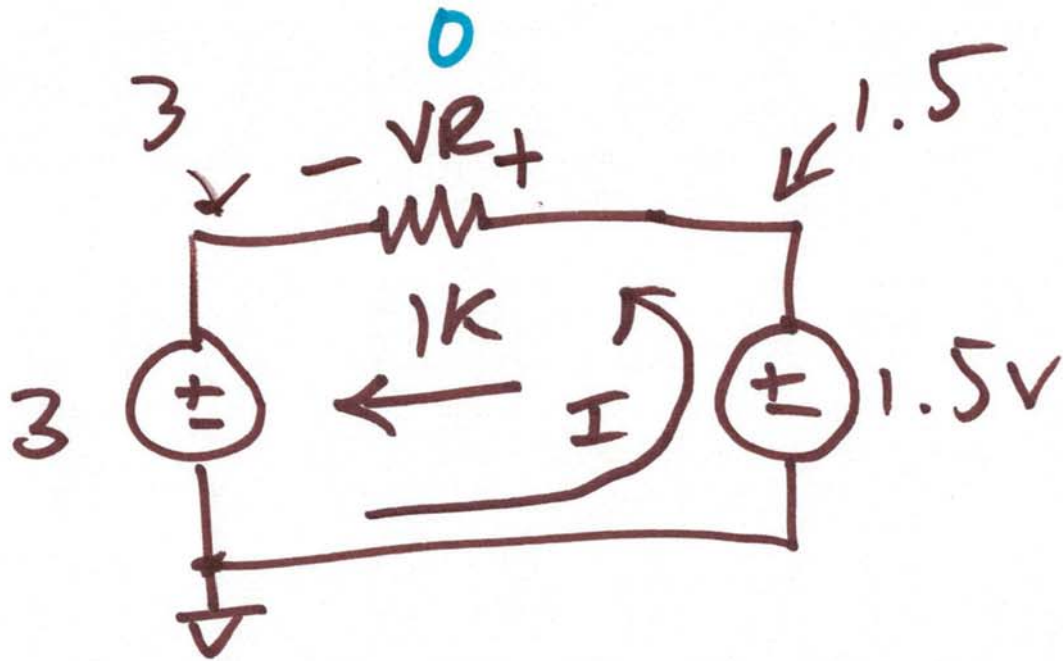

10)

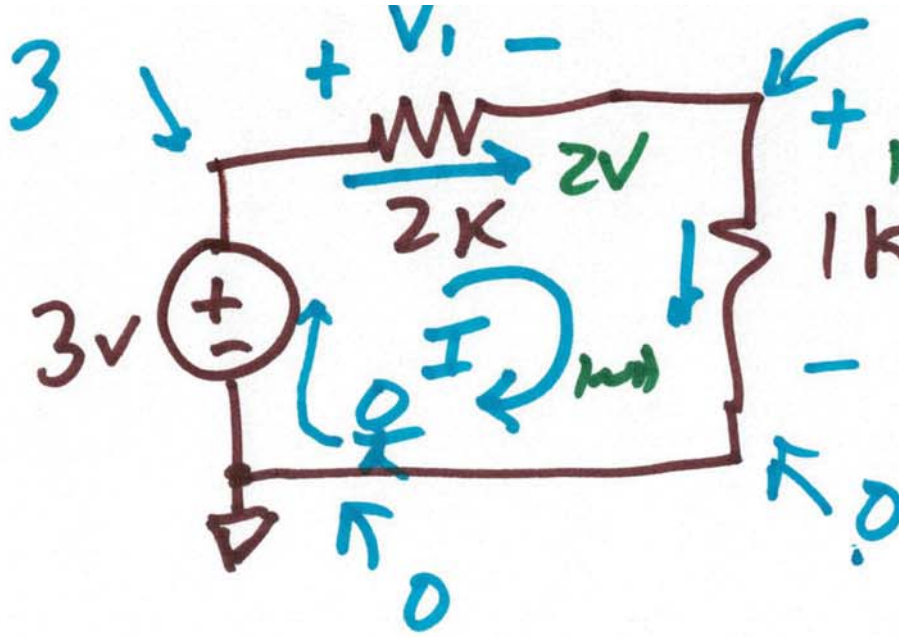

$$V_2 = V_2 - 0$$

$$V_1 = 3 - V_2$$

$$V_1 = I \cdot 2k$$

$$V_2 = I \cdot 1k$$



$$I \cdot 2k = 3 - I \cdot 1k$$

$$R_1 + R_2$$

$$I = \frac{3}{3k} = 1 \mu A$$

11)