
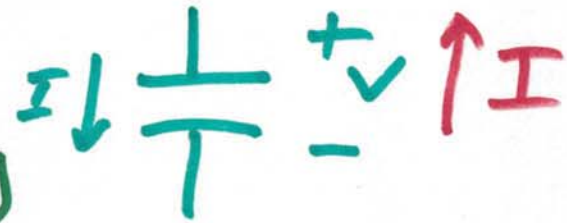


EE 220 circuits I



Lecture 20

-I.1K - V = 0 NOV. 8, 2017
 $V(0) = 5V$

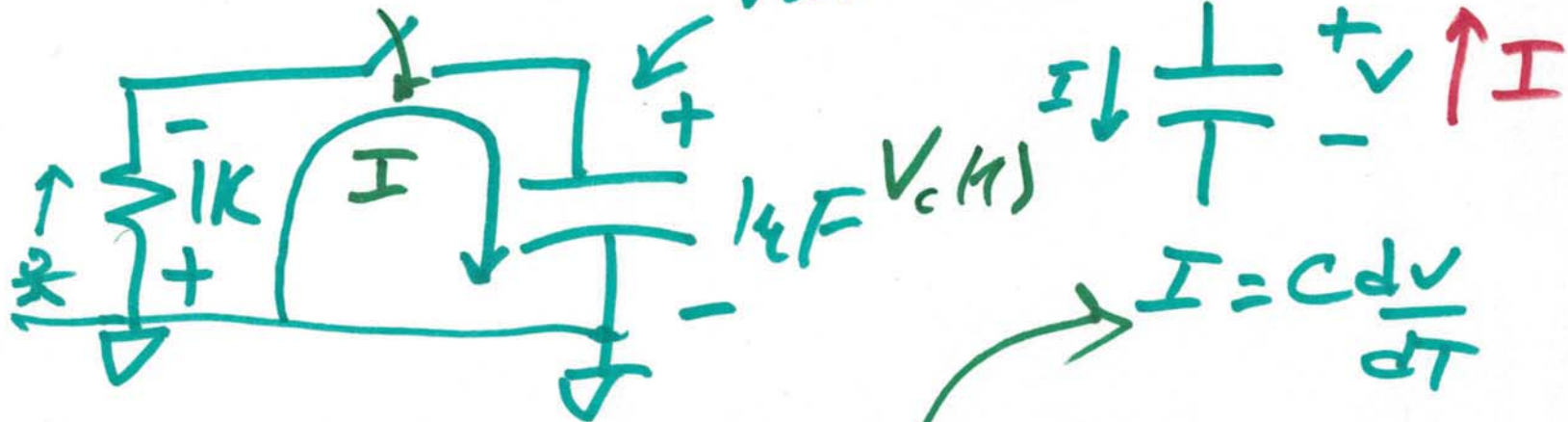

$$I = C \frac{dV}{dt}$$

$$-I = C \frac{dV}{dt}$$

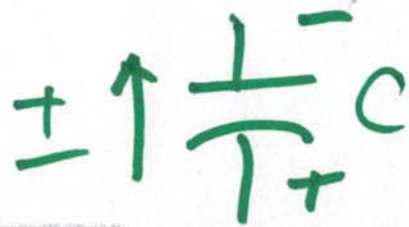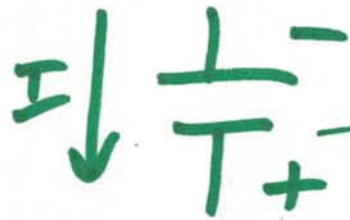

11

$$-I \cdot 1K - V = 0, \quad I = C \frac{dV}{dt}$$

$$0 = -\dot{I} \cdot 1K - \frac{1}{10^{-6}} \int_5^{v_c(t)} I \cdot dt \quad V = \frac{1}{C} \int_5^{v_c(t)} I \cdot dt$$

come back

$$-I \cdot 1K - V = 0$$

RC

$$-1K \cdot 10^{-6} \cdot \frac{dV}{dt} - V = 0$$

$$\frac{v_c(t)}{5} = e^{-t/10^{-3}}$$

$$v_c(t) = 5e^{-t/10^{-3}}$$

$$\ln x \Big|_5^{v_c(t)}$$

$$\ln \frac{v_c(t)}{5}$$


$$-10^{-3} \cdot \frac{dV}{dt} = V$$

$$\int_5 \frac{dV}{V} = \int_0^t \frac{dt}{-10^{-3}}$$

$$= -\frac{t}{10^{-3}}$$

CMOSedu.com

2) $\ln v_c(t) - \ln 5$

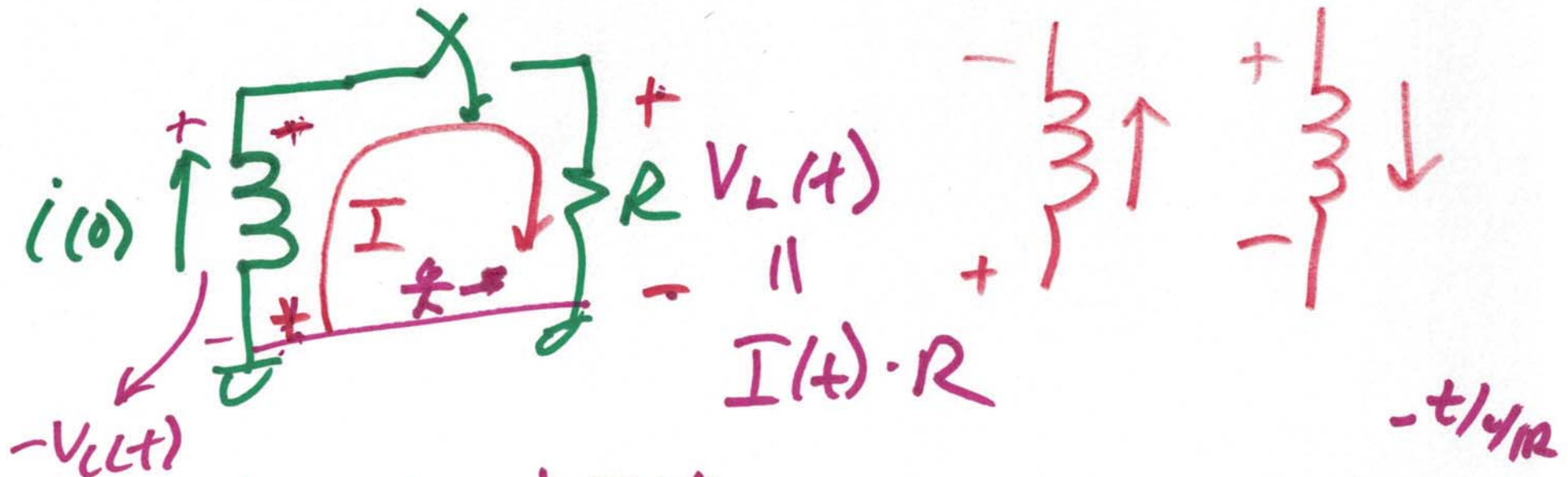

$$V_L(t) = L \cdot \frac{dI(t)}{dt}$$


$$V_L(t) = R \cdot I(t)$$

$$I(t) \cdot R + V_L(t) = 0 = I(t) \cdot R + L \cdot \frac{dI(t)}{dt}$$

$$-t/4R = -\frac{R}{L} \int_0^t dt = \int \frac{dI}{I}$$

$$I(t) = I(0) e^{-t/4R}$$

3)

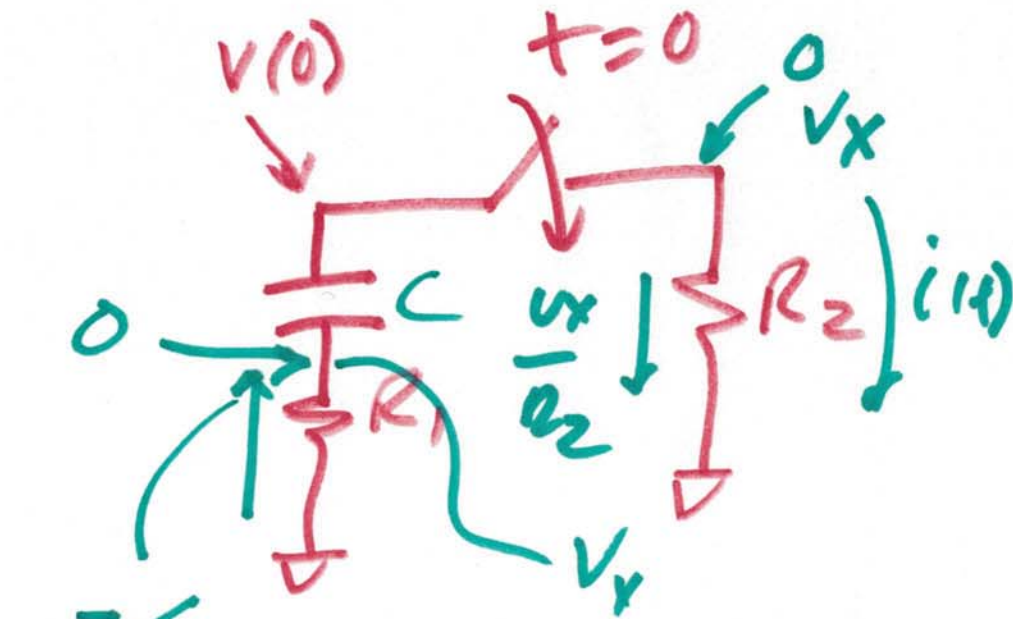

$$-V_y \frac{V_y}{R_1} = \frac{V_x}{R_2}$$

$$\tau = C \cdot (R_1 + R_2)$$


$$i(t) = \frac{V(0^-)}{R_1 + R_2} e^{-t/\tau}$$

$$I(0^+) = \frac{V(0^-)}{R_1 + R_2}$$

$$V_x = V(0^-) \frac{R_2}{R_1 + R_2} e^{-t/\tau}$$

$$V_y = V(0^-) \cdot \frac{R_1}{R_1 + R_2} e^{-t/\tau}$$

4)

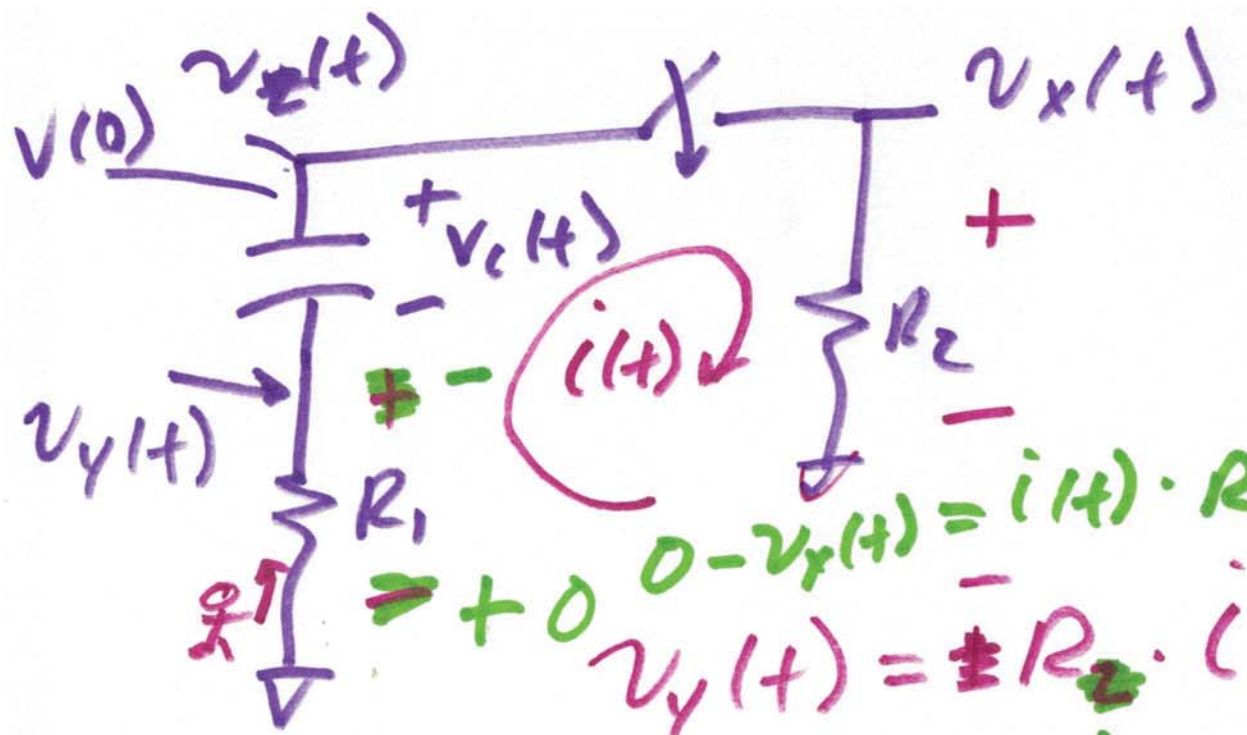

$$-i(t) = C \frac{dv_c(t)}{dt}$$

$$v_x(t) = R_2 \cdot i(t)$$

$$0 - v_y(t) = i(t) \cdot R_2$$

$$v_y(t) = R_2 \cdot i(t)$$

$$R \begin{cases} \downarrow I = \frac{v}{R} \\ \uparrow -I = \frac{v}{R} \end{cases}$$


$$v_y(t) + v_c(t) - v_x(t) = 0$$

$$-R_2 \cdot i(t) + v_c(t) - i(t) \cdot R_2 = 0$$

$$v_c(t) = v(0) \cdot e^{-\frac{t}{\tau}}$$

$$-R_1 \cdot i(t) + v_c(t) - i(t) \cdot R_2 = 0$$
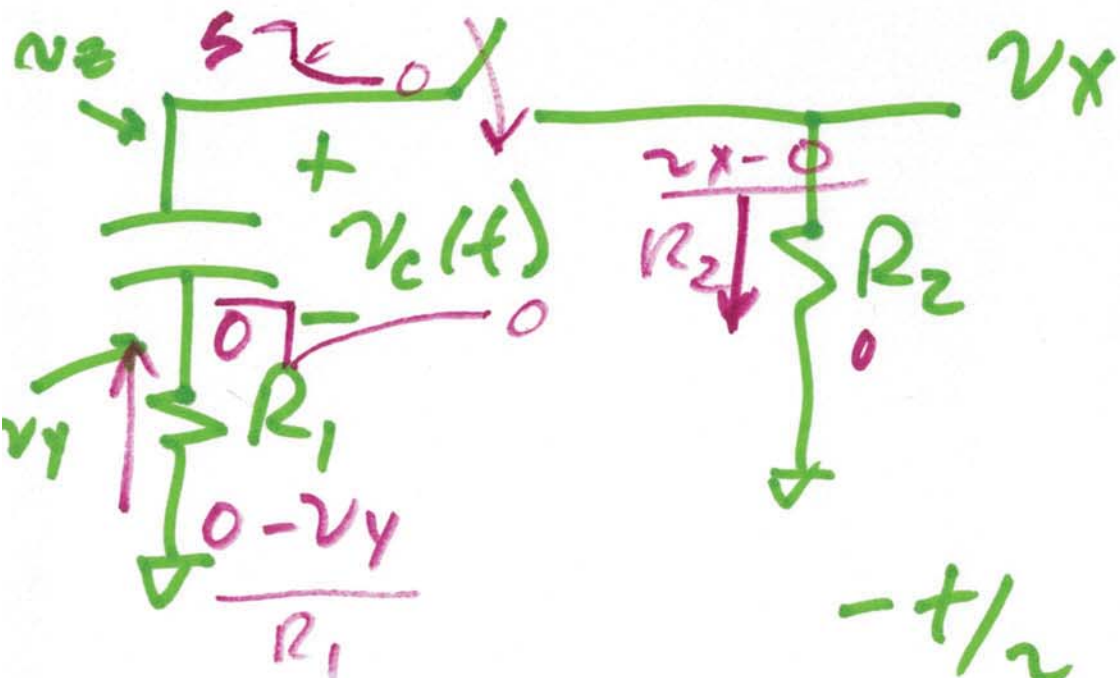
$$\frac{-(R_1 + R_2)C \frac{dv_c(t)}{dt}}{\tau} = v_c(t)$$



$$i(t) = \frac{v_x}{R_2} = -\frac{v_y}{R_1}$$

$$v_c(t) = v(0) e^{-t/\tau} = v_x - v_y$$

$$i(t) = C \frac{dv_c(t)}{dt} = C \cdot \left(\frac{v(0)}{C(R_1 + R_2)} \right) \cdot e^{-t/\tau}$$

$$i(t) = \frac{v(0)}{R_1 + R_2} \cdot e^{-t/\tau}$$

