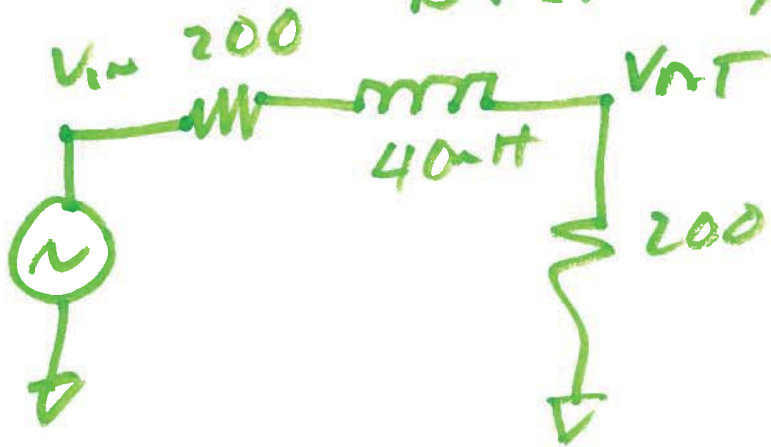


EE 220 Circuits 1

Lecture 27

$$s = \sigma + j\omega$$

Dec. 6, 2017




$$V_{out} = V_{in} \cdot \frac{200}{200 + 200 + j\omega(0.04)}$$

$$\frac{V_{out}}{V_{in}} = \frac{200}{400 + j \cdot 2\pi \cdot (0.04) \cdot f}$$


$$f_p \Rightarrow 2\pi(0.04) \cdot f_p = 400$$

$$f_p = 1.59 \text{ kHz}$$

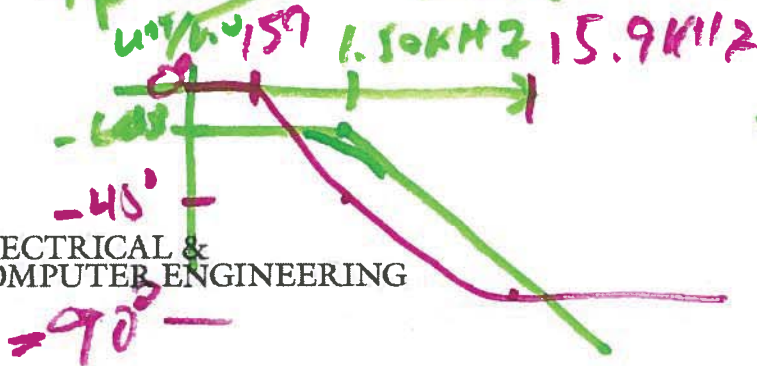

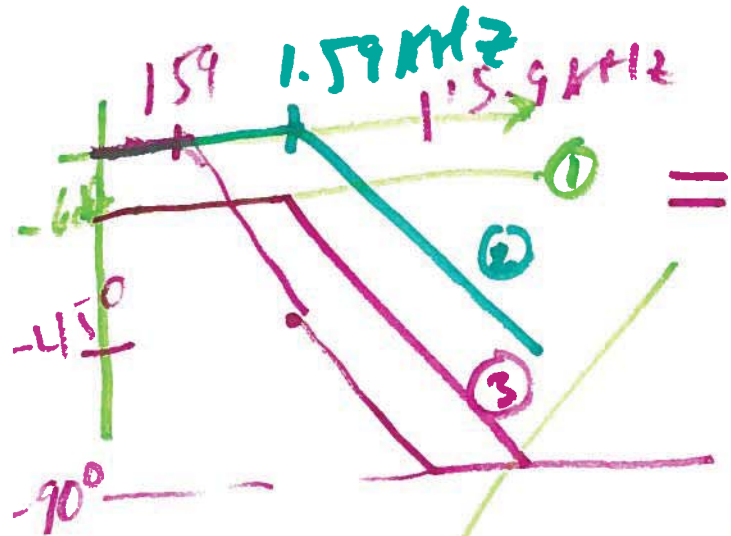1)

$$\frac{V_{out}}{V_{in}} = \frac{200}{400 + j2\pi(0.04) \cdot f}$$



$$\frac{200}{400} \cdot \frac{1}{1 + j2\pi(0.04) \cdot \frac{f}{400}}$$

$$f_p = \frac{1}{2\pi \cdot \frac{(0.04)}{400}} = 1.59 \text{ kHz}$$

$$\angle \frac{V_{out}}{V_{in}} = -\tan^{-1} \frac{f}{1.59 \text{ kHz}}$$

$$2\pi \cdot \frac{(0.04)}{400} = \frac{1}{f_p}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{2} \cdot \frac{1}{1 + j \frac{f}{f_p}} = \left(\frac{1}{2}\right) \cdot \frac{1}{1 + j \frac{f}{1.59 \text{ kHz}}}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{\left(\frac{1}{2}\right)^2 + 0^2}{\sqrt{1^2 + \left(\frac{f}{1.59 \text{ kHz}}\right)^2}}$$

$$\frac{V_{NT}}{V_{IN}} = \frac{- \cdot 100 + j \cdot 10000 \cdot f}{200 + j \cdot 10,000 \cdot f}$$


$$= \frac{100 \cdot (-1 + j0)(1 + j10f)}{200(1 + j \cdot 50f)}$$

$$= \frac{(\frac{1}{2} + j \cdot 0)(-1 + j0)(1 + j \frac{f}{0.1})}{(1 + j \frac{f}{0.02})}$$

$$\angle \frac{V_{NT}}{V_{IN}} = \tan^{-1} \frac{0}{\frac{1}{2}} + \tan^{-1} \frac{0}{-1} + \tan^{-1} \frac{f}{0.1} - \tan^{-1} \frac{f}{0.02}$$

$$\tan^{-1} \frac{0}{\frac{1}{2}}$$


$$\tan^{-1} \frac{0}{-1}$$

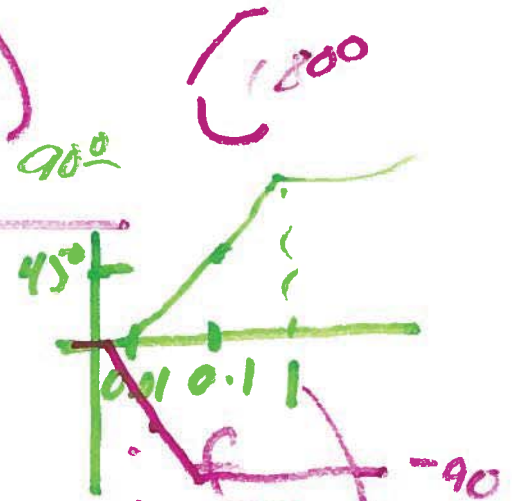

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{\sqrt{\left(\frac{1}{2}\right)^2 + 0^2} \cdot \sqrt{(-1)^2 + (0)^2} \cdot \sqrt{1 + \left(\frac{f}{0.1}\right)^2}}{\sqrt{1 + \left(\frac{f}{0.02}\right)^2}}$$

→ FINAL EXAM ←

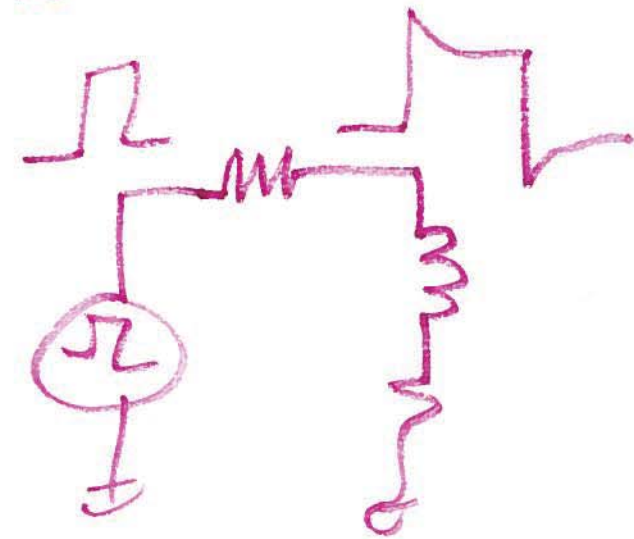- Bode plots
- PHASOR ANALYSIS
- Integrators ←
- RMS



First-order circuits → time domain

RC, CR
 LR, RL
 $\tau = RC$
 $= \frac{1}{R}$


Dependent sources
 power
 mesh Analysis
 superposition
 op-amp, Ohm's law KVL, KCL

$$\frac{1}{2\pi \cdot 10^{-3} \cdot 159} = 1 \quad (0\text{dB})$$

$$\frac{1}{2\pi \cdot 10^{-3} \cdot 1590} = 10 \quad (20\text{dB})$$

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{1}{2\pi \cdot 10^{-3} \cdot f}$$
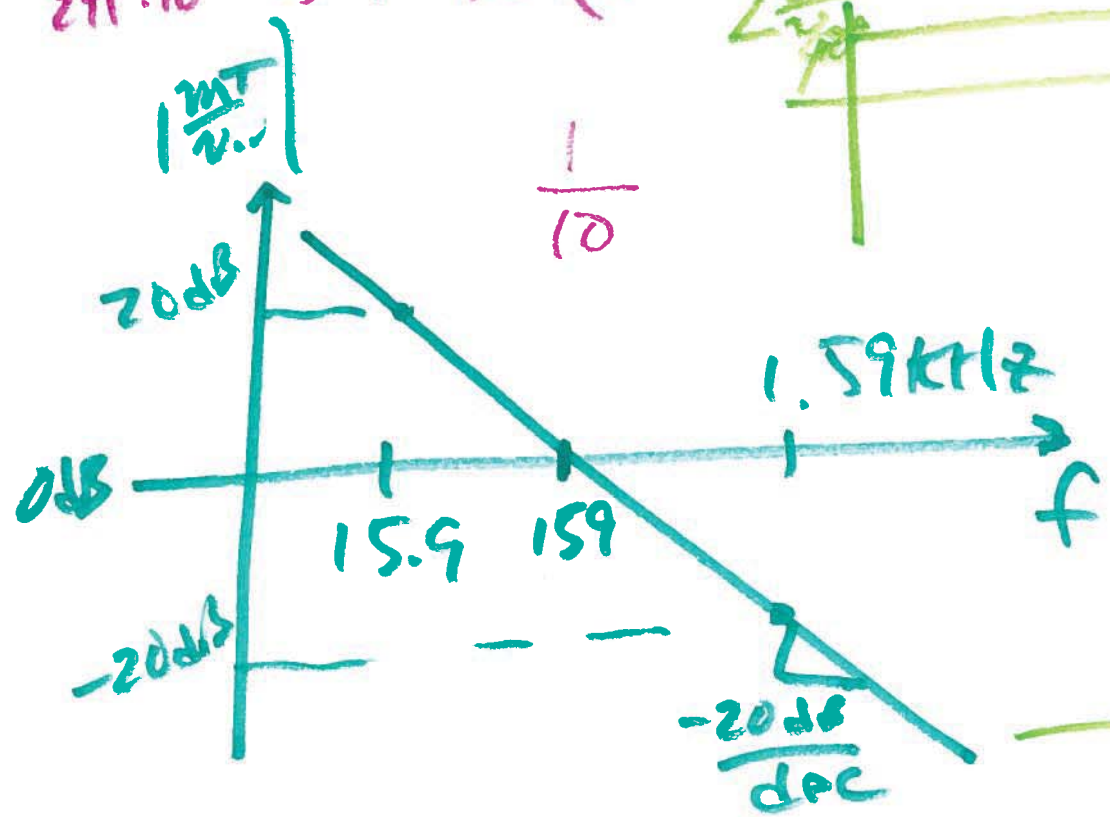
$$\angle \frac{v_{out}}{v_{in}} = 180^\circ - 90^\circ = +90^\circ$$




$$- \frac{1}{j \cdot 2\pi \cdot 10^{-3} f} \cdot \frac{j}{j}$$

$$= \frac{j}{2\pi \cdot 10^{-3} f}$$

$$\frac{1}{2\pi \cdot 10^{-3} \cdot 10} = 1 \rightarrow f = \frac{1}{2\pi \cdot 10^{-3}} = 159 \text{ Hz}$$

6)



Frequency Response of an integrator

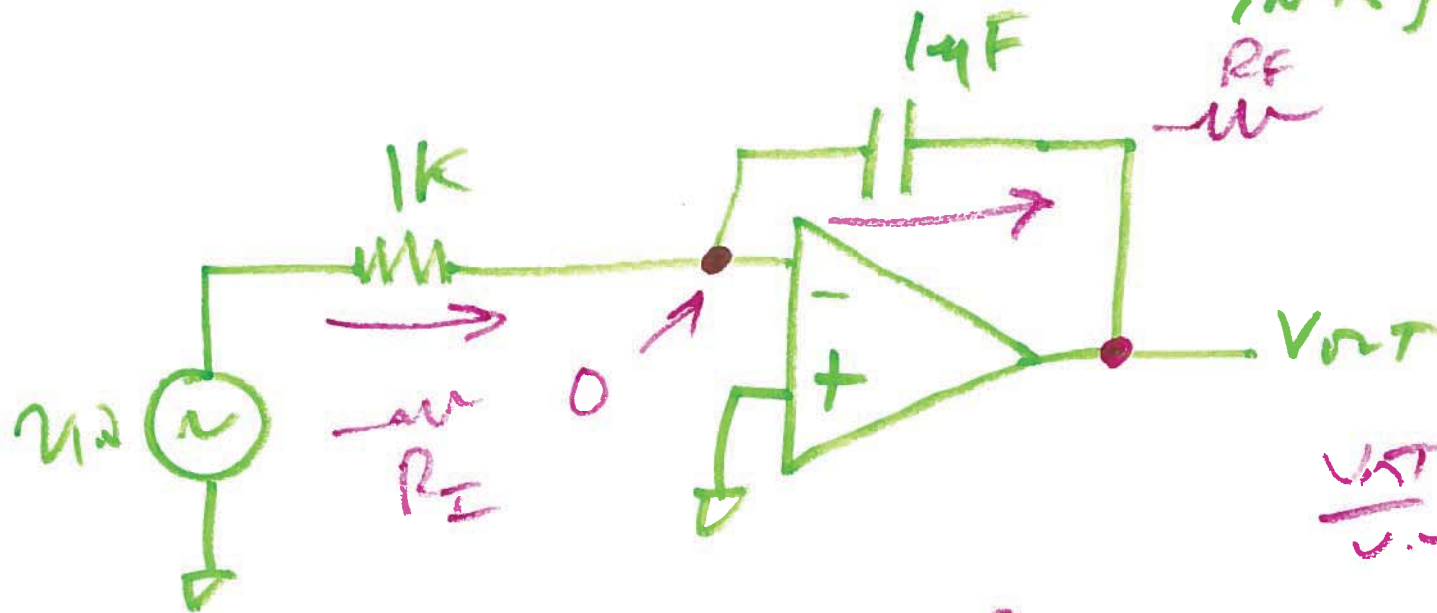

$$\frac{v_o(t)}{v_i} = -\frac{R_F}{R_I}$$

$$\frac{v_i \sin(\omega t)}{1k} = \frac{0 - v_o(t)}{1/j\omega \cdot 1\mu F}$$

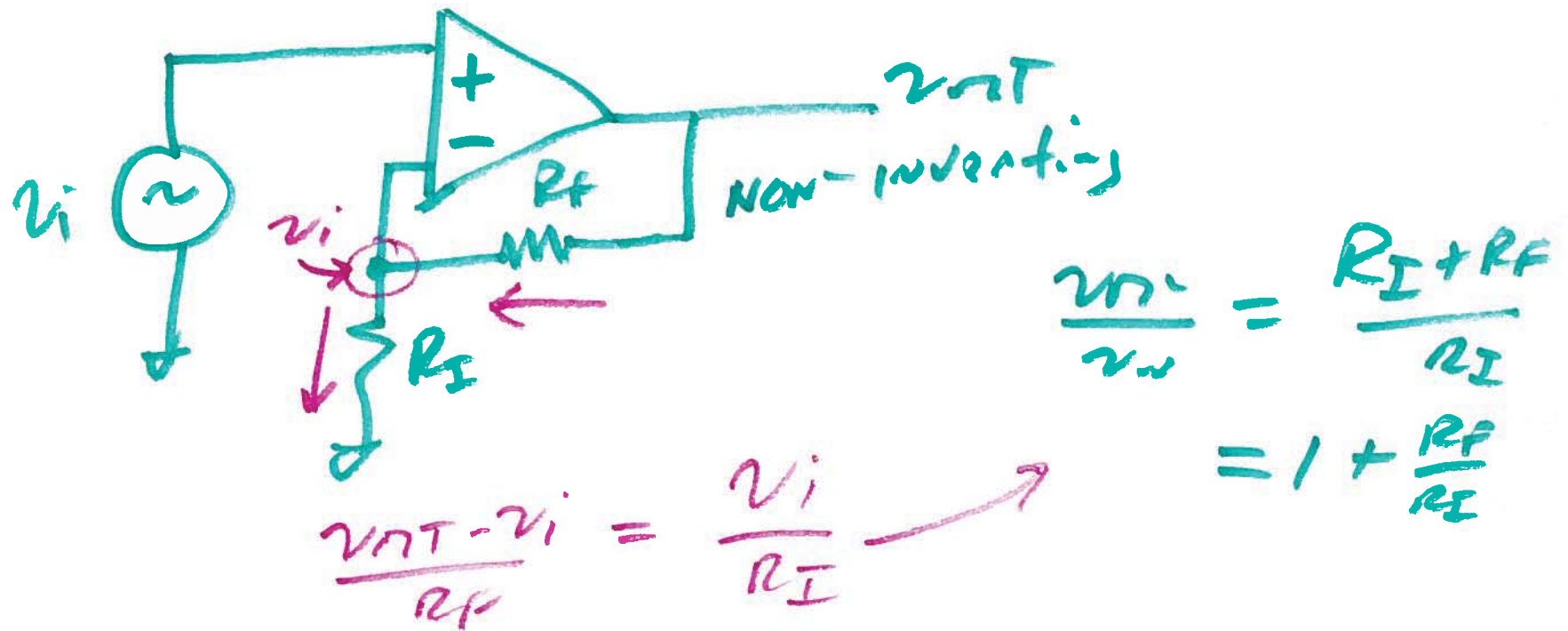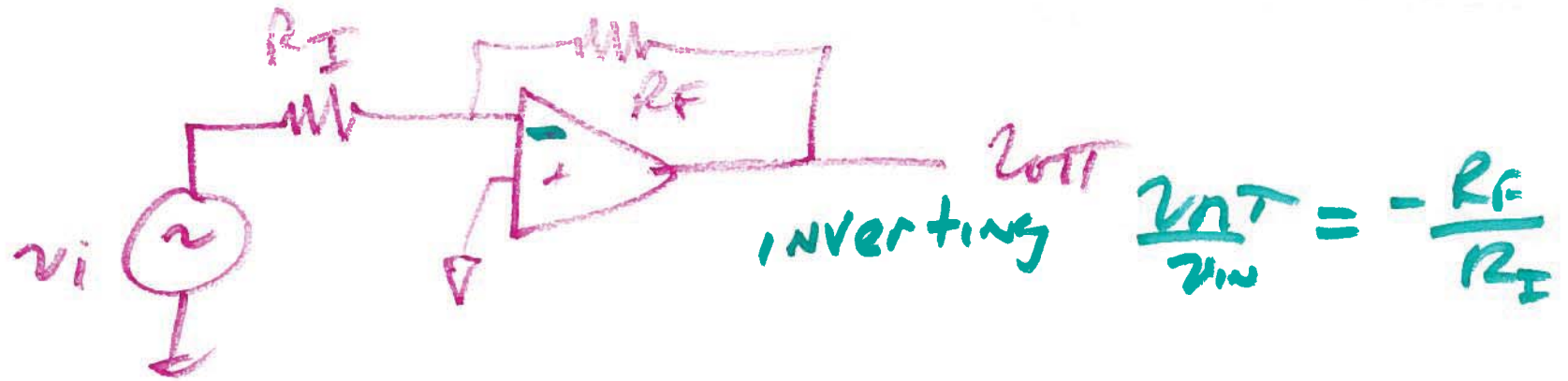
$$\frac{v_o(t)}{v_i} = -\frac{1/j\omega \cdot 1\mu F}{1k} = -\frac{1}{j \cdot 2\pi \cdot 10^{-3} \cdot f}$$



Q)

RMS
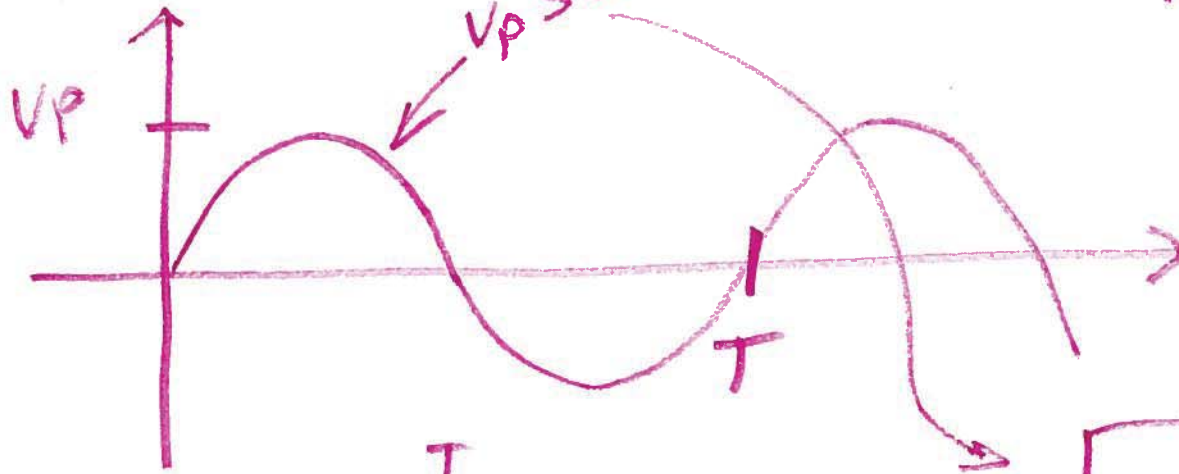
$$P = \frac{V_{RMS}^2}{R} = I_{RMS}^2 \cdot R$$



$$V_{RMS}^2 = \frac{1}{T} \int_0^T V_P^2 \sin^2 2\pi f \cdot t \, dt$$

$$\sin^2 x = \frac{1}{2}(1 - \cos 2x)$$


$$= \left(\frac{V_P^2}{T} \right) \int_0^T (1 - \cos 2(2\pi f \cdot t)) \cdot dt$$

$$u = 2\pi f \cdot t$$

$$du = 2\pi f \cdot dt$$

$$dt = \frac{du}{2\pi f}$$

9)

$$= \frac{V_P^2}{T^2} \int_0^T dT - \frac{1}{\pi T} \int_0^T \cos u \cdot du$$


$$V_{RMS}^2 = \frac{V_P^2}{2\pi} \cdot (\pi - 0)$$

$$V_{RMS}^2 = \frac{V_P^2}{2}$$

$$V_{RMS} = \frac{V_P}{\sqrt{2}}$$