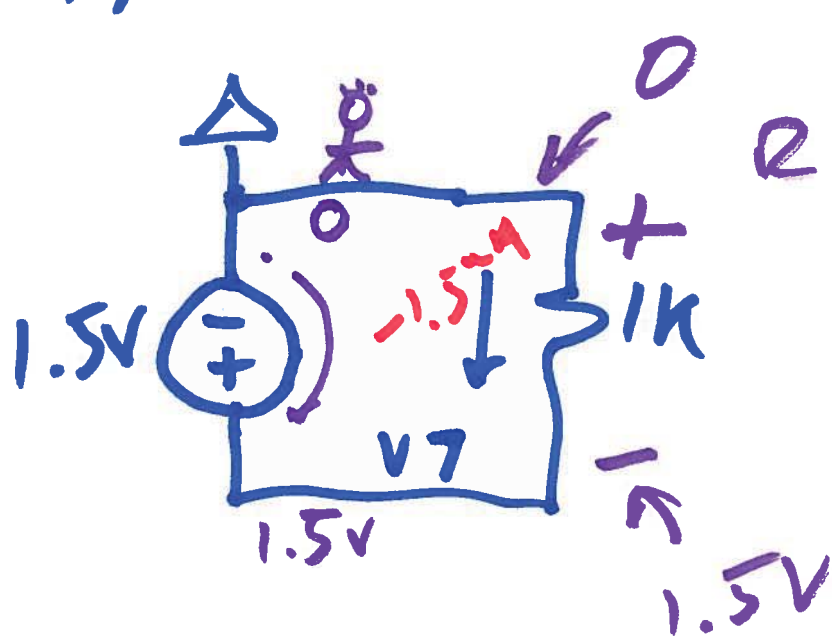


# EE 220 Circuits I

Lecture 2  
Aug. 30, 2017


1)



$$V = I \cdot R \text{ (ohm's law)}$$

$$I = \frac{0 - 1.5}{1k} = -1.5 \mu A$$


1)

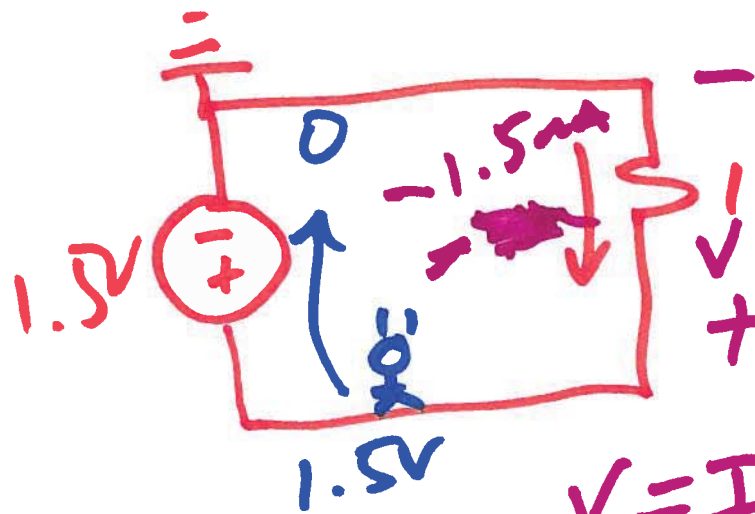

$$\begin{aligned}
 & \left. \begin{array}{l} 0 \\ + \\ - \\ 1.5 \end{array} \right\} v = 0 - 1.5 \\
 & v = -1.5V
 \end{aligned}$$



$$\begin{aligned}
 & V_+ - V_- = -1.5V \\
 & I = \frac{V}{R} = \frac{1.5 - 0}{1k} = 1.5\mu A
 \end{aligned}$$
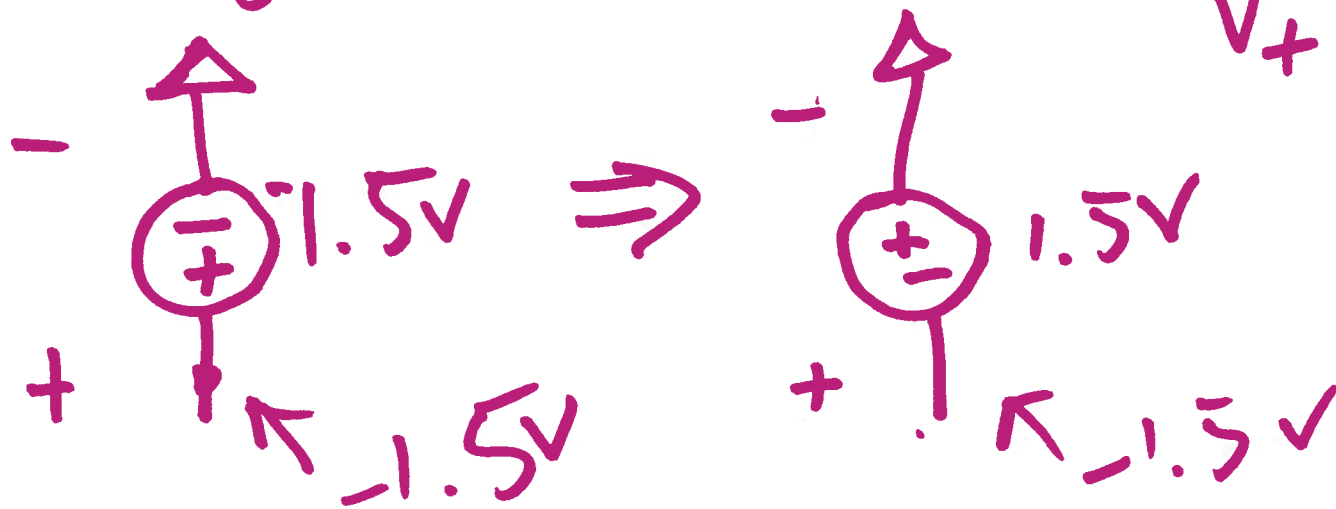
$$I = \frac{V}{R} = \underline{\underline{-1.5\mu A}}$$




$$\begin{aligned}
 & V_+ - V_- = -1.5V \\
 & V_+ = -1.5V
 \end{aligned}$$

2)

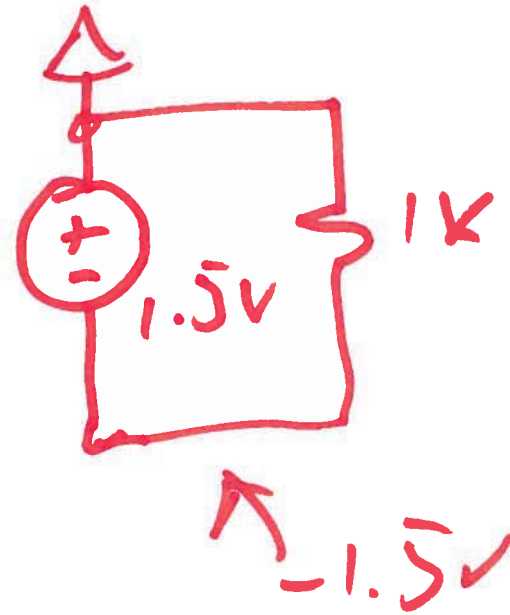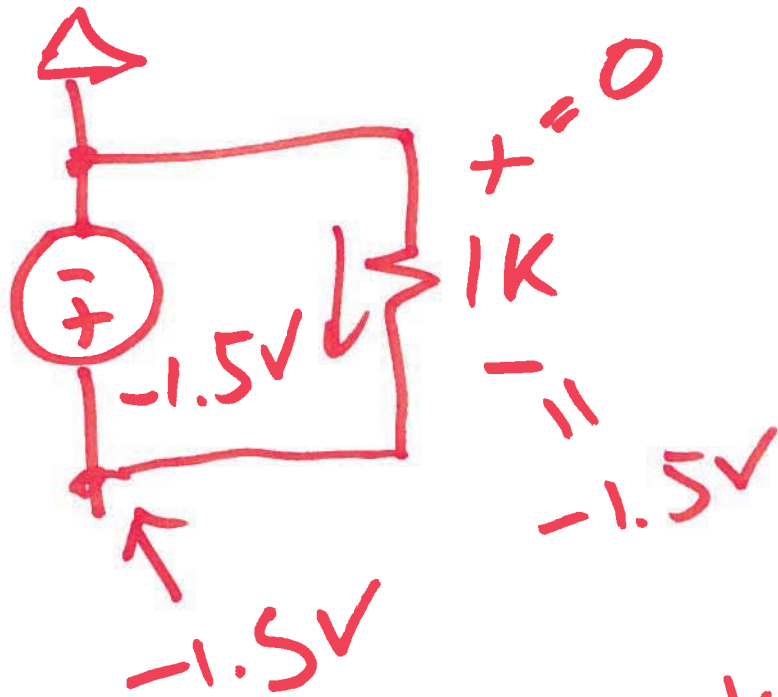

$$I = \frac{V_+ - V_-}{1k} = \frac{0 - (-1.5V)}{1k} = \underline{\underline{1.5mA}}$$

3)

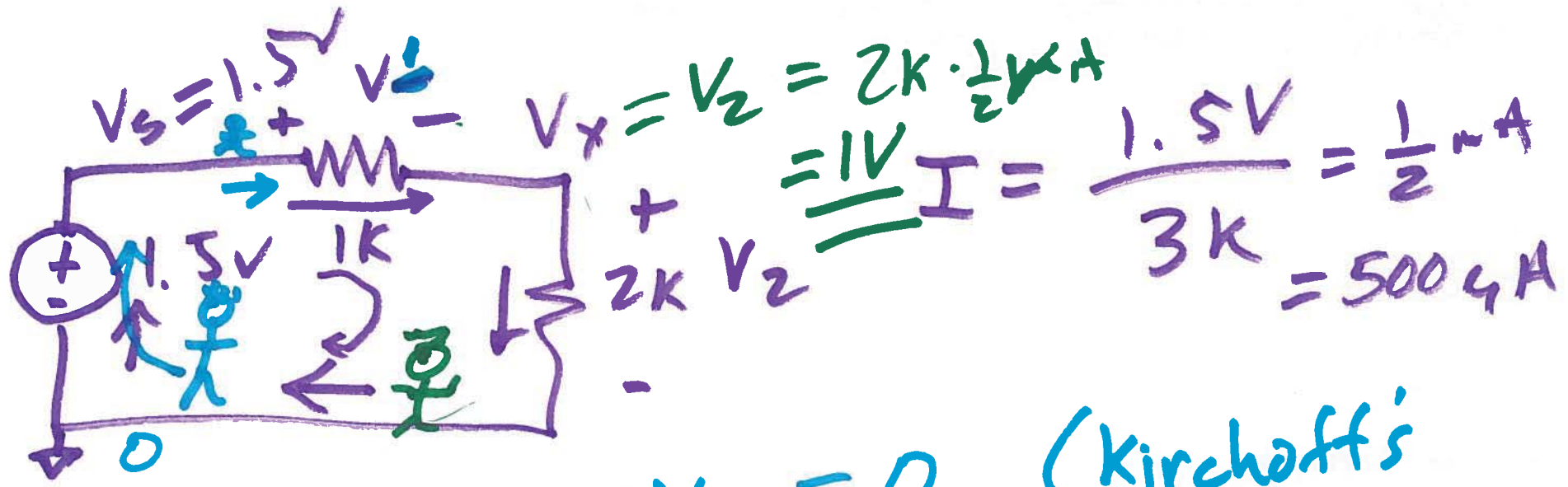


$$1.5V - V_1 - V_2 = 0 \quad (\text{Kirchoff's Voltage Law})$$

$$V_2 + V_1 - 1.5 = 0$$


$$I \cdot 2k + I \cdot 1k - 1.5 = 0$$

$$I = \frac{1.5}{3k} = \frac{1}{2} \mu A$$

4)

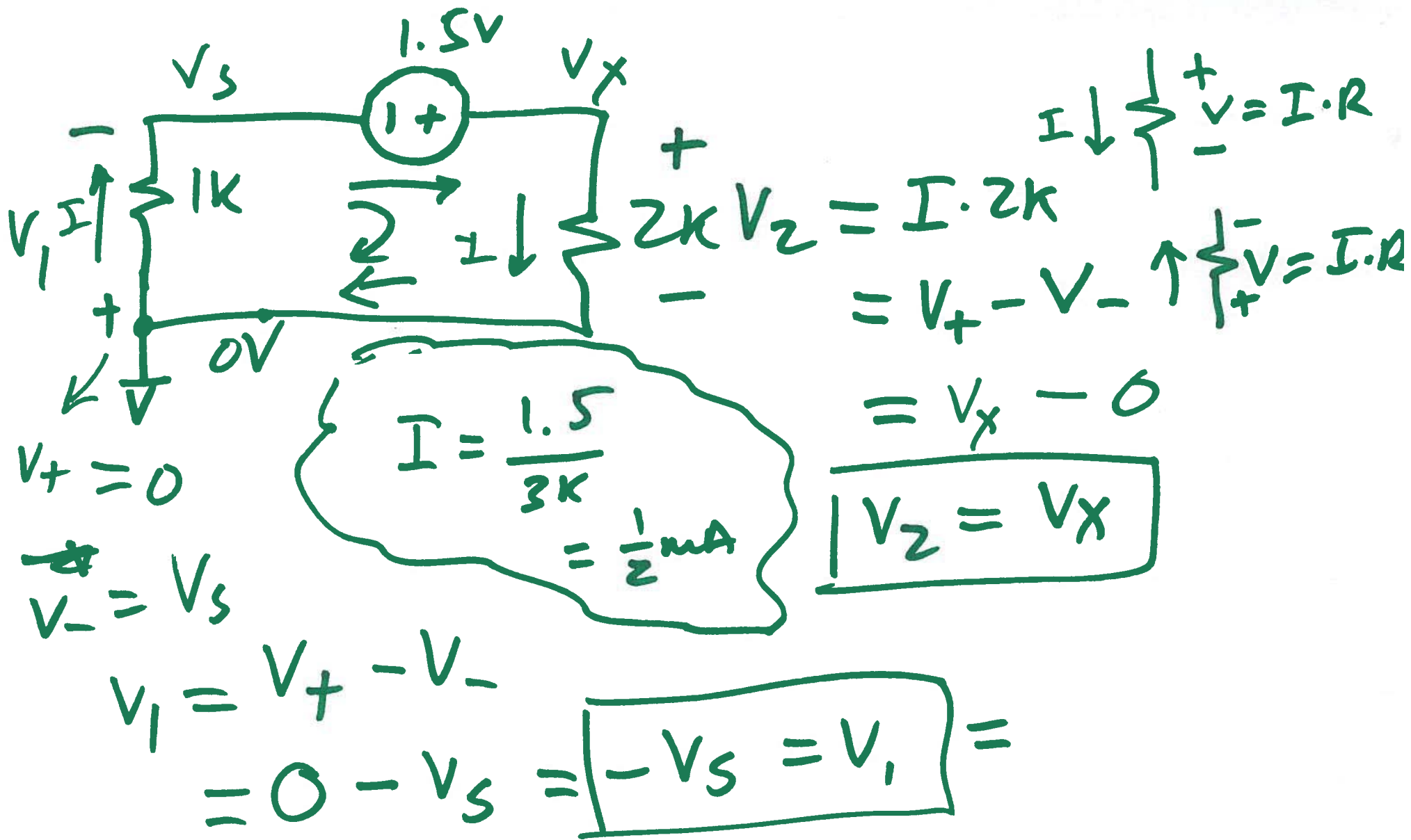

5)

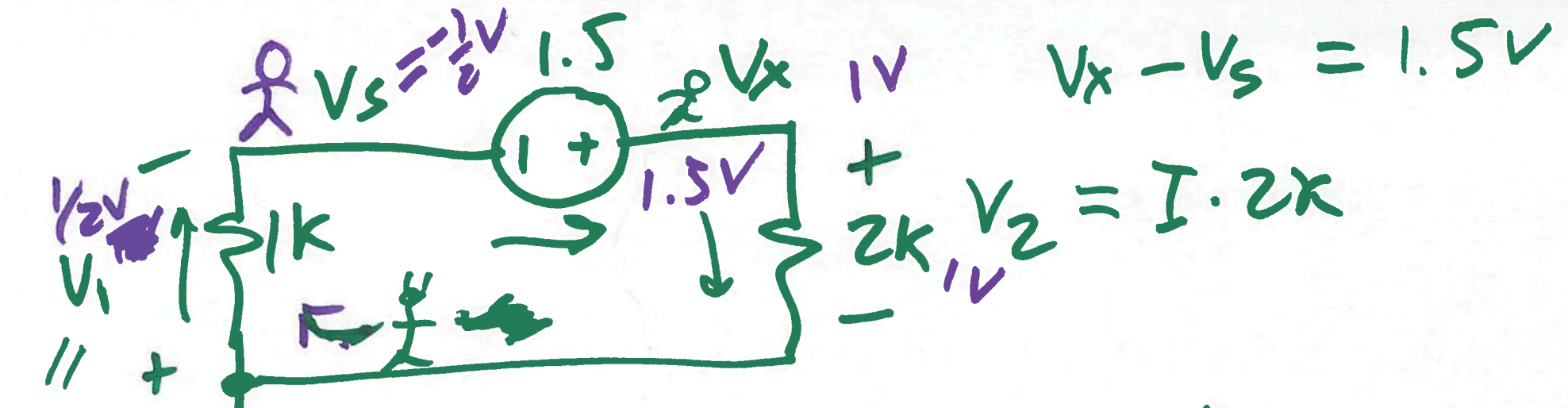

$$I \cdot 1k \quad V_2 - 1.5 + V_1 = 0$$


$$V_s = -0.5V \quad I \cdot 2k - 1.5 + I \cdot 1k = 0$$

$$-0.5V + 1.5V - 1V = 0 \quad I = \frac{1.5}{3k} = \frac{1}{2} \mu A$$

$$V_2 = \frac{1}{2} \mu A \cdot 2k = 1V$$


$$V_1 = \frac{1}{2} \mu A \cdot 1k = \frac{1}{2} V$$

b)

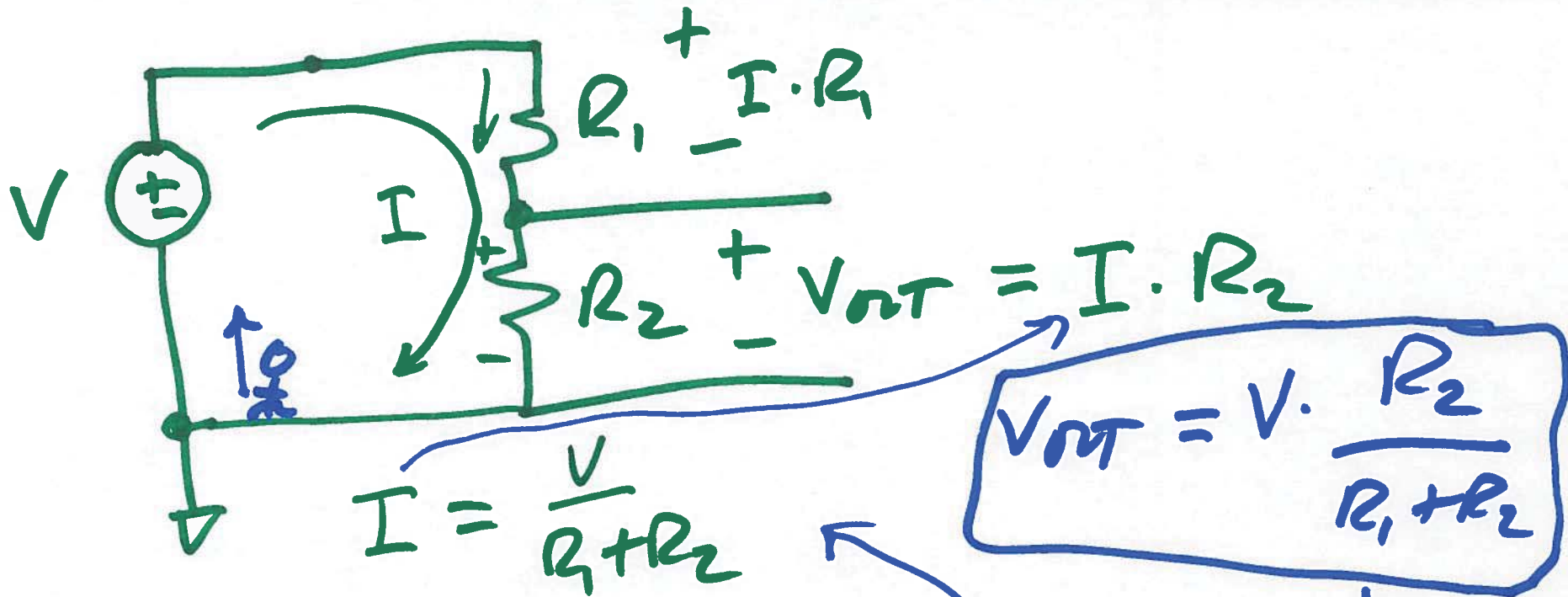

$$V - I \cdot R_1 - I \cdot R_2 = 0 \quad \downarrow$$

voltage divider equation

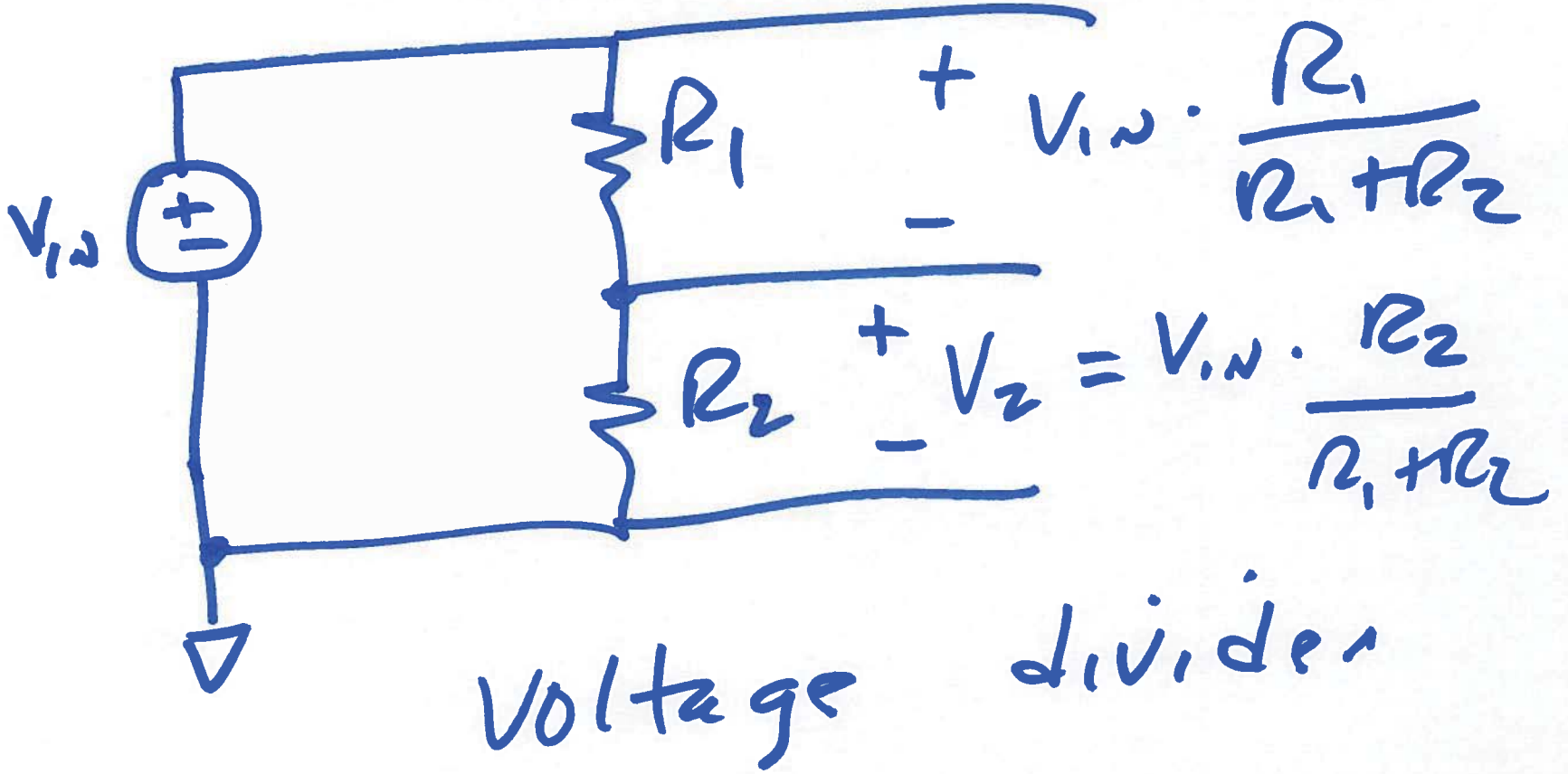


8)



# Example

## Problem 1

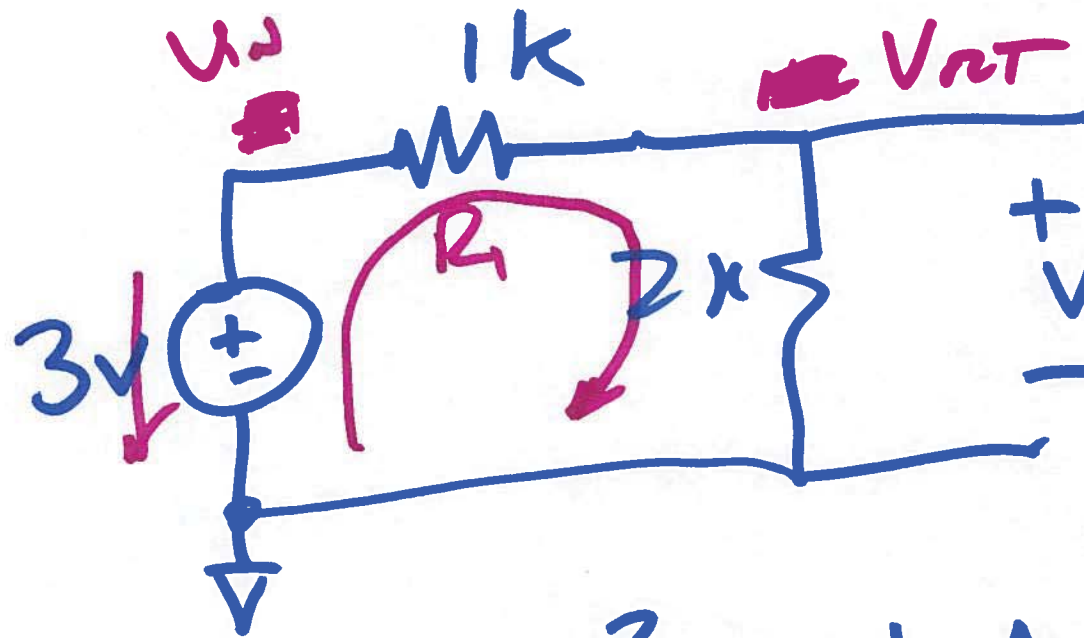

```


VI  VIN  0  DC  3V
R1  V.1  Vout  1k
R2  Vout  0  2k
    
```


$V_{out} = ?$   
 + .OP  
 - .END

$$I = \frac{3}{3k} = 1mA$$

$$\begin{aligned}
 V_{out} &= \frac{3 \cdot 2k}{2k + 1k} \\
 &= \frac{6k}{3k} = \underline{\underline{2V}}
 \end{aligned}$$

9)

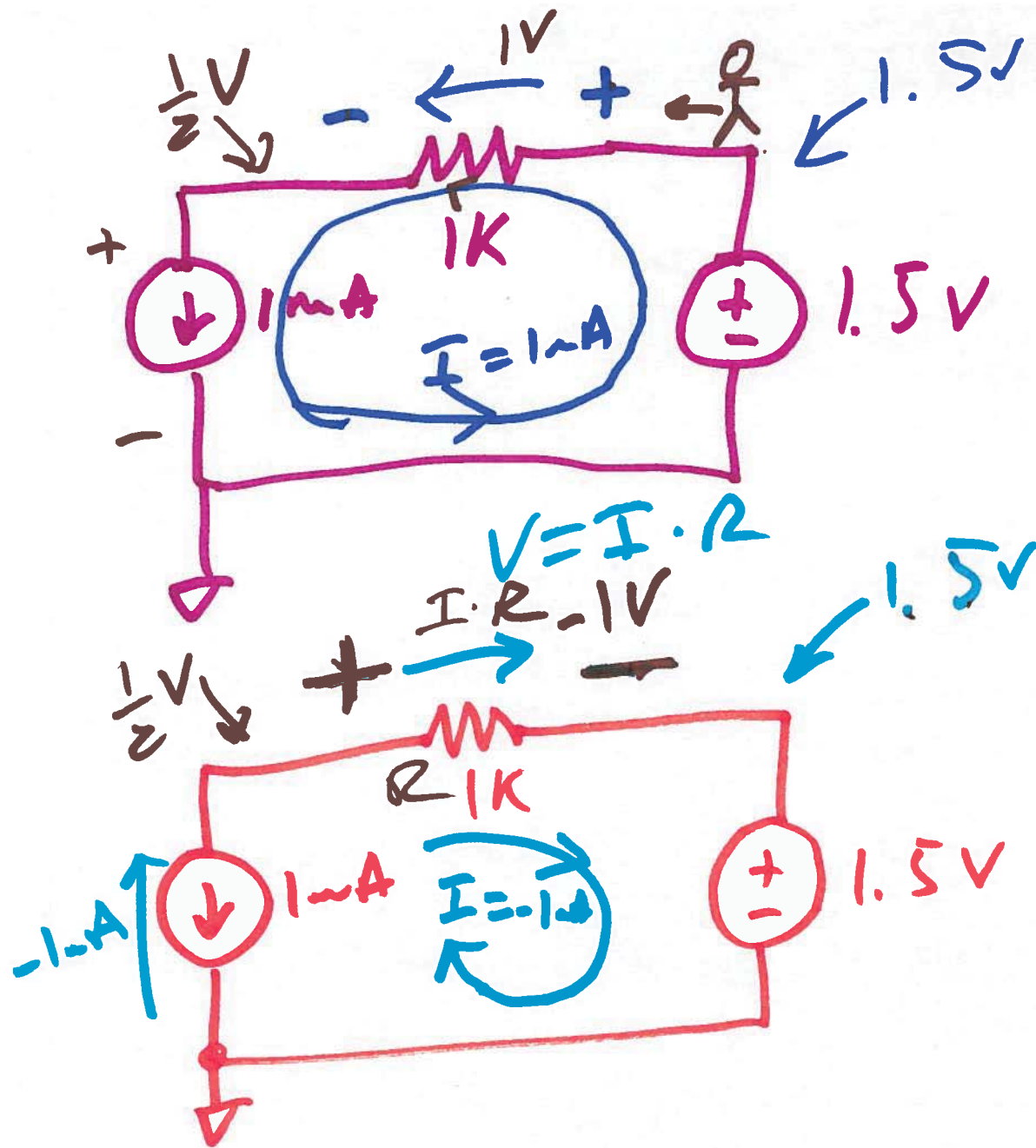

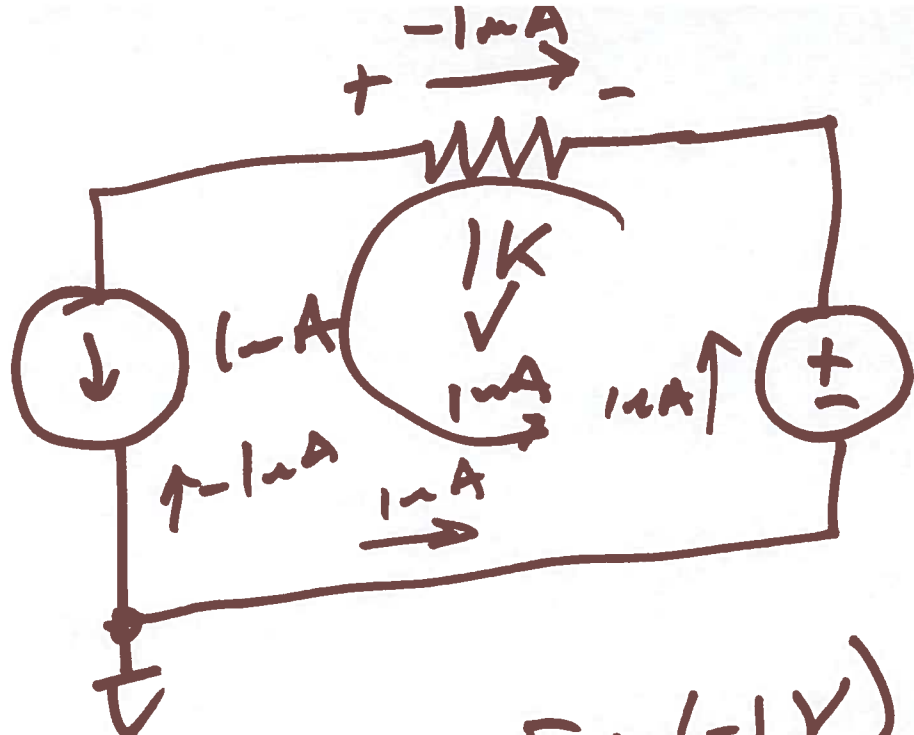


$$V = I \cdot R$$

$$= (-1.0 \mu A) \cdot 1k$$


$$= -1V$$

$$1.5 + (-1V) = \frac{1}{2} V = 0.5V$$

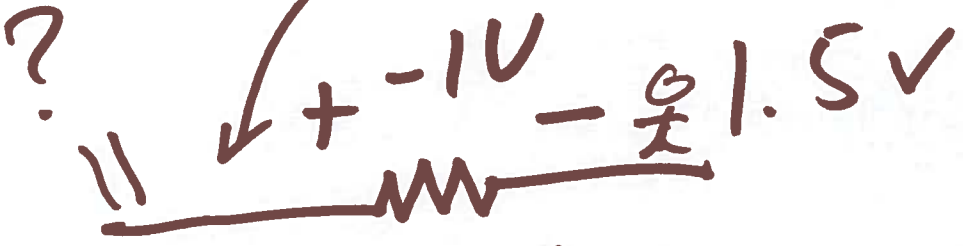

$$1.5 - 1V = \frac{1}{2} V$$

11)

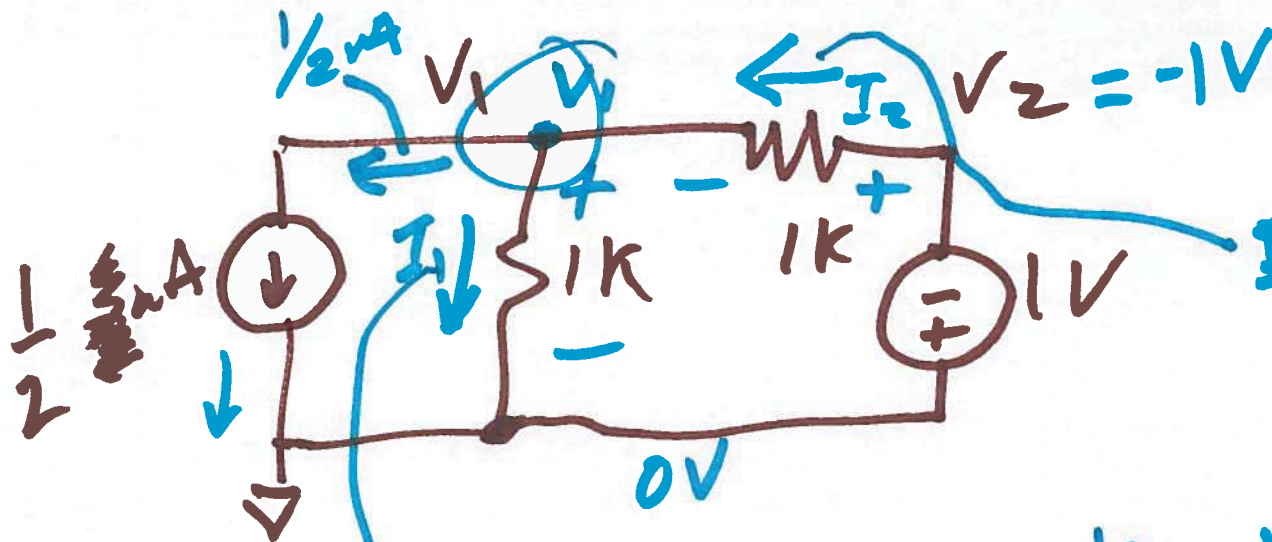


$$I_2 \cdot 1k = \frac{V}{2} - V_1 - 1V$$

$$I_1 \cdot R = V_1$$


$$I_1 = \frac{V_1}{R}$$

Kirchoff's current law

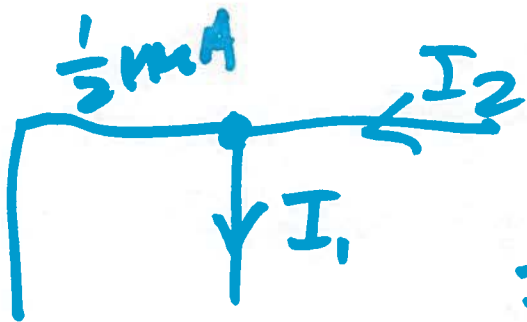Sum of currents into a node must equal zero


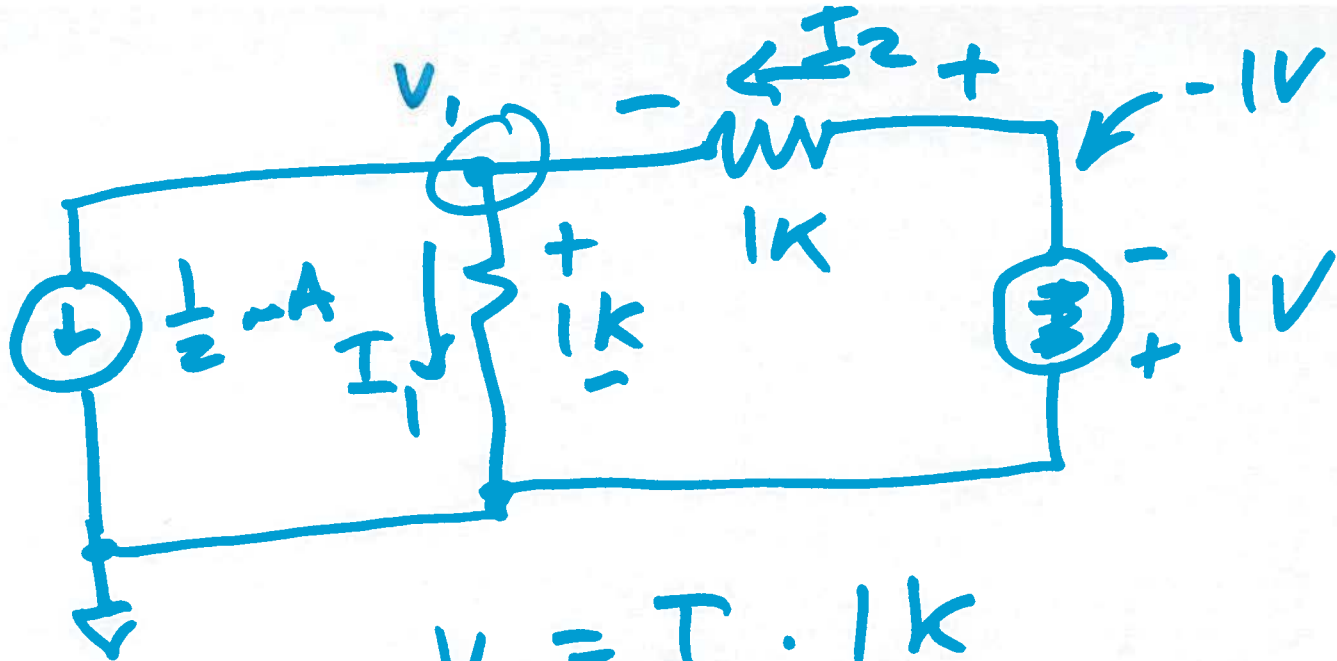
$$\frac{1}{2} \text{ mA} + I_1 + I_2 = 0$$



$$V_1 = I_1 \cdot 1k$$

$$-1 - V_1 = I_2 \cdot 1k$$

$$\frac{1}{2} \mu A + I_1 - I_2 = 0$$