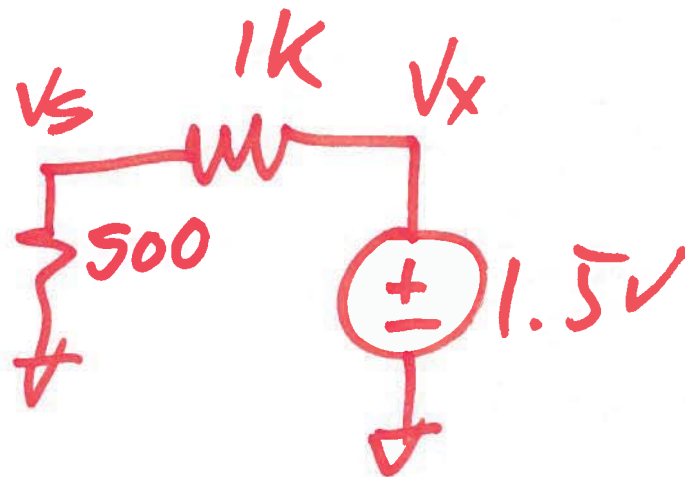


EE 220

Circuits I

9/11/2017


Lecture 4



$$V_s = 1.5 \cdot \frac{500}{500 + 1000}$$


$$V_s = 0.5 \text{ V} \\ = \underline{\underline{500 \text{ mV}}}$$

1)

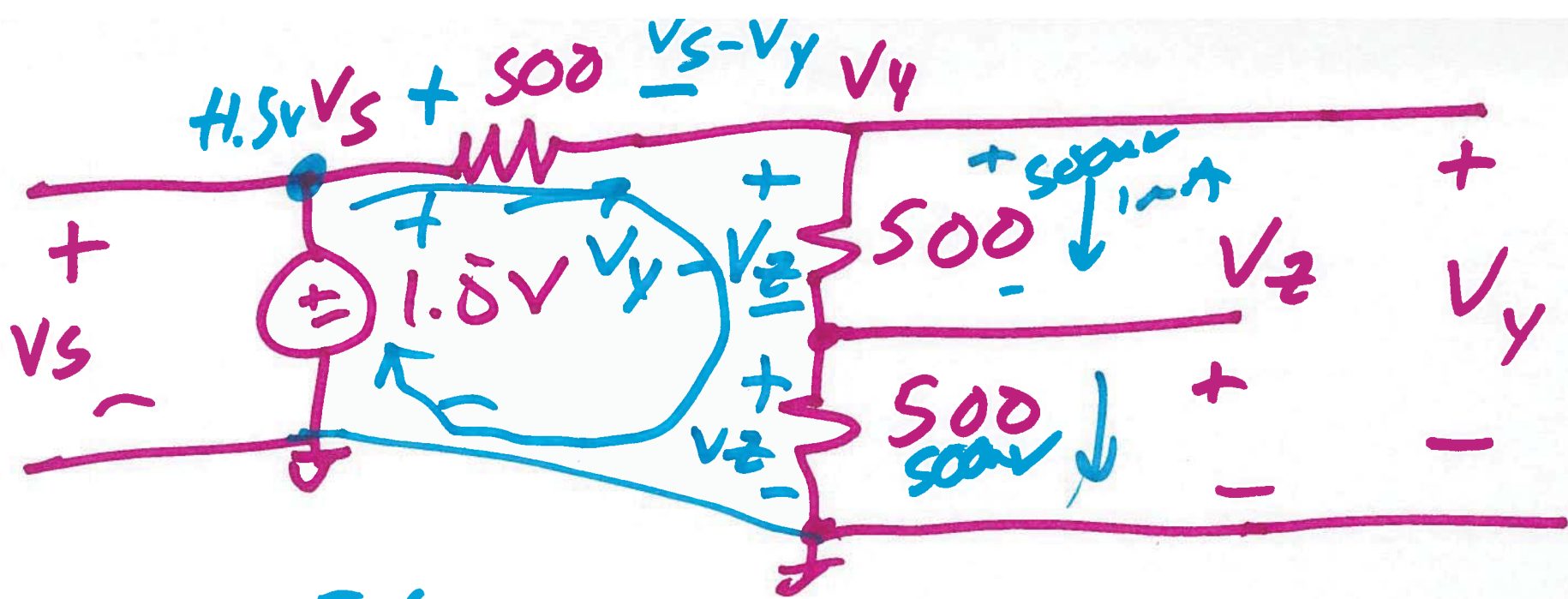


$$\frac{1.5V}{500 + 500 + 500} = \frac{1.5V}{1.5K} = 1\ \mu A$$

$$1.5 \cdot 500 / (500 + 500 + 500) =$$

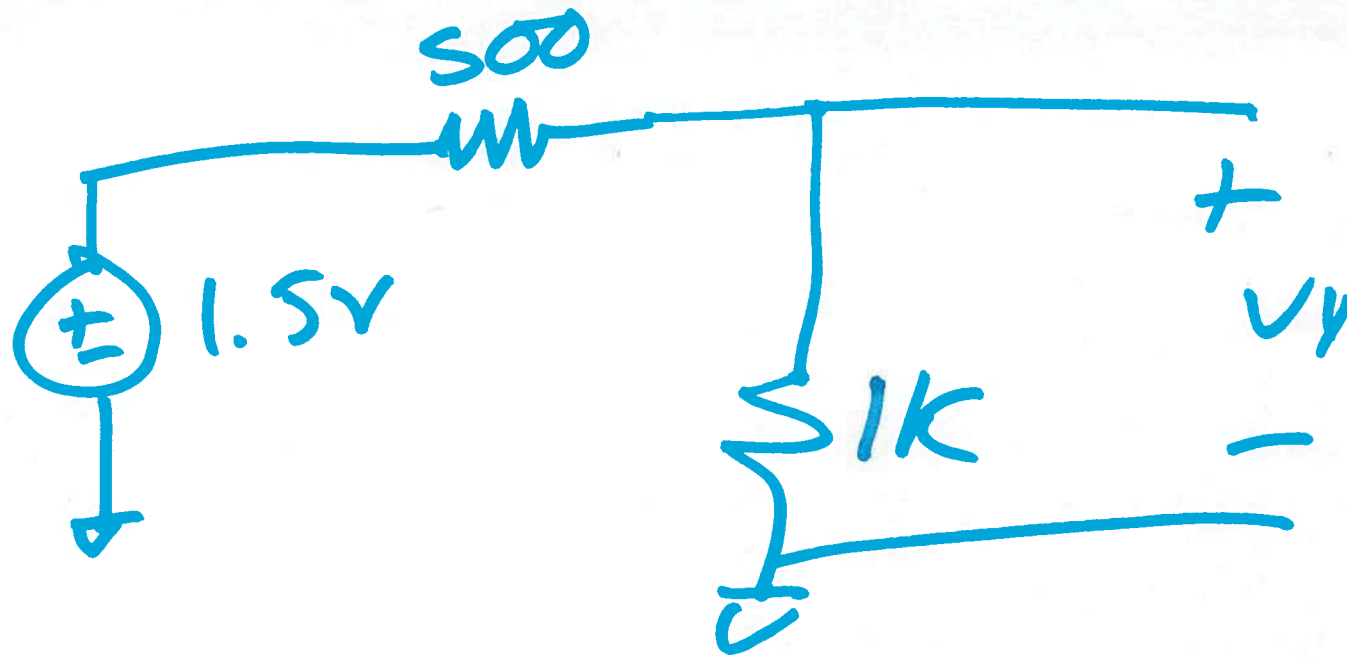

$$V_Y = 1.5 \cdot \frac{1K}{1K + 500}$$


$$V_Y = 1V$$

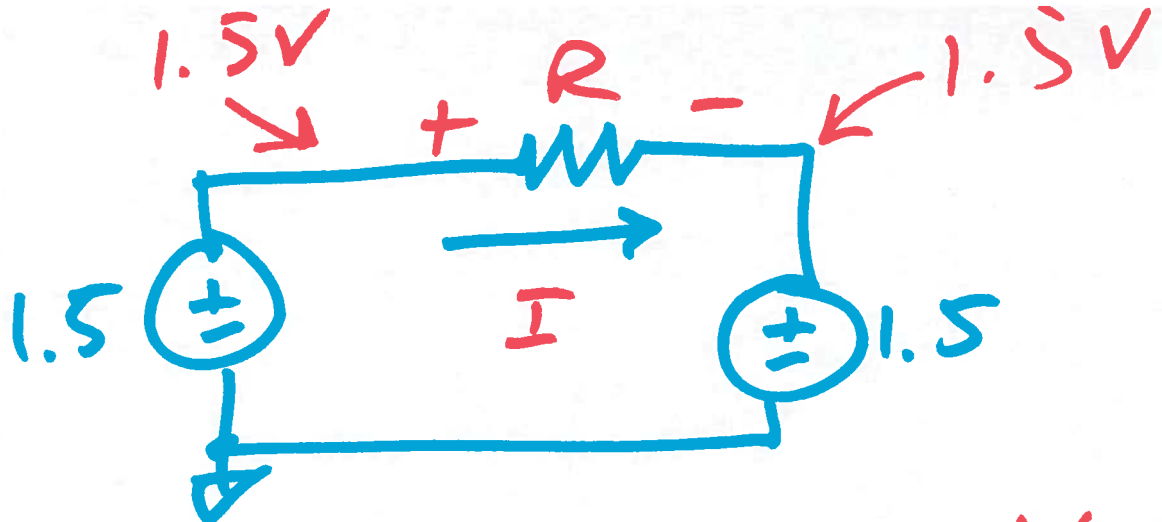


$$I = \frac{V_+ - V_-}{R} = \frac{1.5 - 1.5}{R}$$

$$I = 0$$

4)

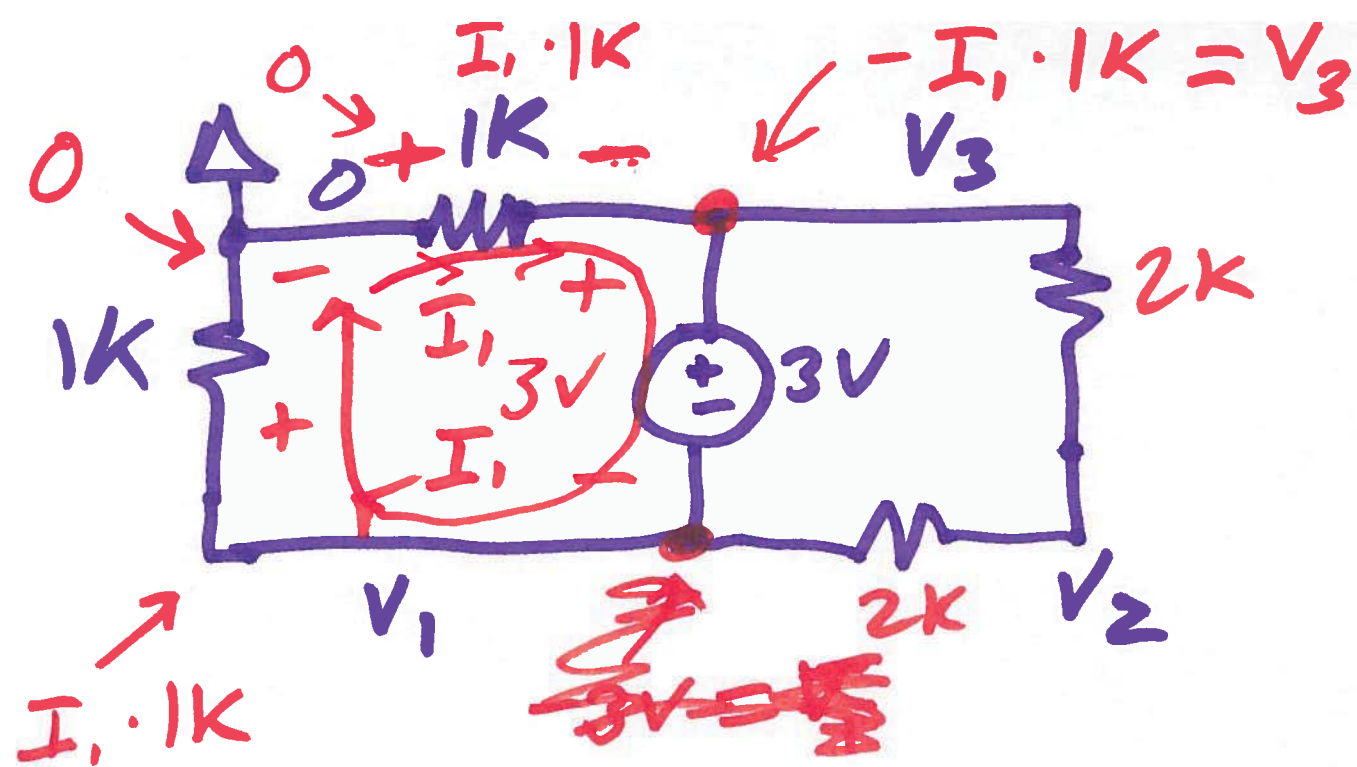

$$V_+ - V_- = I_1 \cdot 1K$$

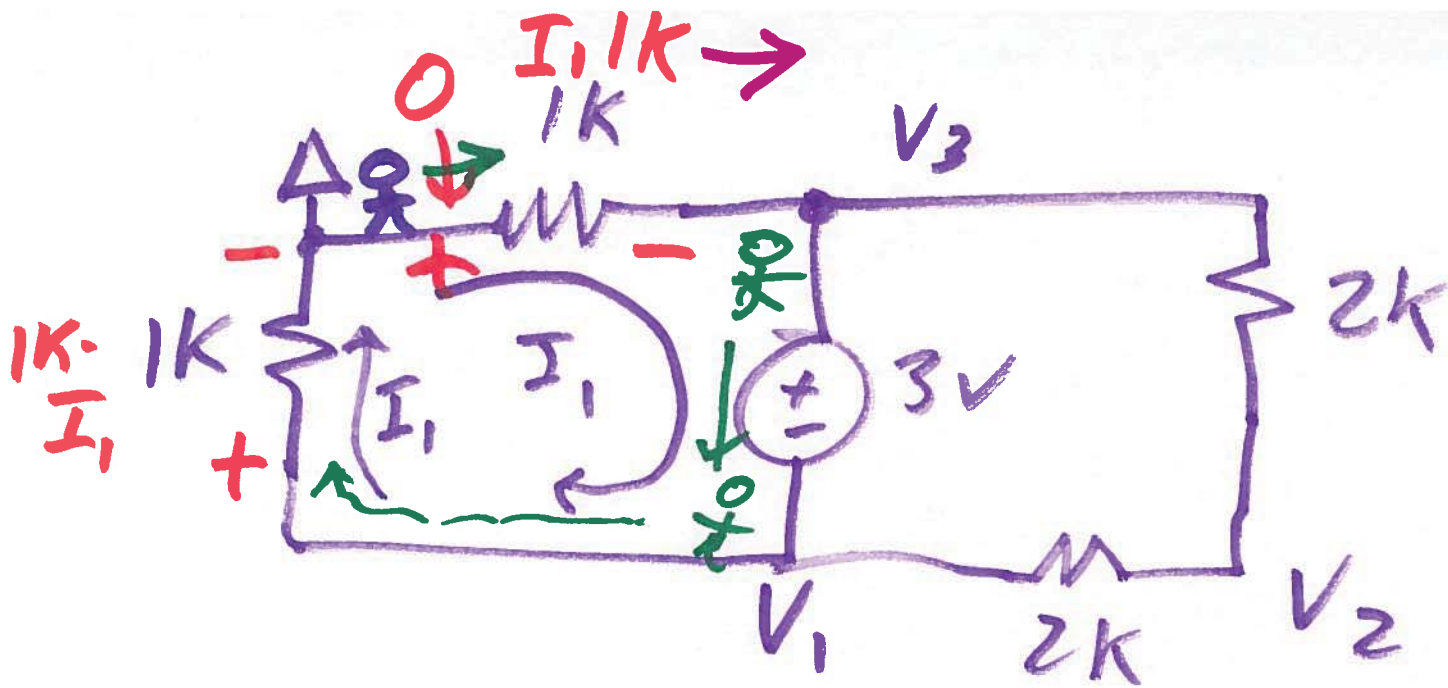


$$I_1 \cdot 1k = \frac{V_1}{1k} - \frac{V_3}{1k}$$

$$V_3 = -I_1 \cdot 1k$$

$$-I_1 \cdot 1k - 3V - I_1 \cdot 1k = 0$$


$$-3V = I_1 \cdot 2k$$

$$I_1 = -1.5 \mu A$$

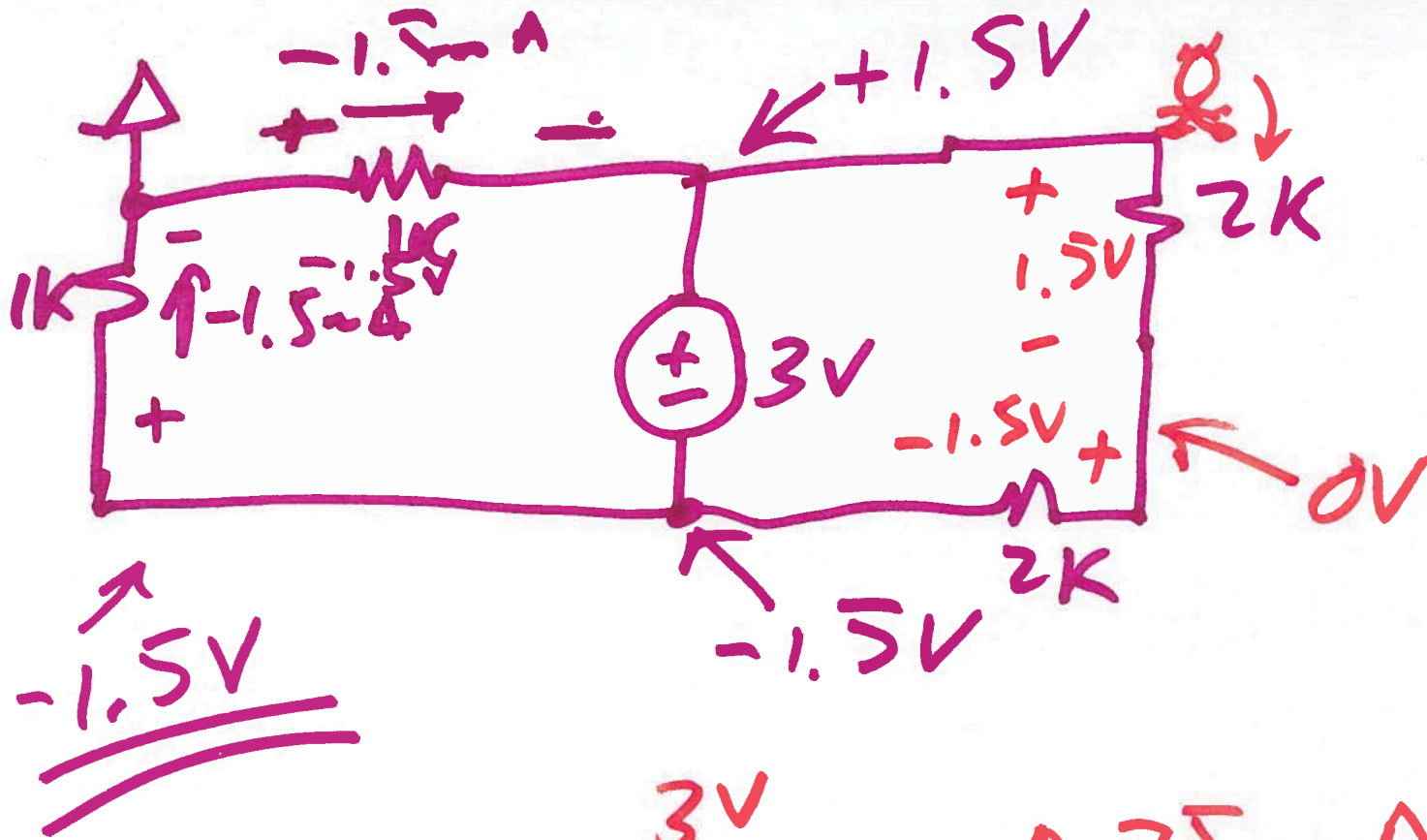

$$\frac{3V}{2k + 2k} = 0.75 \mu A$$

7)

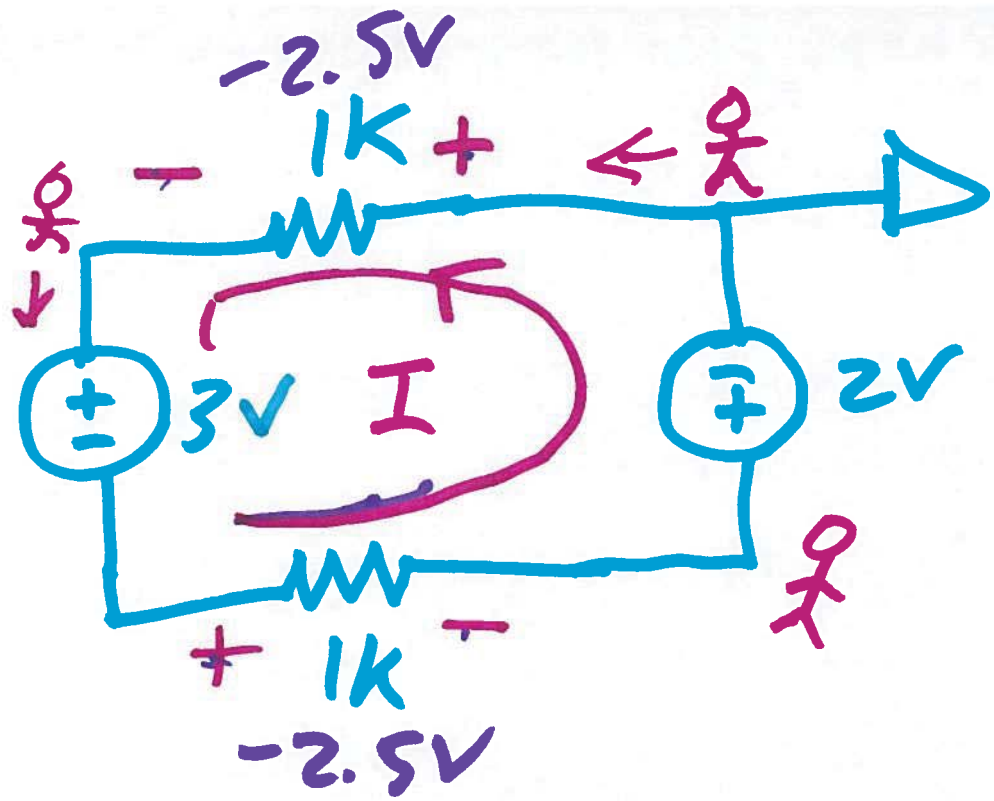


$$-I \cdot 1k - 3 - I \cdot 1k - 2 = 0$$

$$I = \frac{-5}{2k} = 2.5 \mu A$$

$$-(-2.5V) - 3 - (-2.5) - 2 = 0$$

8)



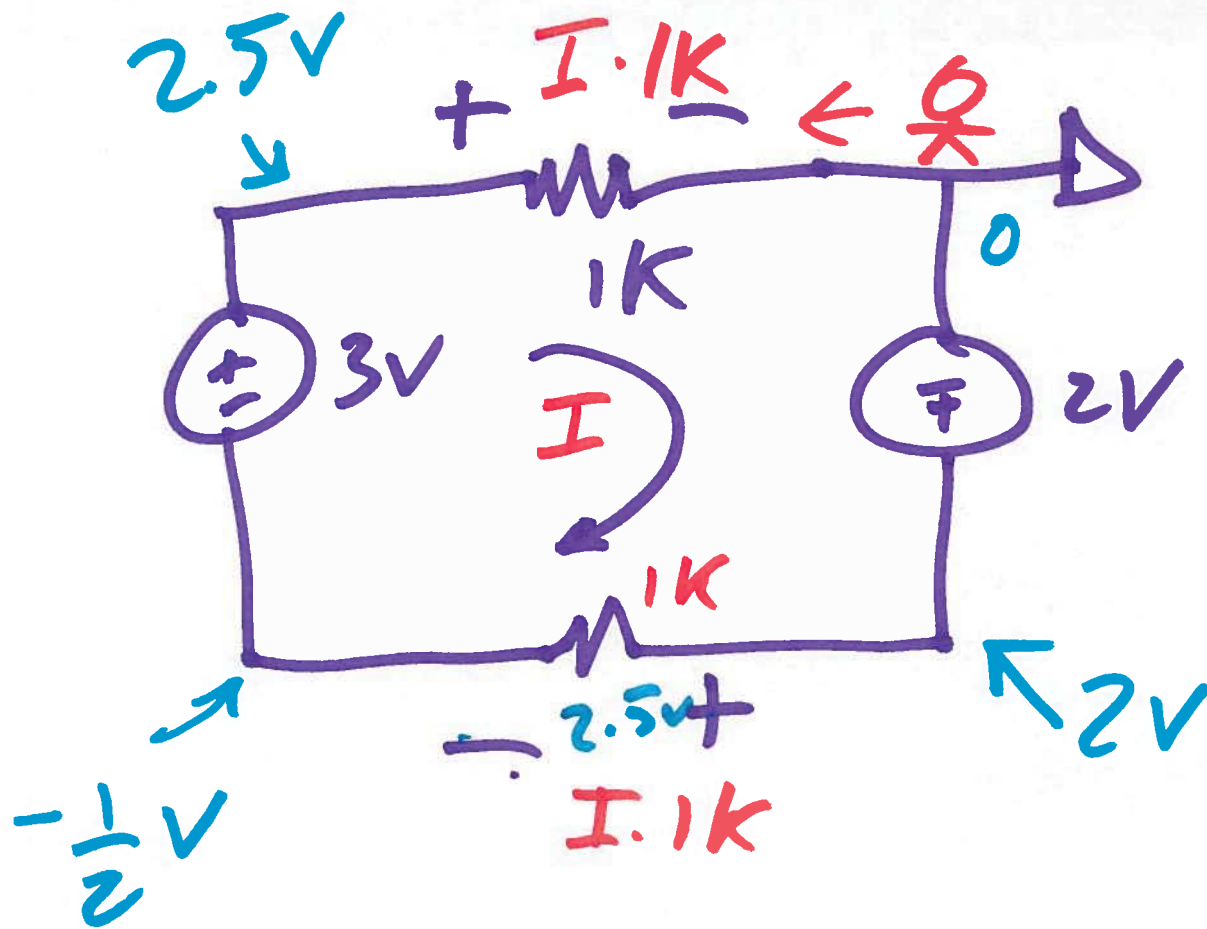


$$+I \cdot 1k - 3V + I \cdot 1k - 2V = 0$$

$$I = +2.5 \mu A$$

9)


# Current divider

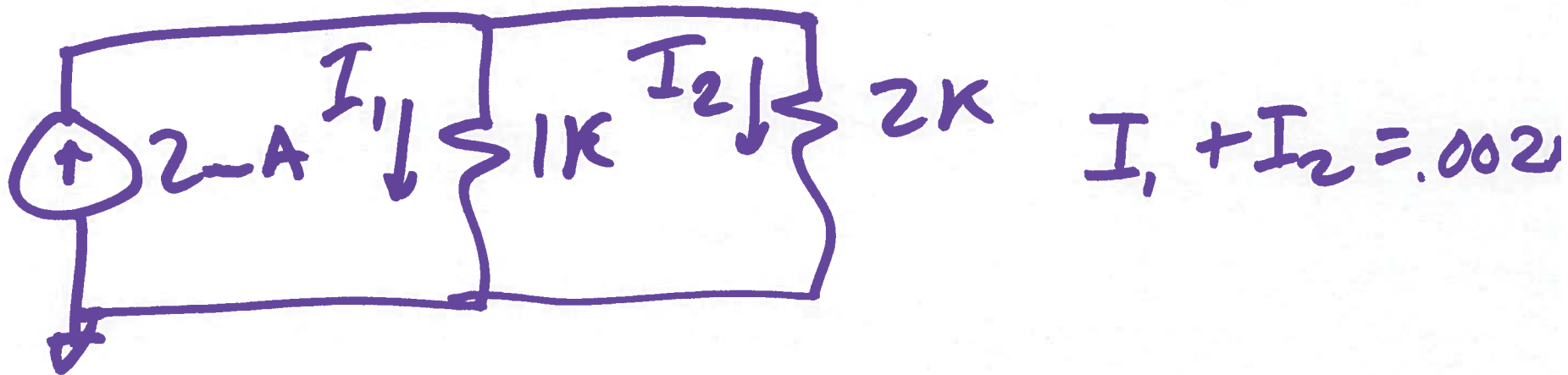

$$I_1 = 2mA \cdot \frac{2k}{2k + 1k}$$

$$I_2 = 2mA \cdot \frac{1k}{2k + 1k}$$

# Voltage divider

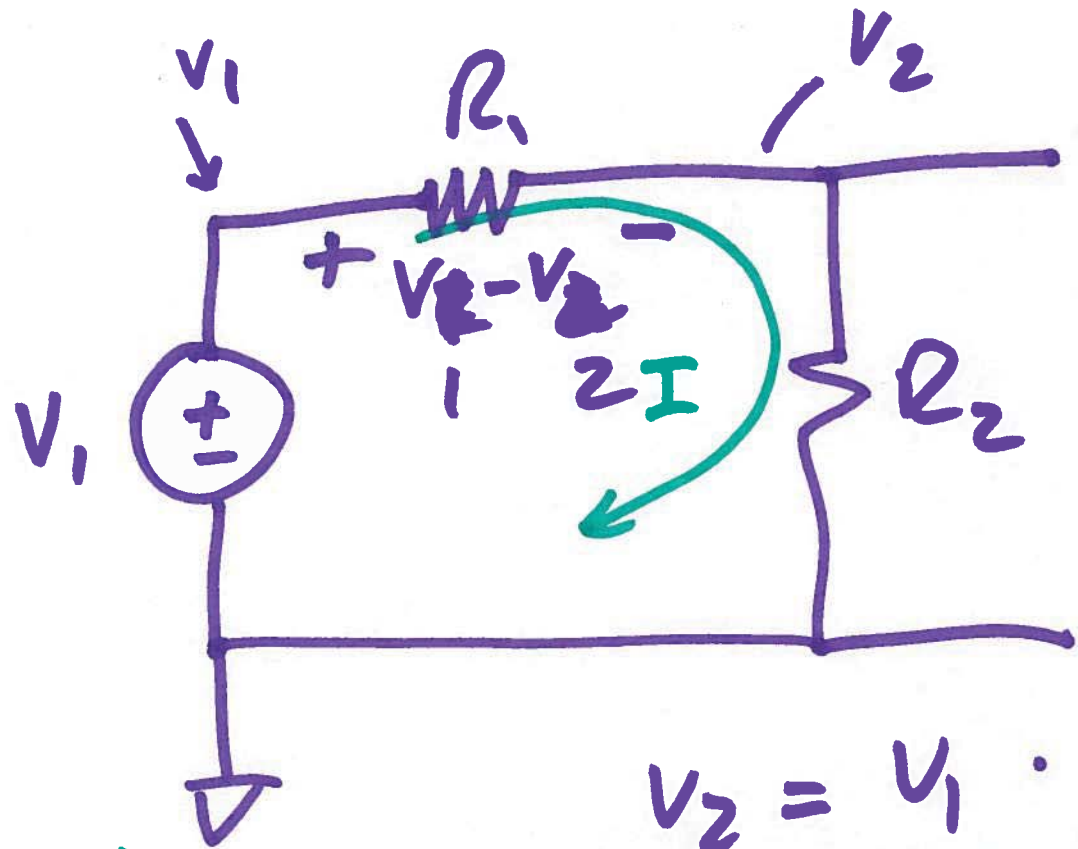

$$V_2 = I \cdot R_2$$

$$+ = V_1 \cdot \frac{R_2}{R_1 + R_2}$$


$$-$$

$$V_2 = V_1 \cdot \frac{R_2}{R_1 + R_2}$$


$$I = \frac{V_1}{R_1 + R_2}$$

$$V_1 - V_2 = V_1 \cdot \frac{R_1}{R_1 + R_2}$$

11)

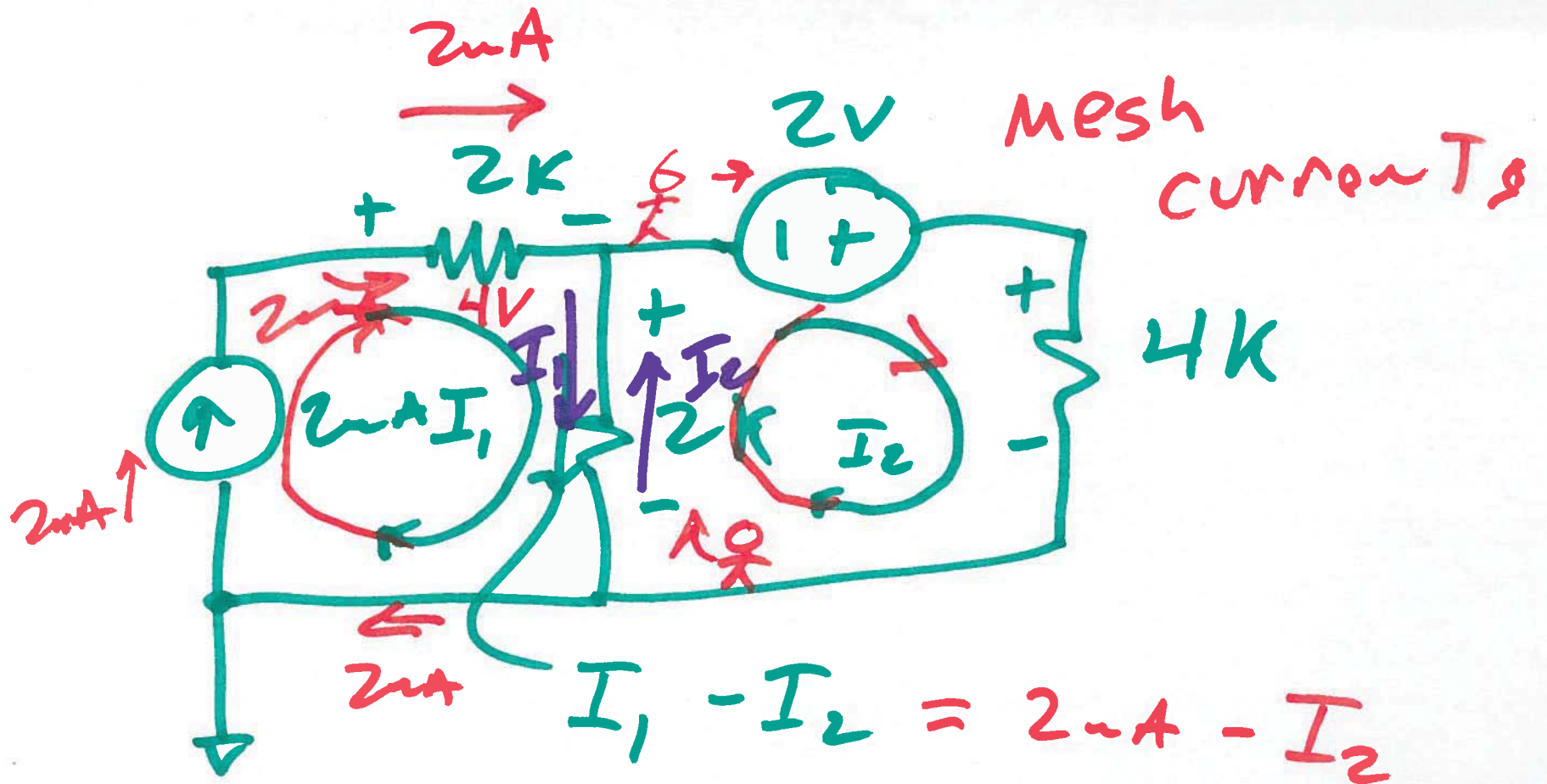

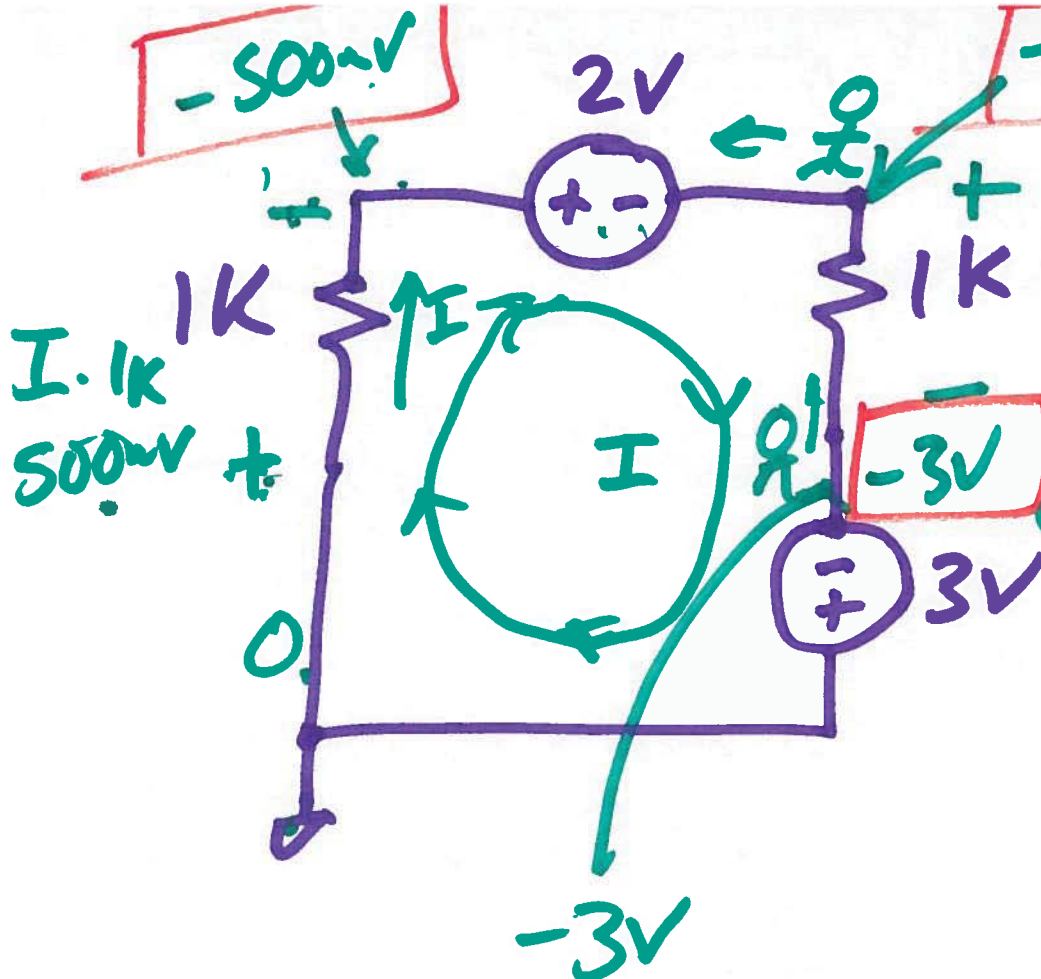
$$+ 2k(2\mu A - I_2) + 2V - 4k \cdot I_2 = 0$$



$I \cdot 1k = \frac{1}{2} V$  KVL  
 $0 = +2V + I \cdot 1k - 3 + I \cdot 1k$   
 $1V = I \cdot 2k \cdot 10^{-6}$   
 $I = 500 \mu A$   
 $= \frac{1}{2} \mu A = 0.0005 A$


Voltage sources  $\rightarrow$  Short  
 Current sources  $\rightarrow$  open

13)

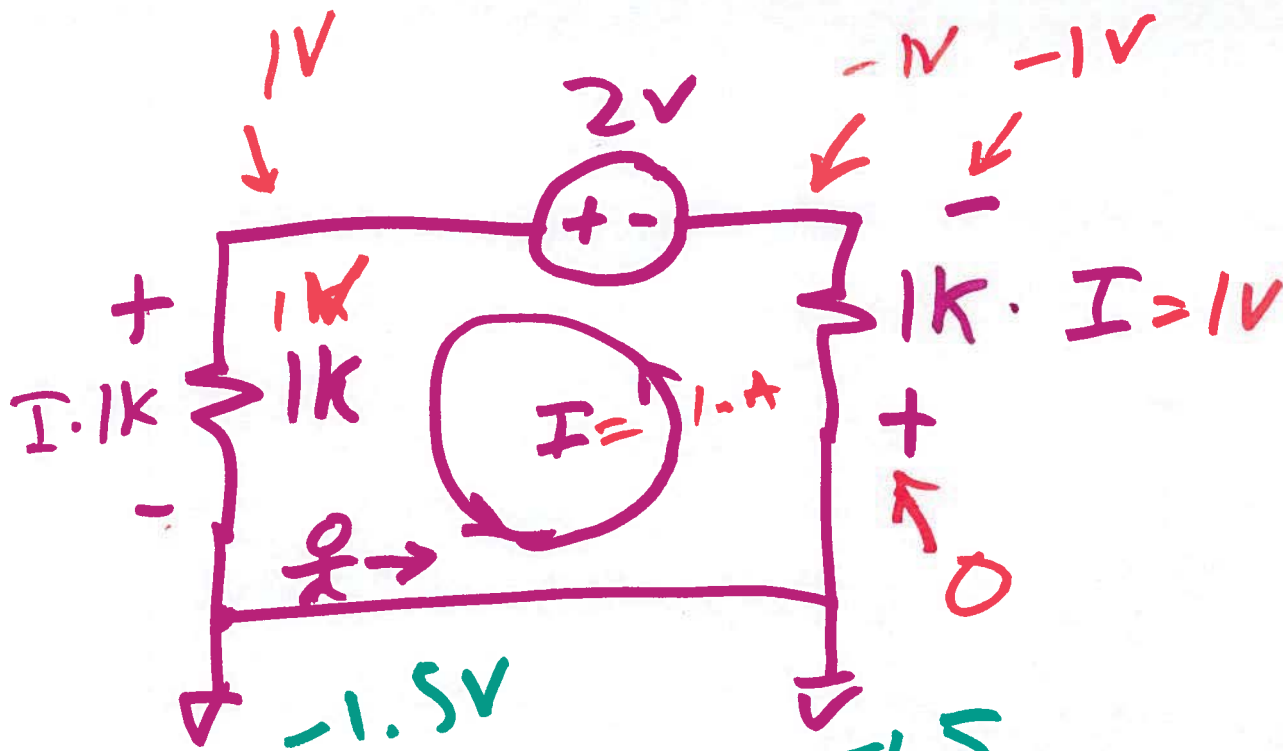

$$-1k \cdot I + 2 - I \cdot 1k = 0$$

$$I = \frac{2}{2k} = 1 \mu A$$

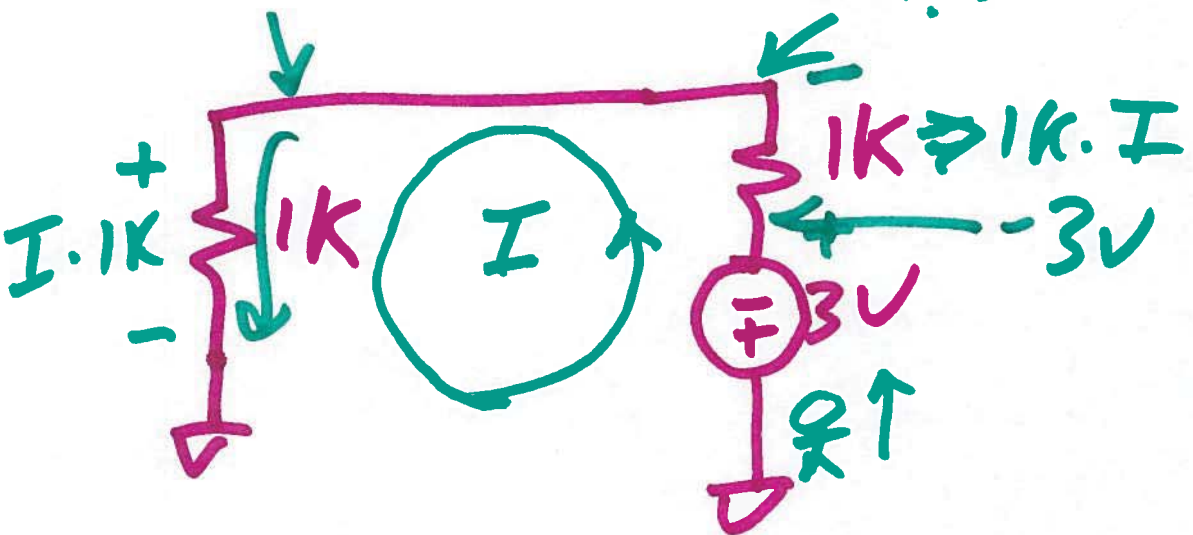

$$-3V - I \cdot 1k - I \cdot 1k = 0$$

$$I = -1.5 \mu A$$