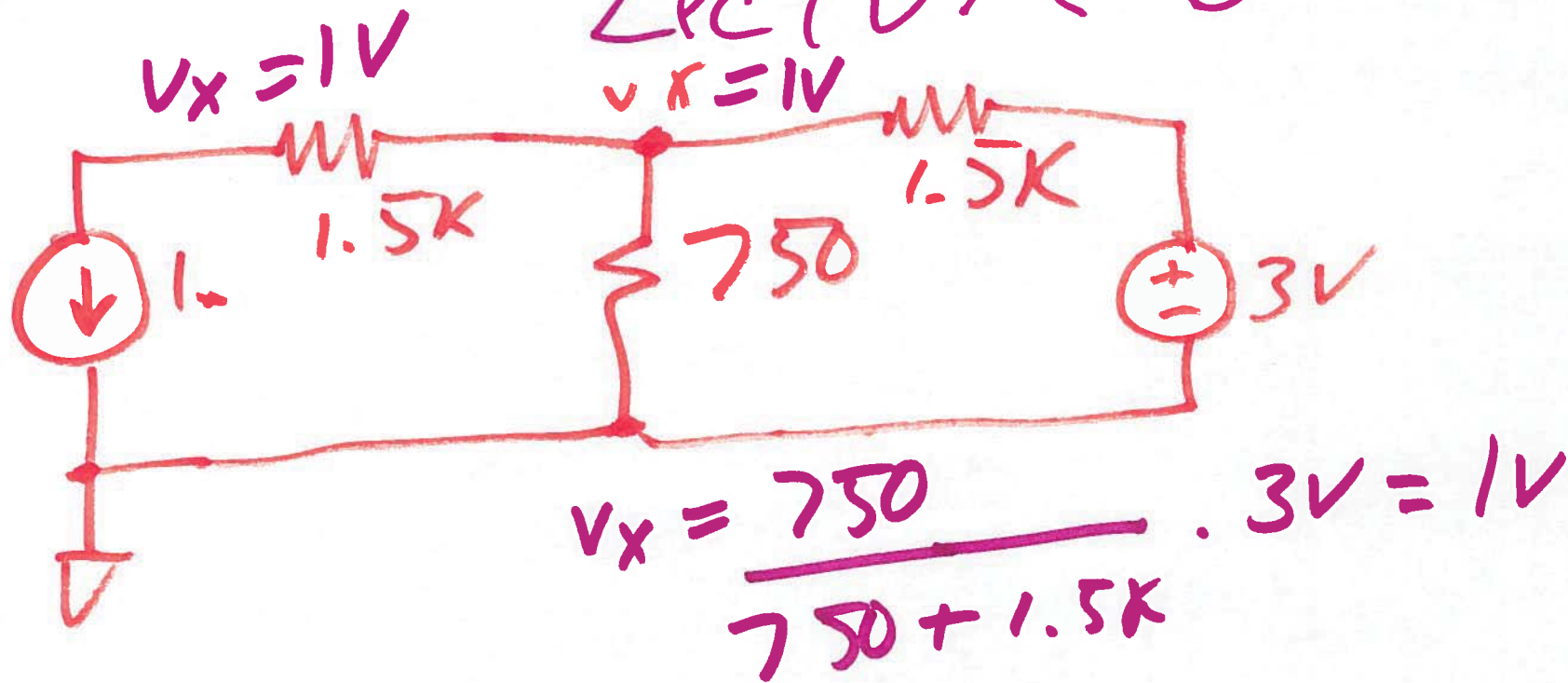



EE 220
circuits I

Sept. 18, 2017

Lecture 6



1)

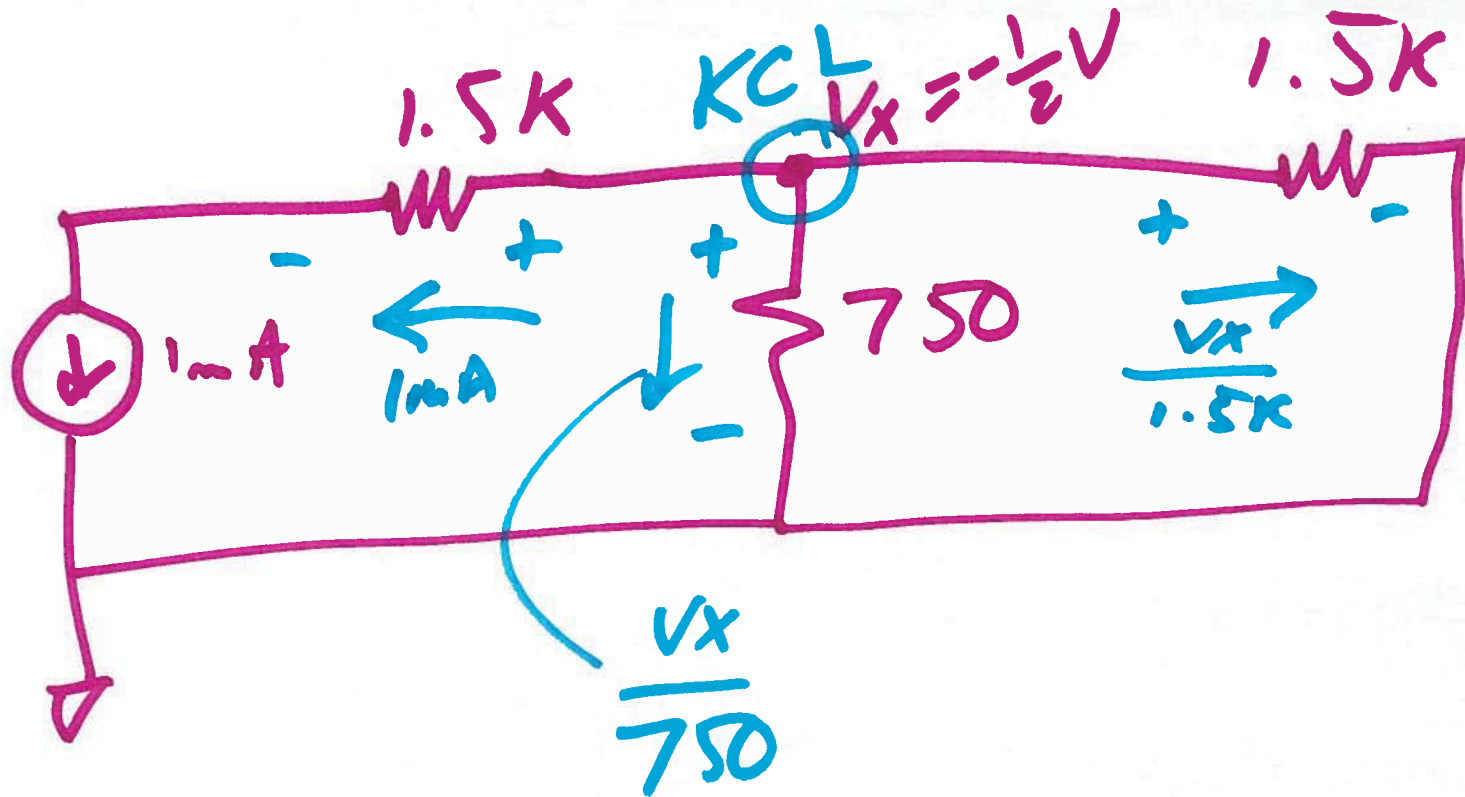



$$1mA + \frac{V_x}{750} + \frac{V_x}{1.5K} = 0$$

$$1.5V + 2V_x + V_x = 0$$

$$V_x = -\frac{1}{2} V$$

2)

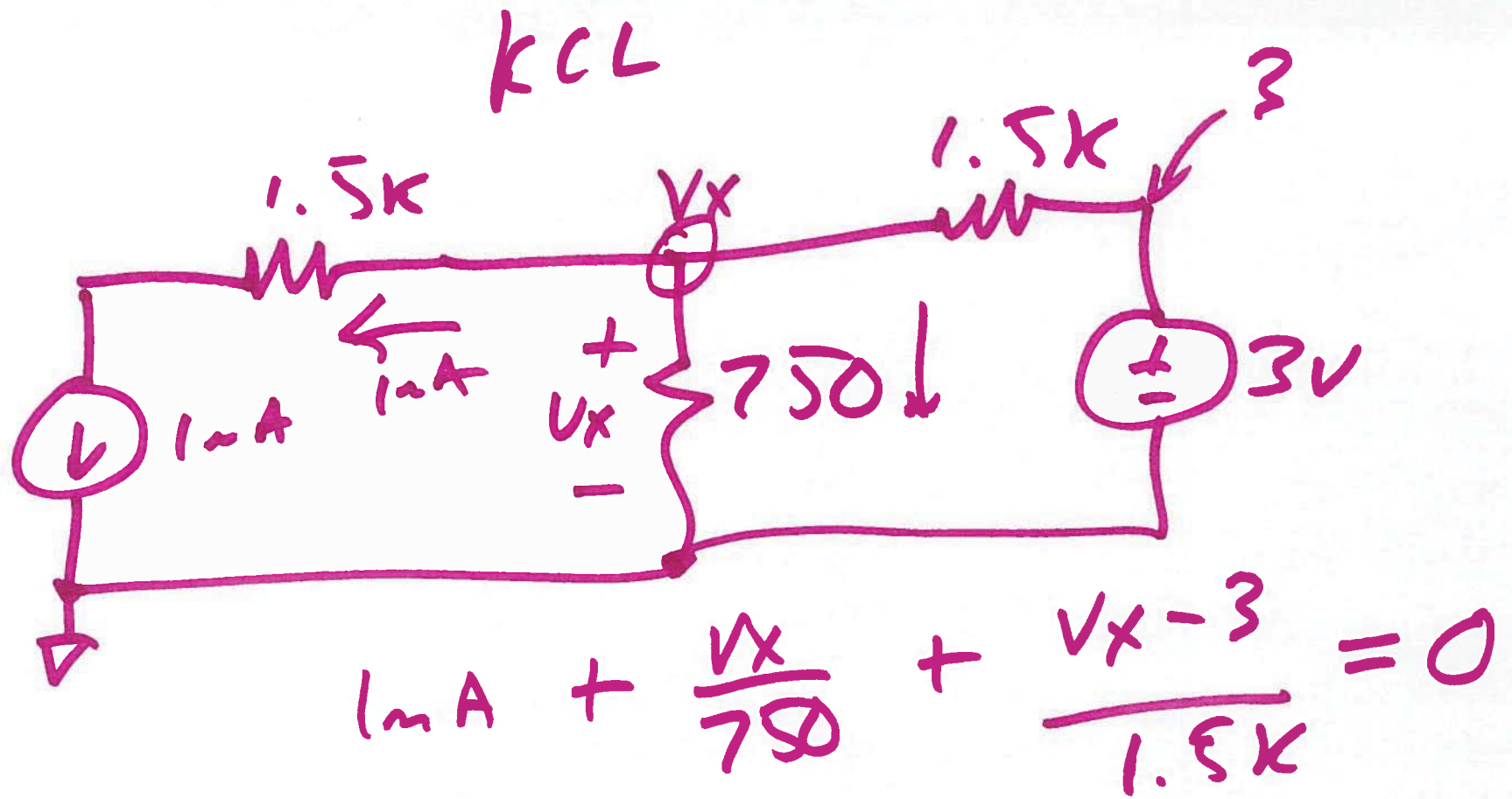


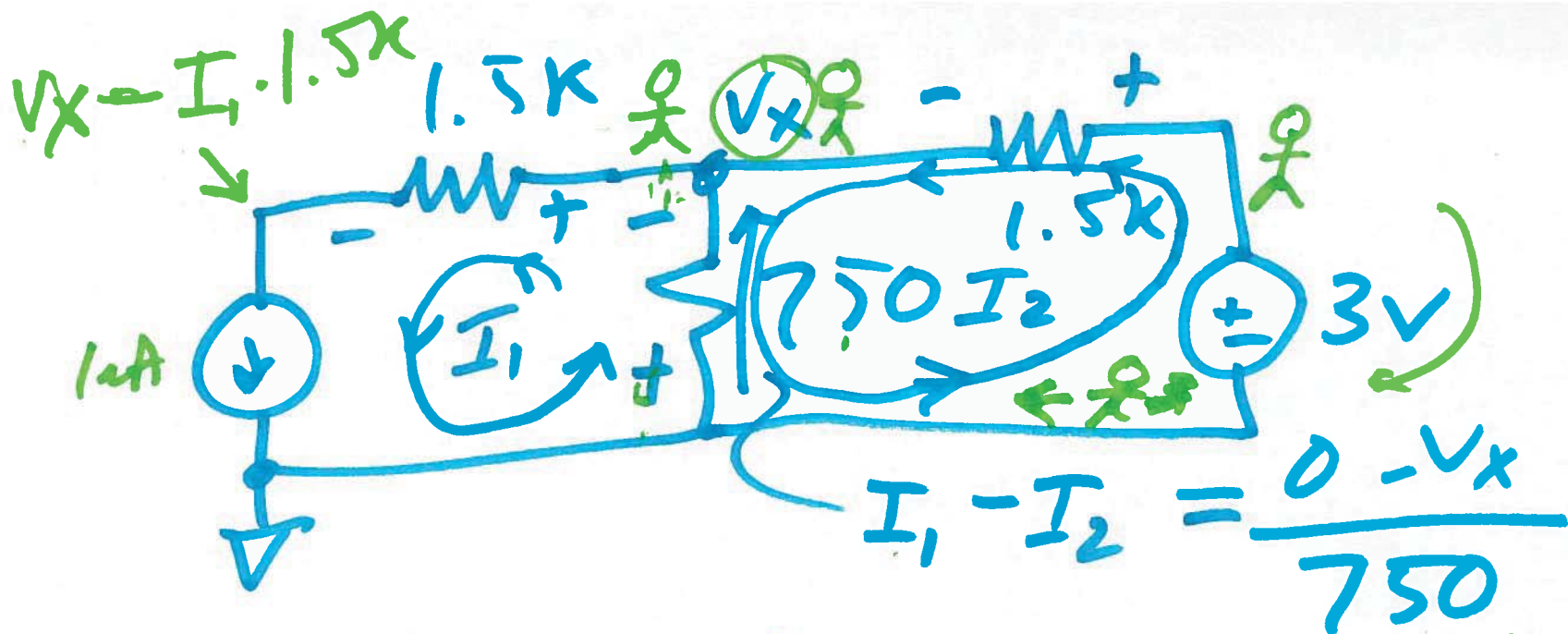


$$-750 \cdot (I_1 - I_2) + 1.5k I_2 - 3 = 0$$


$$I_1 = 1 \text{ mA}$$

$$V_x = I_1 \cdot 1.5k$$

$$V_x = -750 \cdot (I_1 - I_2)$$

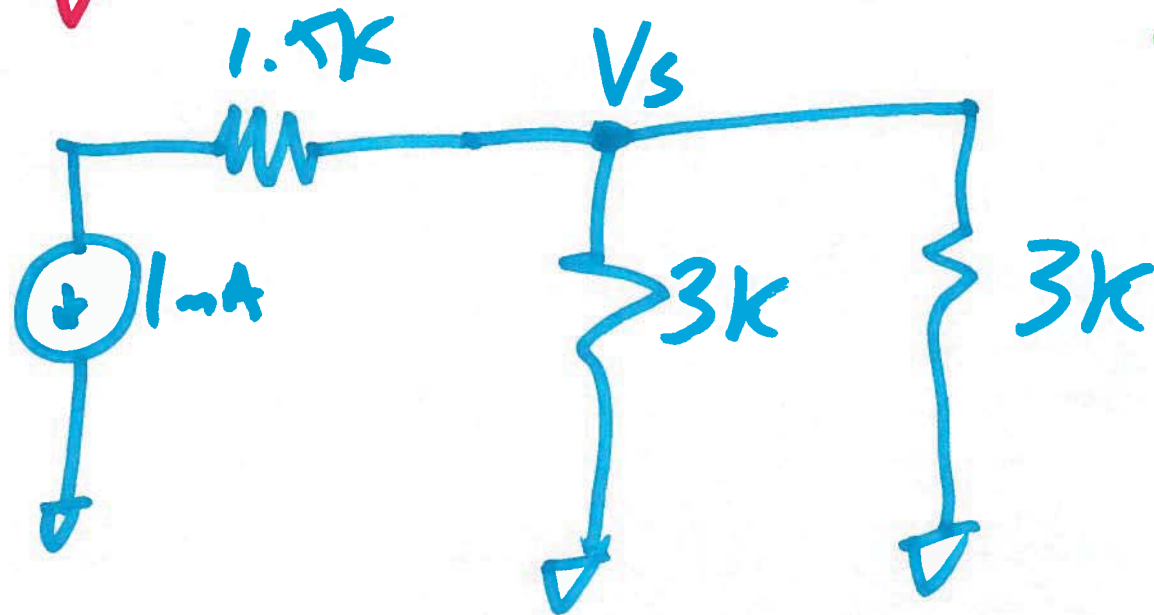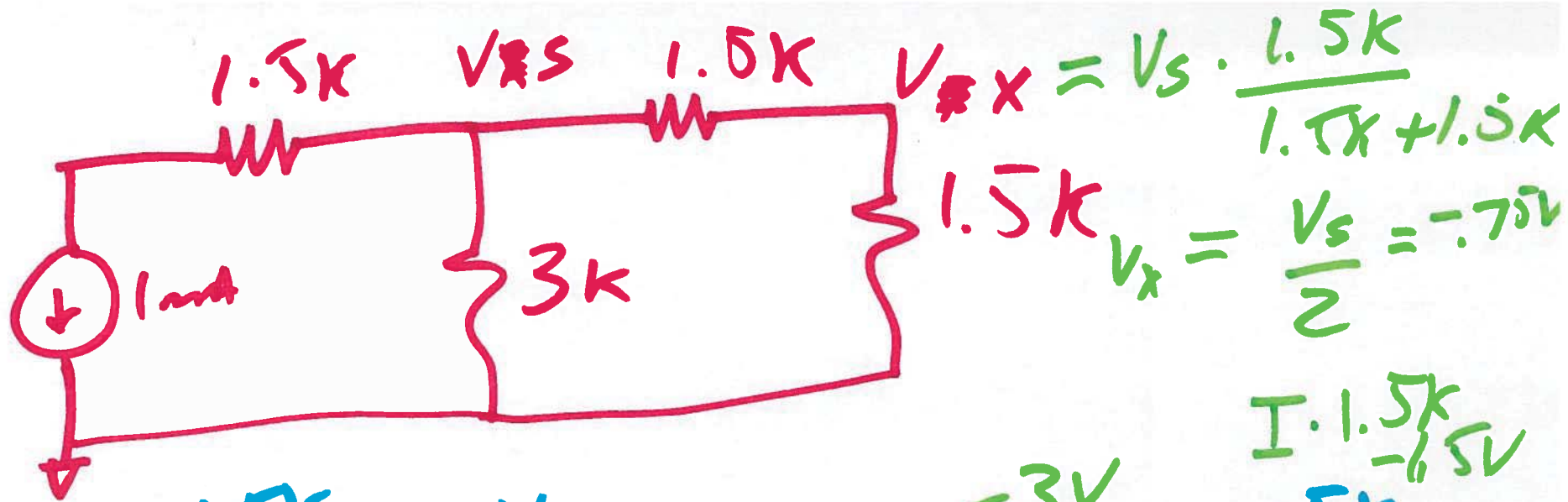



$V_s = I \cdot 1.5k$
 $= -1.5V$

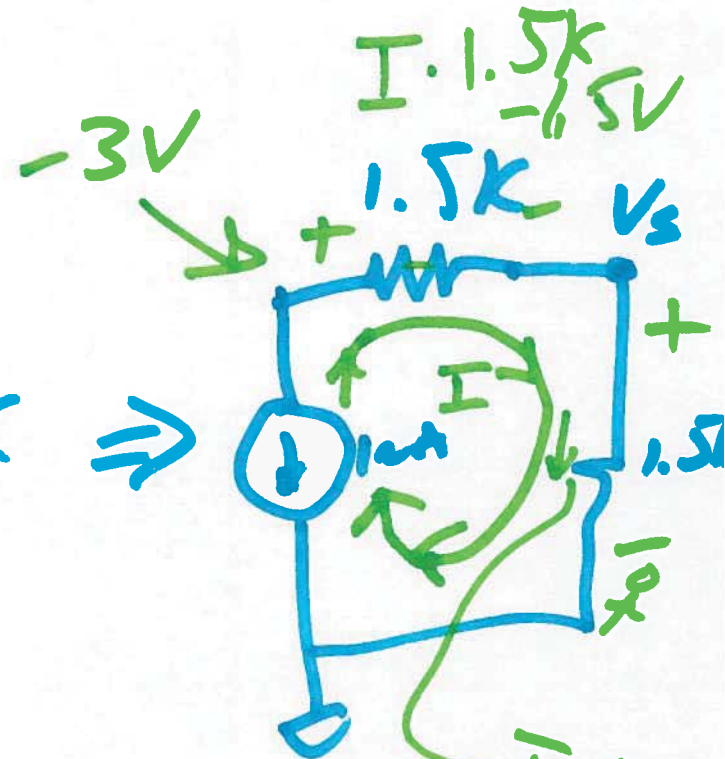


$I = -1\mu A$

s)


THEVENIN'S THEOREM

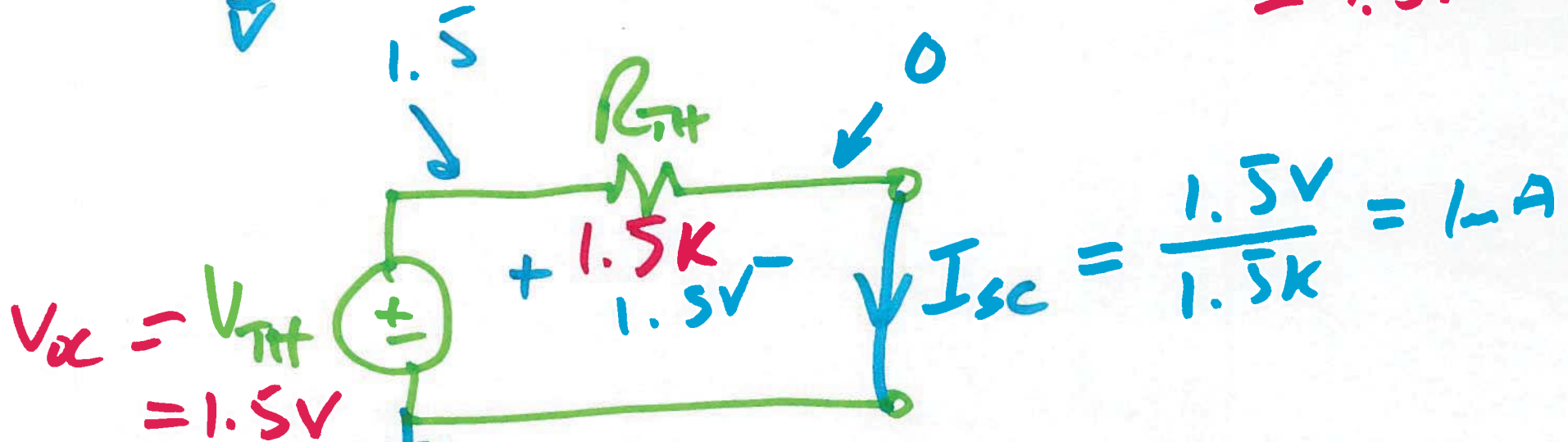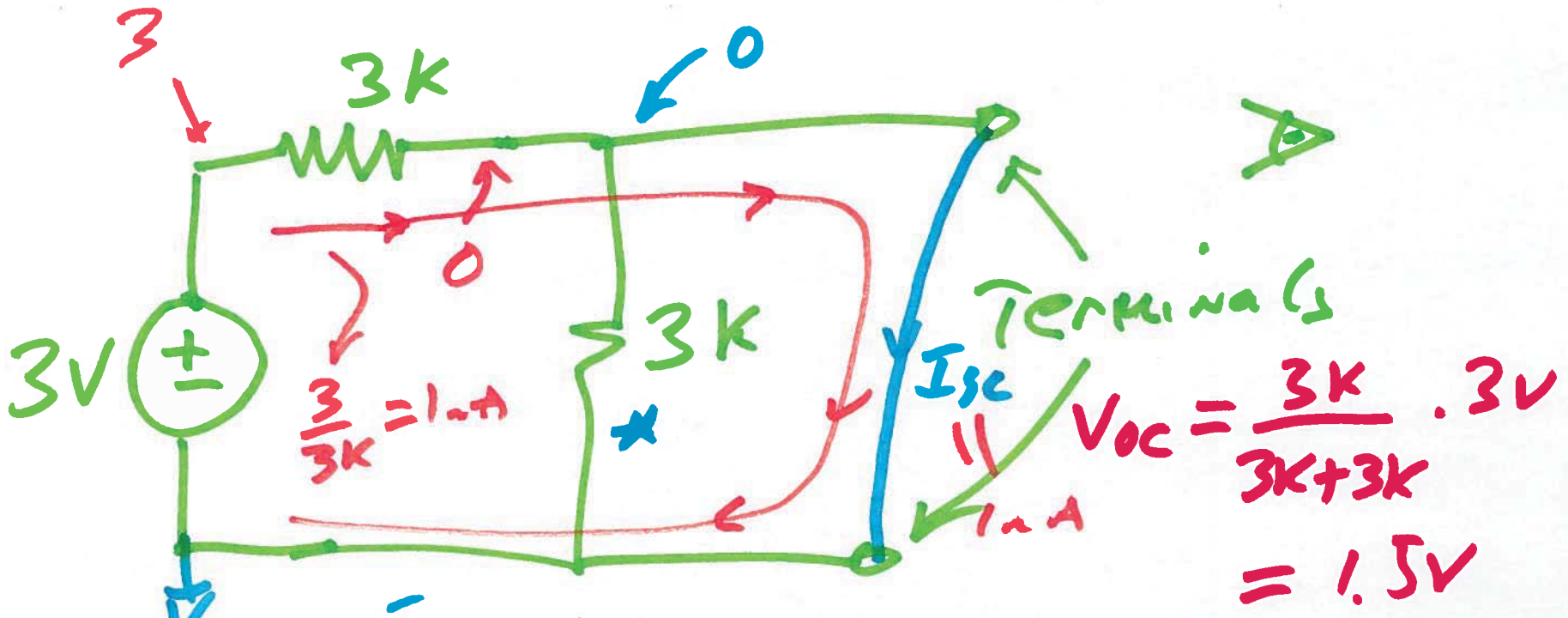

b)

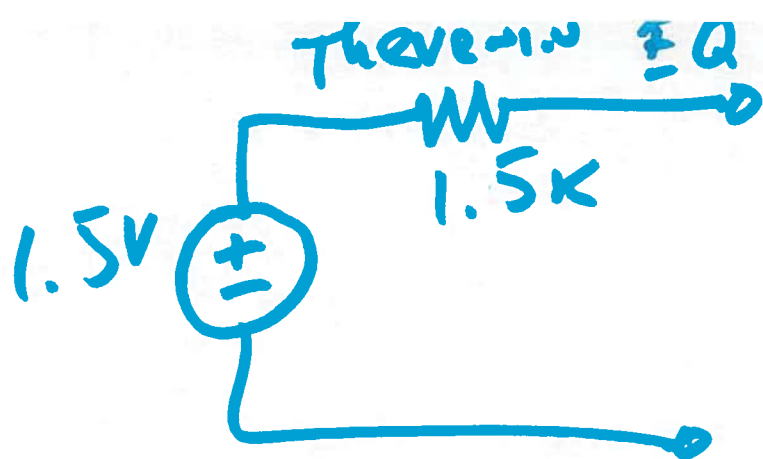


NORTON'S EQUIVALENT

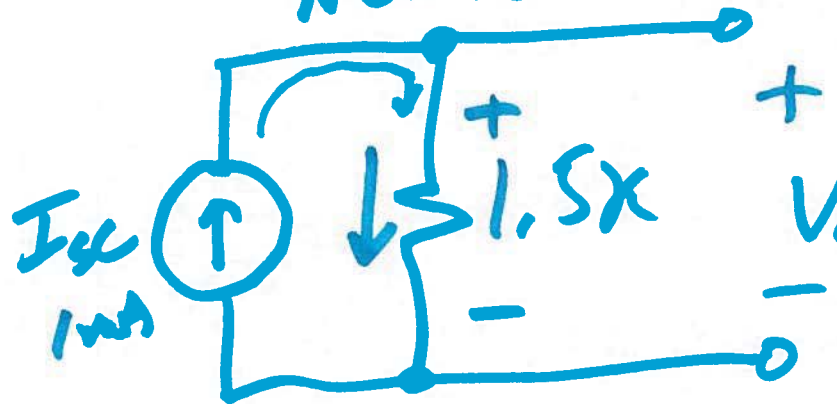

$$V_{OC} = 1\mu A \cdot 1.5k = 1.5V$$



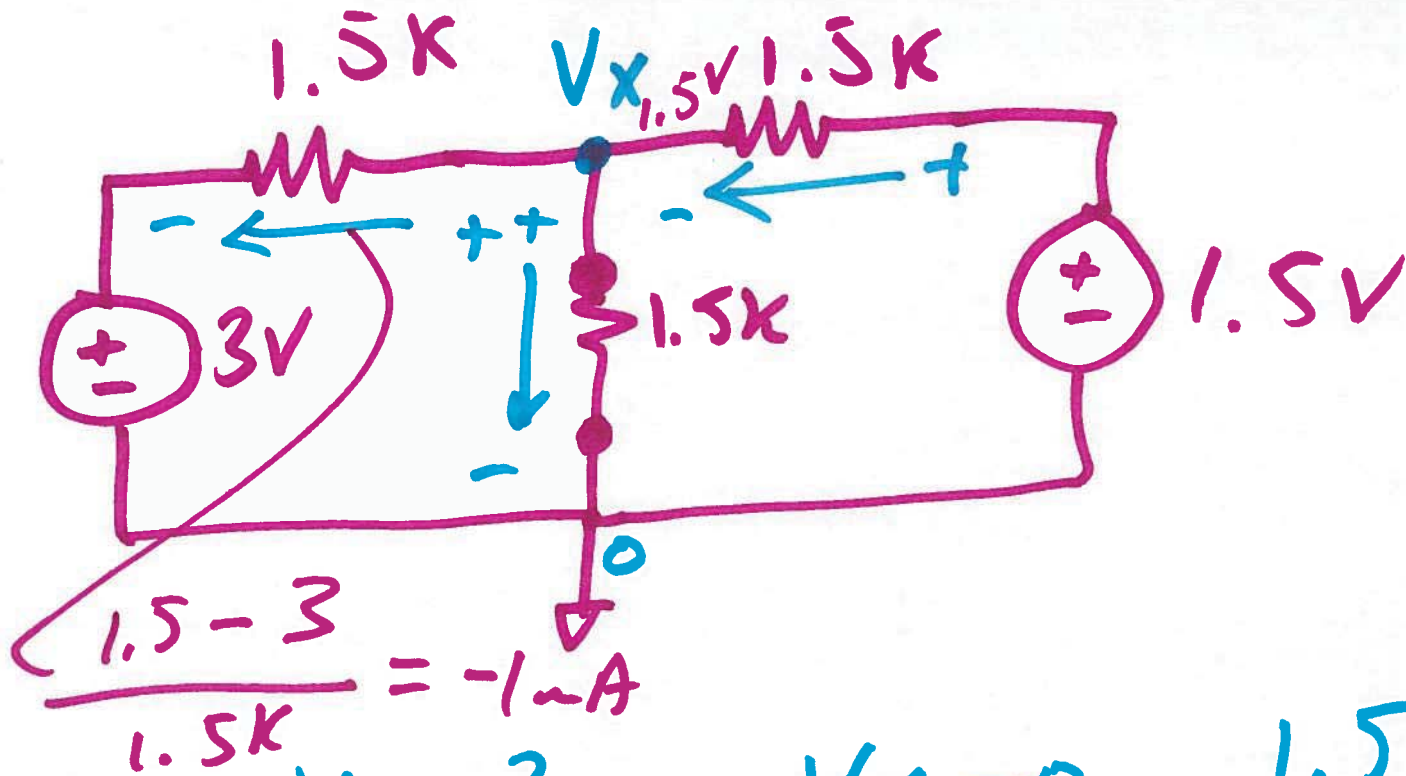

$$\frac{1.5 - 3}{1.5k} = -1 \mu A$$


$$\frac{V_x - 3}{1.5k} + \frac{V_x - 0}{1.5k} = \frac{1.5 - V_x}{1.5k}$$

$$2V_x - 3 = 1.5 - V_x$$

$$3V_x = 4.5$$

$$V_x = 1.5V$$

8)

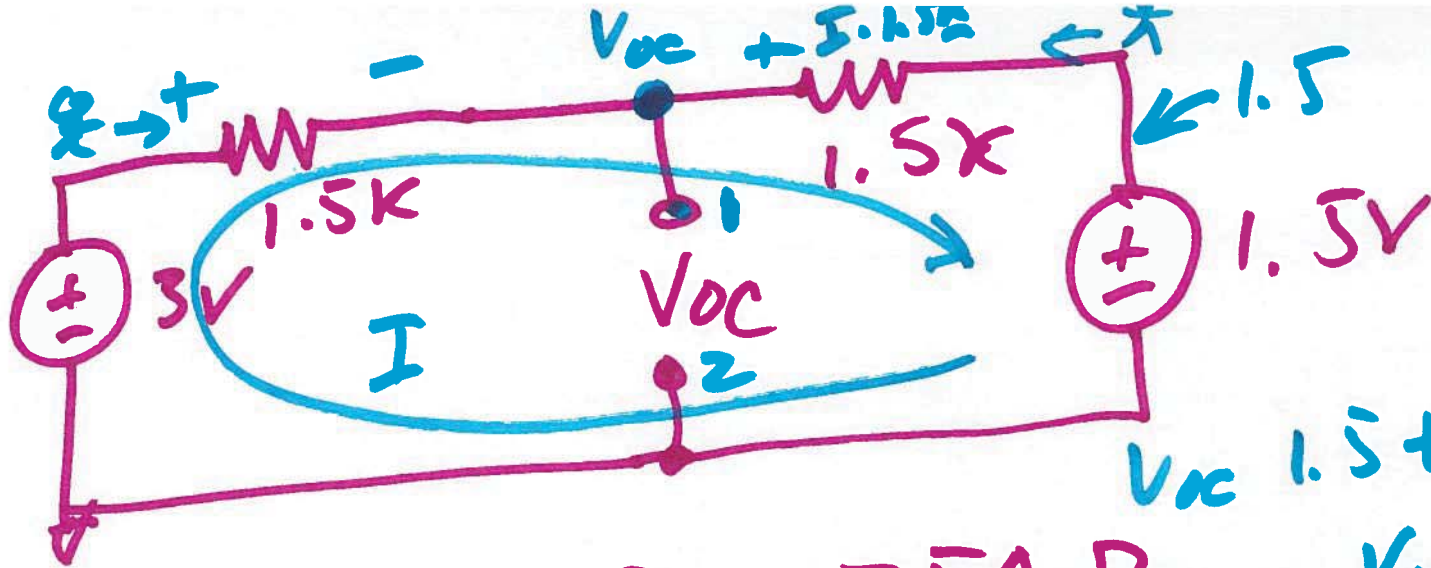

$$R_{TH} = 750 \Omega$$

$$V_{OC} = 1.5 + 1.5k \cdot \frac{1}{2} mA$$


$$\underline{\underline{V_{OC} = 2.25V}}$$

$$-I \cdot 1.5k - I \cdot 1.5k - 1.5V + 3 = 0$$

$$-I \cdot 3k = -1.5V$$

$$I = \frac{1}{2} mA = 500 \mu A$$

$$\underline{\underline{= 0.5 mA}}$$

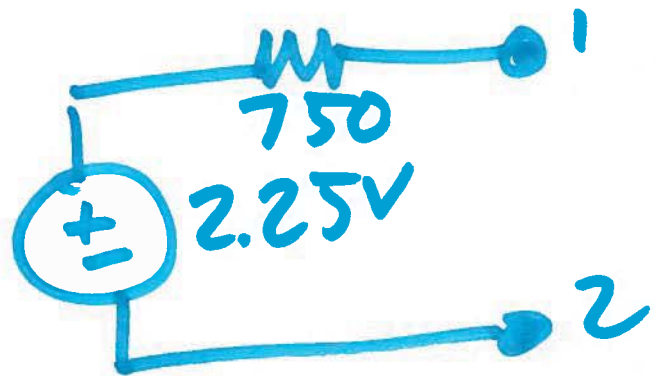

9)

