

Quiz #5 EE 220 Fall 2017 Name: _____

Closed book and notes.

Show your work for credit! Put boxes around your answers.

1. Find the voltages in the following circuit. (5 point)

