

Quiz #7 EE 220 Fall 2017 Name: _____

Closed book and notes.

Show your work for credit!

1. Find the Thevenin and Norton equivalent circuits, with R_2 removed, at the terminals marked by red dots seen below. (5 points)

