

Quiz #8 EE 220 Fall 2017 Name: \_\_\_\_\_

Closed book and notes.

Show your work for credit!

1. Find  $V_{out}$  in the following circuit. Note that  $G1$  is a voltage-dependent current source. (5 points)

