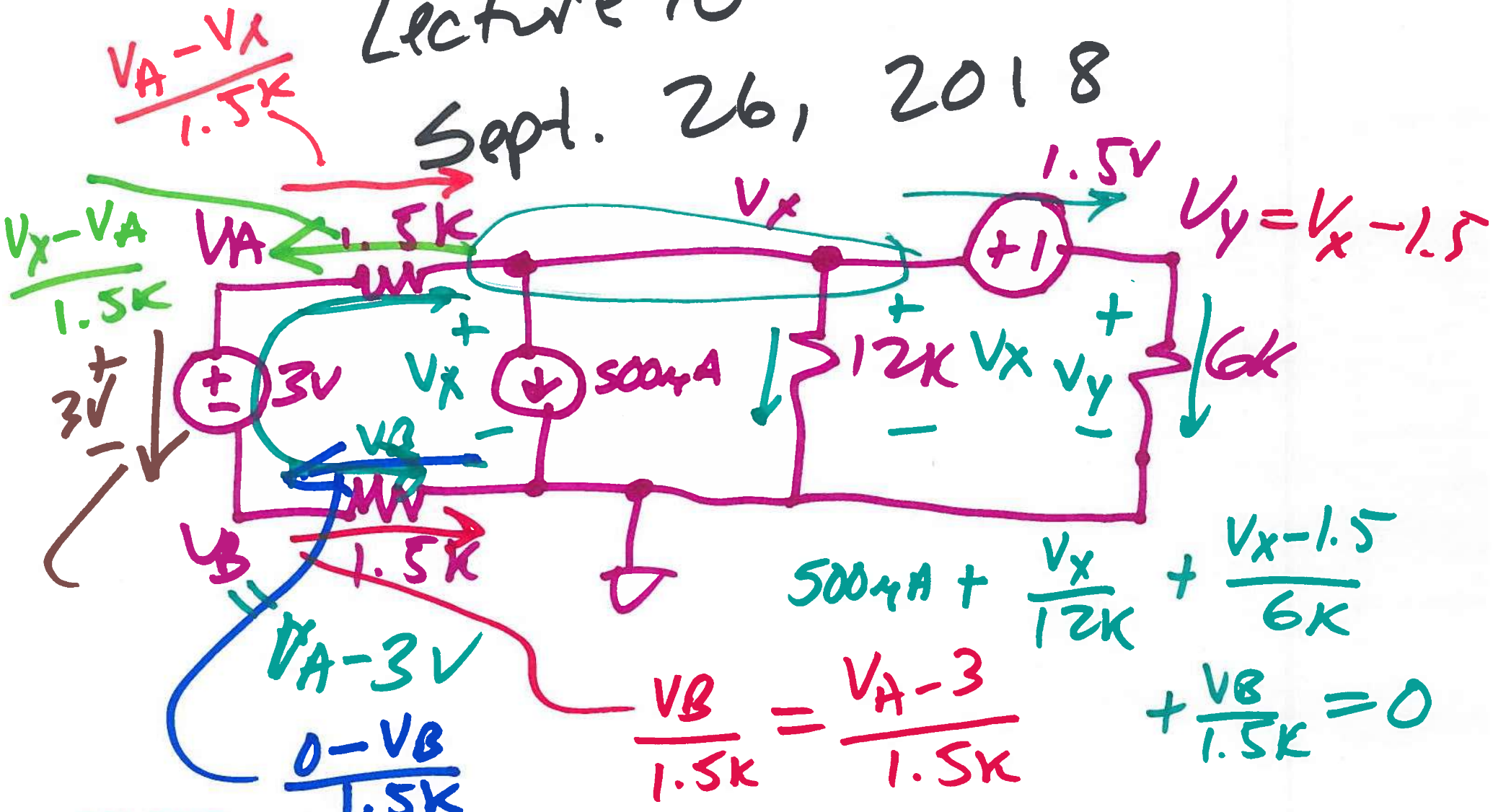



# EE 220 Circuits 1

Lecture 10

Sept. 26, 2018



1)

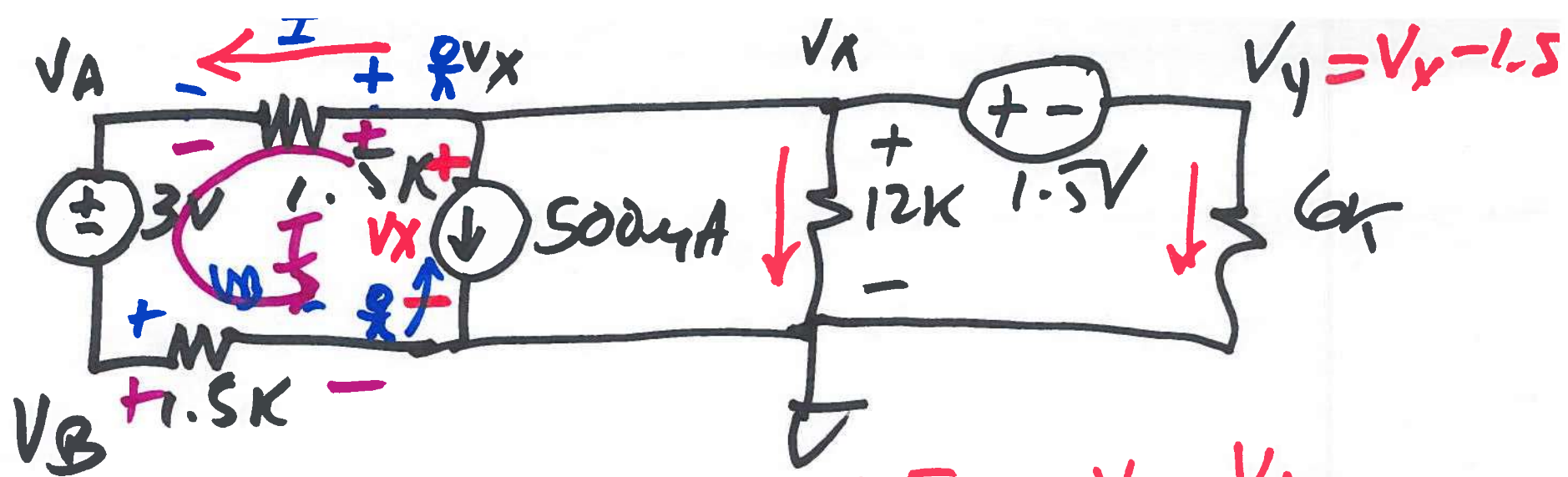


$$500\mu A + \frac{V_x}{12K} + \frac{V_x - 1.5}{6K} + \frac{V_x - V_A}{1.5K} = 0$$

$$V_x - (V_x - V_A) - 3V - V_B = 0$$

$$V_A - 3 = V_B$$

$$V_x - 1.5K I - 3V - 1.5K I = 0$$

$$I = \frac{V_x - 3}{3K}$$

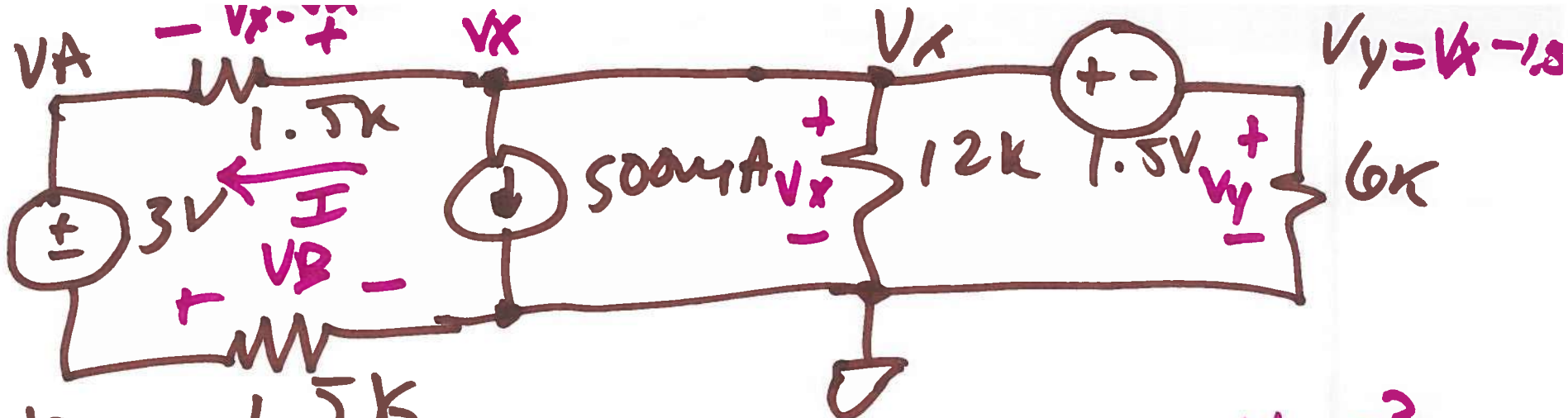

$$V_y = V_x - 1.5$$

$$\frac{V_x - V_A}{1.5k} = \frac{V_B}{1.5k} = \frac{V_A - 3}{1.5k}$$


$$V_x = 2V_A - 3$$

$$I = \frac{V_x - 3}{3k}$$


$$\frac{V_x - 3}{3k} + 500\mu A + \frac{V_x}{12k} + \frac{V_x - 1.5}{6k} = 0$$

$$4V_x - 12 + 6V + V_x + 2V_x - 3 = 0$$
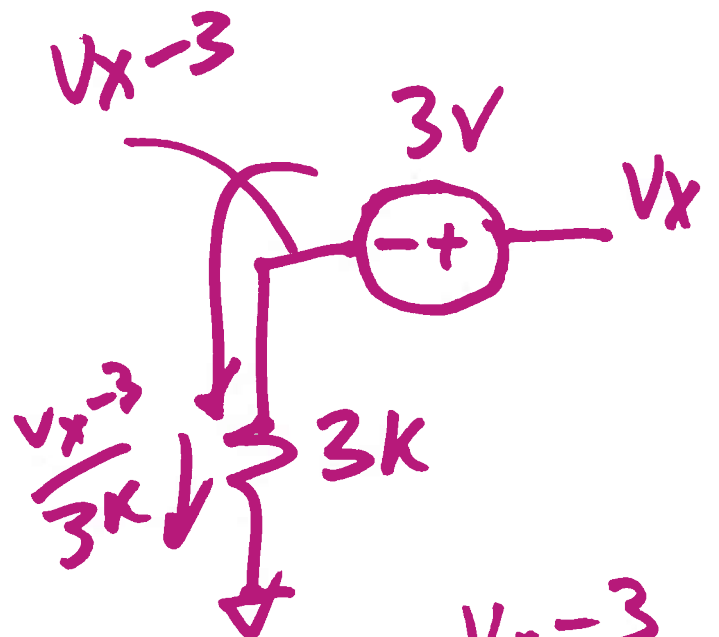
$$7V_x = 9 \quad \boxed{V_x = \frac{9V}{7}}$$





3)

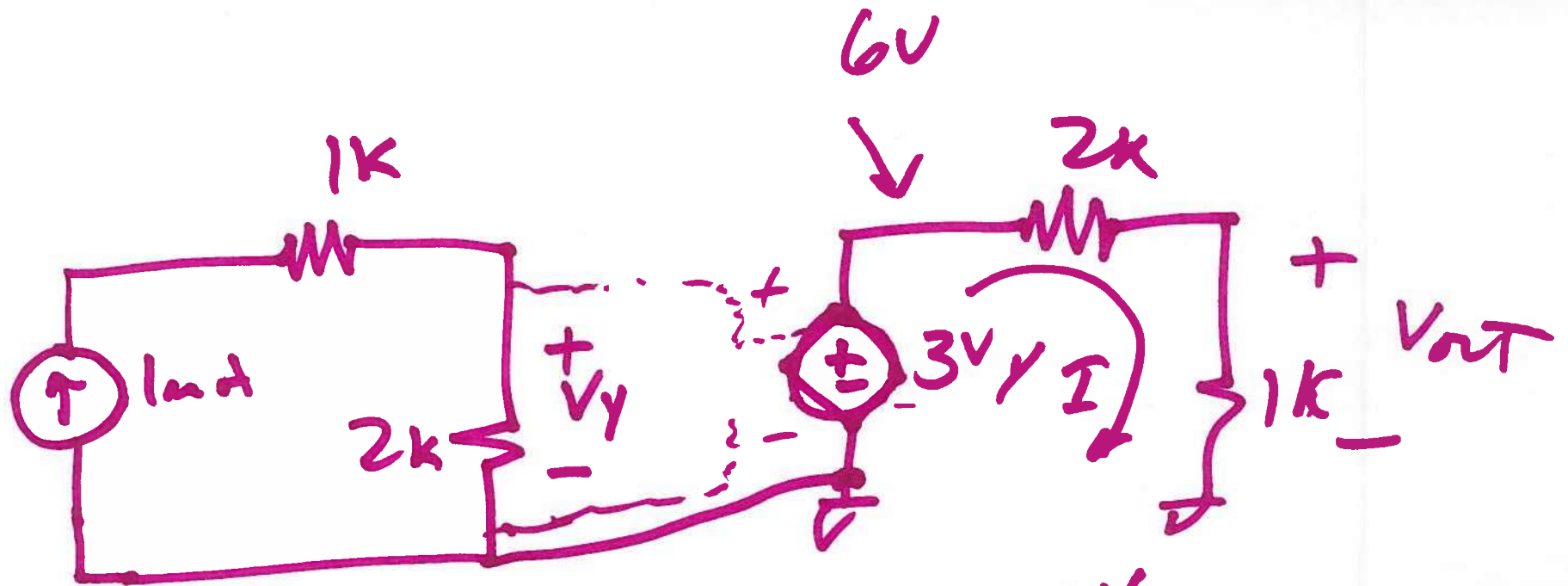

$$V_y = 1\text{mA} \cdot 2\text{k} = 2\text{V}$$

$$V_{OUT} = 6 \cdot \frac{1\text{k}}{1\text{k} + 2\text{k}} = 2\text{V}$$
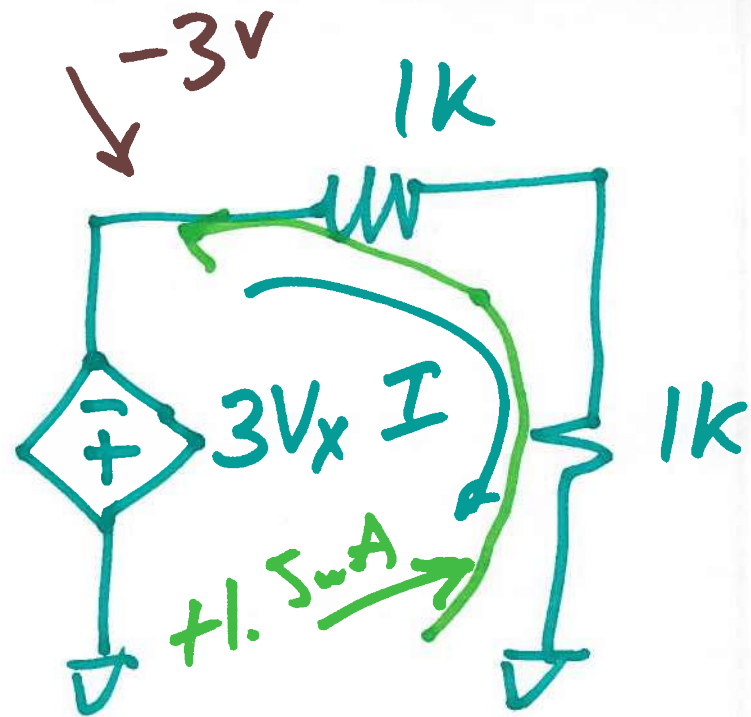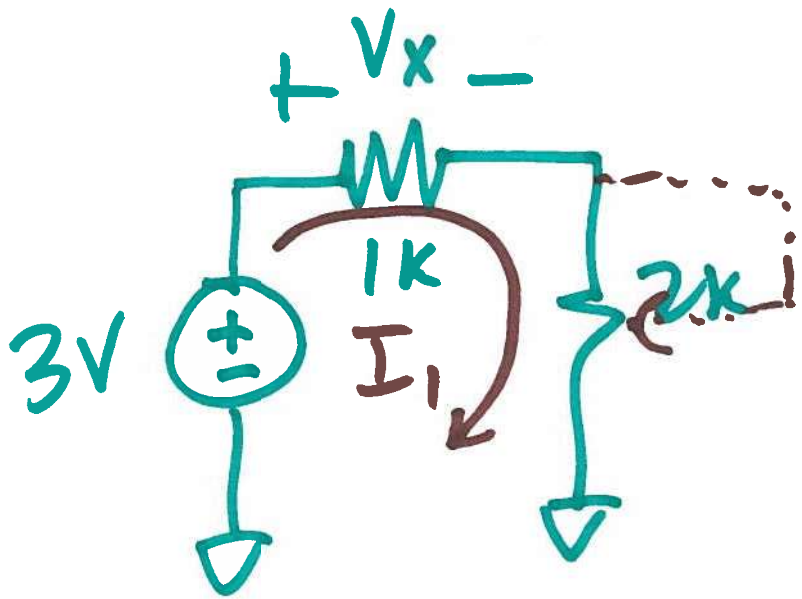
$$I = \frac{2\text{V}}{1\text{k}} = \underline{\underline{2\text{mA}}}$$



$$V_x = 3 \cdot \frac{1k}{1k + 2k} = \underline{\underline{1V}}$$


$$I = \frac{-3V - 0}{2k} = -1.5mA$$

$$\frac{V^2}{R} = I^2 R = \text{Power} = V \cdot I \quad (\text{DC ckt's})$$


$$\text{WATTS} = \frac{\text{Joules}}{s}$$




Energy = Joules

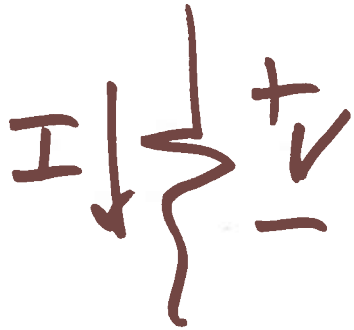


$$\text{Power} = I \cdot V$$

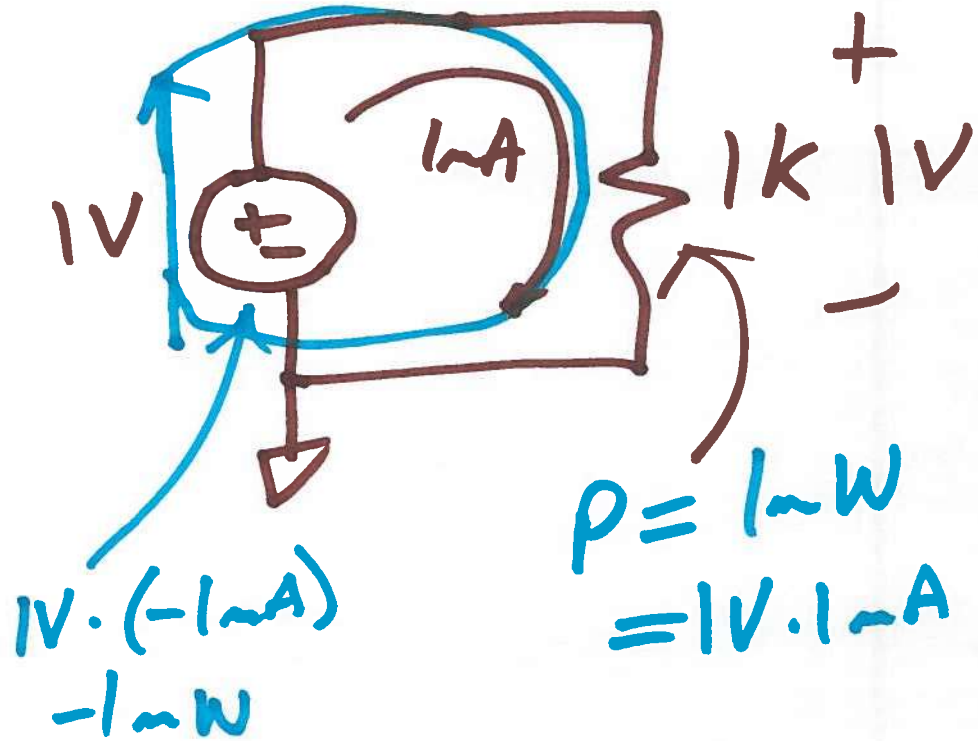



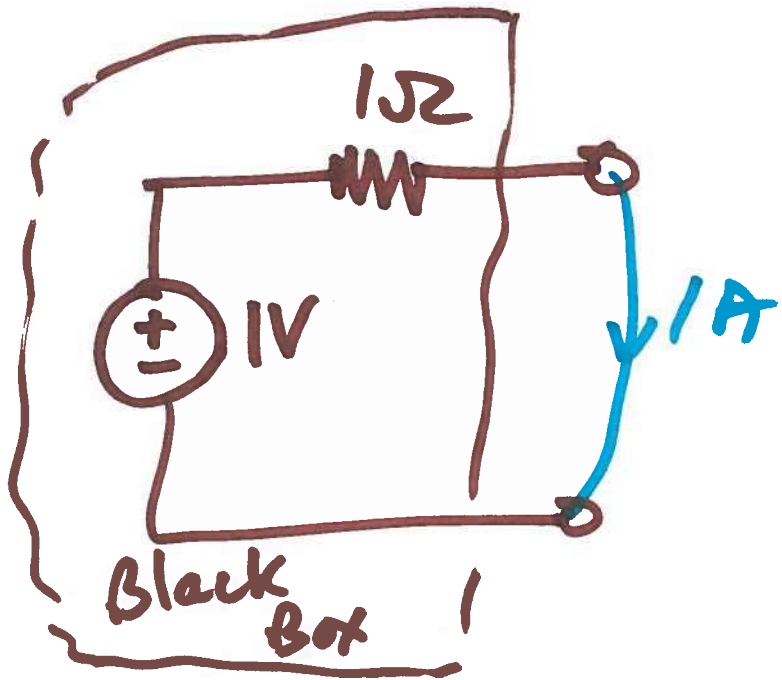

THEVENIN

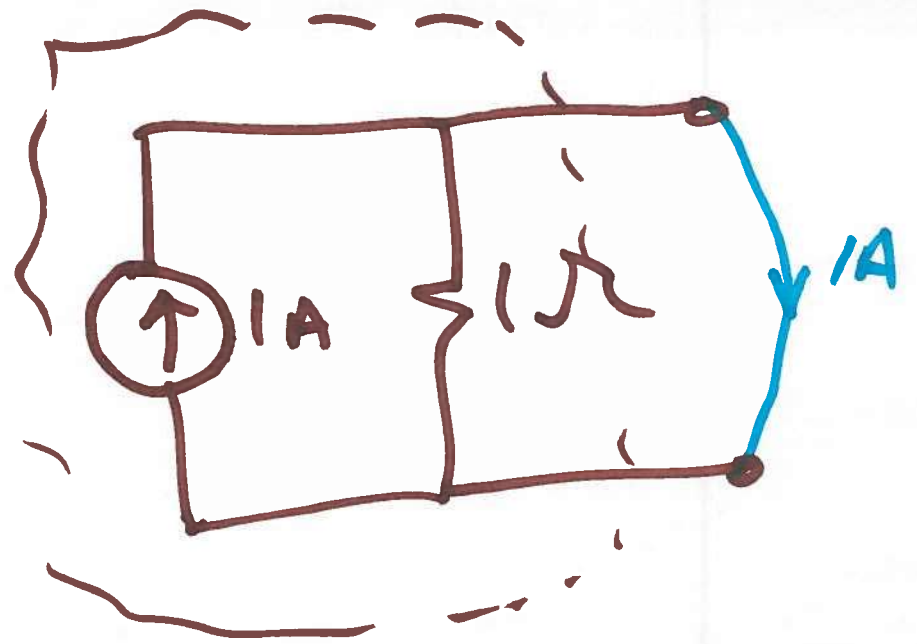

NORTON

